

Hydraulics & Pneumatics

Chapter 3: Electro-fluids (Circuit Design

by Dr. Mohd Fadzil Faisae Faculty of Mechanical Engineering ffaisae@ump.edu.my

Lesson Outcome

- By the end of this lecture, student should be able to:
 - Design and analyze advanced electrohydraulic circuit with multiple actuators using solenoid valves.



Multi Actuator Circuit

- More than 1 actuator
- 1 cylinder needs 1 valve
- Tips for circuit design:
 - -Identify sequence of movement
 - -Identify limit switch/sensor status

CC

Multi Actuator Circuit

- Example:
- A hydraulic actuated drilling machine contains two double acting cylinders (DACs). When the work piece is located at its position, cylinder A will clamp the work piece. Then, the drilling process starts, where the spindle is controlled by cylinder B. After completion of drilling, cylinder B will retract to the initial position, before the clamping cylinder retracts.
- Sequence: A (extend) -> B (extend) -> B (retract)
 -> A (retract)

Step 1: Sequence

Identify sequence of movement
 A+ B+ B- A-



Step 2: Grouping

• Make the group

A+ B+ B- A-K1 K2

- A group must contain different elements
- 1 group represents 1 coil



Step 3: Limit switch/sensor status

Identify limit switch/sensor status



Step 4: Rephrase

Rephrasing the sequence and limit switch/sensor status



Designing of Hydraulic Circuit





ising Technology



$A+ \rightarrow K1 \equiv Start \equiv A0$







$B \rightarrow K2 \equiv B1$ K2 due to changing group







Exercise

- Design an electro hydraulics to conduct this sequence:
 - Cylinder 1 & 3 extend simultaneously
 - Cylinder 2 extend
 - Cylinder 2 retract
 - Cylinder 1 & 3 retract simultaneously

Summary

• We have learn how to design an electrohydraulics circuit with multiple actuators.