

DEE 3143 BASIC ELECTRICAL MACHINE & POWER SYSTEMS

CHAPTER 1 TRANSFORMER


by

Mohd Ikhwan Muhammad Ridzuan, Norhafidzah Mohd Saad, Marlina Yakno

Faculty of Electrical and Electronic
correspond author: ikhwanr@ump.edu.my

Power factor

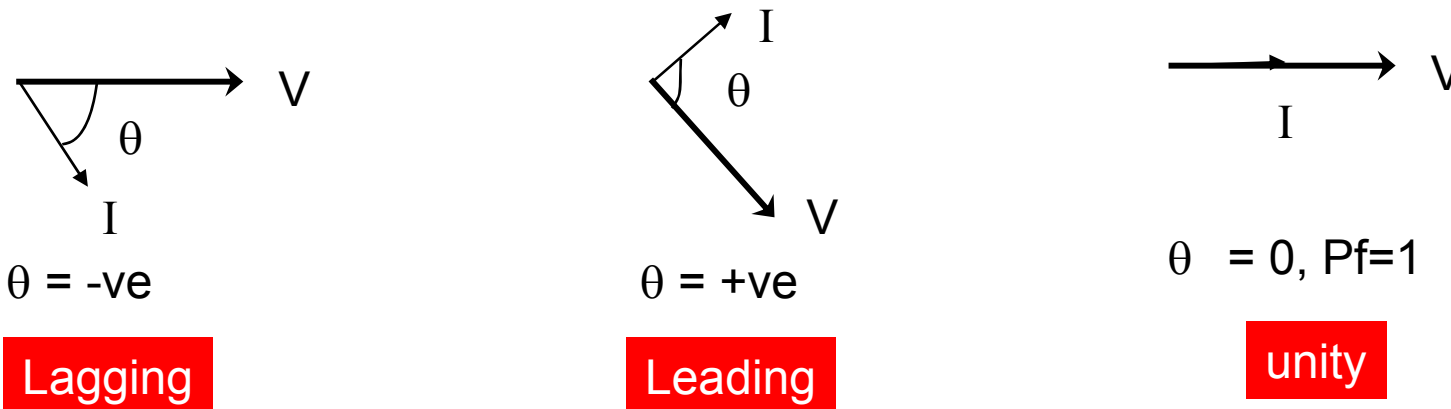Power factor = angle between voltage and current, $\cos \theta$.



For real power transformer, the power factor is always lagging

Transformer Efficiency

$$\begin{aligned}\eta &= \frac{P_{out}}{P_{in}} \times 100\% \\ &= \frac{P_{out}}{P_{out} + P_{losses}} \times 100\% \\ &= \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + P_c + P_{cu}} \times 100\%\end{aligned}$$

$$* P_c = V_1^2 / R_C$$

$$* P_{Cu} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{eq,1} = I_2^2 R_{eq,2}$$

$$\begin{aligned}\eta_{(full\ load)} &= \frac{VA \cos \theta}{VA \cos \theta + P_c + P_{cu}} \times 100\% \\ \eta_{(load\ n)} &= \frac{nVA \cos \theta}{nVA \cos \theta + P_c + n^2 P_{cu}} \times 100\%\end{aligned}$$

Where, if 1/2 loaded, hence $n = 1/2$,
1/3 loaded, $n = 1/3$,
90% of full load, $n = 0.9$

Voltage Regulation

- To measure voltage drop between no load and full load

$$V.R = \frac{V_{S,NL} - V_{S,FL}}{V_{S,NL}} \times 100\%$$

$$V.R = \frac{V_P - aV_S}{aV_S} \times 100\%$$


$$V.R = \frac{V_P/a - V_{S,FL}}{V_{S,FL}} \times 100\%$$

Measurement for Transformer

- Two type of tests
- The tests are conducted to determine the parameters of the transformer.
 - Open circuit test
 - Short circuit test



Open Circuit Test For Transformer

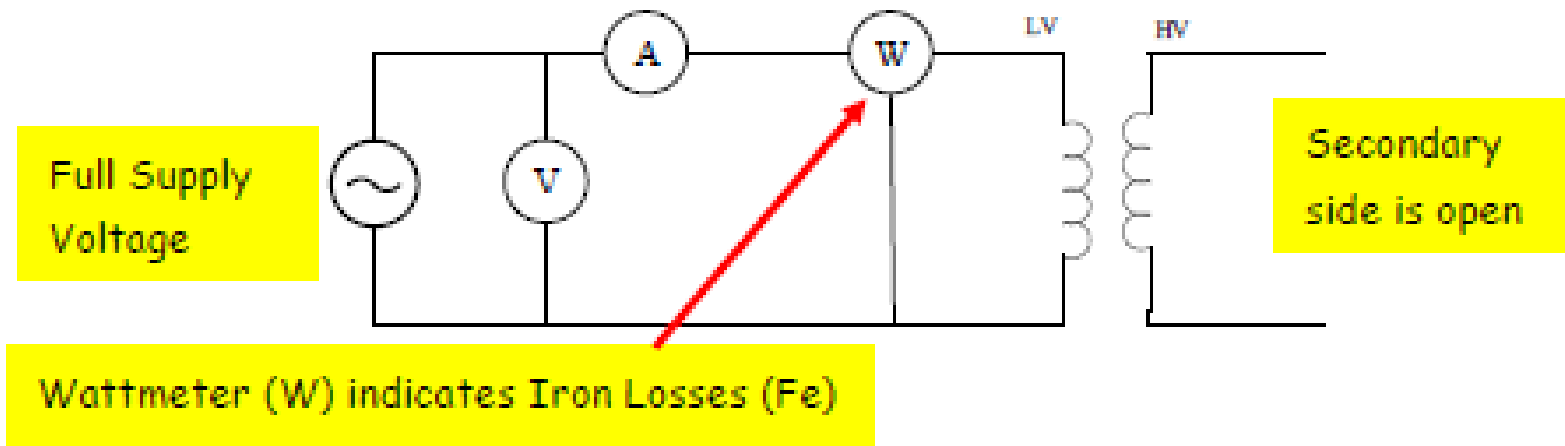- Open circuit test is conducted to determine magnetism parameters, R_c and X_m
- Measurements are at high voltage side – transformer's secondary winding is open-circuited.



Open Circuit Test

From a given test parameters

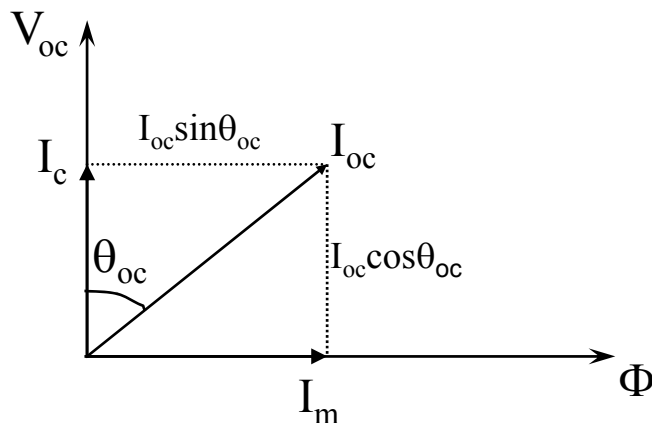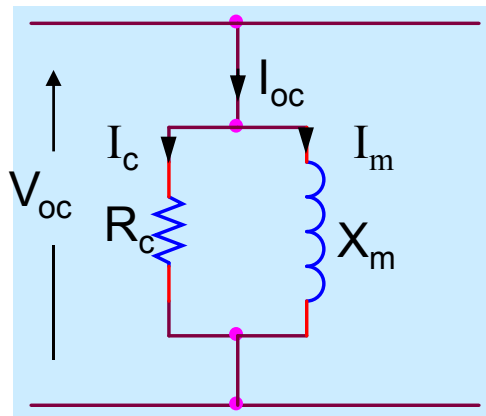

Magnitude of the excitation admittance branch :

$$|Y_{oc}| = \frac{I_{oc}}{V_{oc}}$$

The angle of admittance :

$$PF = \cos \theta_{oc} = \frac{P_{oc}}{V_{oc} I_{oc}}$$

PF angle :

$$\theta_{oc} = \cos^{-1} \left(\frac{P_{oc}}{V_{oc} I_{oc}} \right)$$

PF always lagging for the real transformer :


$$\begin{aligned} |Y_{oc}| &= \frac{I_{oc}}{V_{oc}} \angle -\theta \\ &= \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1} PF \end{aligned}$$

Thus the complex admittance can be expressed as,

$$|Y_{oc}| = |Y_{oc}| \angle -\theta = G_c - jB_M = \frac{1}{R_c} - j \frac{1}{X_M}$$

Short Circuit Test For Transformer

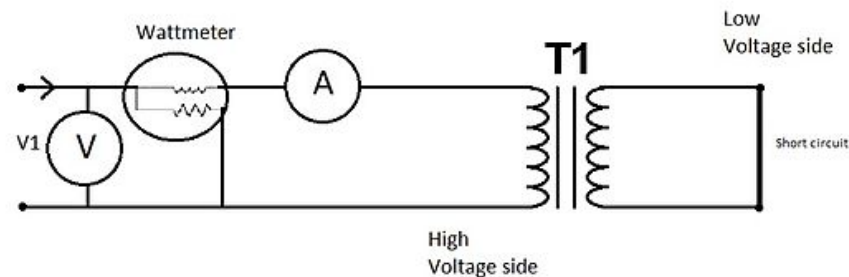- The short circuit test is for determine the copper parameters based on which side it test. If the test is at primary, hence the parameters are R_{01} and X_{01} and vice-versa.
- If the given test parameters are taken on primary side, R_{01} and X_{01} will be obtained. Or else, vice-versa.




Source: https://commons.wikimedia.org/wiki/File:Short_Circuit_test.jpg



Short Circuit Test

From a given test parameters

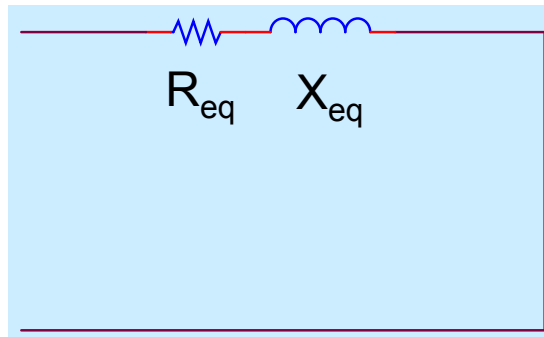

For a case referred to
Primary side

The magnitude of the series impedance :

$$|Z_{SE}| = \frac{V_{SC}}{I_{SC}}$$

The power factor of the current :

$$PF = \cos \theta = \left(\frac{P_{SC}}{V_{SC} I_{SC}} \right)$$

The current angle :

$$\theta = \cos^{-1} \left(\frac{P_{SC}}{V_{SC} I_{SC}} \right)$$

Therefore ,

$$|Z_{SE}| = \frac{V_{SC} \angle 0^\circ}{I_{SC} \angle -\theta^\circ} = \frac{V_{SC}}{I_{SC}} \angle 0^\circ$$

The series impedance :

$$\begin{aligned} Z_{SE} &= R_{eq} + jX_{eq} \\ &= (R_p + a^2 R_s) + j(X_p + a^2 X_s) \end{aligned}$$

1.3 THREE-PHASE TRANSFORMER

Introduction

- Most of utility company use 3-phase systems for generation, transmission and distribution
- The main advantages:
 - It occupies less floor space for equal rating.
 - Weighs less.
 - Costs about 15% less, and further.



Three-phase transformer bank




Source: https://commons.wikimedia.org/wiki/File:37.5kVA_three_phase_utility_stepdown.jpg


Construction

- The transformer can be constructed in two form:

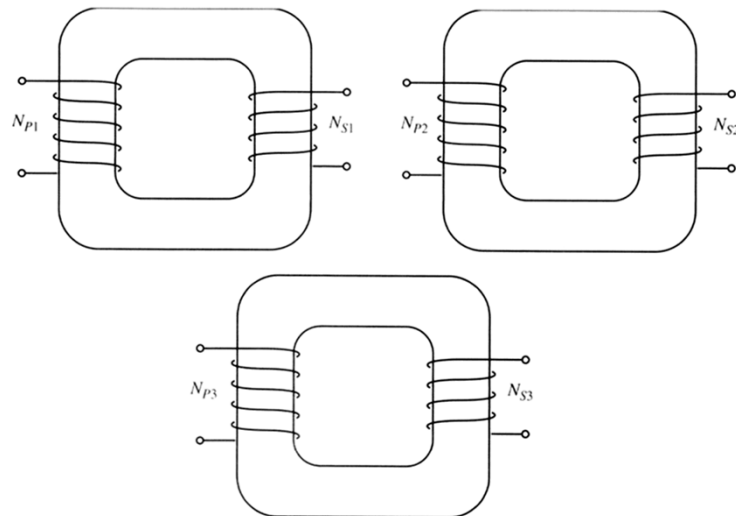3-phase of independent identical transformers



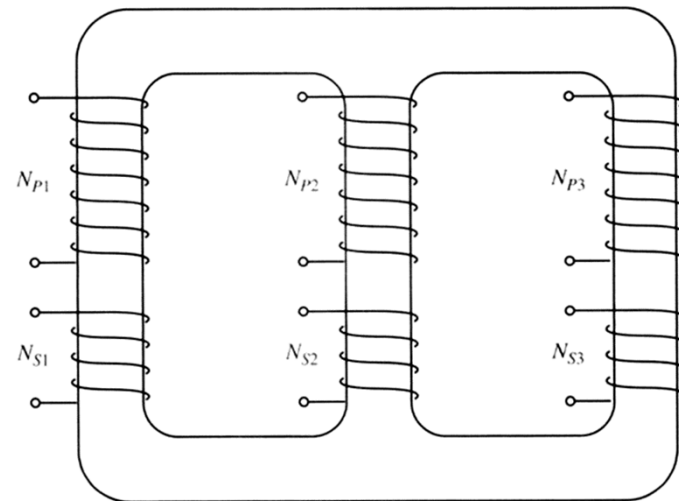
Single transformer wound with single 3-legged core



Source: <http://machineryequipmentonline.com/electric-equipment/transformersthree-phase-transformers/>

Connection Technique

- Two possible connection technique are:

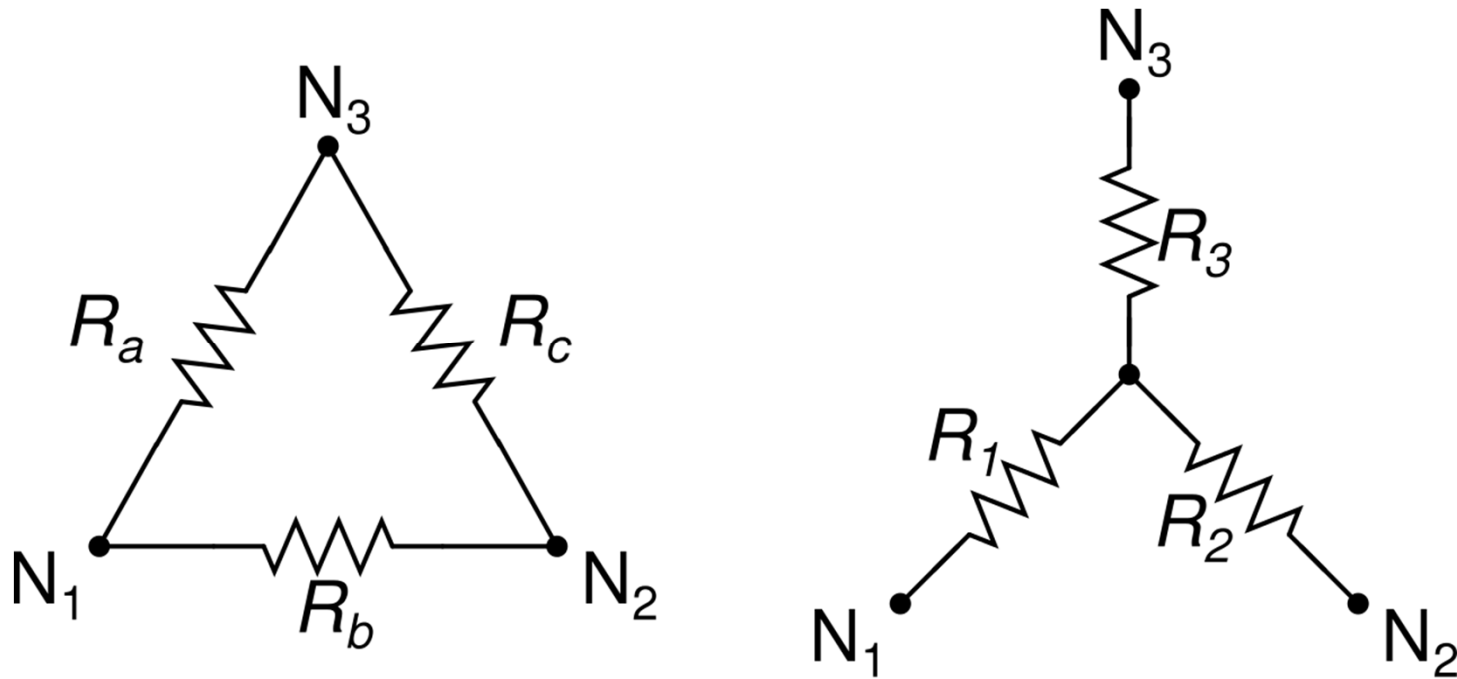


Source: wikipedia



Delta Winding Connection

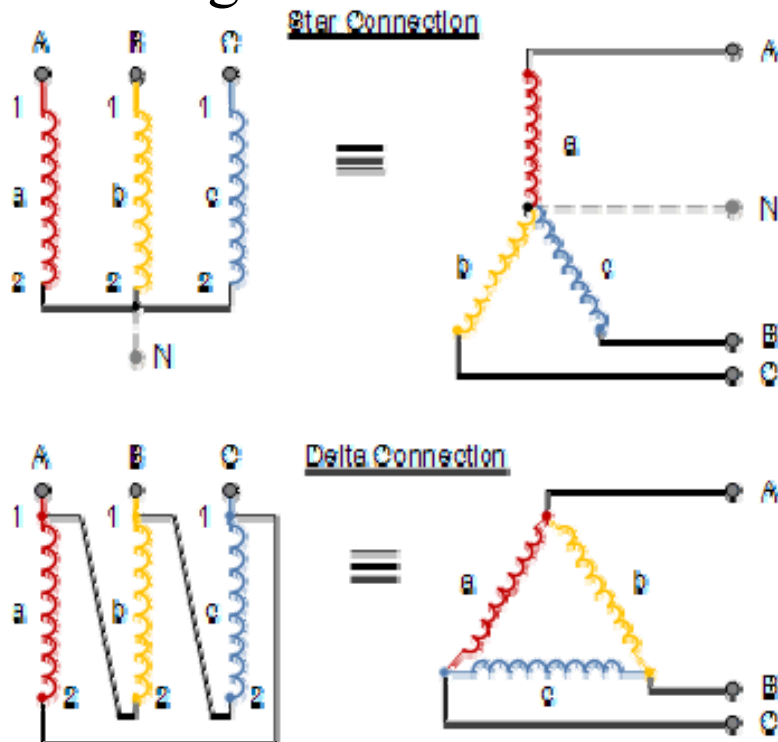- Each windings are constructed by connecting each end of a winding to a different winding.




Voltage across a delta winding = line voltage
Current in a delta winding = $\frac{\text{Line current}}{\sqrt{3}}$

Source: <http://www.electronics-tutorials.ws/transformer/three-phase-transformer.html>

Star Winding Connection

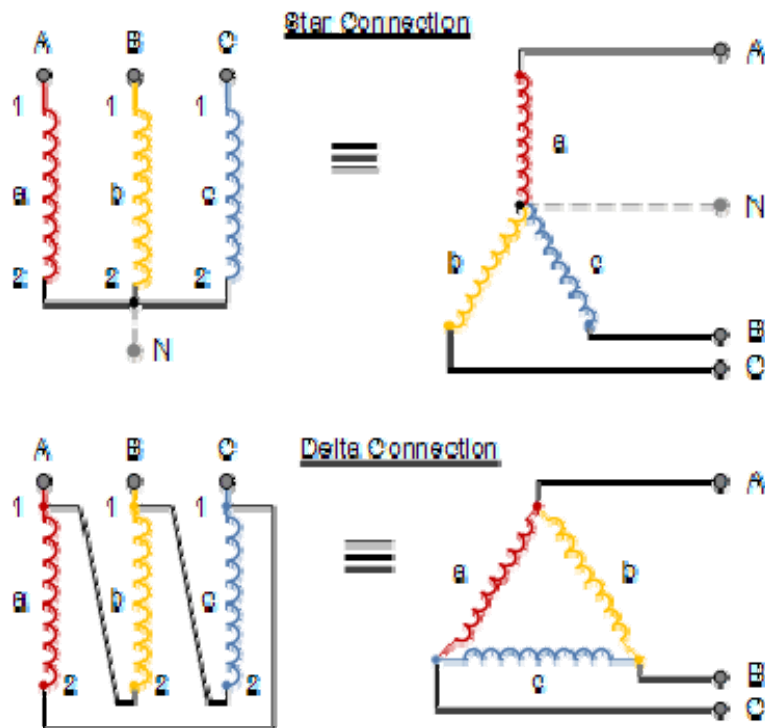- Star connected windings are constructed by connecting one end of each winding together.




$$\text{Voltage across a delta winding} = \frac{\text{Line voltage}}{\sqrt{3}}$$

Current in a delta winding = line current

Source: <http://www.electronic-tutorials.ws/transformer/three-phase-transformer.html>


Connection Type

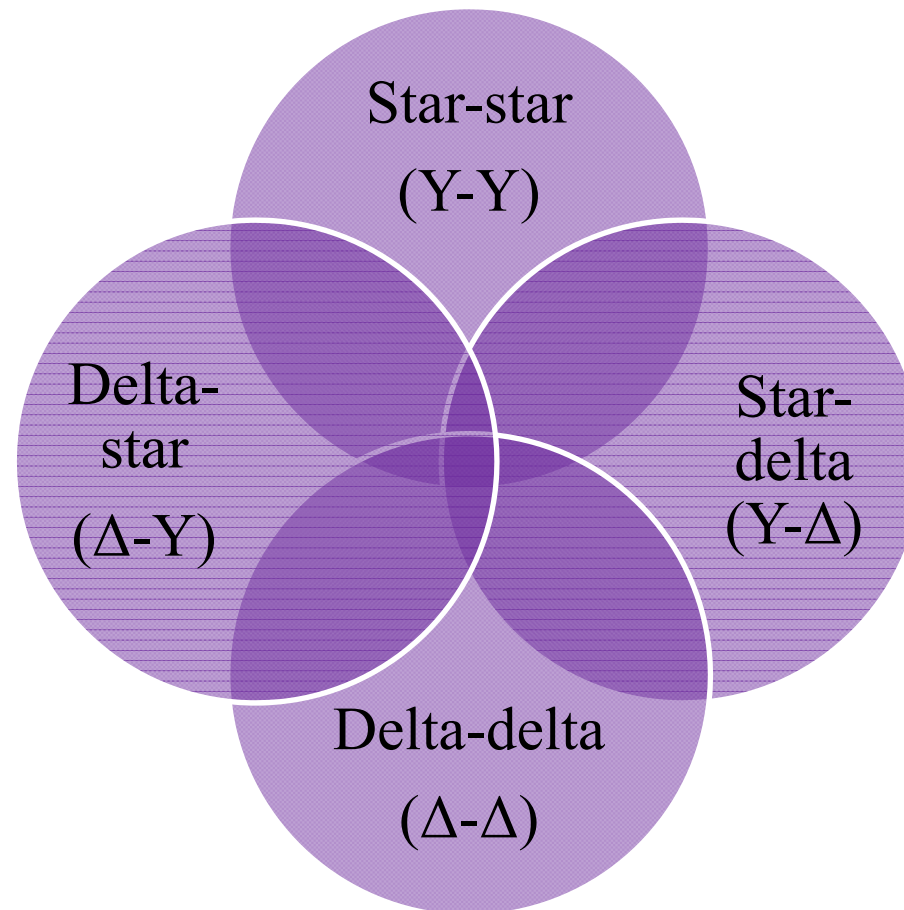Four possible connections for three phase transformer:



Star-star (Y-Y) Connection

$$V_{\phi P} = \frac{V_{LP}}{\sqrt{3}}$$

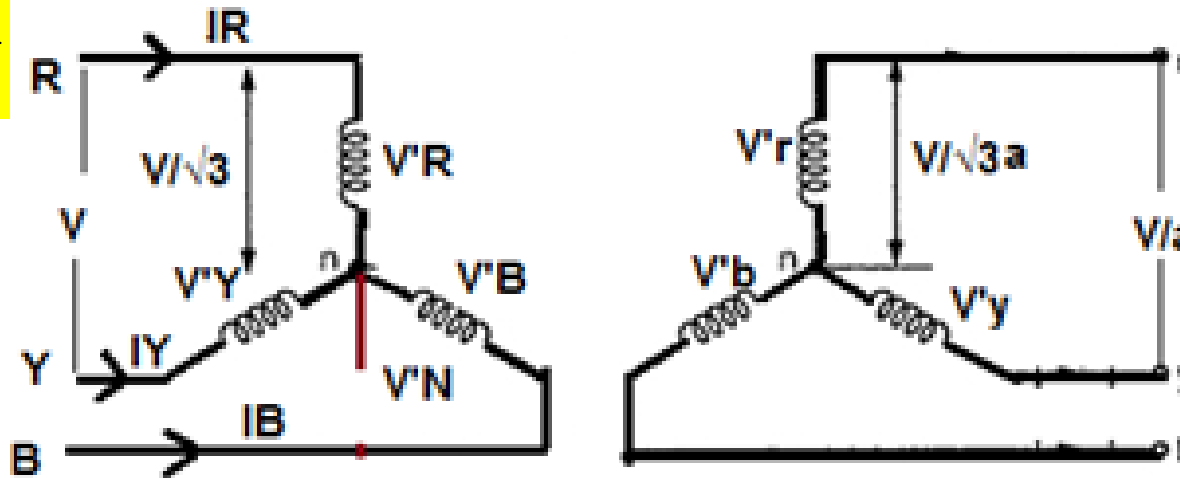

$$V_{LS} = \sqrt{3}V_{\phi S}$$

Source: <https://electricalnotes.wordpress.com/2012/04/30/star-star-connection-of-transformer/>

- × $V_{\phi S}$ = secondary-phase voltage
- × V_{LP} = primary-line voltage
- × V_{LS} = secondary-line voltage

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{\sqrt{3}V_{\phi S}} = a$$

Star-star (Y-Y) Connection


Advantages

- Economic: less number of turns and quantity of insulation.
- The windings able to handle heavy loads and short circuit.


Disadvantages

- Unbalanced voltage.
- The presence of third harmonic voltage.

Star-delta (Y-Δ) Connection

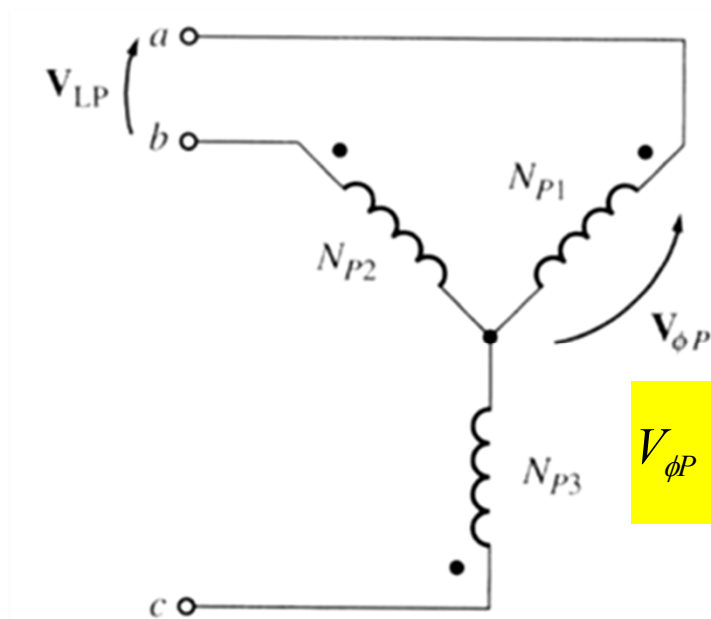

$$V_{\phi P} = \frac{V_{LP}}{\sqrt{3}}$$

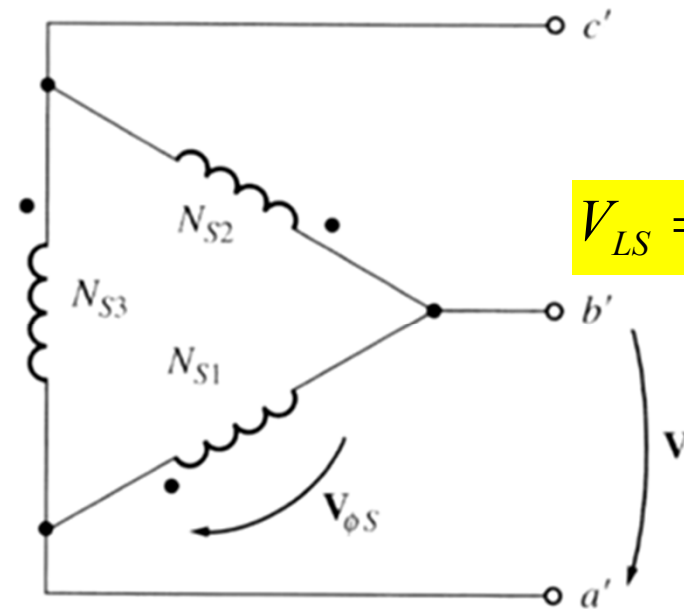

$$V_{LS} = V_{\phi S}$$

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{V_{\phi S}} = \sqrt{3}a$$

Star-delta (Y- Δ) Connection


Advantages

- Economic: less number of turns and quantity of insulation.
- No third harmonic voltage problem.
- Stable with respect to unbalanced load.

Disadvantages

- The secondary voltage is shifted 30° from the primary one.

Delta-delta (Δ - Δ) CONNECTION

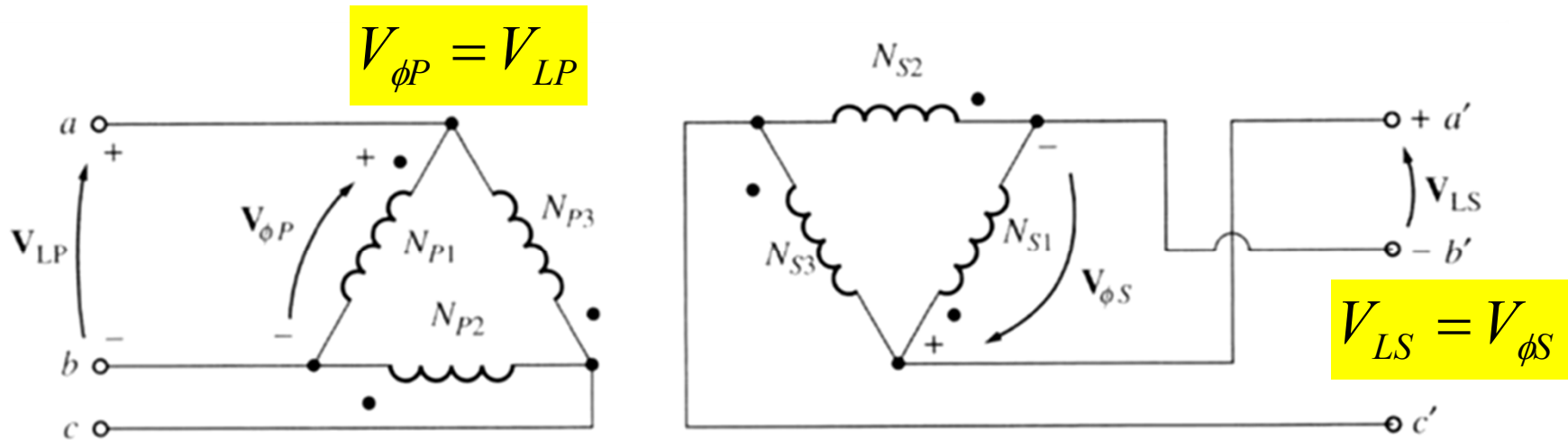

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a$$

Delta-delta (Δ - Δ) CONNECTION

Advantages


- Economic: cross-section of the winding is low.
- No third harmonic voltage problem.
- Stable with respect to unbalanced load.

Disadvantages

- It is not possible for 3-phase four wire system because neutral point is absent.

Delta-star ($\Delta - y$) Connection

$$V_{\phi P} = V_{LP}$$

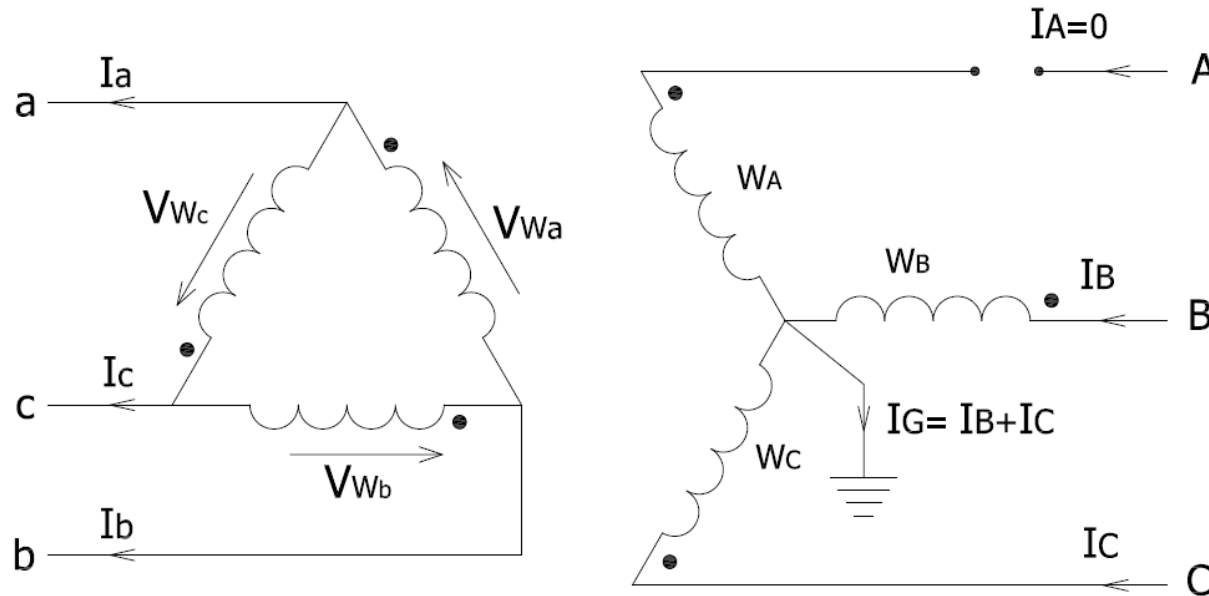

$$V_{LS} = \sqrt{3}V_{\phi S}$$

Fig. 9. Open Phase in a $Y_g - \Delta$ Transformer

Source: <http://generalpac.com/transformers/open-phase-condition-in-transformers>

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{\sqrt{3}V_{\phi S}} = \frac{\sqrt{3}}{a}$$

Delta-star (Δ -y) Connection

Advantages

- No third harmonic voltage problem.
- Stable with respect to unbalanced load.

Disadvantages

- The secondary voltage is shifted 30° from the primary one.

Applications

CONNECTION TYPES	APPLICATIONS
STAR-STAR	Most economical for small high voltage transformers
STAR-DELTA	Commonly used in a step-down transformer (i.e. employed at the substation)
DELTA-DELTA	Suitable for large, low voltage transformers
DELTA-STAR	Commonly used in a step-up transformer (i.e. at the beginning of a HT transmission line)

Mohd Ikhwan Muhammad Ridzuan, PhD
Faculty of Electrical and Engineering
Universiti Malaysia Pahang
ikhwanr@ump.edu.my

Research interest: Reliability, Distribution
network, smart grid, risk asesment