

# DEE 3143 BASIC ELECTRICAL MACHINE & POWER SYSTEMS

## CHAPTER 3 DIRECT CURRENT MOTOR


by

Mohd Ikhwan Muhammad Ridzuan, Norhafidzah Mohd Saad, Marlina Yakno

Faculty of Electrical and Electronic  
correspond author: [ikhwanr@ump.edu.my](mailto:ikhwanr@ump.edu.my)


## 2.3 PRINCIPLES OF OPERATION

# DC Motor Operation

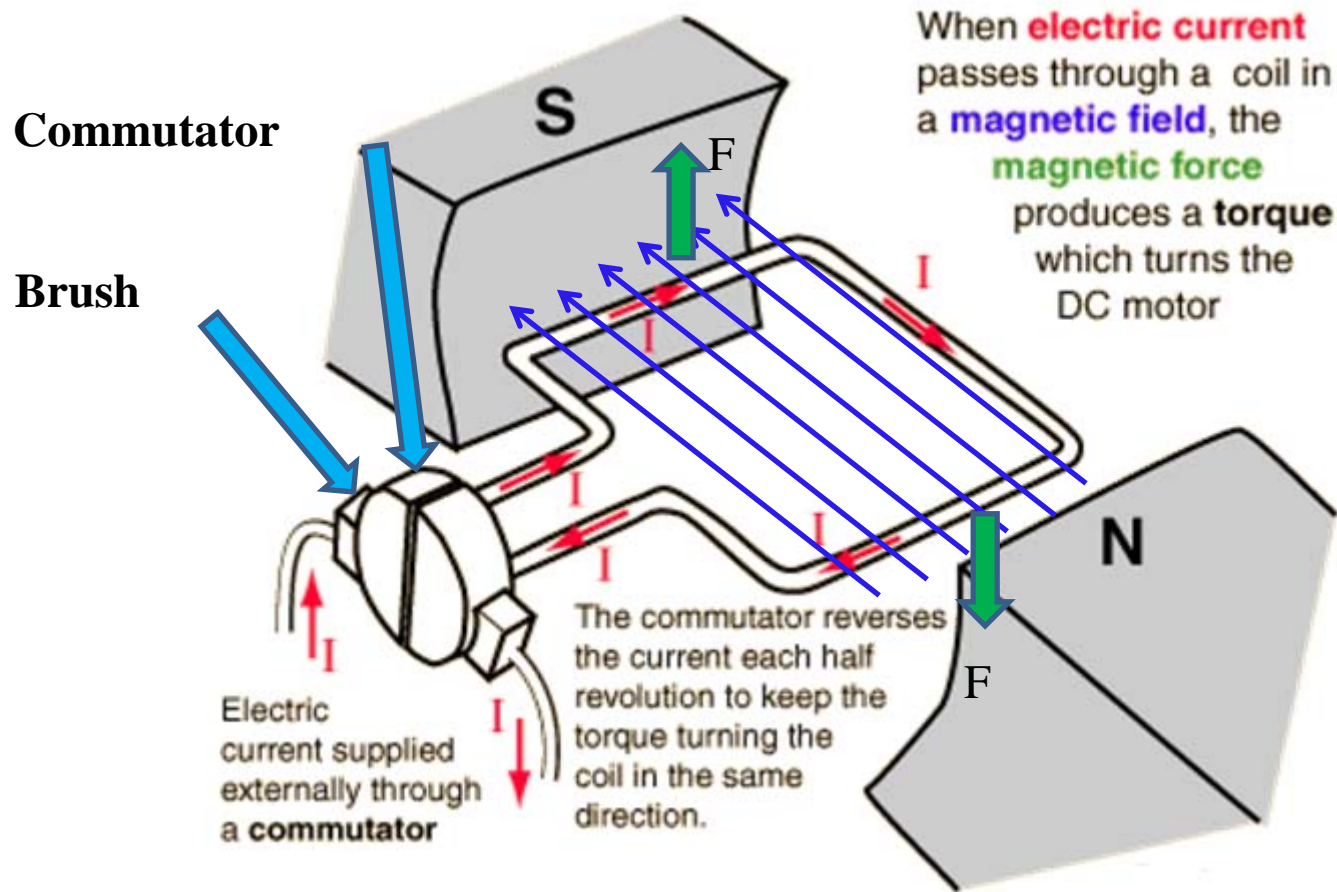

Source: <http://hyperphysics.phy-astr.gsu.edu/hbase/magnetic/motdc.html>

# Fleming left hand rule

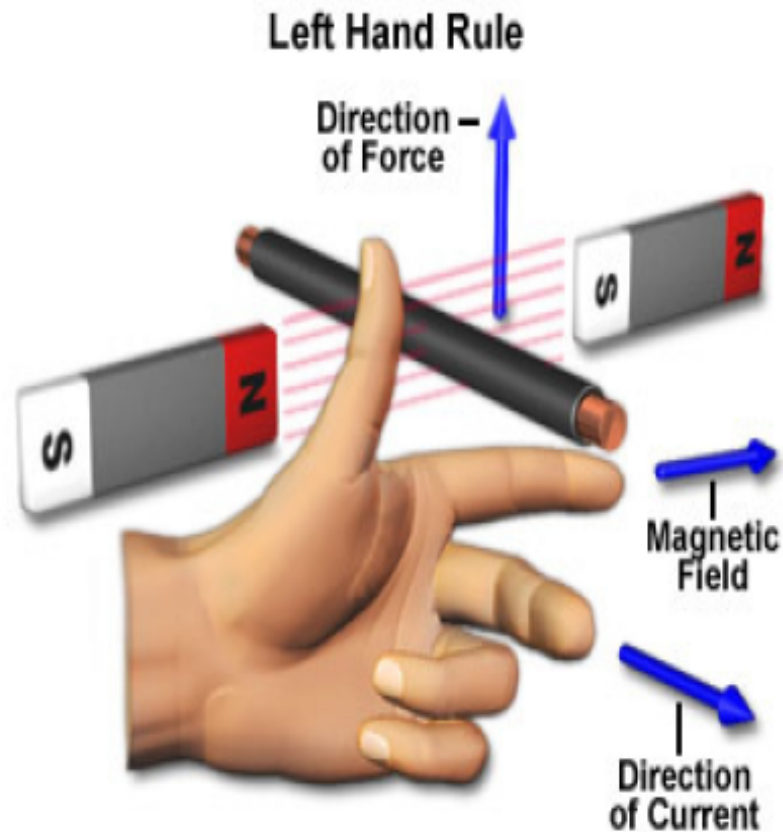

Magnitude of force in motor:

$$F = B l I \text{ (N)}$$

$B$  = flux density due to the flux produced by the field winding

$l$  = length of the conductor

$I$  = magnitude of the current passing through conductor

Source: <https://www.electrical4u.com/fleming-left-hand-rule-and-fleming-right-hand-rule/>

# Back EMF

- An EMF induced due rotational of coil within magnetic field, which the flux field changes at different positions
- The EMF induced in several coils:

$$E_a = \frac{\phi ZNP}{60a} = V - I_a R_a$$

- Ø Flux per pole
- Z no of conductors in the armature
- P no of poles
- a no of parallel paths
- N speed of the motor
- V supply voltage
- I<sub>a</sub> Armature current
- R<sub>a</sub> Armature resistance

# Developed torque

- The force acting on the rotor:  $F = il \times B$
- The rotor rotates at a speed of N rpm, so the angular speed of the rotor:

$$\omega_m = \frac{2\pi N}{60} \text{ rad / sec}$$

- Current in a single conductor is:

$$I_{cond} = \frac{I_a}{a}$$

- The total induced torque is:


$$\tau_{ind} = \frac{ZP\phi I_a}{2\pi a} = K\phi I_a \quad \text{where } K = \frac{ZP}{2\pi a}$$

- The mechanical power generated is:

$$P_{dev} = E_a I_a \\ = \tau \omega_m$$

## 2.4 TYPES OF DC MOTOR

# DC Motor (Equivalent circuit)

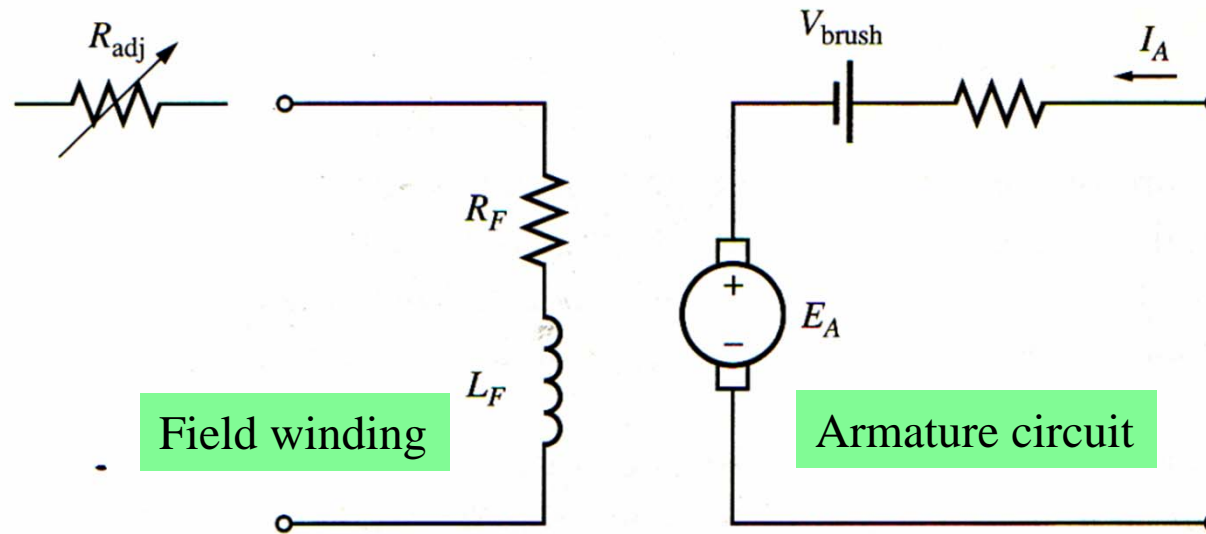


Source: <https://amornsak.co/diagrams/permanent-magnet-dc-motor-equivalent-circuit-diagram>.

- ×  $E_A$  = voltage source of armature circuit
- ×  $R_A$  = resistor for armature circuit
- ×  $V_{brush}$  = brush voltage drop
- ×  $L_F$  = inductor of field winding
- ×  $R_F$  = resistor of field winding
- ×  $R_{adj}$  = external variable resistor


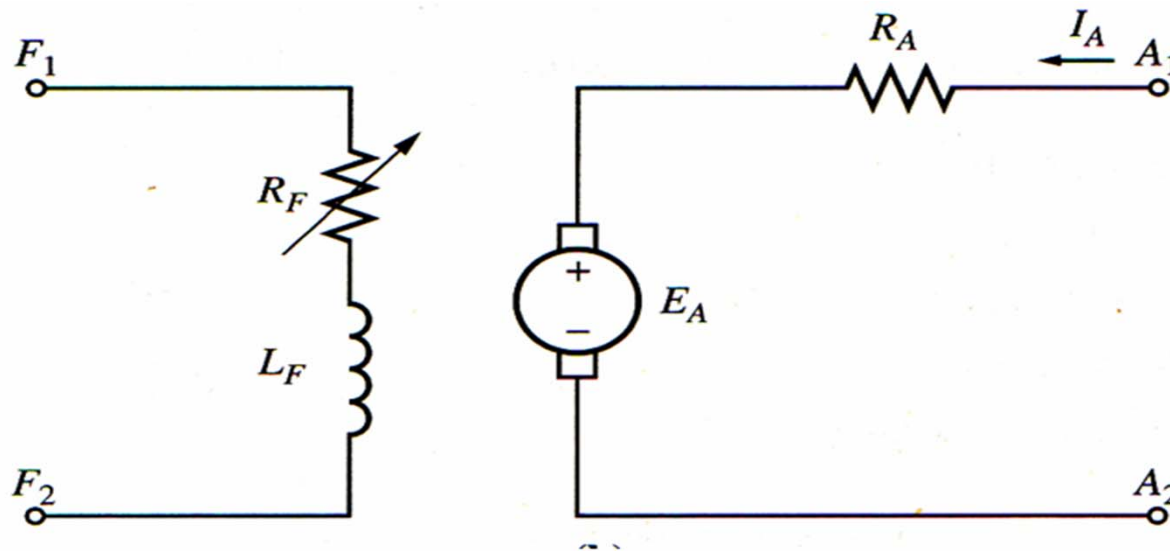
# Simplified Equivalent circuit of dc motor

- Some variation and simplifications can be made:
  - $V_{brush}$  may be left out ( $V_{brush} \ll E_A$ ) or included in  $R_A$
  - The total of  $R_F$  and  $R_{adj}$  is called variable resistor,  $R_F$



internal voltage :

$$E_A = K\phi\omega$$


induced torque :

$$\tau_{ind} = K\phi I_A$$

Source: <https://amornsak.co/diagrams/permanent-magnet-dc-motor-equivalent-circuit-diagram.php>

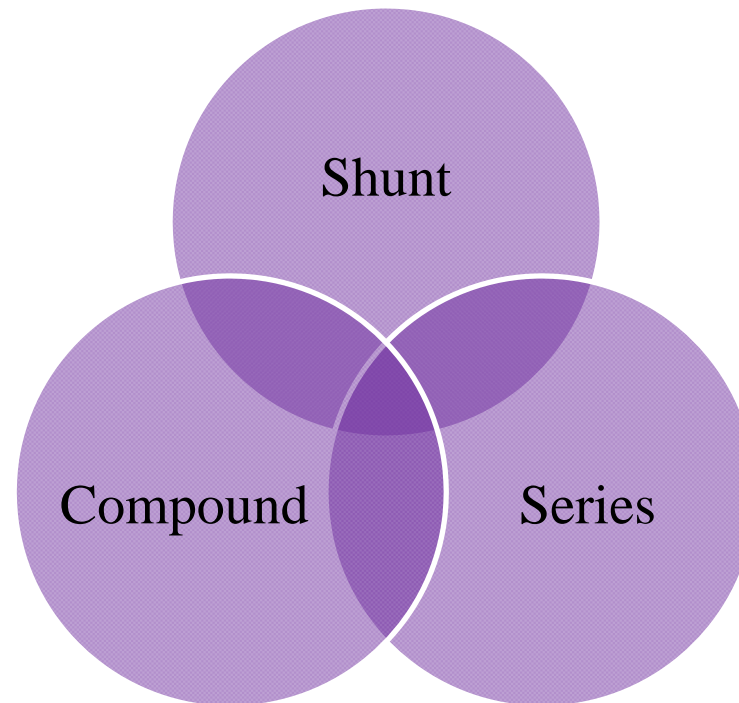
# Types of DC Motor

- DC motor can be classified according to the electrical connections of the armature winding and the field windings.
- There are three major types of dc motor in general use:


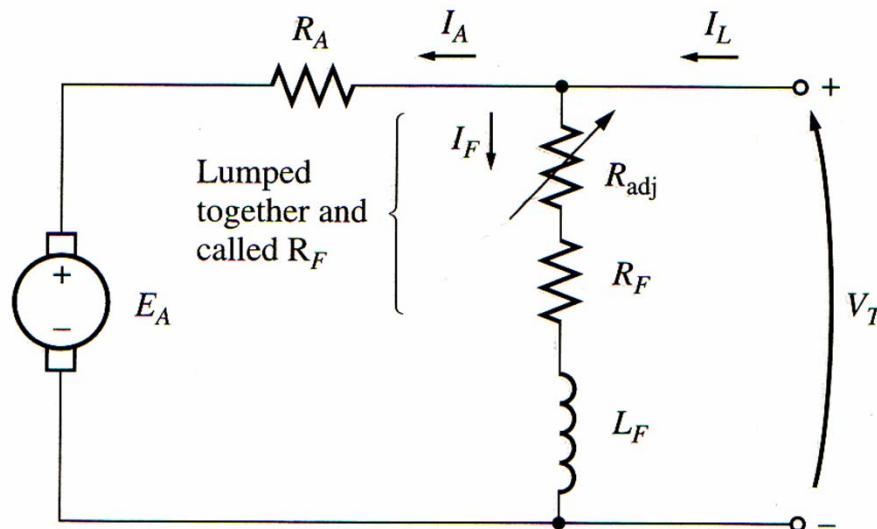
# Shunt DC Motor


- The armature and field winding are modelled in **parallel** configuration.



$$I_F = \frac{V_T}{R_F}$$
$$I_L = I_A + I_F$$
$$V_T = E_A + I_A R_A$$

Source: <https://www.quora.com/How-does-a-DC-shunt-motor-work-and-what-causes-it-to-decrease-the-voltage-when-load-is-increased>

# Speed-torque Characteristic

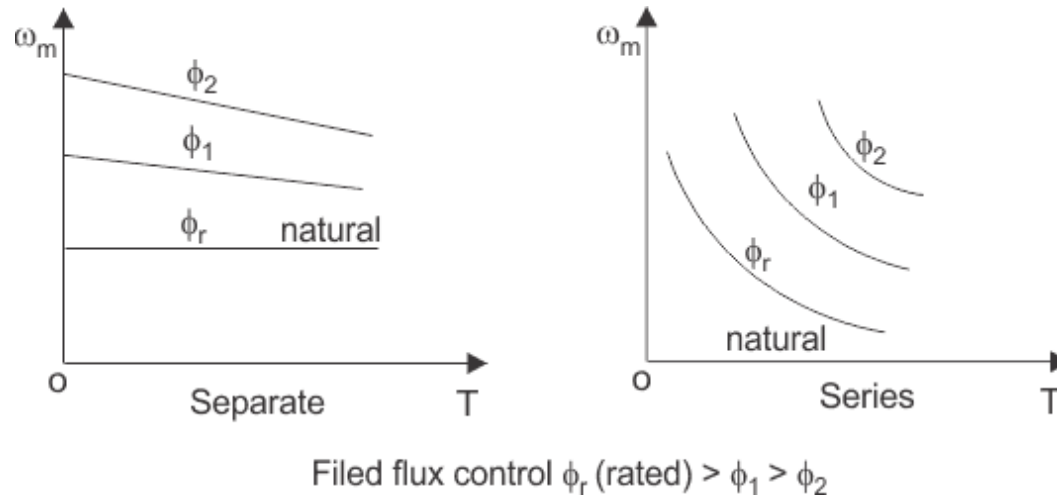

From derivation of induced voltage and torque equations, motor speed is:


$$\omega = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{ind}$$

Source: <https://www.electrical4u.com/dc-motor-drives/>

- *As the load torque increases the speed falls somewhat, but the machine may be regarded as an approximately constant speed motor*
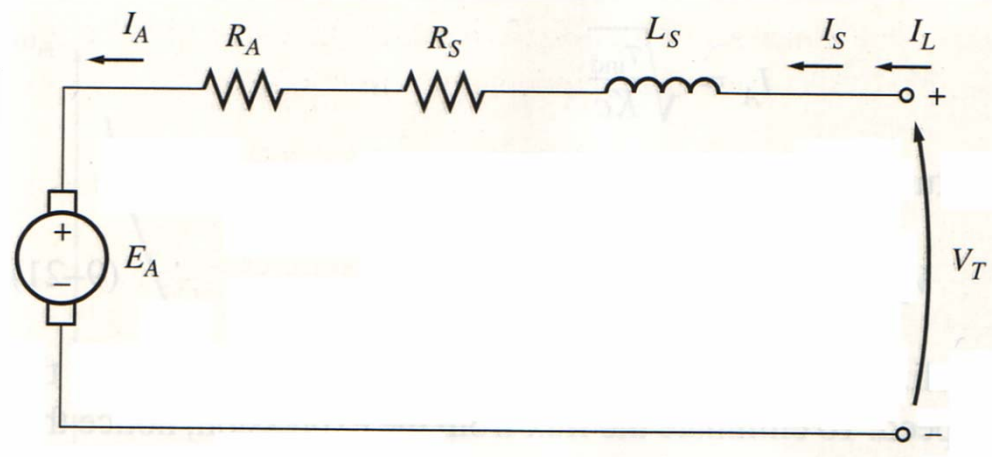
# DC Motor Series

- Armature winding and field winding are modelled in **series configuration**.
- Current in field winding and armature winding are the same.




$$V_T = E_A + I_A (R_A + R_S)$$

$$I_L = I_A = I_S$$

Source: <http://aliveandbloggin.com/dc-series-motor-wiring-diagram.html>
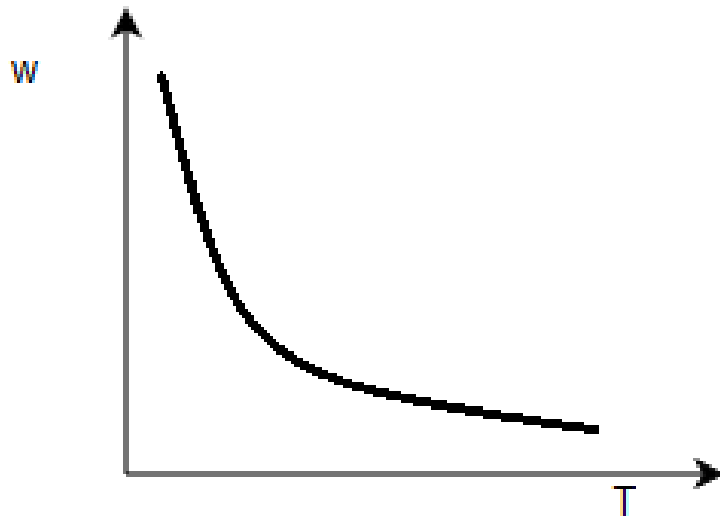
# Speed-torque Characteristic

Source: <http://www.sanfoundry.com/electrical-machines-questions-answers-operating-characteristics-dc-motor/>



- *As the load torque increases the speed falls rapidly.*
- *For no load connected to the motor, it can seriously damage the motor (due to high speed)*

- Different from shunt motor: Flux in series motor is directly proportional to the armature current.

- Induced torque is:


$$\tau_{ind} = K\phi I_a = KcI_a^2$$

- From derivation of induced voltage and torque equations, motor speed is :

$$\omega = \frac{V_T}{Kc} \frac{1}{\sqrt{\tau_{ind}}} - \frac{R_A + R_S}{Kc} \tau_{ind}$$
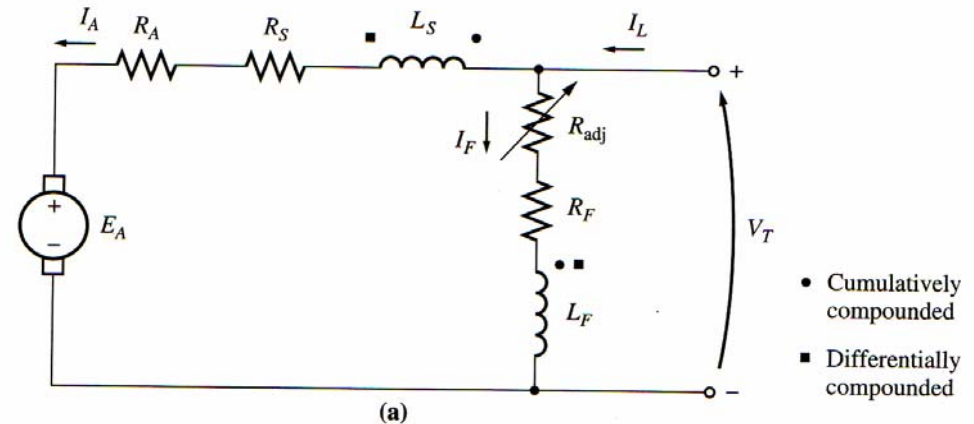
# DC Motor Compound

- Compounded DC motor consist of motor with a shunt and a series field.
- Two types of arrangements in compound motors.
  - Cumulative compound - Magnetic fluxes produced by series and shunt field windings are in the same direction.
  - Differential compound - two fluxes are in opposition direction.




$$V_T = E_A + I_A (R_A + R_S)$$

$$I_A = I_L - I_S$$

$$I_F = \frac{V_T}{R_F}$$

Source: <http://aliveandbloggin.com/dc-series-motor-wiring-diagram.html>

# Speed-torque characteristic

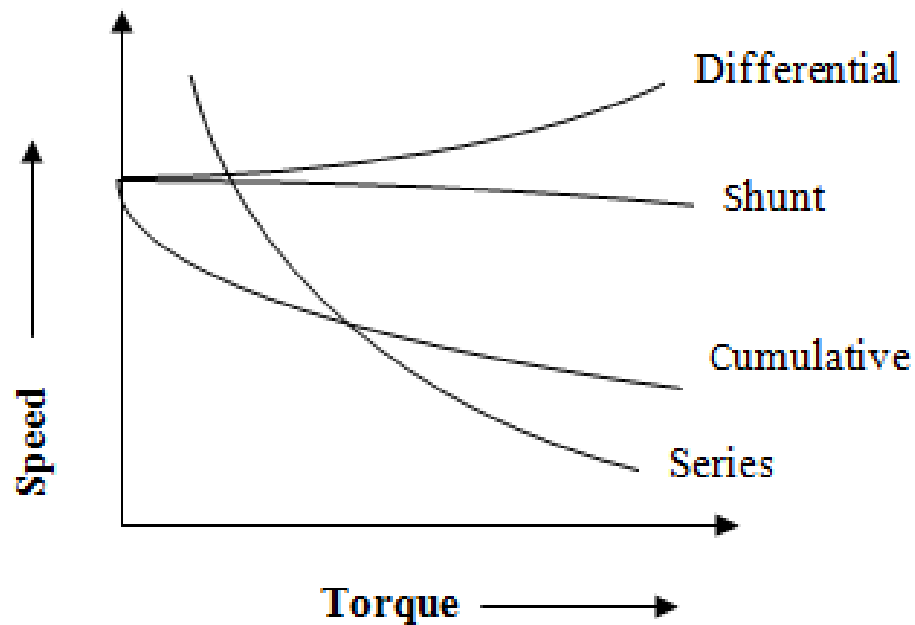


**Cumulative:** The *speed falls appreciably as the torque increases* but on low torques the maximum speed is limited to a safe value.

Source: <https://www.quora.com/What-will-be-the-torque-of-DC-motor-above-its-base-speed>



# Speed-torque Characteristic

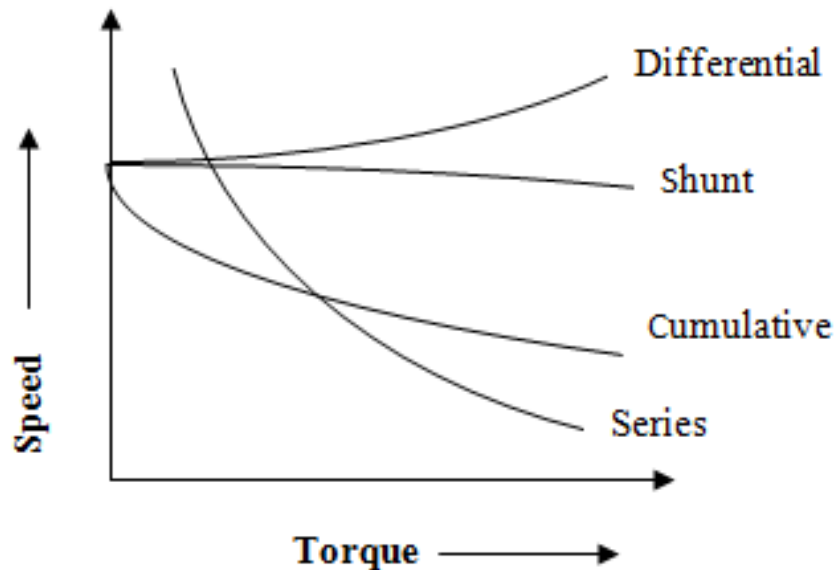


- **Differential:** The *speed at low torque is limited by the shunt winding as in the cumulative compound machine.*
- At high torques, the speed may be arranged to remain constant or with *stronger series field, the speed may rise with increasing load.*

Source: <https://www.quora.com/What-will-be-the-torque-of-DC-motor-above-its-base-speed>

## 2.5 POWER FLOW DIAGRAM

# Losses in DC Motor

- 5 types of losses in DC motor:

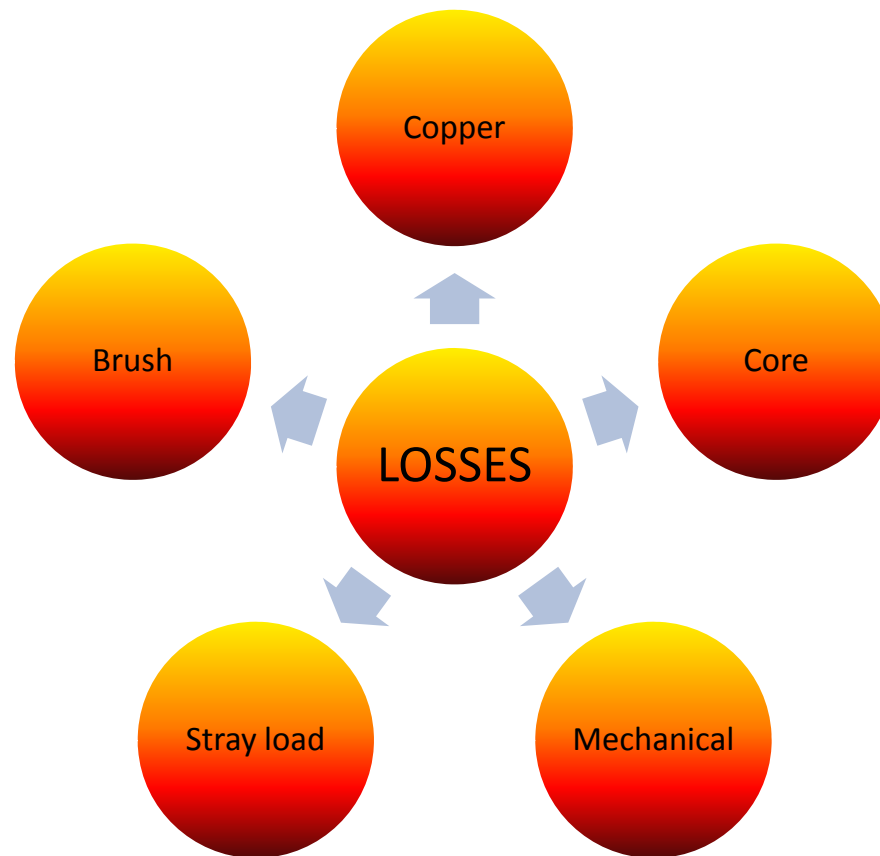

# Power losses

## Core losses

- Consists of hysteresis and eddy current losses


## Mechanical losses

- The losses that related with mechanical effects: friction & windage. Friction losses - friction of the bearings in the machine. Windage - friction between the moving parts of the machine and the air inside the motor casing's.

## Stray (miscellaneous) losses

- Unknown categories.

# Power flow diagram

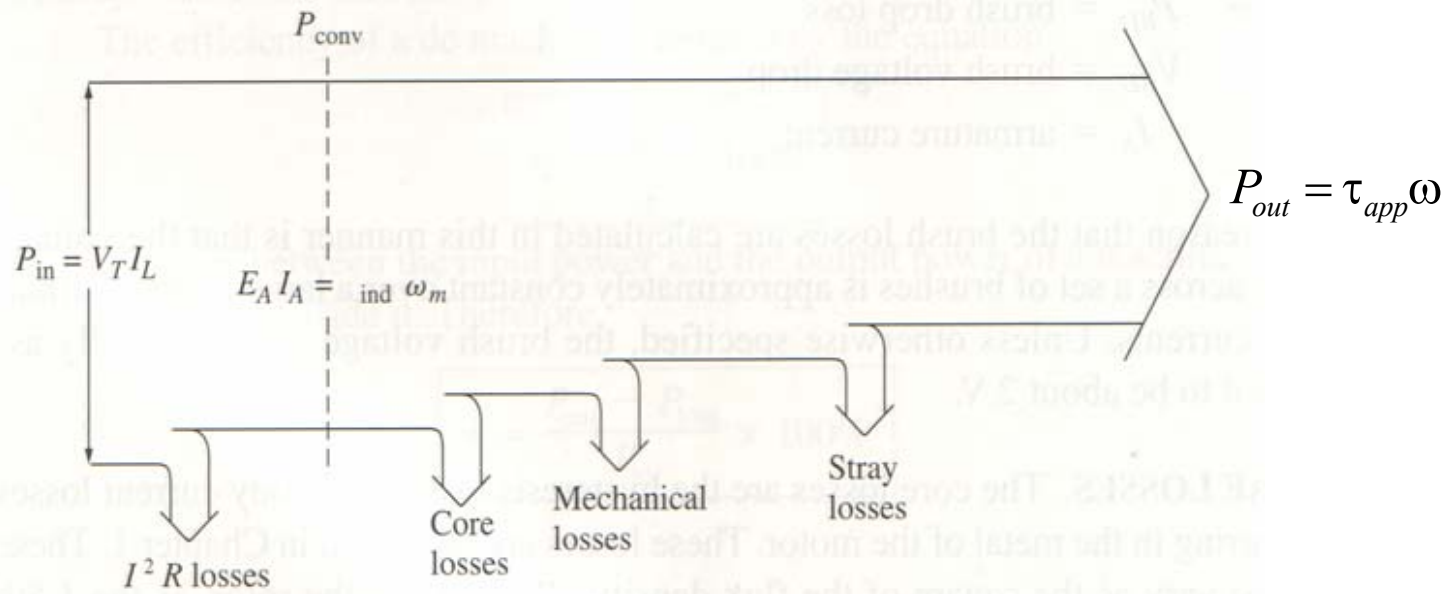

Source: <https://www.slideshare.net/abhinaypotlabathini/chapter-4-dc-machine-autosaved>

- Copper losses:

$$P_{cu} = P_{cu,A} + P_{cu,F}$$

$$P_{cu,A} = I_A^2 R_A$$

$$P_{cu,F} = I_F^2 R_F$$

- Mechanical losses:

$$P_{mech} = P_{fric} + P_{windage}$$

# Formulation of Performances

- Efficiency

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$P_{in} = V_T I_L$$

$$P_{out} = P_{in} - P_{loss}$$

$$P_{loss} = P_{cu} + P_{core} + P_{mech} + P_{stray}$$

- Induced torque

$$\tau_{ind} = \frac{P_{conv}}{\omega}$$

$$P_{conv} = E_A I_A, \quad E_A = K\phi\omega$$

$$P_{conv} = P_{in} - P_{cu}$$

# Formulation of Performances

- Output torque or load torque

$$\tau_{out} = \tau_{load} = \frac{P_{out}}{\omega}$$

- Speed regulation

$$SR = \frac{\omega_{nl} - \omega_{fl}}{\omega_{fl}} \times 100\%$$

$$SR = \frac{n_{nl} - n_{fl}}{n_{fl}} \times 100\%$$

## 2.6 SPEED CONTROL



# Speed control

- The techniques of controlling DC motor speed:

## Shunt, compounded DC motors

- Changing the field resistance
- Changing the armature voltage
- Adding a resistance in armature circuit (designed in series connection)

## Series DC motor

- Adjusting the armature voltage


# Speed control of Shunt DC motor

- **CHANGING FIELD RESISTANCE:**

Increasing $R_F$ causes $I_F$ to decrease	$I_F \downarrow = V_T / R_F \uparrow$
Decreasing $I_F$ decrease $\phi$	
Decreasing $\phi$ lowers $E_A$ instantaneously	$E_A \downarrow = K\phi \downarrow \omega$
Decreasing $E_A$ causes $I_A$ to increase	$I_A \uparrow = (V_T - E_A \downarrow) / R_A$
Increasing $I_A$ , increase $\tau_{ind}$	$\tau_{ind} = K\phi \downarrow I_A \uparrow$
Increasing $\tau_{ind}$ causes $\tau_{ind} > \tau_{load}$ hence motor speeds up, $\omega$	
Since $\omega$ increase, $E_A$ increase again	$E_A \uparrow = K\phi \omega \uparrow$
Increasing $E_A$ causes $I_A$ to decrease	$I_A \downarrow = (V_T - E_A \uparrow) / R_A$
Decreasing $I_A$ , causes $\tau_{ind}$ decrease until $\tau_{ind} = \tau_{load}$ at higher speed $\omega$	$\tau_{ind} \downarrow = K\phi I_A \downarrow$

# Speed control of Shunt dc motor

- *CHANGING THE FIELD RESISTANCE:*

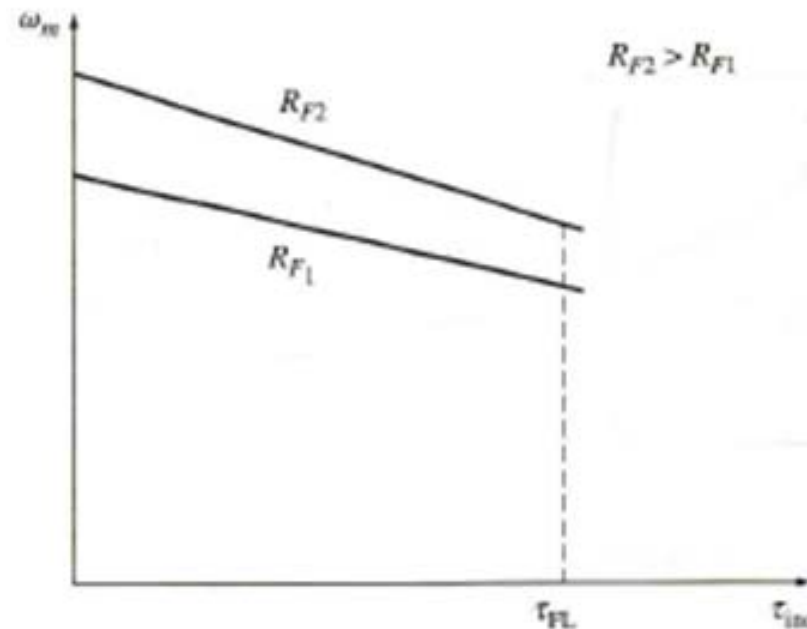


Source: <http://slideplayer.com/slide/4773410/>

Effect of field resistance speed control for a shunt motor's torque-speed characteristics
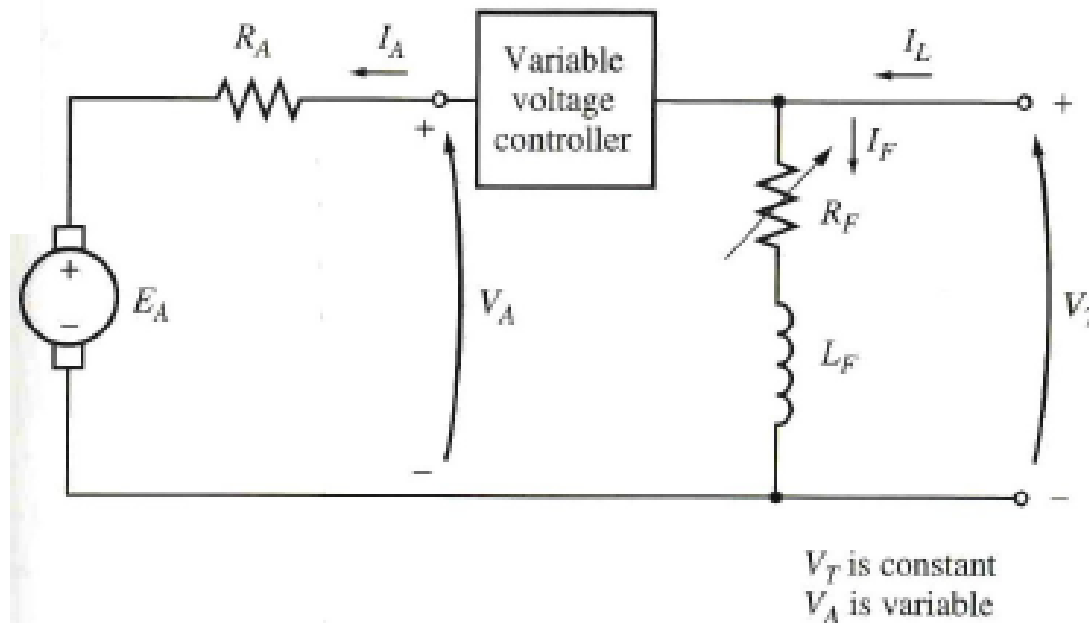
# Speed control of shunt dc motor

- *CHANGING ARMATURE VOLTAGE:*
  - Involves changing the armature voltage (applied to the armature branch) *without changing the voltage applied to the field circuit.*




# Speed control of Shunt dc motor

- *CHANGING ARMATURE VOLTAGE:*

Increasing $V_A$ causes $I_A$ to increase	$I_A \uparrow = (V_A \uparrow - E_A) / R_A$
Increasing $I_A$ increase $\tau_{ind}$	$\tau_{ind} \uparrow = K \phi I_A \uparrow$
Increasing $\tau_{ind}$ causes $\tau_{ind} > \tau_{load}$ hence motor speeds up, $\omega$	
Since $\omega$ increase, $E_A$ increase again	$E_A \uparrow = K \phi \omega \uparrow$
Increasing $E_A$ causes $I_A$ to decrease	$I_A \downarrow = (V_A - E_A \uparrow) / R_A$
Decreasing $I_A$ , causes $\tau_{ind}$ decrease until $\tau_{ind} = \tau_{load}$ at higher speed $\omega$	$\tau_{ind} \downarrow = K \phi I_A \downarrow$

# Speed control of shunt dc motor

- *CHANGING THE ARMATURE VOLTAGE:*

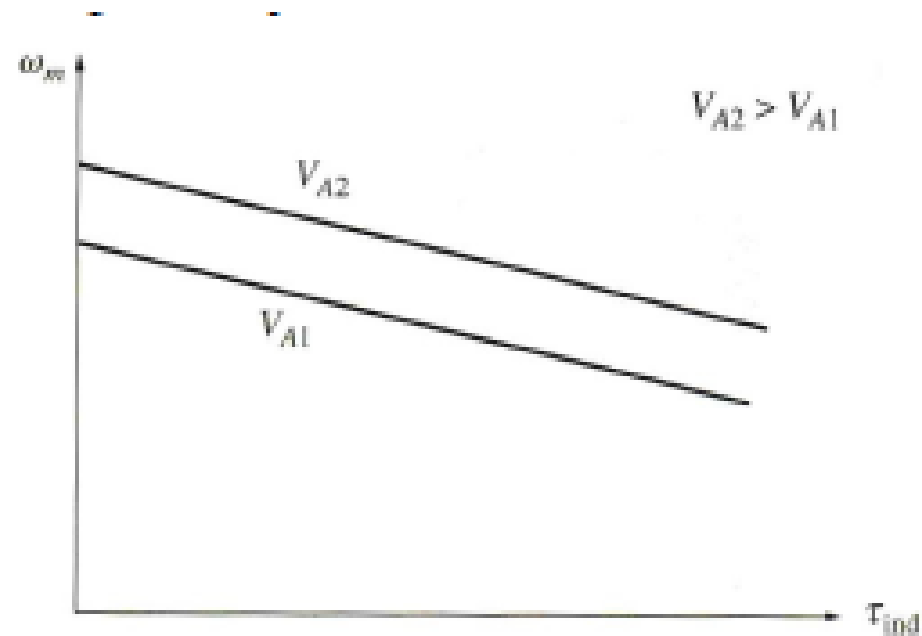


Source: <http://slideplayer.com/slide/4773410/>

Effect of armature voltage speed control for a shunt motor's torque-speed characteristics
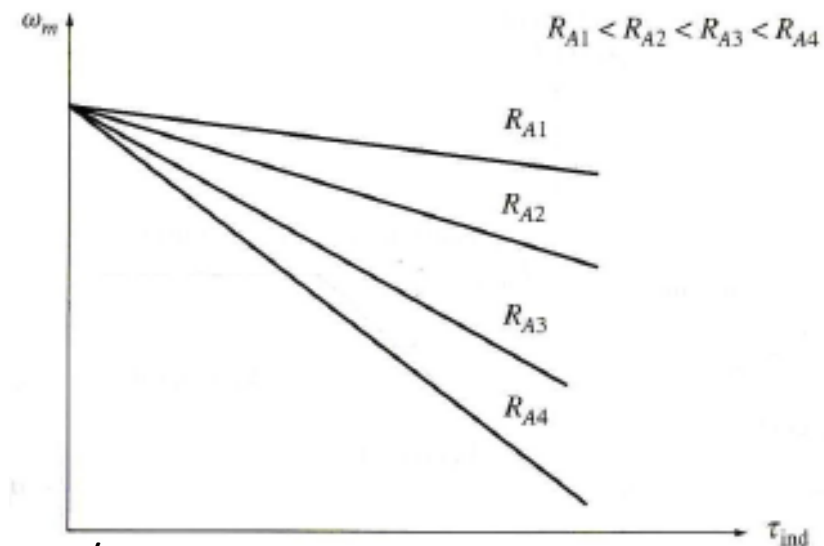
# Speed control of shunt dc motor

- *ADDING A RESISTOR IN ARMATURE CIRCUIT (SERIES CONNECTION):*
  - By connecting resistor in series with armature circuit ( $R_A \uparrow$ ), its escalate the slope of the motor's torque-speed characteristic, making it move/operate more slowly if loaded. – rarely used.

Effect of armature resistance speed control for a shunt motor's torque-speed characteristics



Source: <http://slideplayer.com/slide/4773410/>

# Application Of DC Motors

TYPES OF DC MOTOR	CHARACTERISTICS	APPLICATIONS
<u>Shunt</u>	<ul style="list-style-type: none"><li>• Medium starting torque.</li><li>• It is running in constant speed regardless the load.</li></ul>	Blower fans, centrifugal pumps, conveyers, elevators, woodworking and metalworking machinery.
<u>Series</u>	<ul style="list-style-type: none"><li>• High starting torque.</li><li>• The speed varies automatically with the load.</li><li>• No load condition is very dangerous.</li></ul>	Cranes, trolleys, gates, automobile starter, electric trains.
<u>Cumulative compound</u>	<ul style="list-style-type: none"><li>• High starting torque.</li><li>• No load condition is allowed</li></ul>	Punch Presses, Shears, Bending Machines, Hoists, sudden temporary loads
<u>Differential compound</u>	<ul style="list-style-type: none"><li>• Speed increases as load increases</li></ul>	Not suitable for any practical applications.



Mohd Ikhwan Muhammad Ridzuan, PhD  
Faculty of Electrical and Engineering  
Universiti Malaysia Pahang  
[ikhwanr@ump.edu.my](mailto:ikhwanr@ump.edu.my)

Research interest: Reliability, Distribution  
network, smart grid, risk asesment