

**Faculty of Electrical & Electronics Engineering  
Low Voltage Electrical Installation**

Name: \_\_\_\_\_

ID No. : \_\_\_\_\_


Section: \_\_\_\_\_

Date: \_\_\_\_/\_\_\_\_/2017

(Failed to complete all the particulars above will be penalized 2 marks)

### QUIZ 5

Fig. 5 represents an uncompleted schematic circuit of lighting and doorbell. Please complete this circuit with a correct wiring system and label each cable with different color/shape in the indicator box. **[10 marks]**

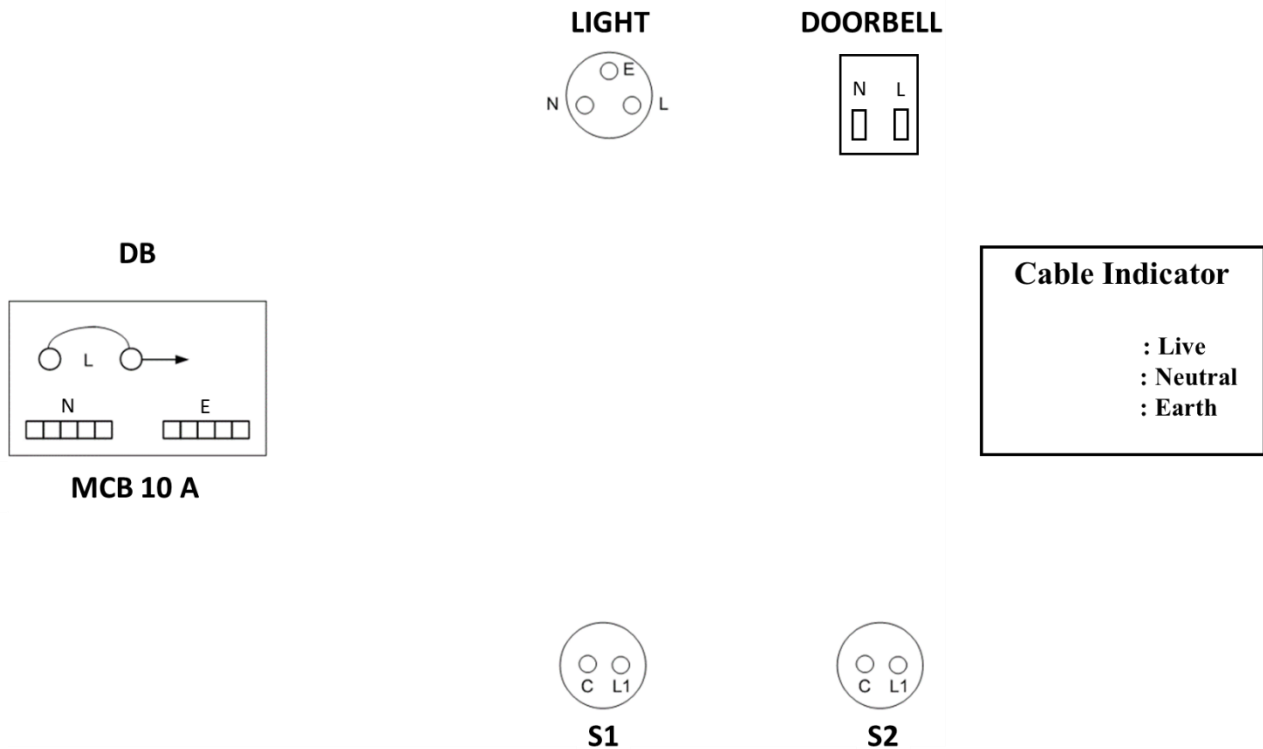

**Fig. 5**