

Basic Programmable Logic Controller

PLC System Wiring and Connection

Norasyikin Fadilah
Faculty of Electrical & Electronics Engineering
norasyikin@ump.edu.my



Learning Outcomes


Identify the wiring of power supply unit, safety protection devices and I/O units.

Draw the wiring connections of I/O devices and modules.

Understand the I/O connections and addressing.




PLC Wiring Diagram

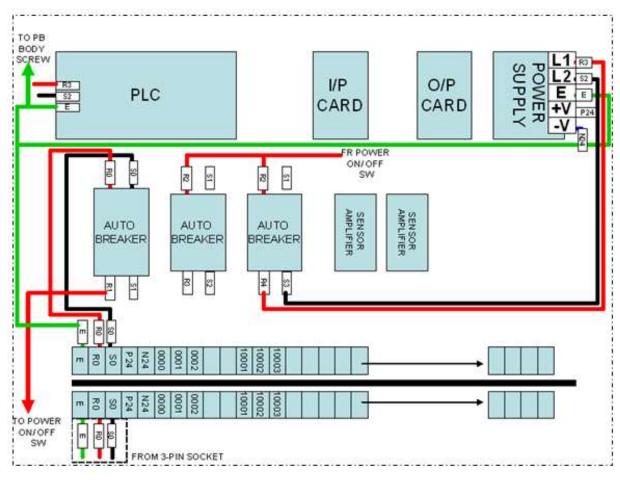

/iring PLC by orasyikin Fadilah




Wiring of Protection Devices

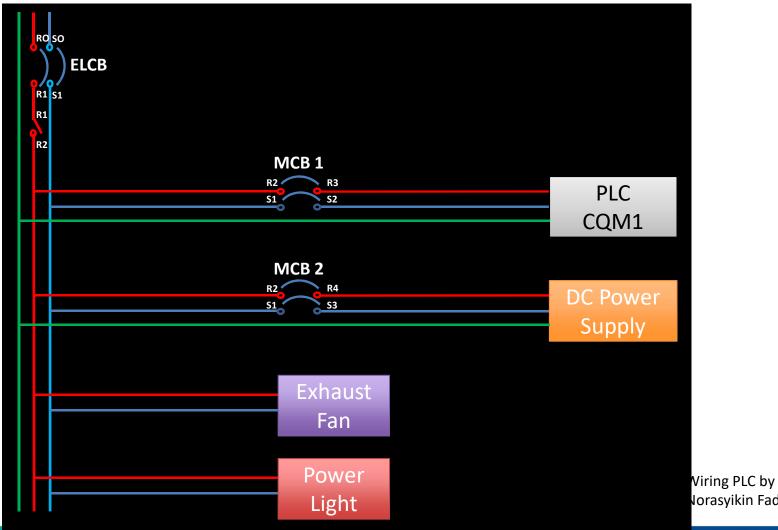


Jorasyikin Fadilah


I/O Devices

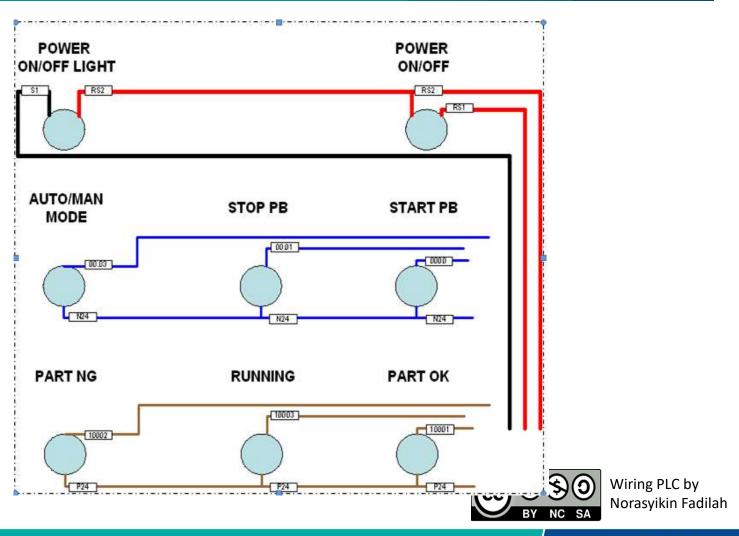

Input Connection

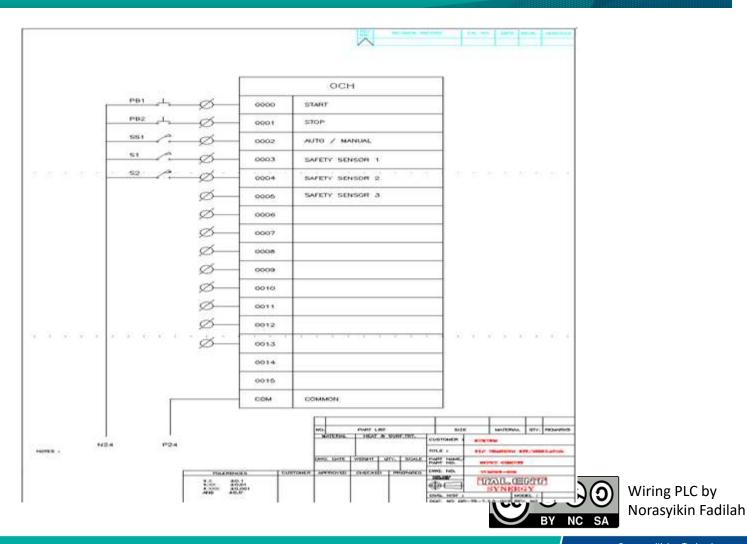

Output Connection

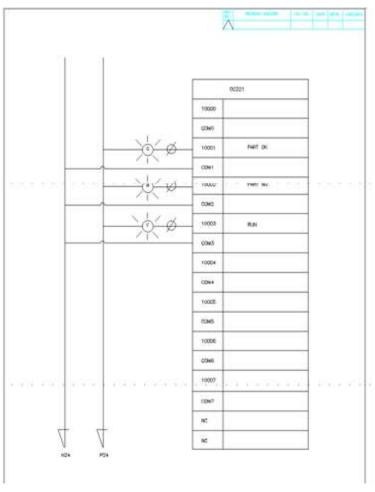







Norasyikin Fadilah
Lecturer, FKEE Universiti Malaysia Pahang
norasyikin@ump.edu.my
Profile:
Google Scholar

Scopus

