

# BEE2143 – Signals & Networks

## Chapter 6 – Applications of the Fourier Transform

Raja M. Taufika R. Ismail

Universiti Malaysia Pahang

September 29, 2017



Circuit analysis

Parseval's theorem

Amplitude modulation


References

## Circuit analysis

- ▶ The Fourier transform generalizes the phasor technique to nonperiodic functions
- ▶ Therefore, we apply Fourier transforms to circuits with nonsinusoidal excitations in exactly the same way we apply phasor techniques to circuits with sinusoidal excitations
- ▶ Thus, Ohm's law is still valid
- ▶ Once we transform the functions for the circuit elements into the frequency domain and take the Fourier transforms of the excitations, we can use circuit techniques
- ▶ Although the Fourier transform method produces a response that exists for  $-\infty < t < \infty$ , Fourier analysis cannot handle circuits with initial conditions

- ▶ The transfer function is defined as the ratio of the output response  $Y(\omega)$  to the input excitation  $X(\omega)$

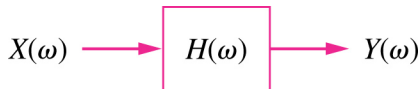
$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$



- ▶ This equation shows that if we know the transfer function and the input, we can readily find the output
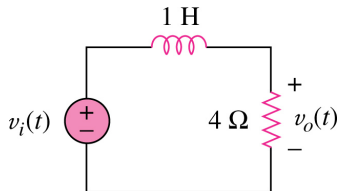
## Practice Problem 18.7, pg. 830 (Alexander & Sadiku, 2009)


Determine  $v_o(t)$  in Fig. 18.19 if  
 $v_i(t) = 5 \operatorname{sgn}(t) = (-5 + 10u(t))$  V.



Answer:  $-5 + 10(1 - e^{-4t})u(t)$  V
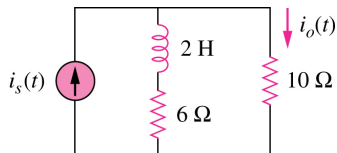
## Practice Problem 18.8, pg. 831 (Alexander & Sadiku, 2009)


Find the current  $i_o(t)$  in the circuit in Fig. 18.21, given that  $i_s(t) = 5 \cos 4t$  A.




Answer:  $2.95 \cos(4t + 26.57^\circ)$  A
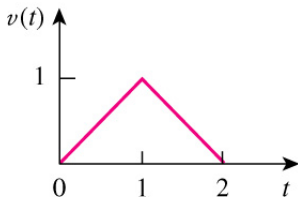
## Problem 18.40, pg. 845 (Alexander & Sadiku, 2009)

Determine the current  $i(t)$  in the circuit of Fig. 18.42(b), given the voltage source shown in Fig. 18.42(a).



(a)

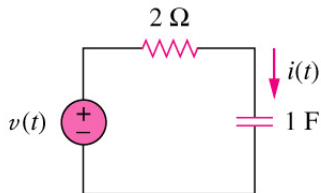


(b)

Answer:

$$i(t) = (1 - e^{-0.5t})u(t) - 2[1 - e^{-0.5(t-1)}]u(t-1) + [1 - e^{-0.5(t-2)}]u(t-2) \text{ A}$$
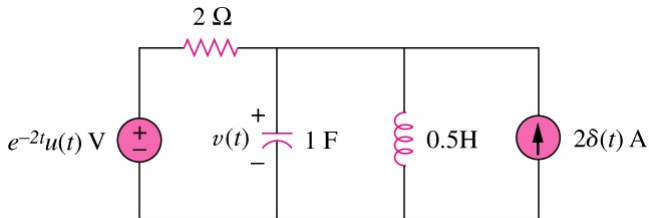
## Problem 18.41, pg. 845 (Alexander & Sadiku, 2009)

Determine the Fourier transform of  $v(t)$  in the circuit shown in Fig. 18.43.



Answer:

$$V(\omega) = \frac{j2\omega(4.5 + j2\omega)}{(2 + j\omega)(4 - 2\omega^2 + j\omega)}$$



## Parseval's theorem

- Parseval's theorem states that the total energy delivered to a  $1\text{-}\Omega$  resistor equals the total area under the square of  $f(t)$  or  $1/2\pi$  times the total area under the square of the magnitude of the Fourier transform of  $f(t)$

$$W_{1\Omega} = \int_{-\infty}^{\infty} f^2(t)dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(\omega)|^2 d\omega$$

- Since  $|F(\omega)|^2$  is an even function, we may integrate from 0 to  $\infty$  and double the result; that is,

$$W_{1\Omega} = \frac{1}{\pi} \int_0^{\infty} |F(\omega)|^2 d\omega$$

- We may also calculate the energy in any frequency band  $\omega_1 < \omega < \omega_2$  as

$$W_{1\Omega} = \frac{1}{2\pi} \int_{\omega_1}^{\omega_2} |F(\omega)|^2 d\omega$$

## Practice Problem 18.9, pg. 834 (Alexander & Sadiku, 2009)

- (a) Calculate the total energy absorbed by a  $1\text{-}\Omega$  resistor with  $i(t) = 5e^{-2|t|}$  A in the time domain.
- (b) Repeat (a) in the frequency domain.

Answer: (a) 12.5 J, (b) 12.5 J

## Practice Problem 18.10, pg. 835 (Alexander & Sadiku, 2009)

A  $2\text{-}\Omega$  resistor has  $i(t) = 2e^{-t}u(t)$  A. What percentage of the total energy is in the frequency band  $-4 < \omega < 4$  rad/s?

Answer: 84.4%

## Amplitude modulation


- ▶ Amplitude modulation (AM) is a process whereby the amplitude of the carrier is controlled by the modulating signal
- ▶ Suppose the audio information, such as voice or music (or the modulating signal in general) to be transmitted is  $m(t) = V_m \cos \omega_m t$ , while the high-frequency carrier is  $c(t) = V_c \cos \omega_c t$ , where  $\omega_c \gg \omega_m$
- ▶ Then an AM signal  $f(t)$  is given by

$$f(t) = [1 + m(t)]c(t) = V_c[1 + m(t)] \cos \omega_c t$$


- ▶ We can use the amplitude modulation property together with the Fourier transform of the cosine function to determine the spectrum of the AM signal:

$$\begin{aligned}F(\omega) &= \mathcal{F}[V_c \cos \omega_c t] + \mathcal{F}[V_c m(t) \cos \omega_c t] \\ &= V_c \pi [\delta(\omega - \omega_c) + \delta(\omega + \omega_c)] + \frac{V_c}{2} [M(\omega - \omega_c) + M(\omega + \omega_c)]\end{aligned}$$

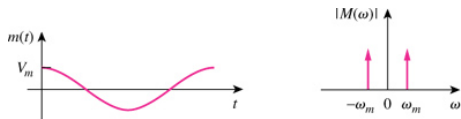
- ▶ The AM signal consists of the carrier and two other sinusoids
- ▶ The sinusoid with frequency is known as the lower sideband, while the one with frequency is known as the upper sideband



(a)

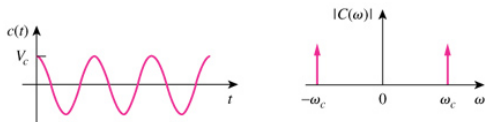

(b)

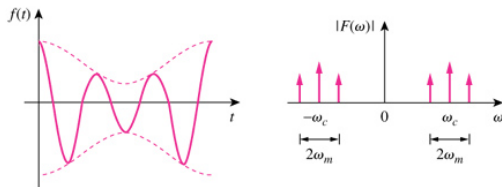

(c)

## Example 18.11, pg. 838 (Alexander & Sadiku, 2009)

A music signal has frequency components from 15 Hz to 30 kHz. If this signal could be used to amplitude modulate a 1.2-MHz carrier, find the range of frequencies for the lower and upper sidebands.

Answer: 1,170,000 to 1,199,985 Hz    and    1,200,015 to 1,230,000 Hz

## Practice Problem 18.11, pg. 838 (Alexander & Sadiku, 2009)

If a 2-MHz carrier is modulated by a 4-kHz intelligent signal, determine the frequencies of the three components of the AM signal that results.

Answer: 2,004,000 Hz, 2,000,000 Hz, 1,996,000 Hz



## List of References

1. C.K. Alexander and M.N.O. Sadiku (2009), Fundamentals of Electric Circuits 4th ed., New York: McGraw-Hill.