

You can preview this quiz, but if this were a real attempt, you would be blocked because:

This quiz is not currently available

Question 1


Not yet answered

Marked out of 1.00

Flag question

Edit question

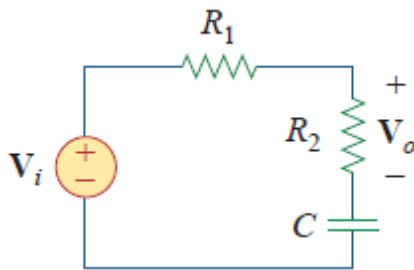What is the type of the following filter?



Select one:

- a. bandstop
- b. lowpass
- c. bandpass
- d. highpass

Question 2


Not yet answered

Marked out of 1.00

Flag question

Edit question

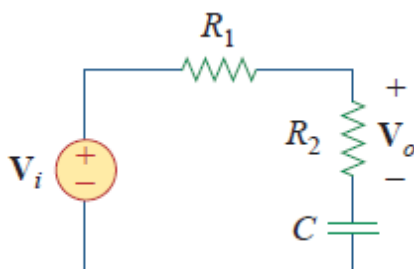The maximum gain of the following filter is



Select one:

- a. 0.5
- b. $R_1/(R_1+R_2)$
- c. $R_2/(R_1+R_2)$
- d. 1

Question 3


Not yet answered

Determine the filter type and the cutoff frequency of the following circuit.

Marked out of 1.00

Flag question

Edit question

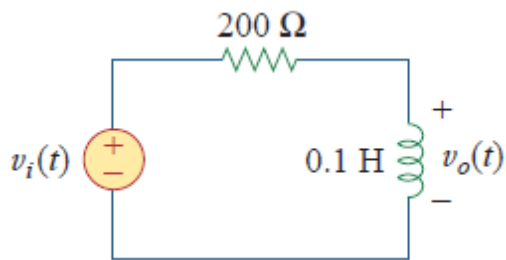

Select one:

- a. lowpass, 2000 rad/s
- b. highpass, 0.5 rad/s
- c. lowpass, 0.5 rad/s
- d. highpass, 2000 rad/s

Question 4


Not yet answered

Marked out of 1.00

Flag question

Edit question

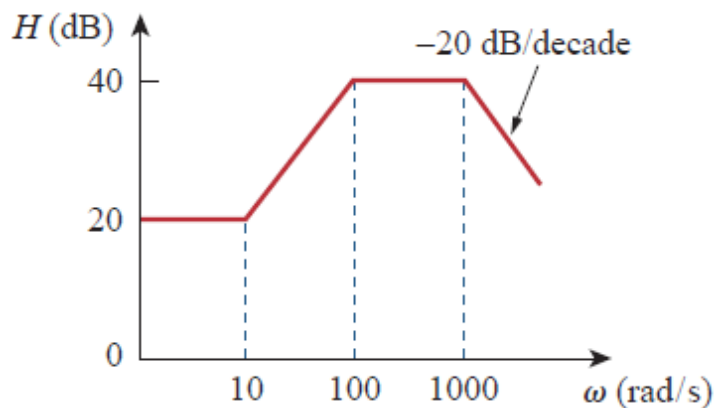The corresponding transfer function of the following bode plot is



Select one:

- a. $\frac{100000(s + 100)}{(s + 10)(s + 1000)}$
- b. $\frac{100000s}{(s + 10)(s + 1000)}$
- c. $\frac{100000(s + 10)}{(s + 100)(s + 1000)}$
- d. $\frac{100000(s + 1000)}{(s + 10)(s + 100)}$

Question 5


Not yet answered

Marked out of 1.00

Flag question

Which transfer function that has the following bode plot? ^

Edit question

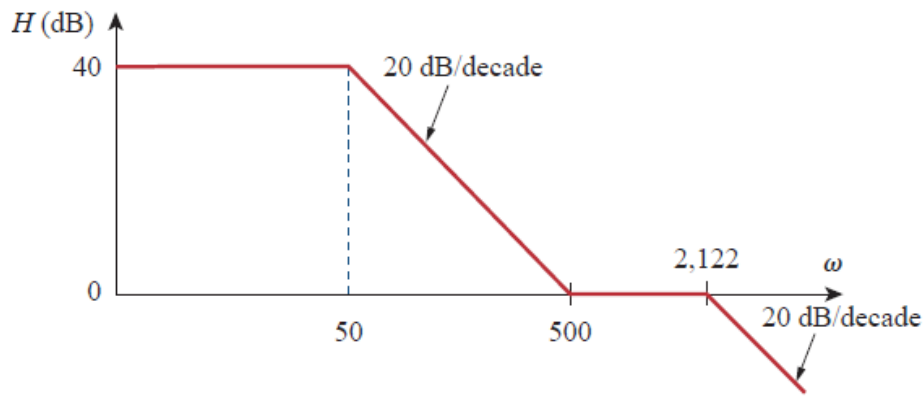

Select one:

- a. $\frac{21220s}{(s + 500)(s + 2122)}$
- b. $\frac{21220(s + 500)}{(s + 50)(s + 2122)}$
- c. $\frac{21220(s + 2122)}{(s + 50)(s + 500)}$
- d. $\frac{21220(s + 50)}{(s + 500)(s + 2122)}$

Question 6

Not yet answered

Marked out of 1.00

Flag question

Edit question

[Questions 6-10 are based on the following information.]

A filter is described by the transfer function

$$H(s) = \frac{s}{(s + 1)(s + 2)}$$

The magnitude of H is

Select one:

- a. $\frac{1}{\sqrt{9 + \left(\omega - \frac{2}{\omega}\right)^2}}$
- b. $\frac{\omega}{\sqrt{(\omega^2 + 1)(\omega^2 + 4)}}$
- c. $\frac{\omega}{(\omega + 1)(\omega + 2)}$
- d. $\frac{1}{\sqrt{4 + \left(\omega - \frac{3}{\omega}\right)^2}}$


Question 7


Not yet answered

The phase angle of H is

Select one:

Marked out of 1.00

 Flag question


 Edit question


- a. $90^\circ - \tan^{-1} \omega - \tan^{-1} \frac{\omega}{2}$
- b. $-\tan^{-1} \omega + \tan^{-1} \frac{\omega}{2}$
- c. $-\tan^{-1} \omega - \tan^{-1} \frac{\omega}{2}$
- d. $90^\circ - \tan^{-1} \omega + \tan^{-1} \frac{\omega}{2}$

Question **8**

Not yet answered

Marked out of 1.00

 Flag question

 Edit question

The type of the filter is


Select one:


- a. bandstop
- b. bandpass
- c. lowpass
- d. highpass

Question **9**

Not yet answered

Marked out of 1.00

 Flag question

 Edit question

The center frequency of the filter in rad/s is


Select one:


- a. 1.414
- b. not applicable
- c. 1.732
- d. 2

Question **10**

Not yet answered

Marked out of 1.00

 Flag question

 Edit question

The maximum gain of H is

Select one:

- a. 0.5
- b. 0.333
- c. 0.25
- d. 1

^

Next

Tracking: " Tracking: " Tracking: "

Tracking: 'FACULTY OF ELECTRICAL & ELECTRONICS ENGINEERING/SIGNALS & NETWORKS/quiz/Quiz 5 Sec EH13 (30 May-5 Jun 2016)'