

# BEE1133 Circuit Analysis

## Chapter 1C Basic Concept

by

Nor Rul Hasma Abdullah  
Faculty of Electrical & Electronics Engineering  
hasma@ump.edu.my



Basic Concept by N.R.H. Abdullah  
<http://ocw.ump.edu.my/course/view.php?id=251>

*Communitising Technology*

# Chapter Description

## Aims

This chapter is aimed to:

1. Explain the voltage division and current division
2. Explain the Delta-wye transformation

## Expected Outcomes

Student should be able to

1. Simplified the circuit and solved the question related to voltage division and current division
2. Recognize the circuit to be solve using Delta-wye transformstion

## References

1. C. Alexander and M. Sadiku, “Fundamentals of Electric Circuits”, 4th ed., McGraw-Hill, 2008.
2. J. Nilsson and S. Riedel, “Electric Circuits”, 8th ed., Prentice Hall, 2008.




# BASIC CONCEPT

- 3.1 Principles of voltage division and current division
- 3.2 Delta-wye transformation



# VOLTAGE DIVIDER

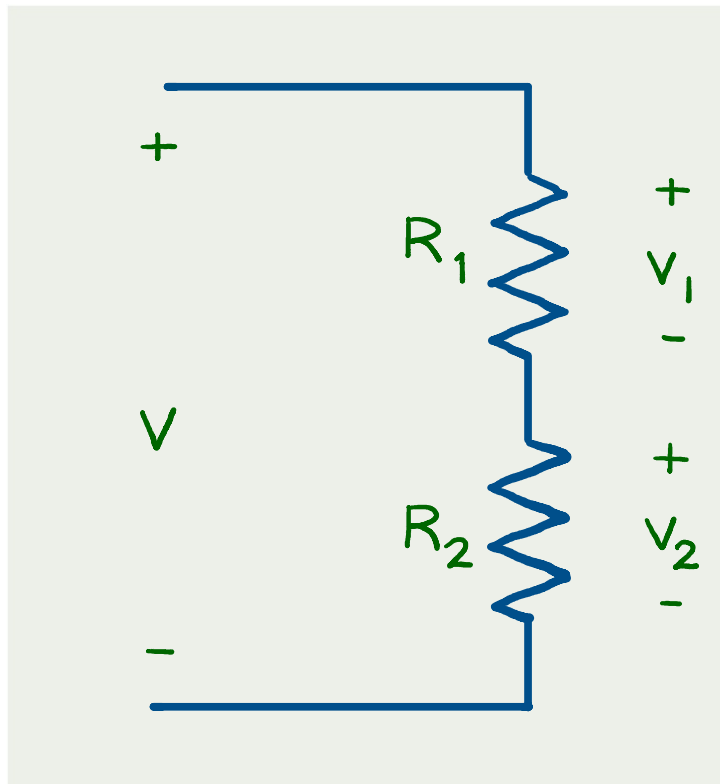


$$V_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = \frac{R_2}{R_1 + R_2} V$$




Basic Concept by N.R.H. Abdullah  
<http://ocw.ump.edu.my/course/view.php?id=251>

# VOLTAGE DIVIDER

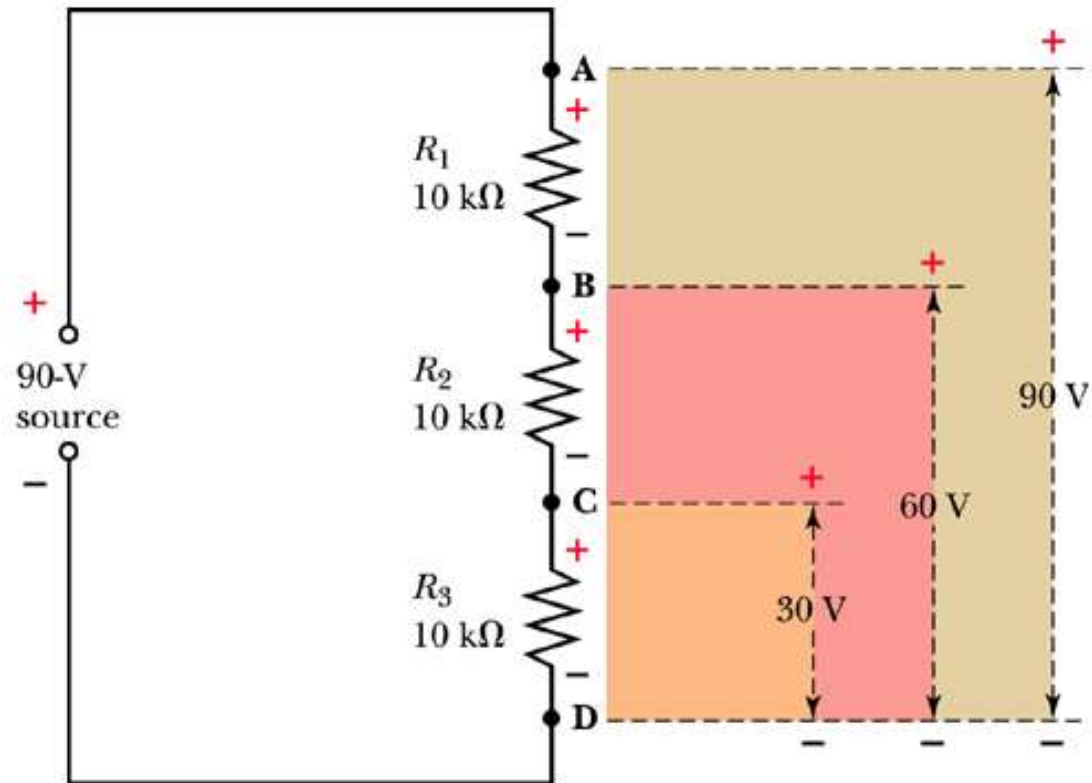

Basic Concept by N.R.H. Abdullah  
<http://ocw.ump.edu.my/course/view.php?id=251>

# CURRENT DIVIDER






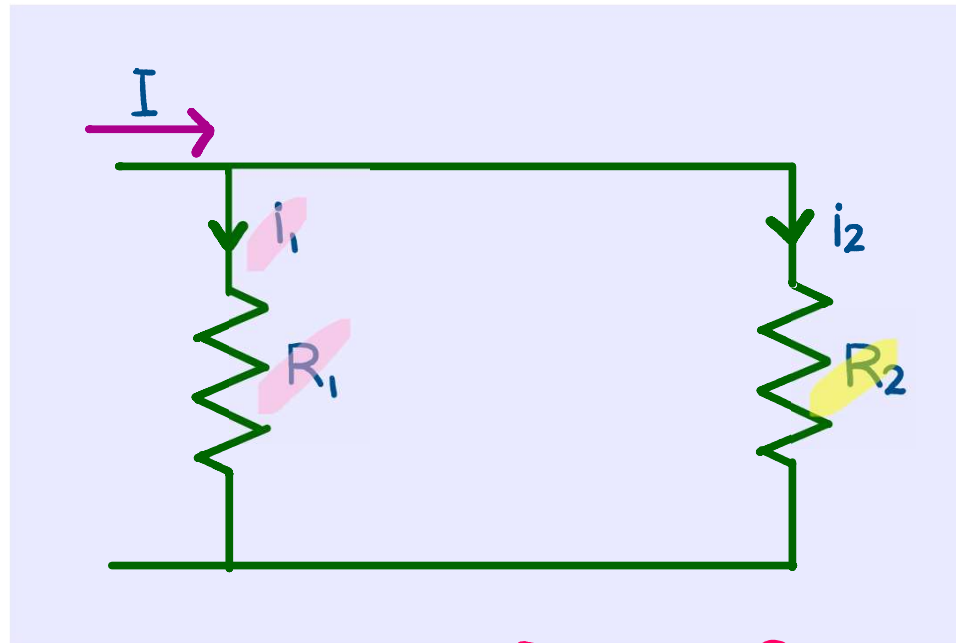


$$i_1 = \frac{R_2}{R_1 + R_2} I$$
$$i_2 = \frac{R_1}{R_1 + R_2} I$$

\* ONLY TWO RESISTOR

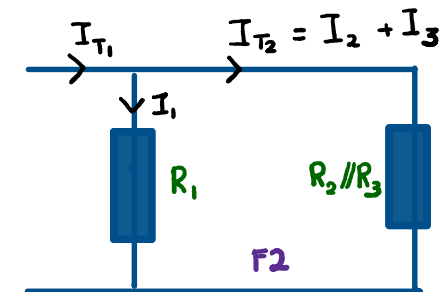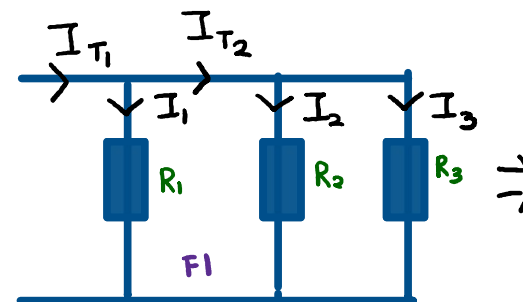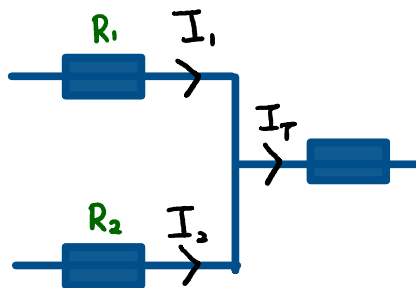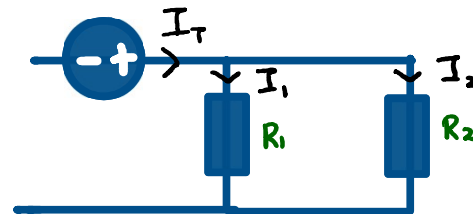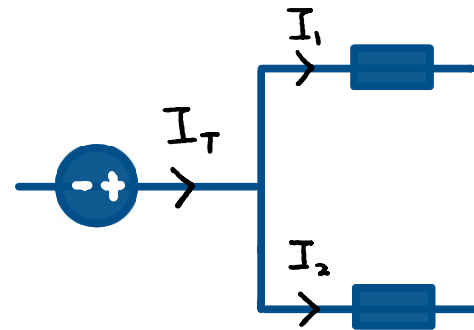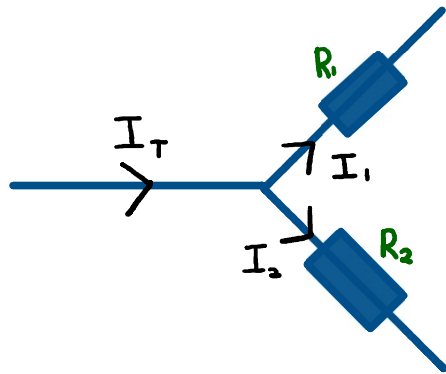If the circuit consist more than 2,  
Simplified the circuit.





Find  $I_3$


- ① Find  $I_{T2}$  using CD-F2
- ② Find  $I_3$  using CD-F1


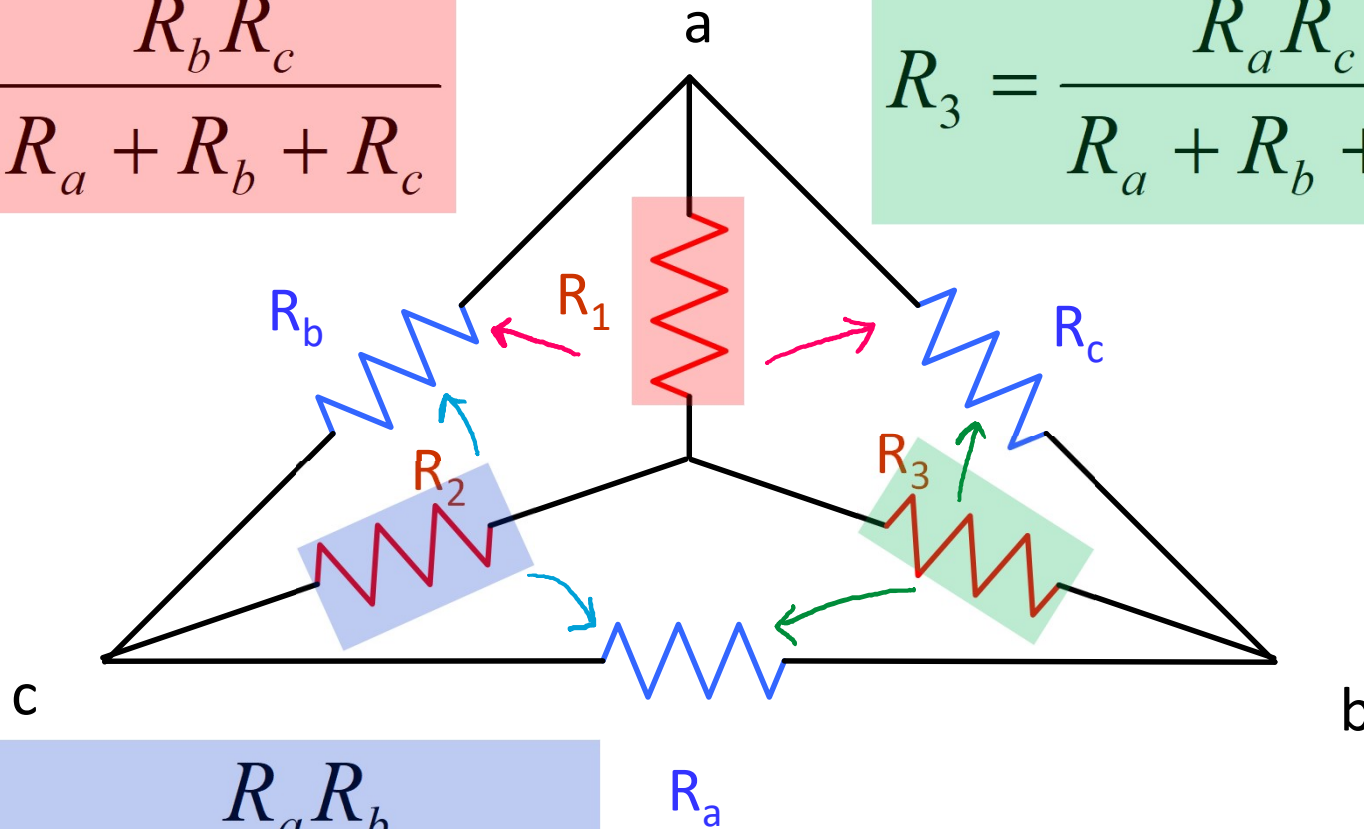
# DELTA( $\Delta$ )-WYE(Y) TRANSFORMATION

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$



$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$





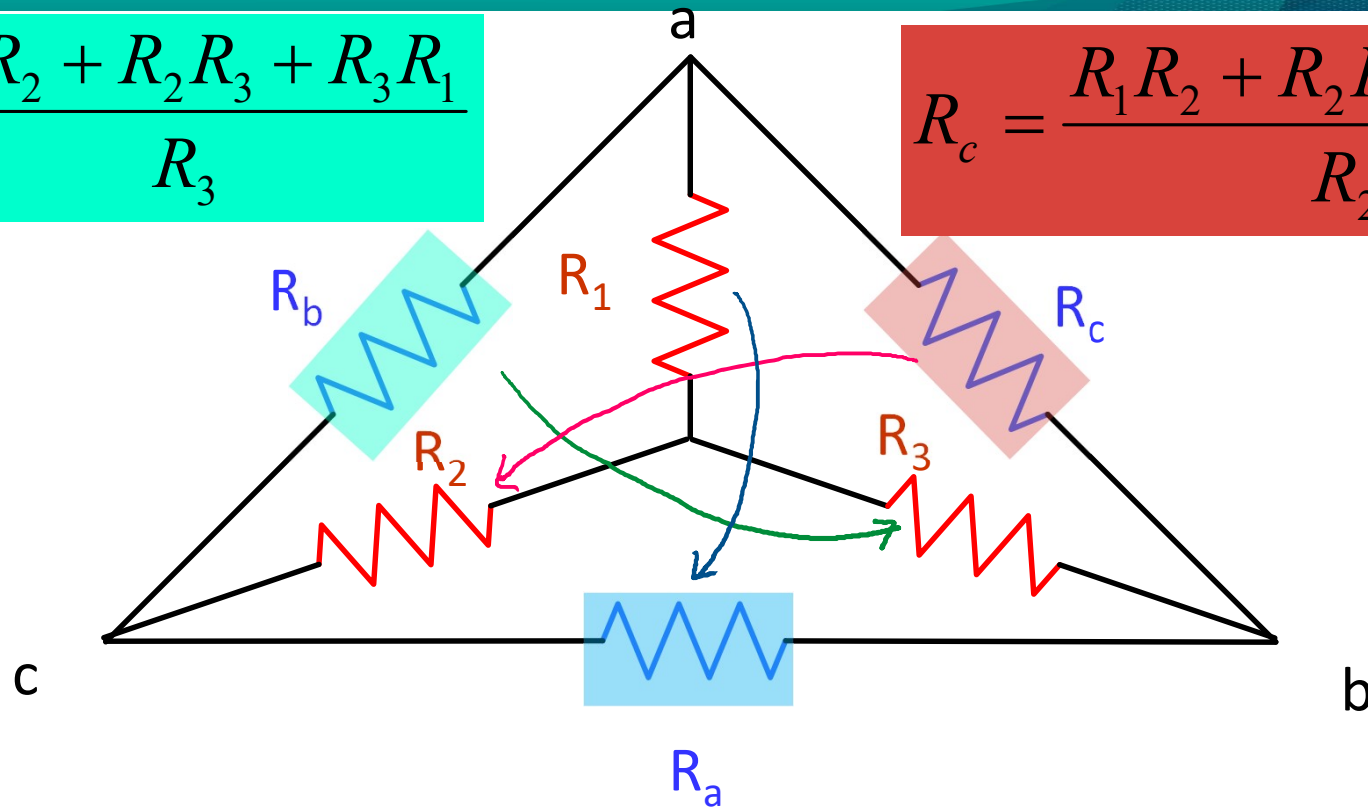
# DELTA( $\Delta$ )-WYE(Y) TRANSFORMATION

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



## Author Information

**Nor Rul Hasma Abdullah (Ph. D)**  
**Senior Lecturer**

**Email:**

**[hasma@ump.edu.my](mailto:hasma@ump.edu.my)**

**Google Scholar:**

**[Nor Rul Hasma](#)**

**Scopus ID :**

**35791718100**

