

BEE1133 Circuit Analysis

Chapter 2B Methods of Analysis (DC Circuits)

by

Nor Rul Hasma Abdullah
Faculty of Electrical & Electronics Engineering
hasma@ump.edu.my



Methods of Analysis by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Chapter Description

Aims

This chapter is aimed to:

1. Explain the Mesh Analysis technique in solving problem related to electric circuit

Expected Outcomes

Student should be able to

1. Identify the loop for circuit
2. Identify the supermesh in the circuit
3. Determine the equation of ohm's law
4. Determine the KVL equation for each loop for solving the electric circuit problem.



References

1. C. Alexander and M. Sadiku, "Fundamentals of Electric Circuits", 4th ed., McGraw-Hill, 2008.
2. J. Nilsson and S. Riedel, "Electric Circuits", 8th ed., Prentice Hall, 2008.



Methods of Analysis by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Basic Concept

- 5.1 Mesh Analysis
- 5.2 Mesh Analysis with current source: Supernode
- 5.3 Nodal versus mesh analysis





Mesh Analysis

- ❑ Mesh Analysis assigns **UNKNOWN MESH CURRENTS** to all the meshes in the circuit
- ❑ Finds the **UNKNOWN MESH CURRENTS** by performing KVL around all meshes.
- ❑ KVL: Summation of voltage in close loop equal to zero
- ❑ We can find any **BRANCH CURRENTS** passing through any element in the circuit after finding the **UNKNOWN MESH CURRENTS** .



Mesh Current and Branch Current

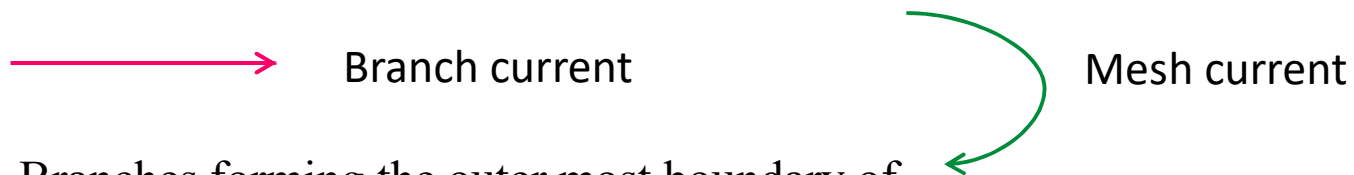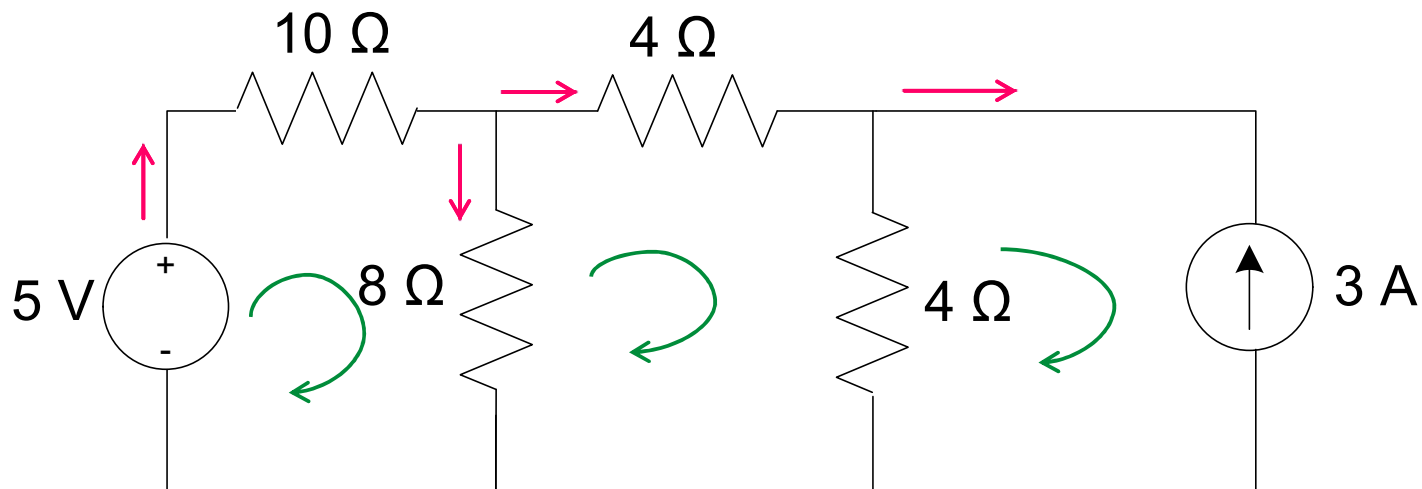

! Branches forming the outer most boundary of the circuit will have its **BRANCH CURRENT** the same as its **MESH CURRENT**



Remember!

Please understand on how to write the equation of voltage, V for each close loop



General Step For Using Mesh Analysis

Step 1

Assign loop for each meshes in clockwise

Step 2

Decide the number of equation

The circuit **ONLY** consist of **R** and **dependent source**

No. of loop=no. of KVL

If the current source exist at the outer branch = No. of KVL -1 , no need to write the KVL equation, since the mesh current already given.

Step 3

Apply KVL for each mesh in the circuit.

The main loop voltage drops, **ADDED** and the voltage at the adjacent loop, **SUBTRACTED**.

Step 4

Calculate the mesh current using Cramer/Calculator




Methods of Analysis by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Reminder!


Finding the voltage

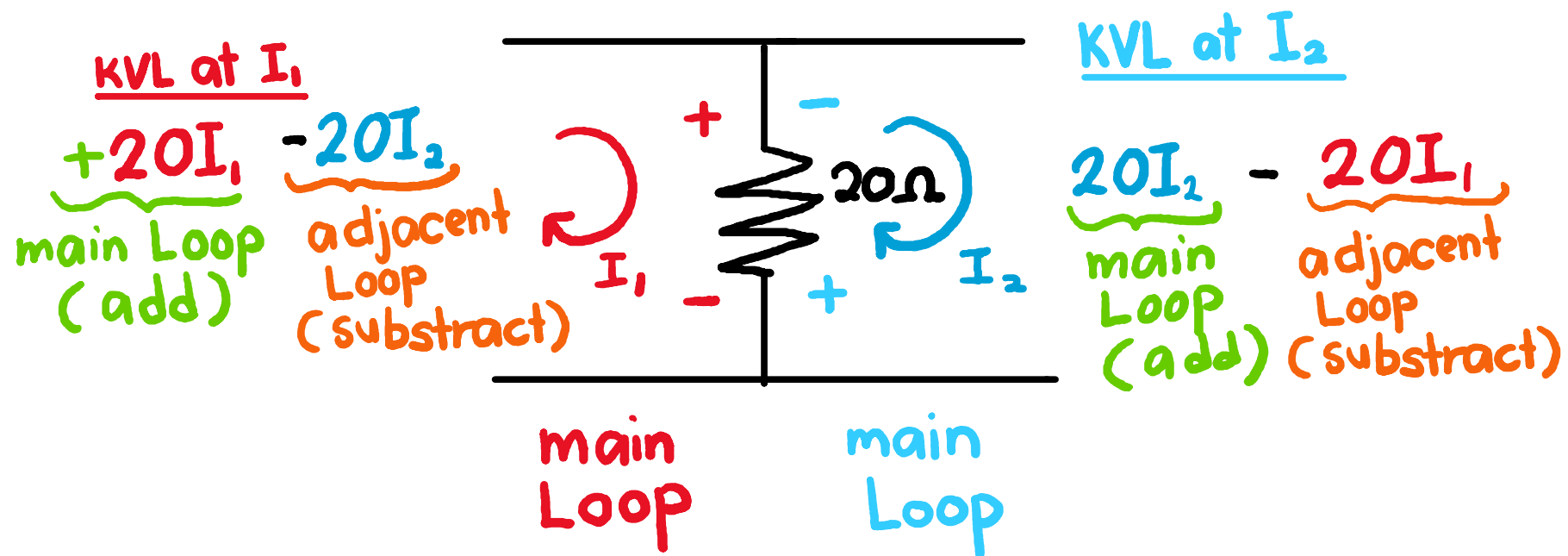Current entering the resistor, the polarity setting is always positive




Circuit with dependent source

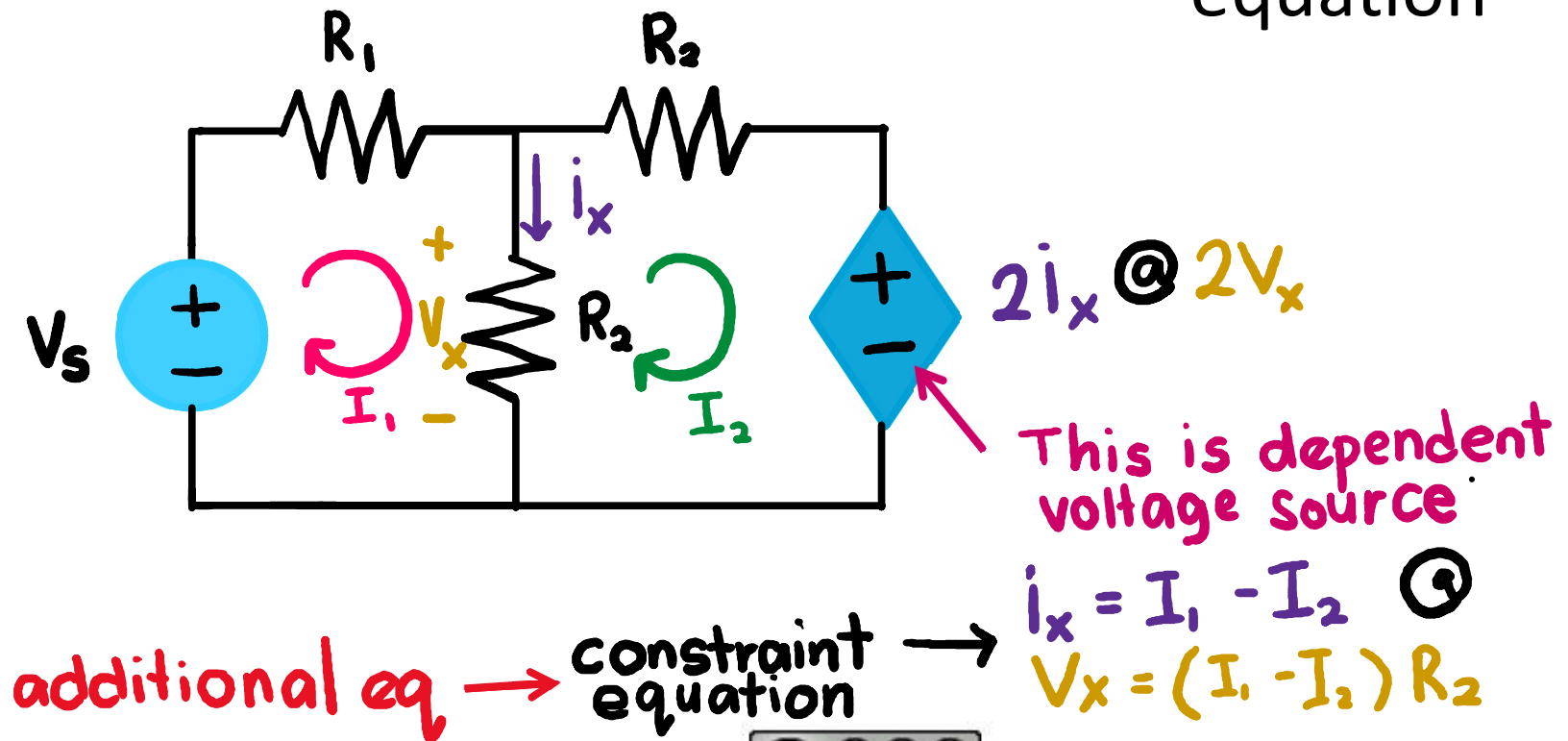
1 dependent source = additional 1 constraint equation



Circuit with current source

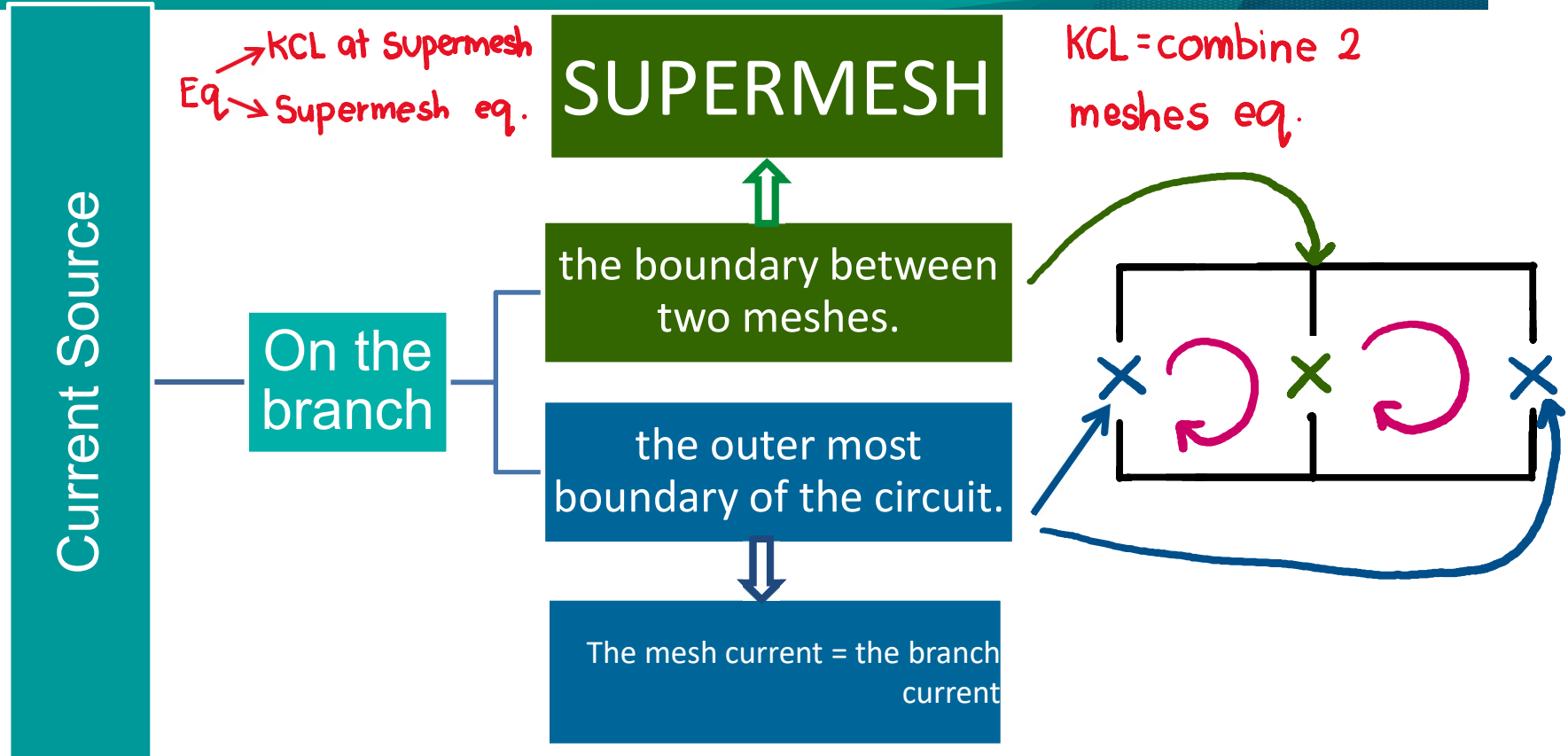

SUPERMESH

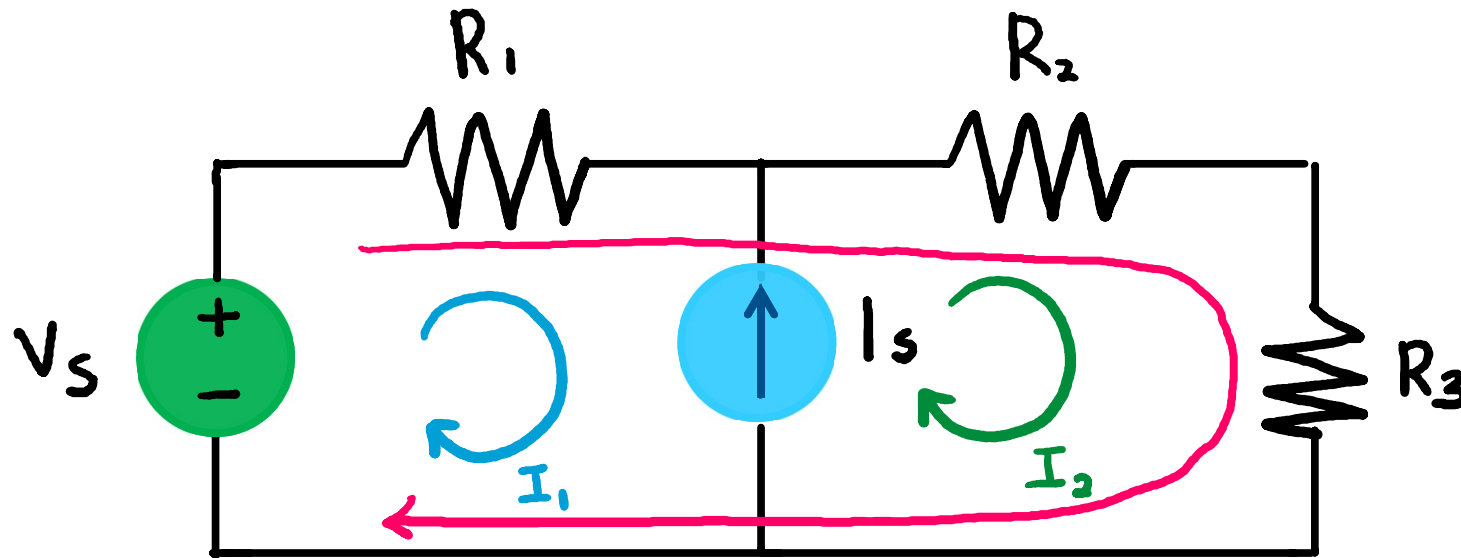


$$\text{KVL at Supernode} : -V_s + I_1 R_1 + I_2 R_2 + I_2 R_3 = 0$$


$$\text{Supernode} : I_s = I_2 - I_1$$



SUPERMESH

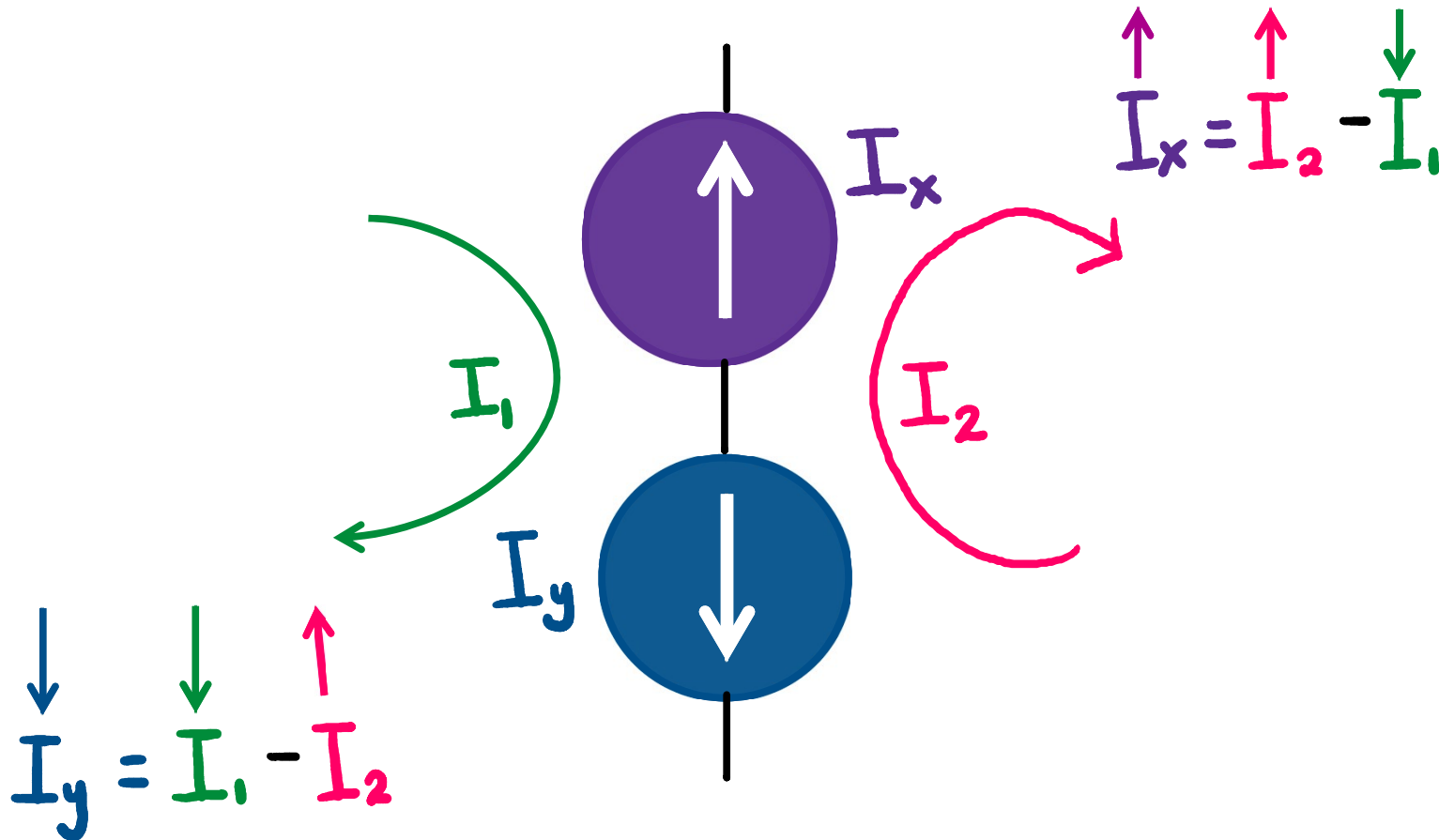

TIPS

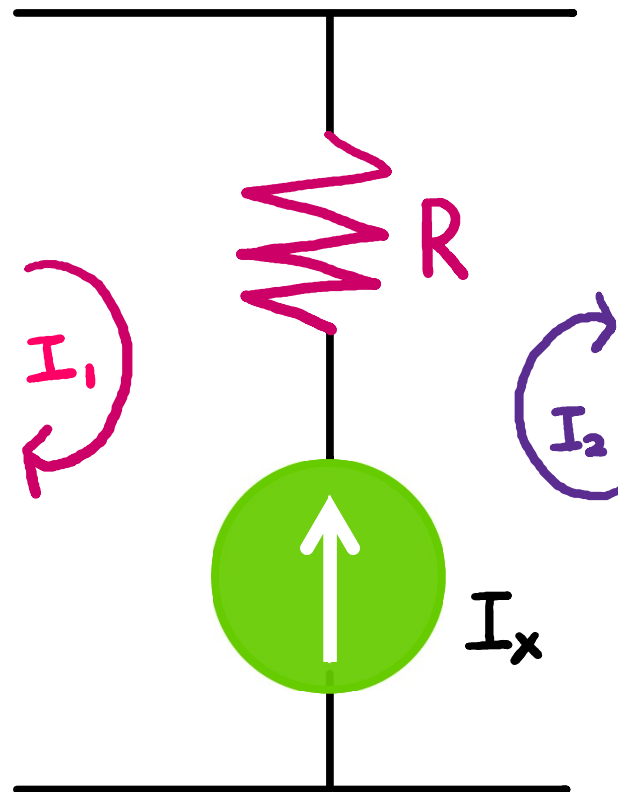

$$I_x = I_2 - I_1$$


The current flow through the branch is I_x .

Therefore, R is ignored or act as short circuit



Methods of Analysis by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>


BASIC STEP

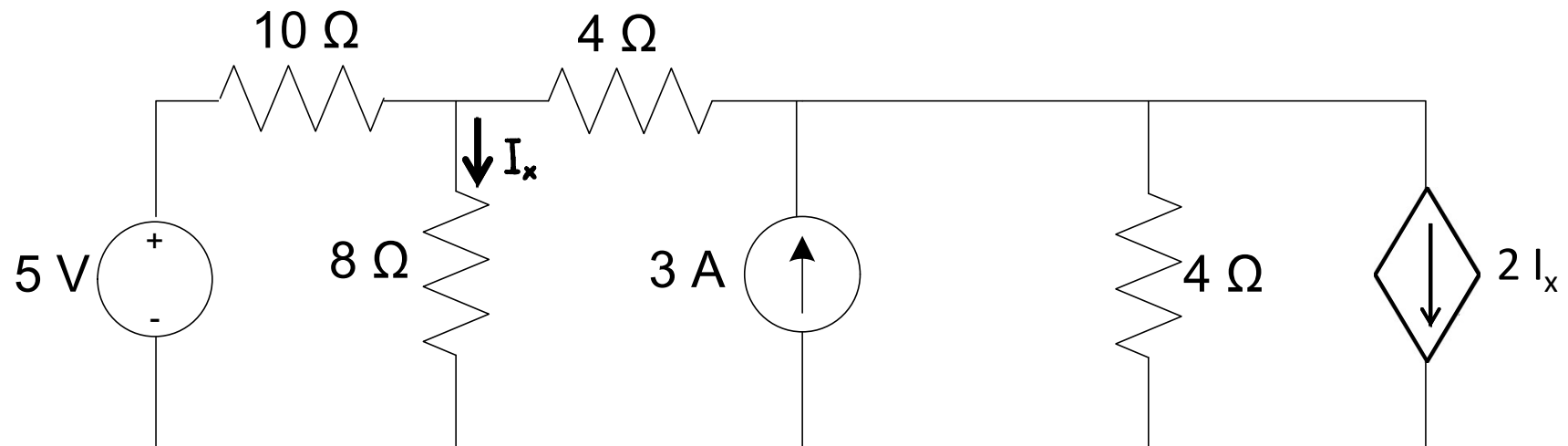


Assume that we are trying to find the voltage across and the current through all the elements



Step 1: Assign loop (clock wise)

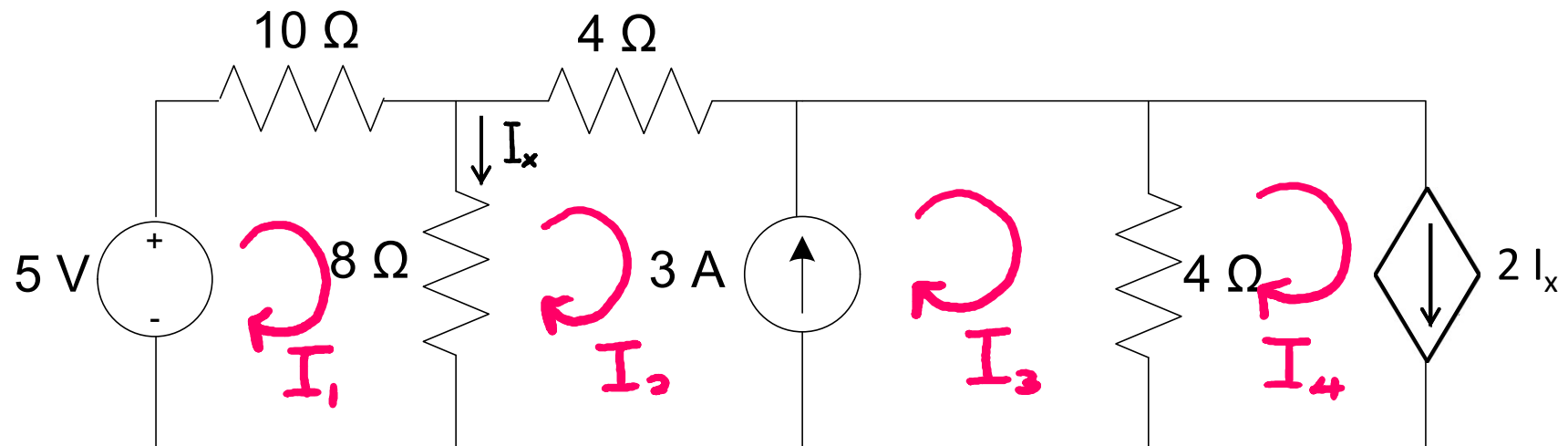

Step 2: Decide no. of equation

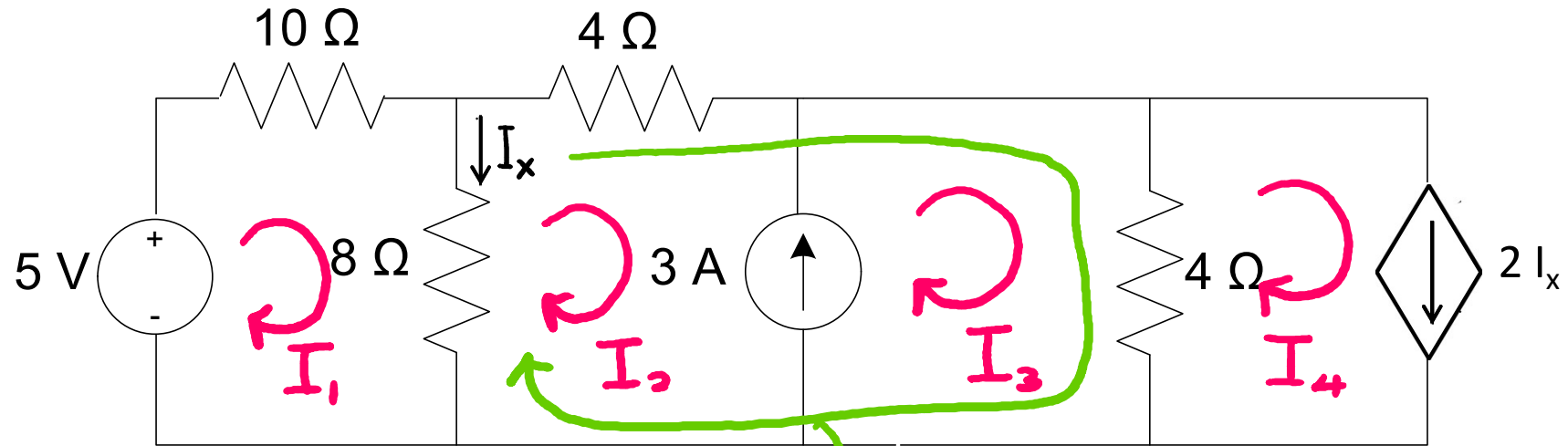

No. of loop = 4

Supermesh = 4 - 1 (supermesh) + 1 (supermesh eq.)

Loop 4 = already know the current value.
(no need to do KVL)

Dependent = + 1 constraint eq
source



Step 3: Decide no. of equation

- 3 KVL Equations
 - ✓ Loop 1
 - ✓ Loop Supermesh(combine loop 2 and loop 3)
 - ✓ Loop 4

- 1 Supermesh Equation

- 1 Constraint Equation

Total = 5 Equations



Step 3: Decide no. of equation (cont)

3 KVL equation

✓ Loop 1

$$-5 + 10I_1 + 8(I_1 - I_2) = 0$$

✓ Loop Supermesh (combine loop 2 and loop 3)

$$8(I_2 - I_1) + 4I_2 + 4(I_3 - I_4) = 0$$

✓ Loop 4

$$I_4 = 2I_x$$

1 Supermesh Equation

$$I_3 - I_2 = 3$$

1 Constraint Equation

$$I_x = I_1 - I_2$$



Step 4: Calculate the mesh currents

Solving the simultaneous equation by applying Cramer's Rule or using calculator



Methods of Analysis by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

KVL at Loop 1

$$-5 + 10I_1 + 8(I_1 - I_2) = 0$$

$$I_1(10 + 8) - I_2(8) = 5$$

$$I_1(18) - I_2(8) = 5 \quad \text{————— ①}$$

KVL at Supermesh

$$8(I_2 - I_1) + 4I_2 + 4(I_3 - I_4) = 0$$

$$I_1(-8) + I_2(8 + 4) + 4I_3 + I_4(-4) = 0$$

$$I_1(-8) + I_2(12) + 4I_3 + I_4(-4) = 0 \quad \text{————— ②}$$

At Loop 4

$$I_4 = 2I_x \quad \text{————— ③}$$

Supermesh Eq.

$$I_3 - I_2 = 3 \quad \text{————— ④}$$

Constraint Eq.

$$I_x = I_1 - I_2 \quad \text{————— ⑤}$$



Substitute (5) –(3)

$$I_4 = 2(I_1 - I_2)$$

$$2I_1 - 2I_2 - I_4 = 0 \text{ ————— } \textcircled{6}$$

From 4

$$I_3 = 3 + I_2 \text{ ————— } \textcircled{7}$$

Substitute (7) –(2)

$$-8I_1 + 12I_2 + 4(3 + I_2) - 4I_4 = 0$$

$$-8I_1 + 12I_2 + 12 + 4I_2 - 4I_4 = 0$$

$$-8I_1 + 16I_2 - 4I_4 = -12 \text{ ————— } \textcircled{8}$$

Rearrange Eq. (1), (6), (8)

$$\begin{bmatrix} 18 & -8 & 0 \\ 2 & -2 & -1 \\ -8 & 16 & -4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_4 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ -12 \end{bmatrix}$$

$$I_1 = \frac{3}{38} = 0.0789A$$


$$I_2 = -\frac{17}{38} = -0.4474A$$

$$I_4 = \frac{20}{19} = 1.053A$$

$$I_3 = 3 + I_2 = 3 - 0.4474 = 2.553A$$



Answer

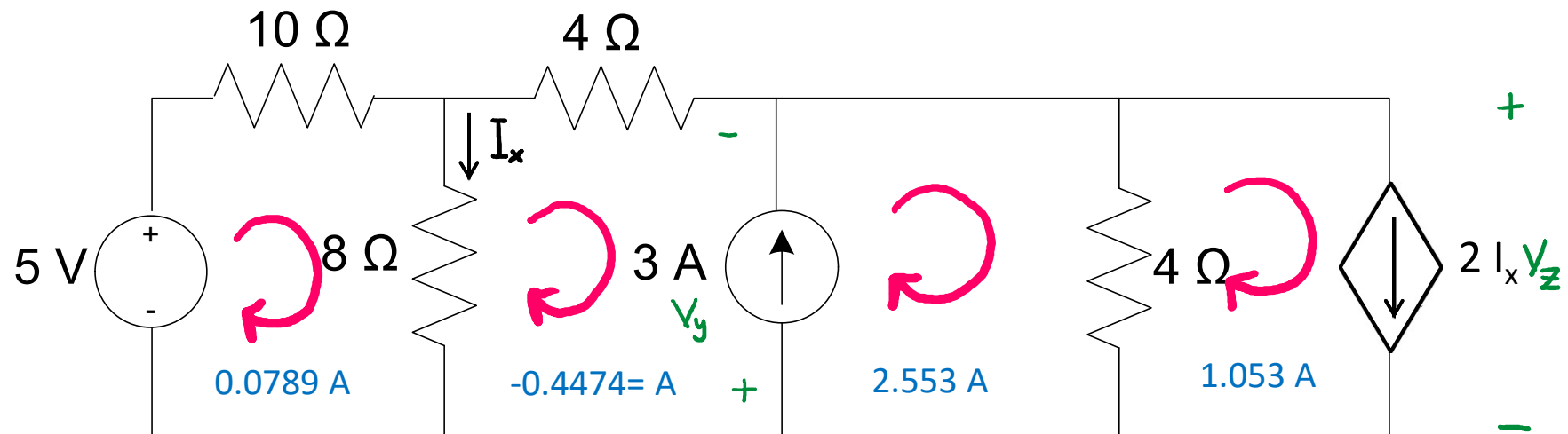

Additional Question (Discuss with friend)

1. Find the voltage at current source, V_y and V_z .
2. Determine the power deliver by **ALL** source.



Nodal VS Mesh

Compare the number of Nodal equations to the number of Mesh equations required.

- ✓ **Choose the less equation would be the better choice.**



Author Information

Nor Rul Hasma Abdullah (Ph. D)
Senior Lecturer

Email:

hasma@ump.edu.my

Google Scholar:

[Nor Rul Hasma](#)

Scopus ID :

35791718100

