

BEE1133 Circuit Analysis

Chapter 5A First Order Circuit

by

Nor Rul Hasma Abdullah
Faculty of Electrical & Electronics Engineering
hasma@ump.edu.my



First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Chapter Description

Aims

This chapter is aimed to:

1. Introduce the source free RC and RL circuit
2. Explain the equation related for both circuit



Expected Outcomes

Student should be able to

1. Determine the source free of both RC and RL circuit

References

1. C. Alexander and M. Sadiku, “Fundamentals of Electric Circuits”, 4th ed., McGraw-Hill, 2008.
2. J. Nilsson and S. Riedel, “Electric Circuits”, 8th ed., Prentice Hall, 2008.




First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

BASIC CONCEPT

- 9.1 Introduction to energy storage elements
- 9.2 The source-free RC circuit
- 9.3 The source-free RL circuit
- 9.4 Unit step function



Practical Application

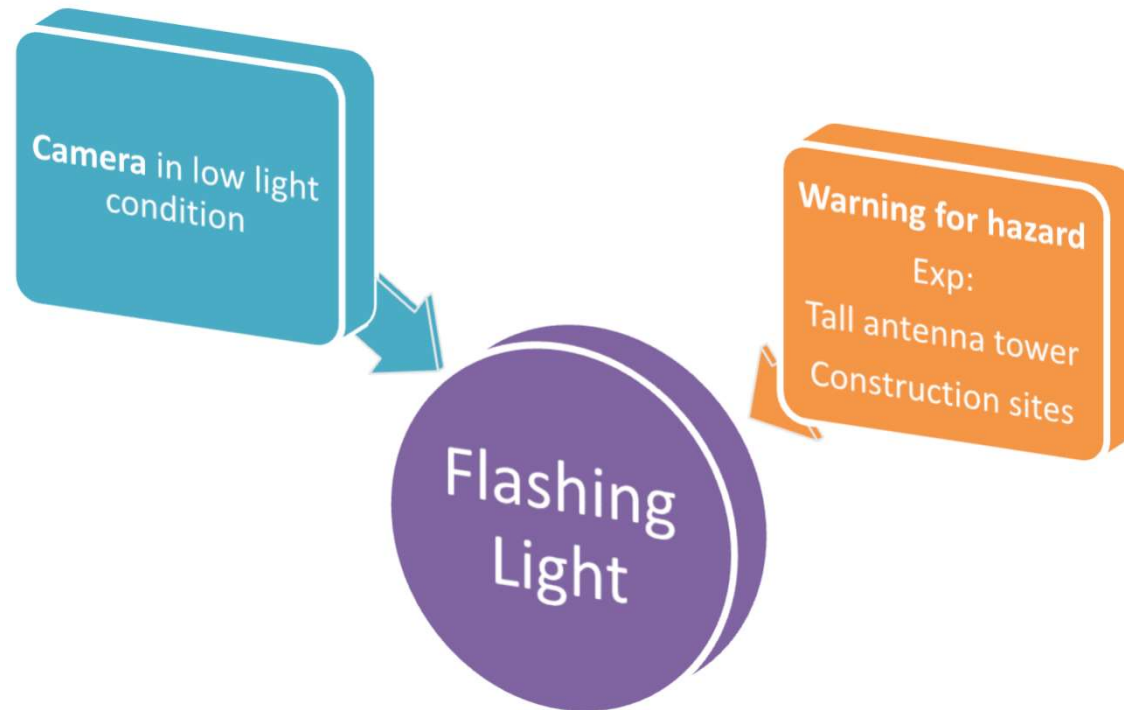

First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

What does First Order mean?


- ❑ Circuits that contain capacitors and inductors can be defined by differential equations
- ❑ circuits with **ONLY ONE** capacitor **OR** **ONLY ONE** inductor can be defined by a first order differential equation



Source FREE?

Source
Free

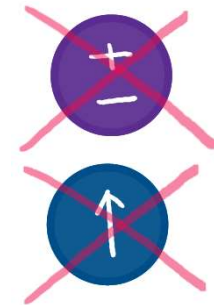
DC source is suddenly
DISCONNECTED
(No source in the circuit)




The energy stored in the
capacitor or inductor
RELEASED to R
(DISCHARGED)



Source FREE?

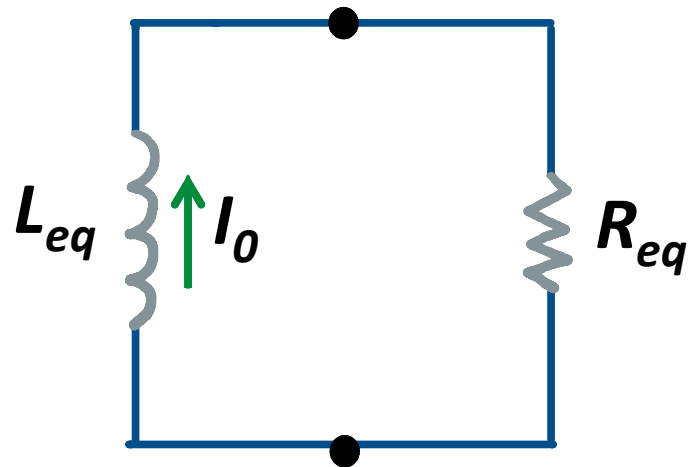

RL Circuit

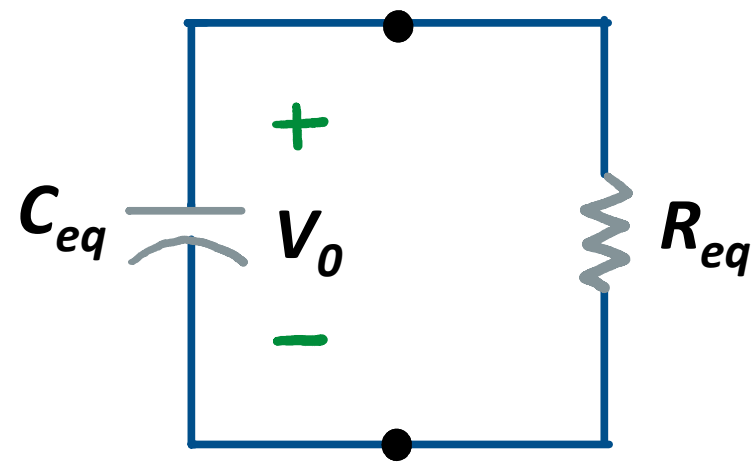


RC Circuit



Switch



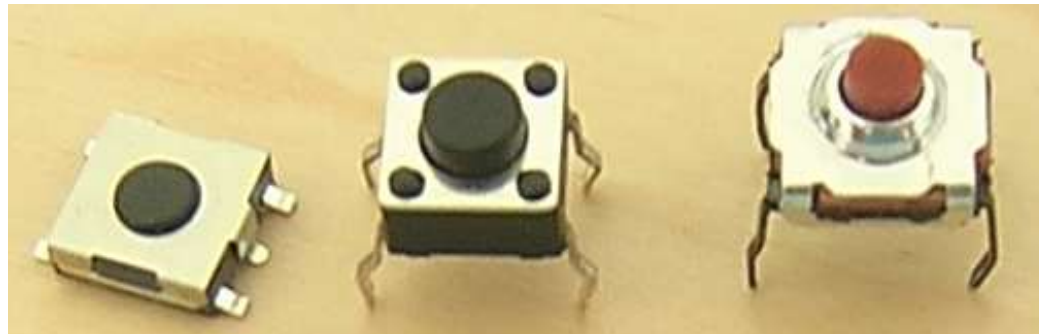Source:
<https://electronics.stackexchange.com>



Source:
http://en.wikipedia.org/wiki/file:tactile_switches.jpg


Please refer to this website for more information regarding the type of electronic switch
<http://tech.txdi.org/switchtypes>




First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Communitising Technology



Circuit Symbol

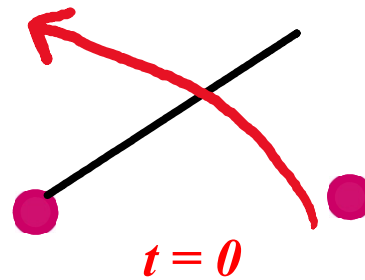


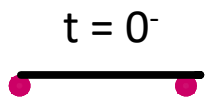
CLOSED for a long time before it **OPEN** at $t=0$




the time just prior to switching

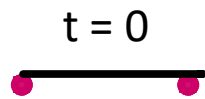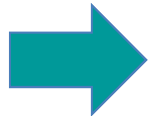

the instant when the switch is opened

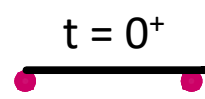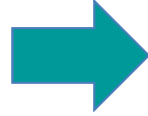

the time immediately following switching

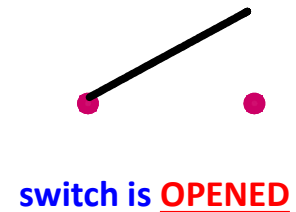


$t > 0$


$t(0)$




Circuit Symbol

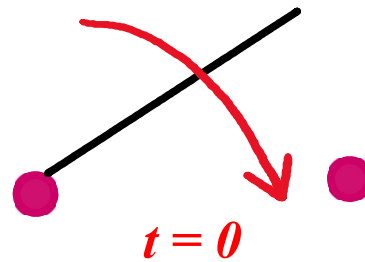

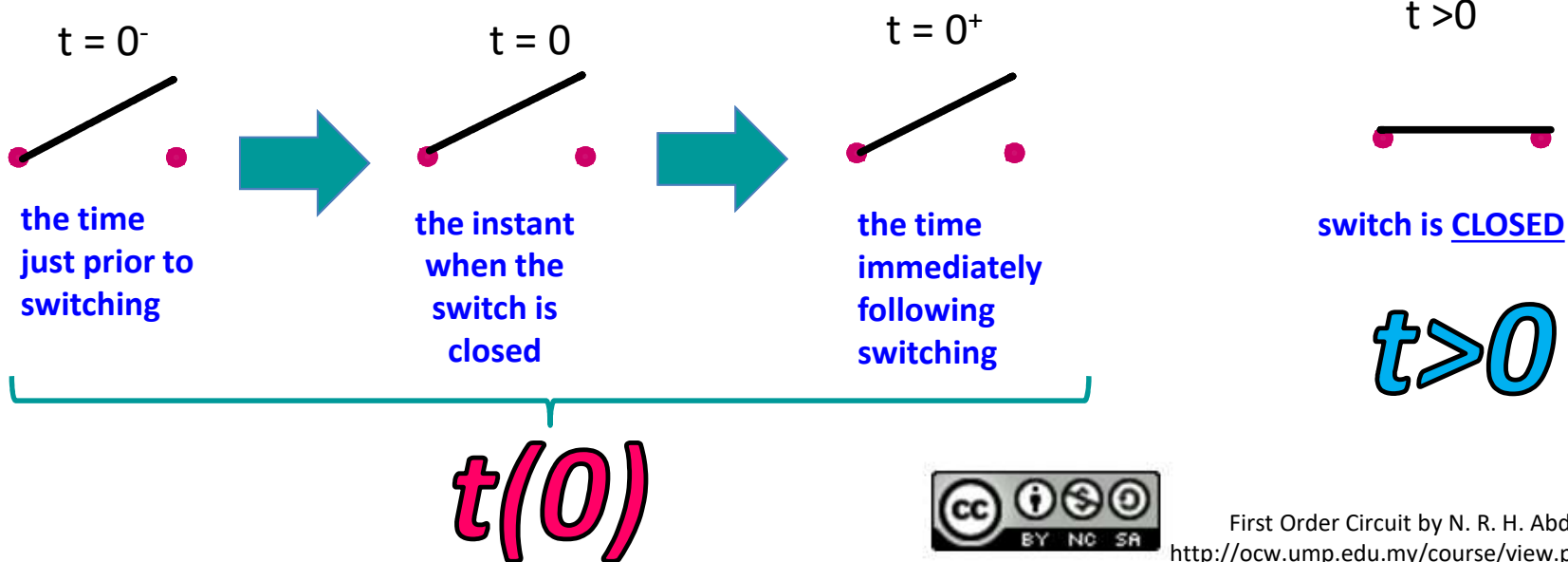OPEN for a long time before it **CLOSED** at $t=0$



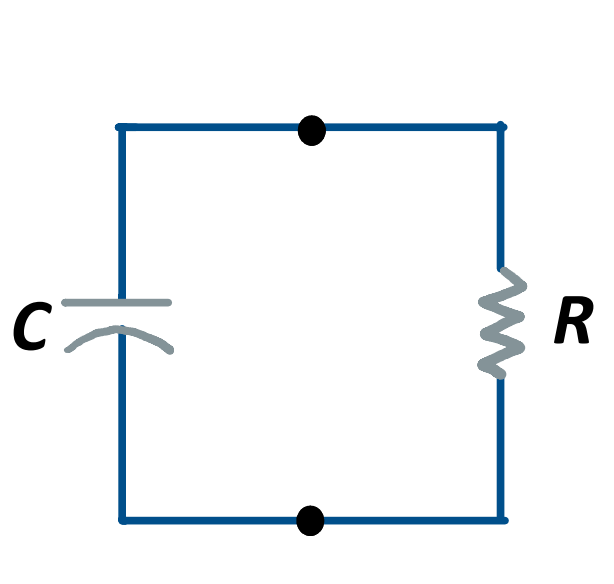

RC CIRCUIT



Thing's To Remember for Capacitor


- If the $V = \text{Constant}$ or DC, I across terminal $C = 0$.

(C is **OPEN CIRCUIT**)

- V cannot change instantaneously across capacitor; that is, such a change would produce infinite voltage.



t > 0

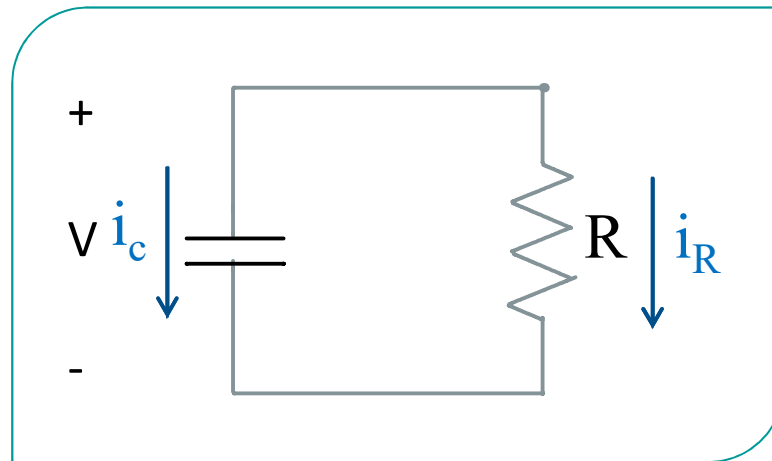

$$I_c + I_R = 0 \quad I_c = C \frac{dV}{dt}$$

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

∴

$$V(t) = V(0) e^{-\frac{t}{RC}}$$

↓
V_o


τ = RC

time constant
(s)

∴ $V(t) = V_o e^{-\frac{t}{\tau}}$



Voltage Response

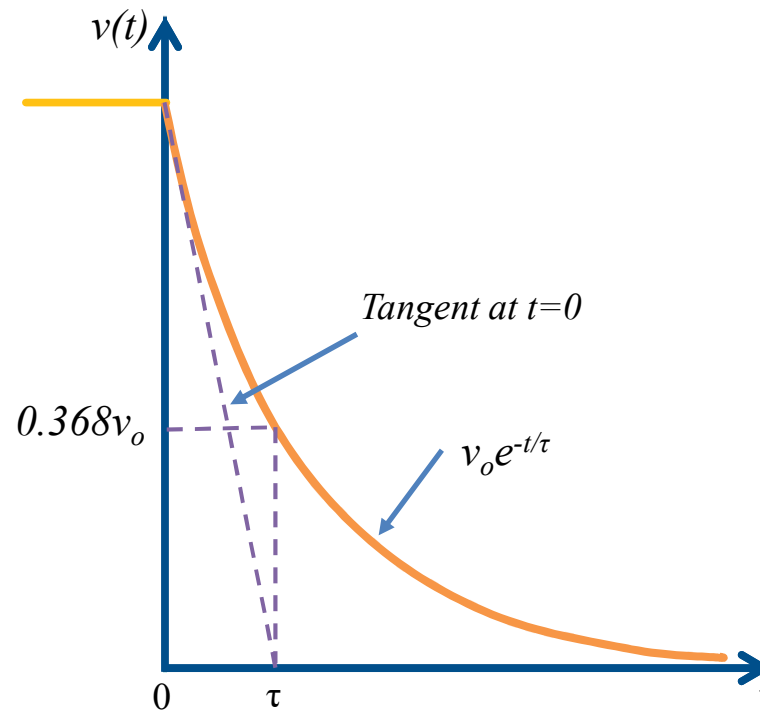

RC Circuit

$$V(t) = V_o e^{-\frac{t}{\tau}}$$

t=0

Find the voltage
across C
(C is open circuit)


t>0

Calculate $\tau=1/RC$
(no source exist in
the circuit when
the switch
started to
operate)



First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

RC Circuit

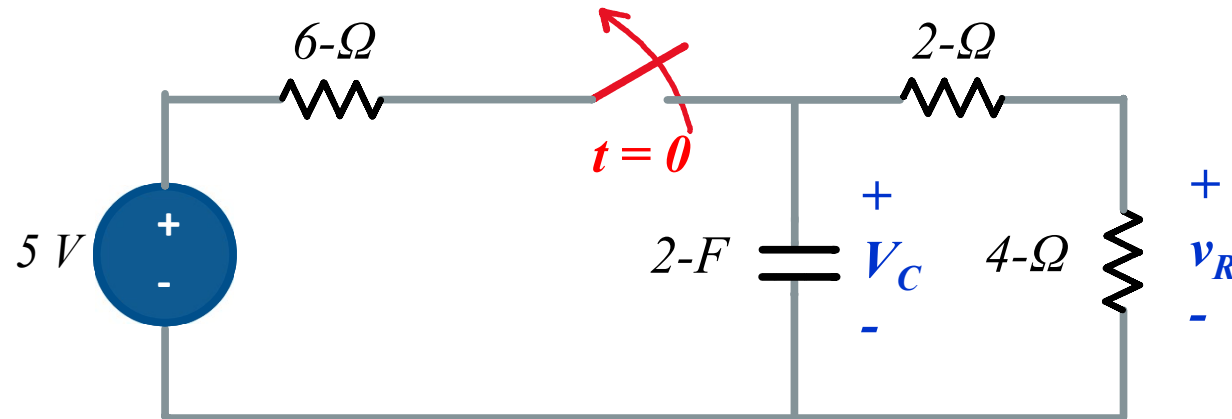


The switch in the circuit has been closed for a long time before it opens at $t=0$. Find

- i. $i_L(t)$ for $t \geq 0$.
- ii. $i_R(t)$ for $t \geq 0$.
- iii. $v_R(t)$ for $t \geq 0$.



STEP 1: Find the initial voltage, $V_C(0)$ across the capacitor, $t = 0$ (C open circuit)

Switch Closed

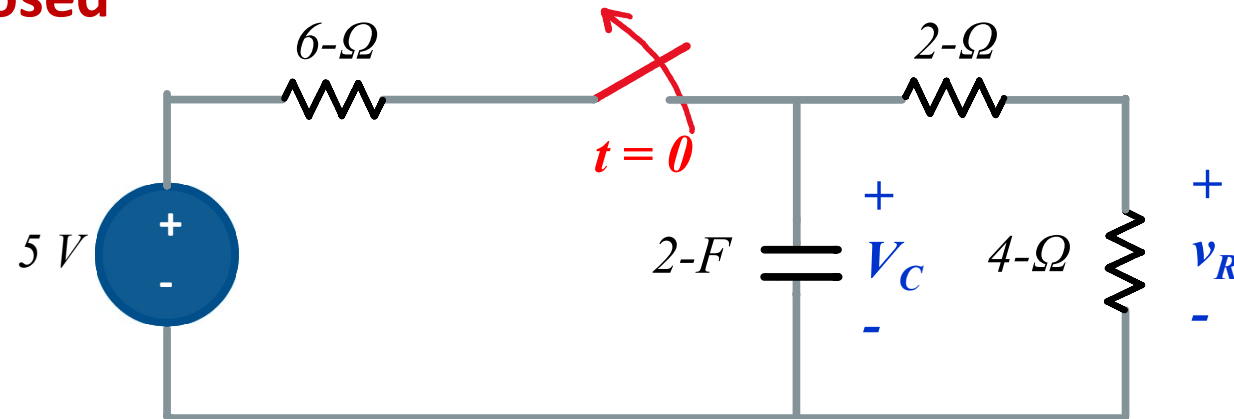


- Assume, 5 V = constant current/dc & switch closed for a long time
- C appears **O/C** prior to release of the stored energy



Cont.

Switch Closed

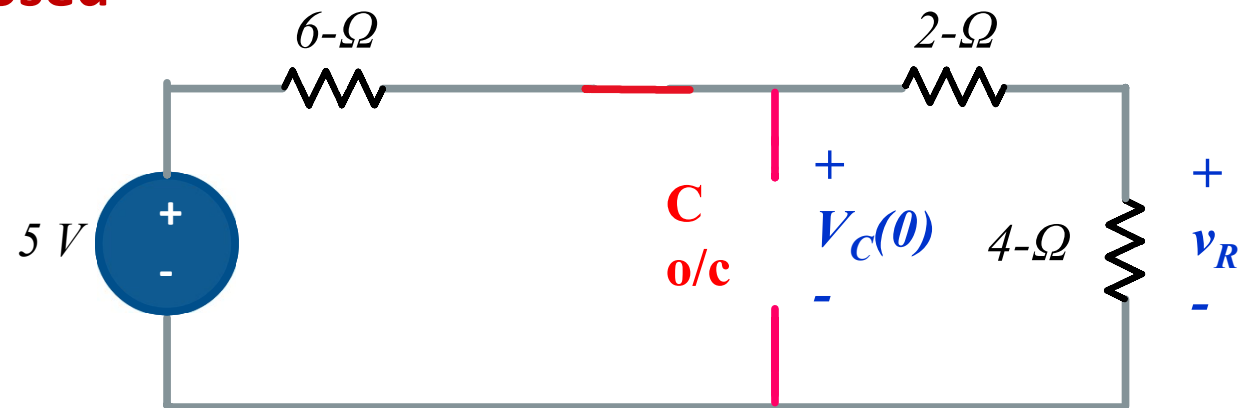


Find $V_C(0)$ using voltage divider,

$$V_C(t) = \frac{2 + 4}{2 + 4 + 6} (5) = 2.5 V$$



STEP 2: Find the time constant of the circuit, τ ($t > 0$)

Switch Open

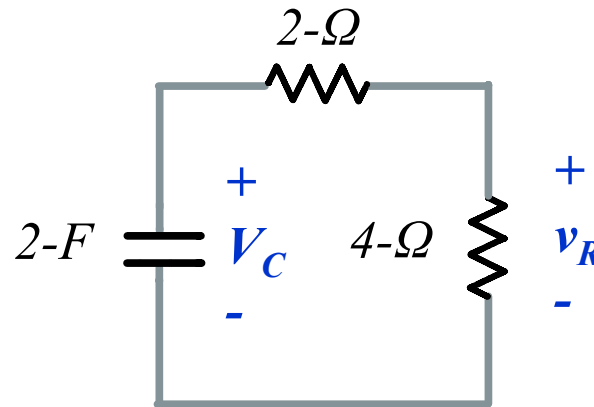

$$\tau = RC = (6)(2) = 12$$



$$V_c(t)$$

i. $V_c(t)$ for $t \geq 0$.

$$\begin{array}{l} t = 0 \\ t > 0 \end{array} \left\{ \begin{array}{l} V_c(0) = 2.5 \text{ V} \\ \tau = 12 \end{array} \right.$$


Substitute

$$\begin{aligned} V_c(t) &= V_c(0) e^{-\frac{t}{\tau}} \\ &= 2.5 e^{-\frac{t}{12}} \text{ V} \end{aligned}$$



$$v_R(t)$$


ii. $v_R(t)$ for $t \geq 0$.

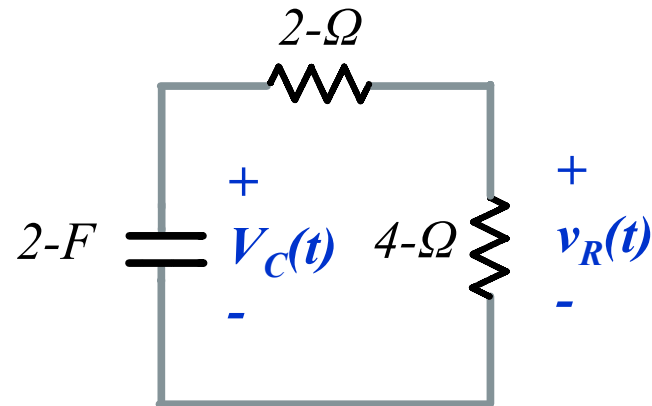

Using Voltage Divider,
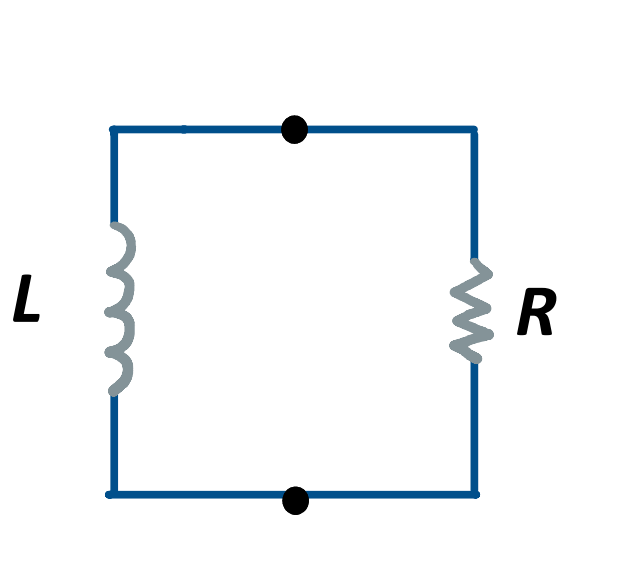
$$v_R(t) = \frac{4}{2+4} (V_C(t)) = \frac{4}{6} (2.5 e^{-\frac{t}{12}}) = 1.67 e^{-\frac{t}{12}} V$$





RL CIRCUIT




Thing's To Remember for Inductor

- If the $I = \text{Constant}$ or DC, V across ideal $L = 0$.
(L is **SHORT CIRCUIT**)
- I cannot change instantaneously in an inductor; that is, the current cannot change by a finite amount in zero time.

Example: When someone opens the switch on an inductive circuit in an actual system, the current initially continues to flow in the air across the switch.



$t > 0$

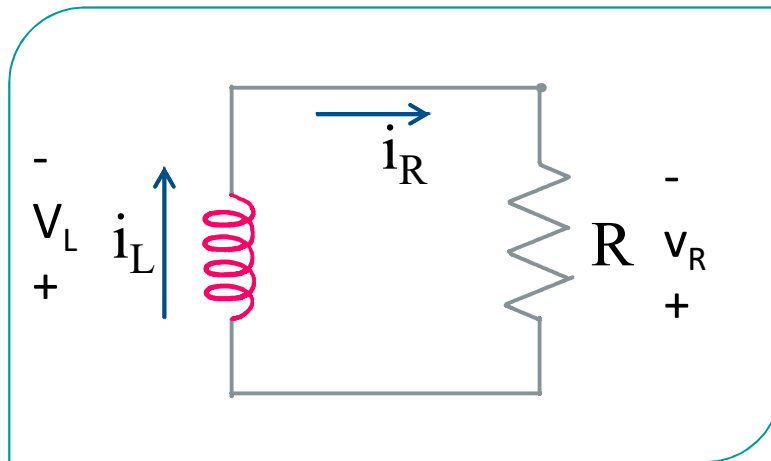

$$V_L + V_R = 0 \quad V_L = L \frac{di}{dt}$$

$$L \frac{di}{dt} + Ri = 0$$

\vdots

$$i(t) = i(0) e^{-\left(\frac{R}{L}\right)t}$$

i_0

$$\tau = \frac{L}{R}$$

time constant
(s)


$$\therefore i(t) = i_0 e^{-\frac{t}{\tau}}$$



RL Circuit

$$i(t) = i_0$$

$$e^{-\frac{t}{\tau}}$$

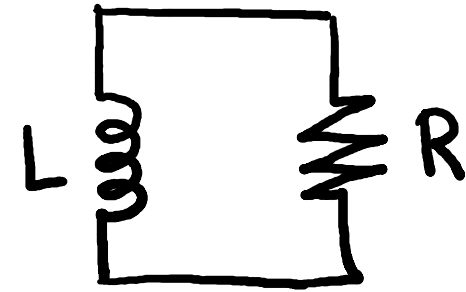


t=0

Find the current flow through L (L is short circuit)


t>0

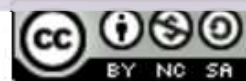Calculate $\tau=L/R$ (no source exist in the circuit when the switch started to operate)




First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Current Response

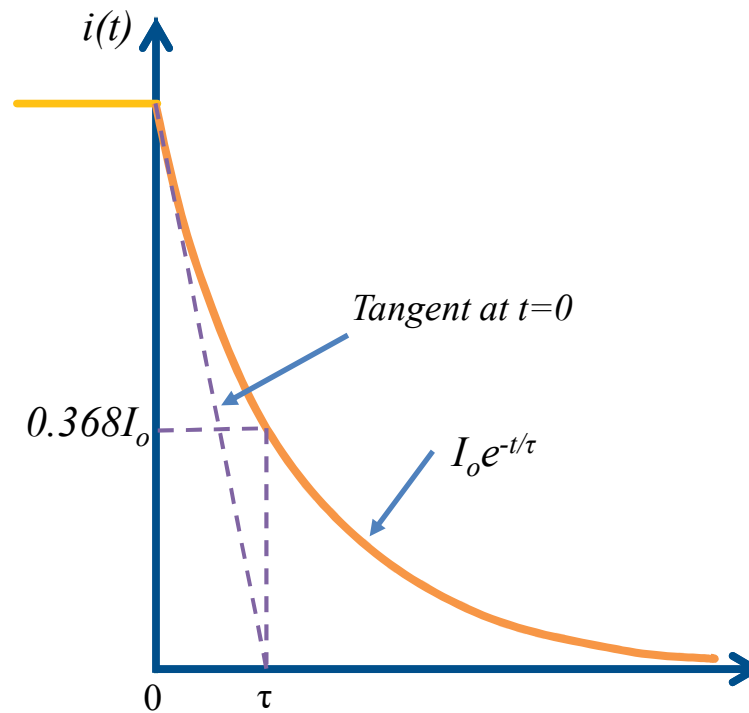

RL Circuit

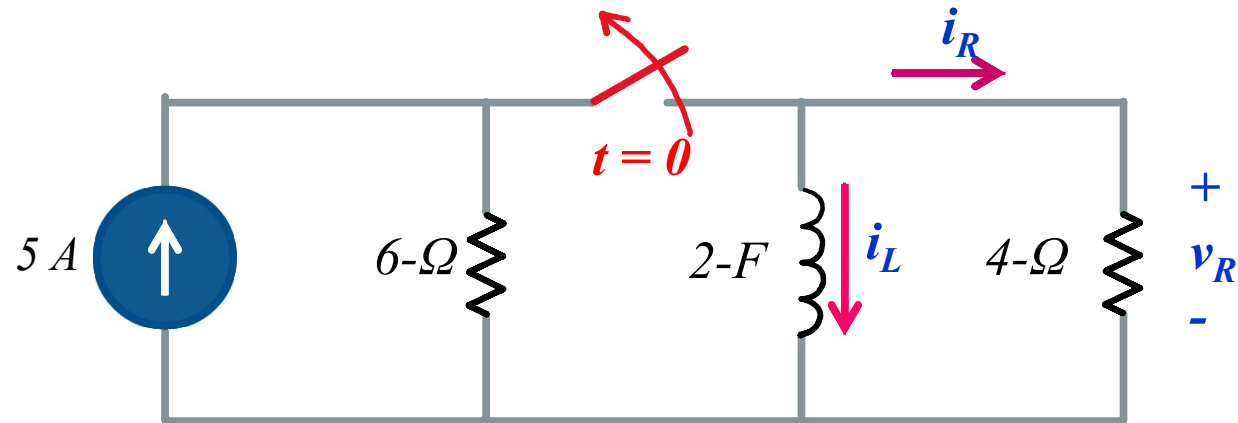


The switch in the circuit has been closed for a long time before it opens at $t=0$. Find

- i. $i_L(t)$ for $t \geq 0$.
- ii. $i_R(t)$ for $t \geq 0$.
- iii. $v_R(t)$ for $t \geq 0$.



STEP 1: Find the initial current, $i_L(0)$ through the inductor, $t = 0$ (L short circuit)

Switch Closed

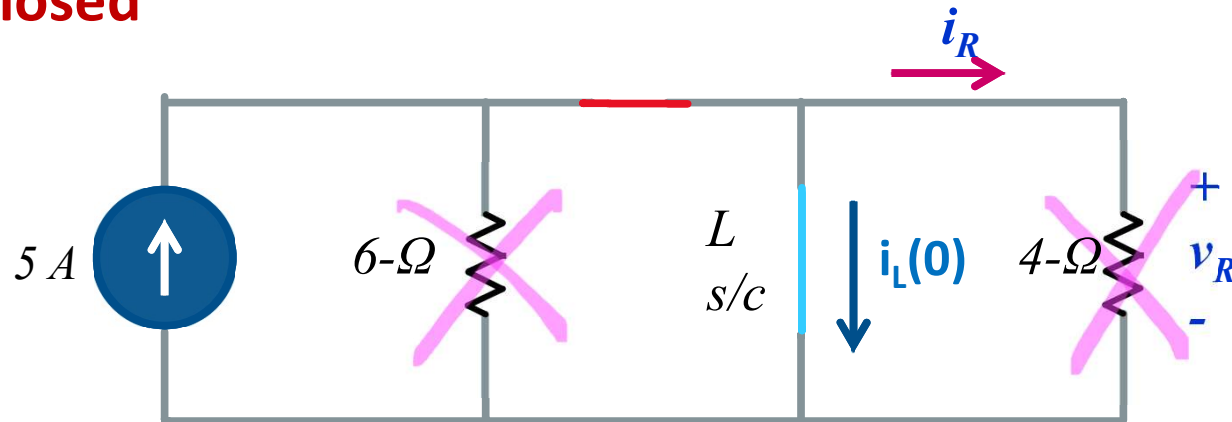


- Assume, 5 A = constant current/dc & switch closed for a long time
- L appears **S/C** prior to release of the stored energy
- Current, 5-A is not flowing across R



Cont.

Switch Closed

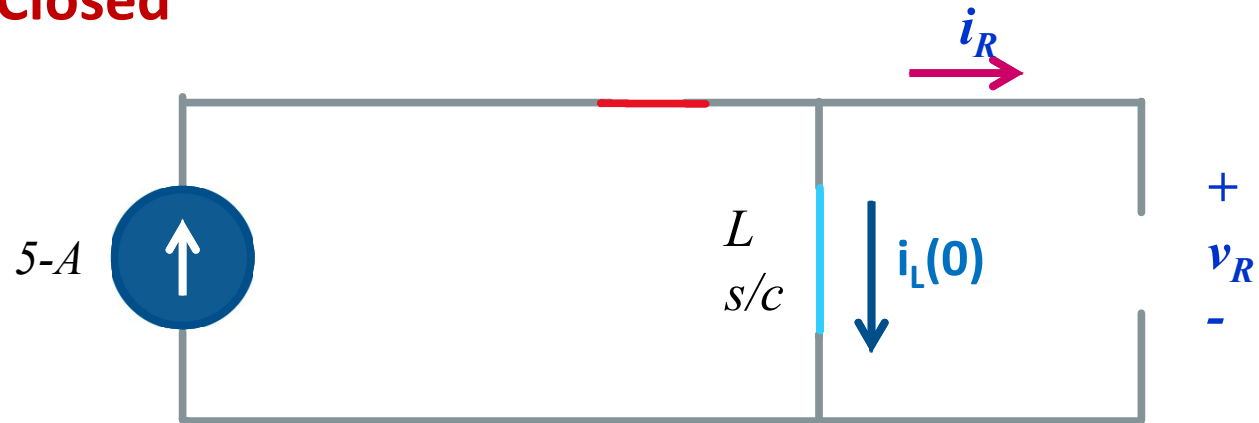


$$i_L(0) = 5 \text{ A}$$



STEP 2: Find the time constant of the circuit, τ ($t > 0$)

Switch Open

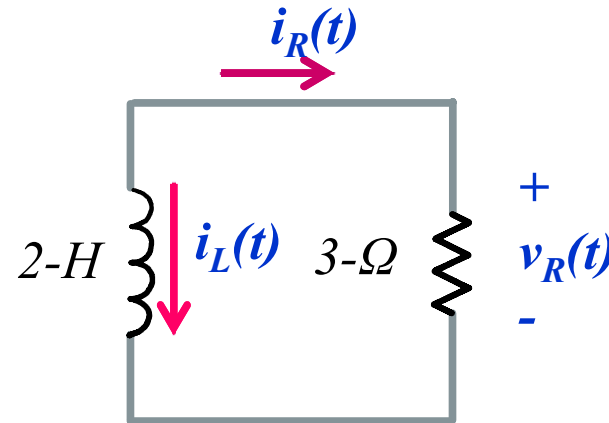

$$\tau = \frac{L}{R} = \frac{2}{4} = 0.5$$



$$i_L(t)$$

i. $i_L(t)$ for $t \geq 0$.

$$\begin{array}{l} t = 0 \\ t > 0 \end{array} \left\{ \begin{array}{l} i_L(0) = 5 \text{ A} \\ \tau = 0.5 \end{array} \right.$$

Substitute


$$\begin{aligned} i_L(t) &= i_L(0) e^{-\frac{t}{\tau}} \\ &= 5 e^{-\frac{t}{0.5}} \text{ A} \\ &= 5 e^{-2t} \text{ A} \end{aligned}$$



$i_R(t)$ and $v_R(t)$

ii. $i_R(t)$ for $t \geq 0$.

iii. $v_R(t)$ for $t \geq 0$.

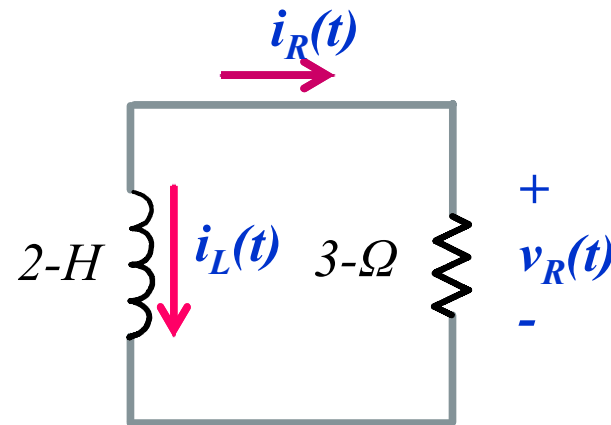

$$i_R(t) = -i_L(t) = -5 e^{-2t} \text{ A}$$

$$v_R(t) = i_R(t) \times R_{3-\Omega} = (-5 e^{-2t})(3) = -15 e^{-2t} \text{ V}$$



Author Information

Nor Rul Hasma Abdullah (Ph. D)
Senior Lecturer

Email:

hasma@ump.edu.my

Google Scholar:

[Nor Rul Hasma](#)

Scopus ID :

35791718100



First Order Circuit by N. R. H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>