



**Faculty of Electrical & Electronics Engineering**  
**BEE1133 Circuit Analysis I**

Name: \_\_\_\_\_

ID: \_\_\_\_\_

Section: \_\_\_\_\_

Date: \_\_\_\_\_

(Failed to complete all the particulars above will be penalized 2 marks)

**QUIZ 4**

**Mapping CO, PO: CO1,PO1**

CO2: Analyze DC circuit problems using circuit theorem, nodal analysis and mesh, and formulate the natural and forced responses of first order circuit.

PO1: Acquire and apply knowledge of sciences and electrical & electronics engineering fundamentals.

The switch in Fig. 1 has been closed for a long time, and it opens at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ .

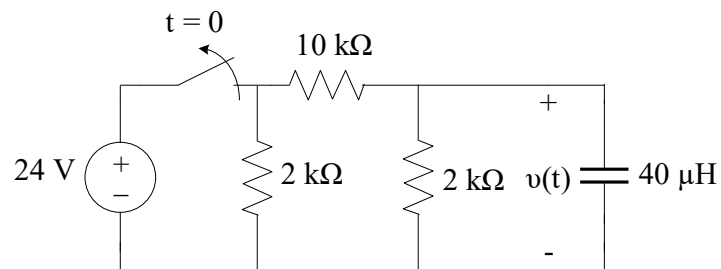


Figure 1

**[10 marks]**