



**FACULTY OF ELECTRICAL & ELECTRONICS ENGINEERING**  
**FINAL EXAMINATION**

<b>COURSE</b>	<b>:</b>	<b>CIRCUIT ANALYSIS I/ ELECTRIC CIRCUITS I</b>
<b>COURSE CODE</b>	<b>:</b>	<b>BEE1133/ BEE1113</b>
<b>LECTURER</b>	<b>:</b>	<b>DR. NOR RUL HASMA BINTI ABDULLAH</b>
<b>DATE</b>	<b>:</b>	
<b>DURATION</b>	<b>:</b>	<b>3 HOURS</b>
<b>SESSION/SEMESTER</b>	<b>:</b>	<b>SESSION 2012/2013 SEMESTER 2</b>
<b>PROGRAMME CODE</b>	<b>:</b>	<b>BEE/BEP/BEC</b>

**INSTRUCTIONS TO CANDIDATES**

1. This question paper consists of **FIVE (5)** questions. Answer **ALL** the questions.
2. All answers to a new question should start on new page.
3. All the calculations and assumptions must be clearly stated.

**EXAMINATION REQUIREMENTS**

**Appendix 1:** Table of Formula

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO**

---

This examination paper consists of **NINE (9)** printed pages including front page

**QUESTION 1**

a) Figure 1 shows an example of an electric circuit. Determine;

(i) Kirchoff's Voltage Law (KVL) equation for each loop.

(ii) The voltage,  $V_2$ .

(iii) The voltage,  $V_3$  if voltage,  $V_4$  is given as 3.3 V.

**[8 Marks]**  
**[CO1, PO1, C3]**

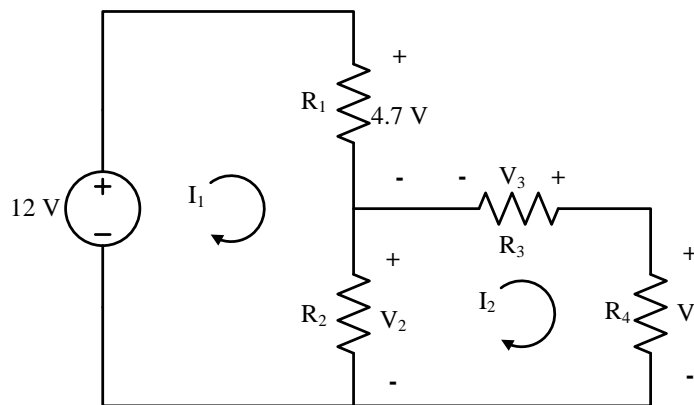


Figure 1

b) By applying  $\Delta \leftrightarrow Y$  transformation technique to the circuit in Figure 2, determine;

- (i) The equivalent resistance,  $R_{eq}$ .
- (ii) The value of current,  $I_o$ .
- (iii) The value of voltage,  $V_o$ .
- (iv) The power dissipated by 4- $\Omega$  resistor at  $V_o$ .
- (v) The power delivered by independent voltage source.

[12 Marks]  
[CO1, PO1, C4]

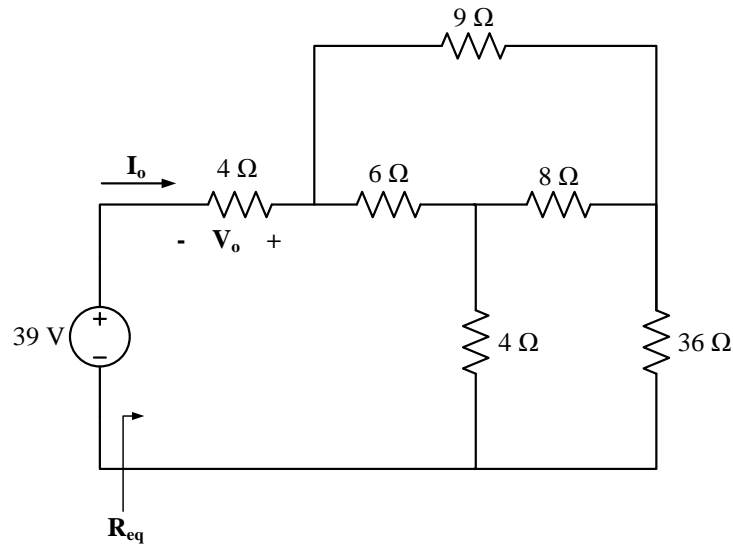


Figure 2

**QUESTION 2**

Perform Mesh analysis to the circuit in Figure 3, then

- Determine all the value of unknown mesh currents,  $I_1$ ,  $I_2$  and  $I_3$ .
- Calculate the power delivered by dependent current source.

[15 Marks]  
[CO2, PO1, C4]

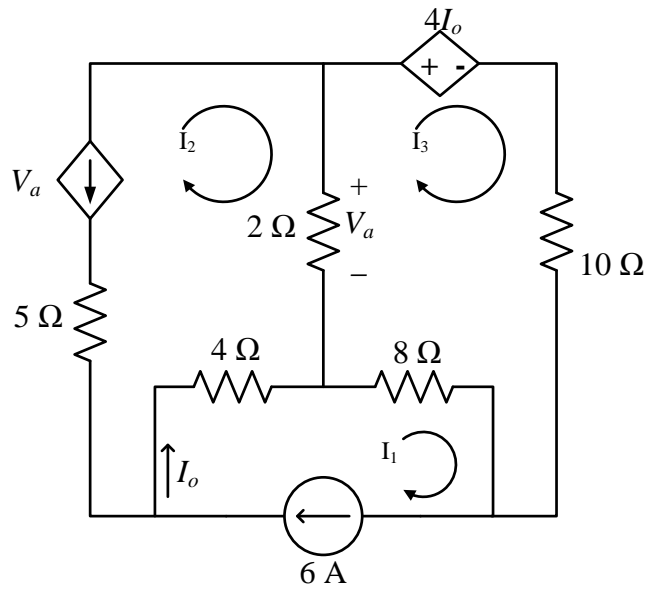


Figure 3

**QUESTION 3**

A modified bridge circuit is shown in Figure 4. By using Thevenin theorem;

- a) Find the Thevenin equivalent resistance,  $R_{th}$  at terminal a-b.
- b) Find the Thevenin voltage,  $V_{th}$  across terminal a-b
- c) Draw the Thevenin equivalent circuit
- d) From 3(c), draw the Norton equivalent circuit and find the current through  $R_L=1\Omega$ .
- e) Calculate the maximum power,  $P_{max}$  transferred to the load.

**[20 Marks]**  
**[CO2, PO1, C4]**

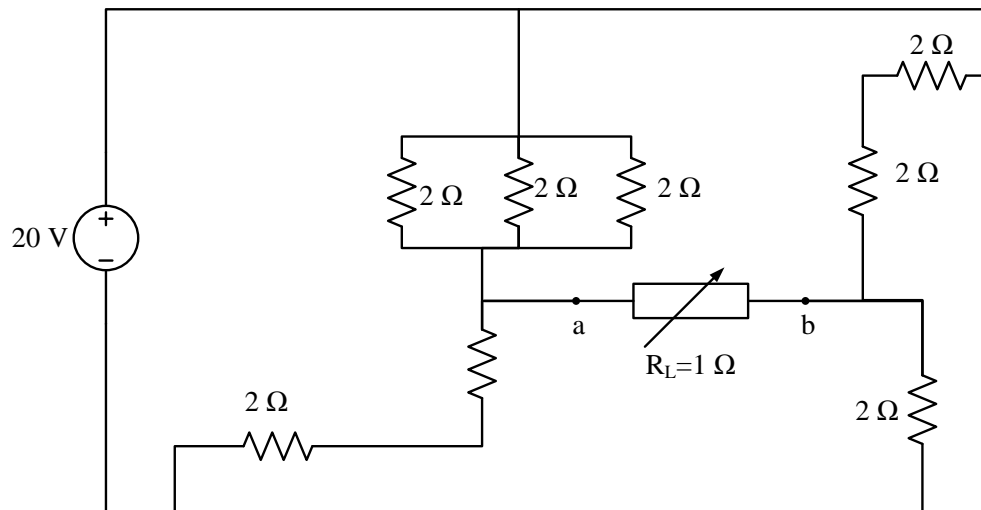


Figure 4

**QUESTION 4**

The switch,  $s$  in Figure 5 was at position 'a' for a long time. At  $t = 0$ , the switch is move to position 'b'. Find the expression for  $v(t)$  for  $t \geq 0$ .

[15 Marks]  
[CO2, PO1, C4]

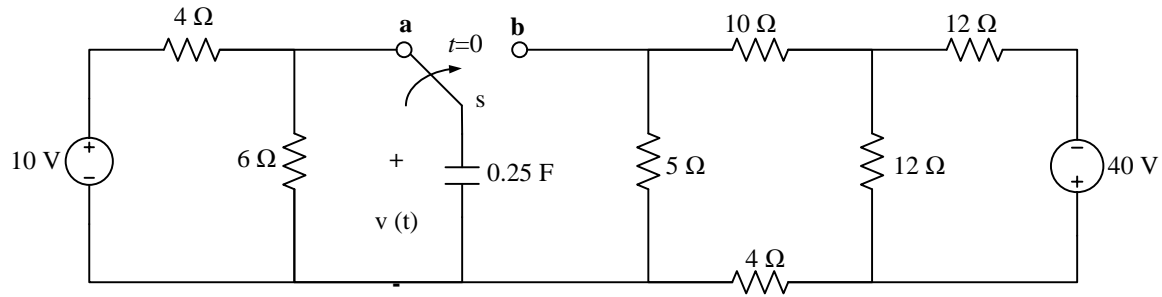


Figure 5

**QUESTION 5**

a) For the circuit shown in Figure 6;

- (i) Obtain the equivalent circuit in frequency domain.
- (ii) Determine the impedance,  $Z_x$  as seen looking into terminals a-b.
- (iii) Find the voltage,  $v_x$ .
- (iv) Calculate the voltage,  $v_o$ .

**[10 Marks]**  
**[CO3, PO1, C4]**

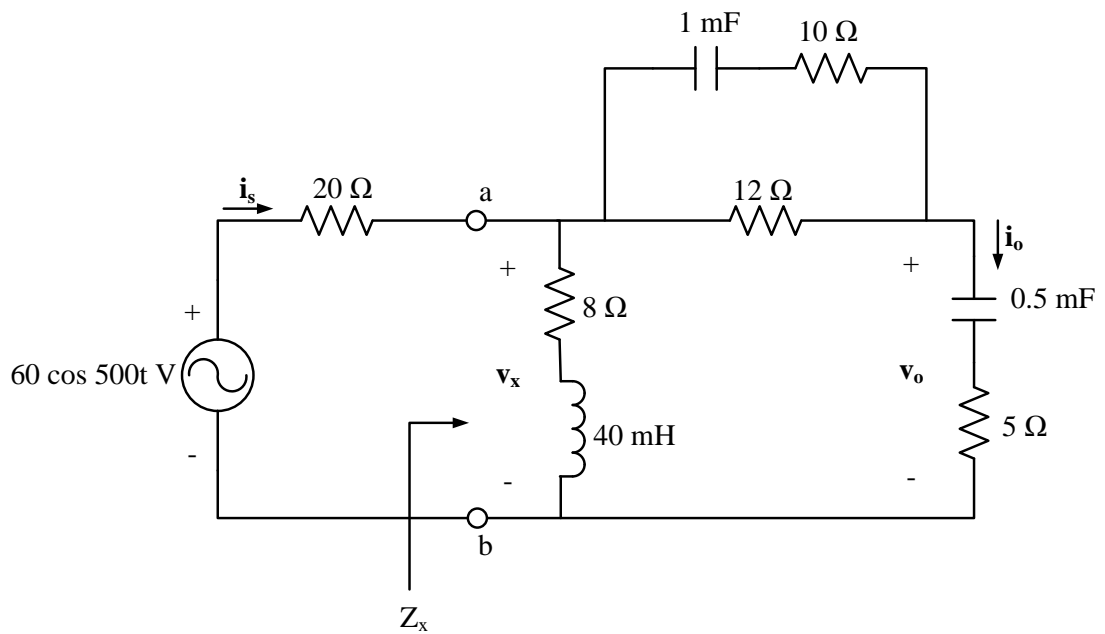


Figure 6

b) Use Nodal analysis to determine the voltage,  $V_x$  and  $V_z$  for the circuit shown in Figure 7.

[20 Marks]  
[CO3, PO1, C5]

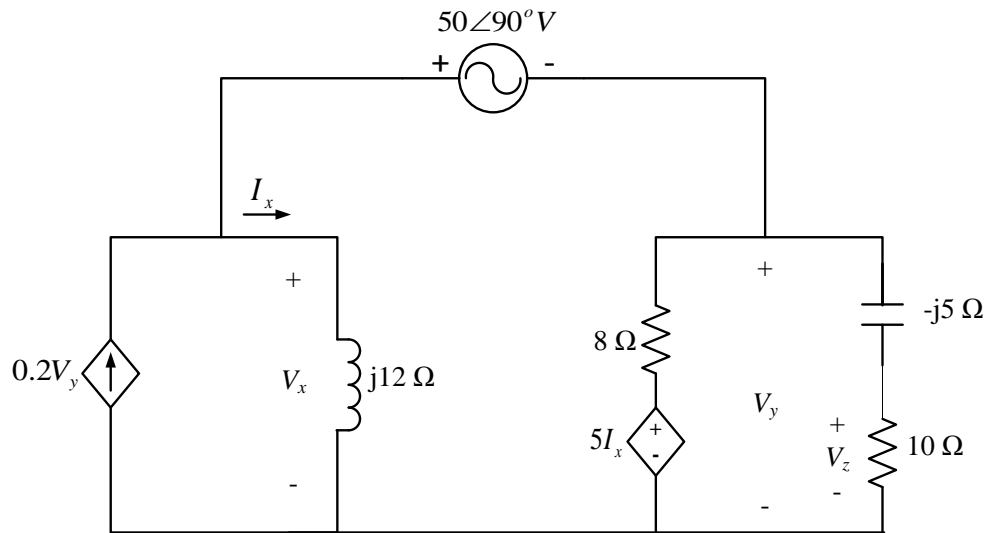


Figure 7

END OF QUESTION PAPER



## APPENDIX I –Table of Formula

<p>(1) Y-<math>\Delta</math> Transformation</p> $R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$ $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$ $R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$	<p>(2) <math>\Delta</math>-Y Transformation</p> $R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$ $R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$
<p>(3)</p> $V_c = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$ $i_L = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$	<p>(4)</p> $i_c = C \frac{dv}{dt};$ $V_L = L \frac{di}{dt}$
<p>(5)</p> $v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$	<p>(6)</p> $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$