

For updated version, please click on
<http://ocw.ump.edu.my>

Antenna & Propagation

Transmission Line Using Smith Chart

by

Nor Hadzfizah Binti Mohd Radi
Faculty of Electric & Electronics Engineering
hadzfizah@ump.edu.my



Smith Chart by
Nor Hadzfizah Mohd Radi

Chapter Synopsis

In this chapter, the student will be exposed to use the Smith Chart as a tool to obtain several measurements in a transmission line.



**Smith Chart by
Nor Hadzfizah Mohd Radi**

Teaching Outcome

At the end of this chapter student should be able to:

- Use the Smith Chart in order to find the measurement of parameters in transmission line.
- Understand the definition of VSWR, reflection coefficient, Return Loss, Impedance and First minimum and maximum voltage.



Smith Chart by
Nor Hadzfizah Mohd Radi

Outline

Introduction

Impedance

Reflection Coefficient

VSWR

First Voltage min and max



Smith Chart by
Nor Hadzfizah Mohd Radi

Introduction

- Philip Smith of Bell Laboratories developed the “Smith Chart” back in the 1930’s to simplify the complex and repetitive solution of certain radio frequency (RF) design problems. These include:

Transmission line problems

RF amplifier design and analysis


L-C impedance matching networks

Plotting of antenna impedance



Smith Chart by
Nor Hadzfizah Mohd Radi

Equivalent of Transmission Line

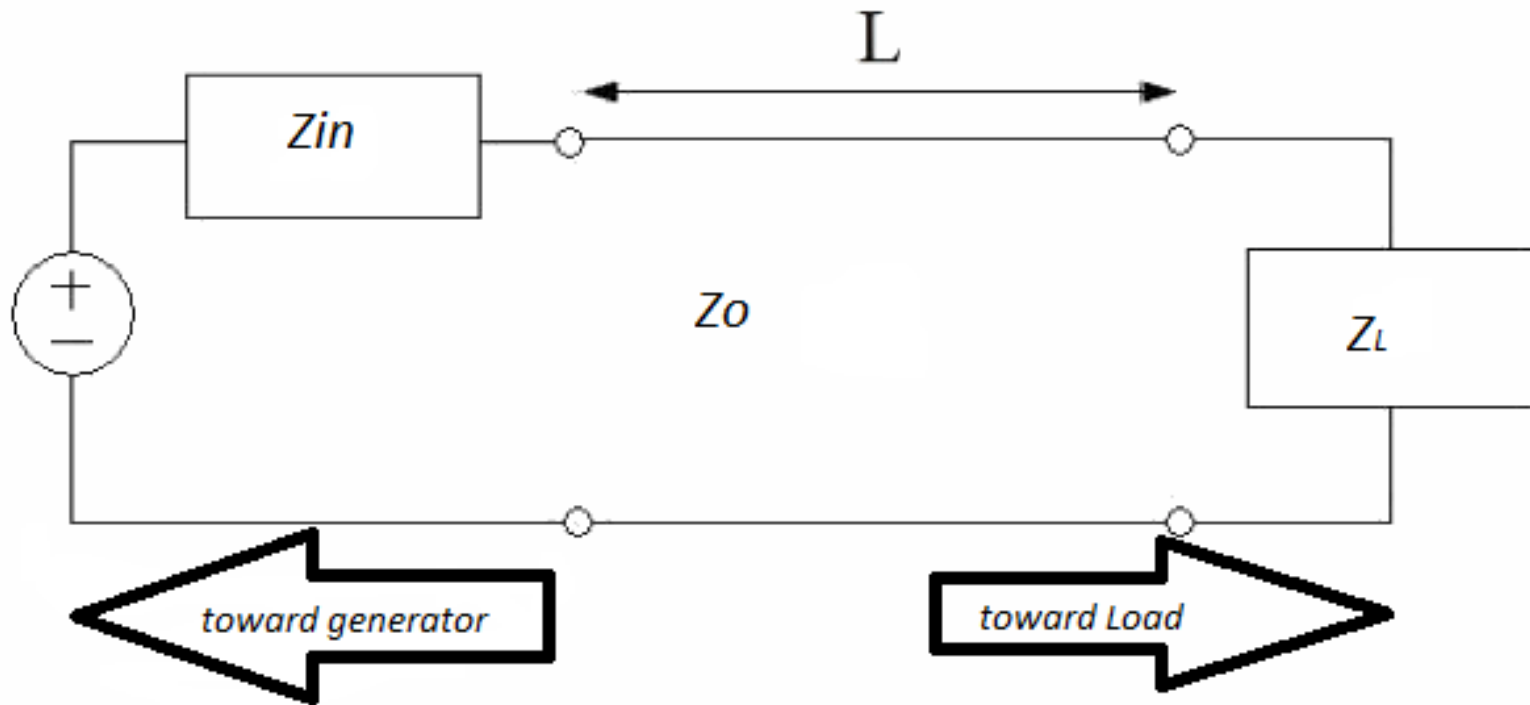

Smith Chart by
Nor Hadzfizah Mohd Radi

Smith Chart Overview

- The Smith Chart is a clever tool for analyzing transmission lines.
- The outside of the chart shows location on the line in wavelengths.
- The combination of intersecting circles inside the chart allow us to locate the normalized impedance and then to find the impedance anywhere on the line.



Smith Chart by
Nor Hadzfizah Mohd Radi

Smith Chart

- The smith chart is available in:

http://www.ieee.hr/download/repository/smithov_dijagram.pdf



Smith Chart by
Nor Hadzfizah Mohd Radi

Steps on How to use Smith Chart


1. Locate the normalized impedance on the chart for $Z_L' = Z_L / Z_o$. (usually Z_o 50 Ω and 75 Ω).
2. Then draw the circle through the point from origin and get the value of SWR. This circle is called SWR circle.
3. Extend the plotted Z_L' to get the angle of reflection coefficient.
4. By given the length of transmission line calculate the distance towards the generator in λ from the extended plot of Z_L' .
5. Find the wavelength and make a line from origin. The intersection between line and circle is a point of Z_{in}' . De-normalized this value by $Z_{in}' \times Z_o$.
6. Get the value of distance for first voltage minimum and maximum by find the distance (in λ) from line of Z_L' to minimum and maximum voltage (v_{max} at 0.25λ) and (v_{min} at 0.0λ).



Smith Chart by
Nor Hadzfizah Mohd Radi

Impedance Axis

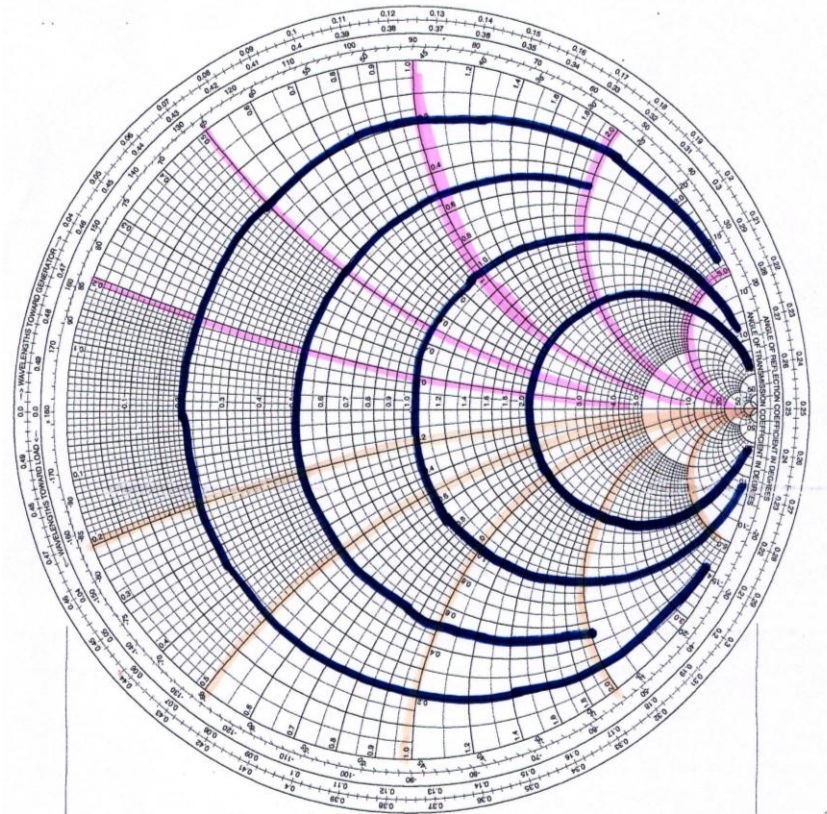- There are real impedance and imaginary axis.
 - ✓ Black represent the real impedance (R_L)
 - ✓ Pink represent the positive imaginary impedance ($+jX_L$)
 - ✓ Orange represent the negative imaginary impedance ($-jX_L$)



Smith Chart by
Nor Hadzfizah Mohd Radi

Reflection Coefficient

- The reflection coefficient is also known as s11 or Return Loss (RL).
- The reflection coefficient is a parameter that describes how much of an electromagnetic wave is reflected by an impedance discontinuity in the transmission medium.
- Can be calculated as:

$$\tau = \frac{Z_L - Z_o}{Z_L + Z_o} \text{ (unitless)}$$



Smith Chart by
Nor Hadzfizah Mohd Radi

VSWR

- The VSWR (Voltage Standing Wave Ratio) and is also referred to as Standing Wave Ratio (SWR) .
- It is measure for how much power is reflected.
- A low valued VSWR indicates that the majority of the incident power is delivered to the antenna and reflections are nearly avoided.
- The VSWR is always a real and positive number for antennas.
- The minimum VSWR is 1.0. In this case, no power is reflected from the antenna, which is called as ideal.
- In practice, if the VSWR is under 2 the antenna match is considered very good.



VSWR

- If the reflection coefficient (τ) is given, then the VSWR is defined by the following formula:

$$vswr = \frac{1 + |\tau|}{1 - |\tau|}$$

- See the table next to see a numerical mapping between reflected power, s_{11} and VSWR.



VSWR Table

VSWR	Power Reflected , Pr(%)	Power Transmitted, Pt(%)	Return Loss, RL(dB)	Reflection Coefficient, τ
1.25	1	99	20	0.11
1.58	5	95	13	0.22
1.92 ~ 2	10	90	10	0.32
5.80	50	50	3	0.71

$$\% Pr = \tau^2 \times 100$$

$$\% Pt = 1 - \tau^2 \times 100$$

$$RL (dB) = 20 \log |\tau|$$


$$\tau = \frac{VSWR-1}{VSWR+1}$$



Smith Chart by
Nor Hadzfizah Mohd Radi

First Voltage Min and Max

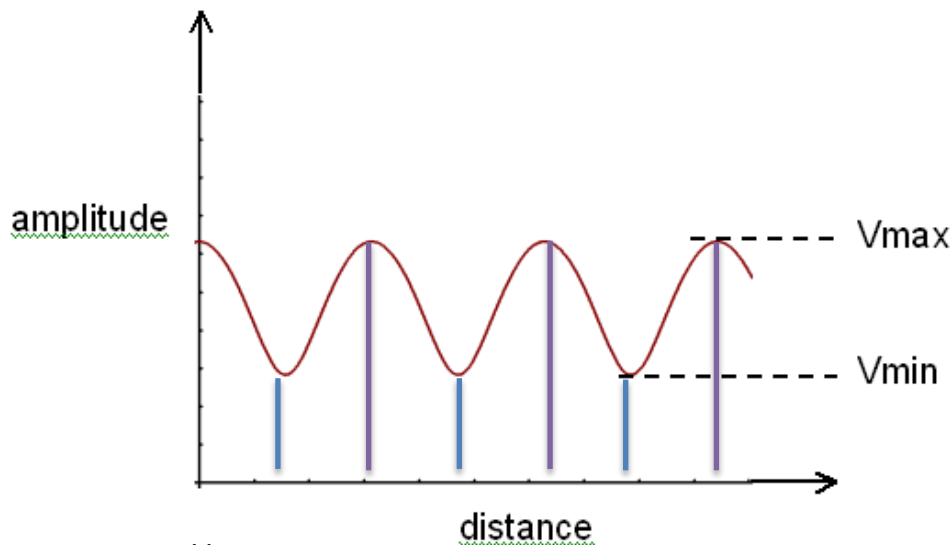- In Smith Chart, the distance of the voltage minimum and maximum from the load can be measured.
- The voltage minimum and maximum repeat every $\lambda/2$.
- Figure below shows the standing wave on the transmission line. The distance occur for voltage minimum are in blue line, while voltage maximum in purple line.



Source: <https://en.wikipedia.org>




Smith Chart by
Nor Hadzfizah Mohd Radi

Example

Figure below shows an equivalent circuit of transmission line. A lossless $Z_o = 50\Omega$ transmission line $L = 0.4\lambda$ in length is terminated in $Z_L = 60 + j50\Omega$. Find the:

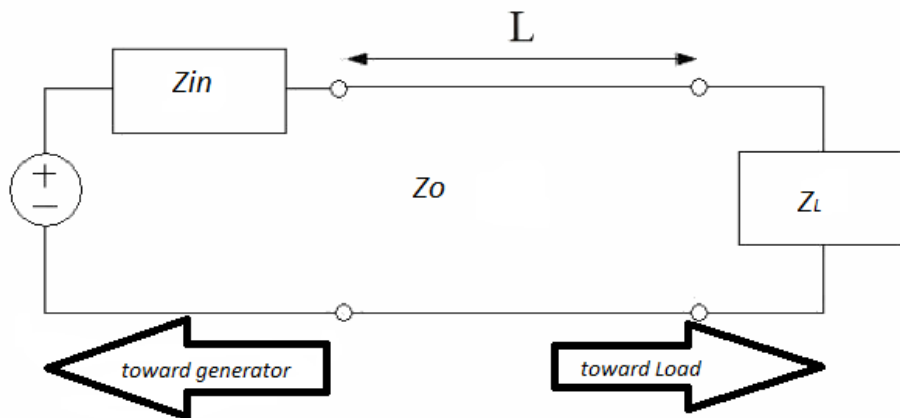- i. VSWR
- ii. Reflection Coefficient
- iii. Input impedance (Z_{in})
- iv. Distance of first voltage minimum and maximum



Smith Chart by
Nor Hadzfizah Mohd Radi

Solution (1)

- First step normalized the $Z_L = 60 + j50 \Omega$ by divide with $Z_o = 50\Omega$. And get $Z_L' = 1.2 + j1 \Omega$
- Plot this Z_L' on the smith chart. (refer next page in Solution (3))
 - i. VSWR, draw the circle and get the value of 2.5
 - ii. Reflection Coefficient,
$$\tau = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{60 + j50 - 50}{60 + j50 + 50} = 0.247 + j0.342 = 0.423 \angle 54.25^\circ$$

Or using the smith chart you can find the reflection coefficient (refer next page)

- iii. Input impedance (Z_{in}), extend the line of Z_L' and get the (WTG) wavelength toward generator (0.175λ). Then plus with 0.4λ and get the value of 0.575λ . Note that smith chart is 0.5λ cycle, so $0.575\lambda - 0.5\lambda = 0.075\lambda$. Draw a line from 0.075λ (WTG) to origin. And the intersection of circle and line is the value of Z_{in}' . De-normalized this value and get $25 + j20 \Omega$



Solution (2)

- iv. Distance of first voltage minimum and maximum from the load to generator:


$$\text{Distance 1}^{\text{st}} V_{\text{max}} = 0.25\lambda - 0.175\lambda = 0.075\lambda$$

$$\text{Distance 1}^{\text{st}} V_{\text{min}} = 0.25\lambda + 0.075\lambda = 0.325\lambda$$

- Note: if given the frequency operation, the value of distance can be presented in unit meter.



Solution (3)

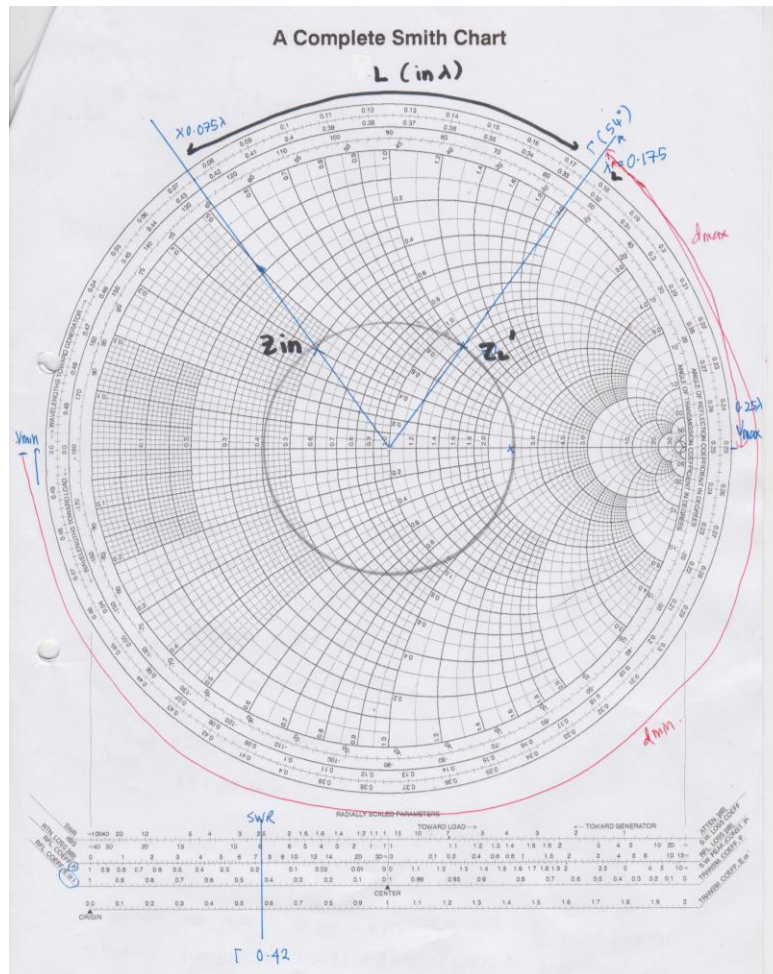

Smith Chart by
Nor Hadzfizah Mohd Radi

References

- [1] C.A. Balanis: "Antenna Theory: Analysis & Design", John Wiley & Sons, 2012.
- [2] Stutzman and Thiele, *Antenna Theory and Design*, John Wiley, 2012.
- [3] T. A. Milligan, "Modern Antenna Design" John Wiley, 2nd edition, 2005.



Smith Chart by
Nor Hadzfizah Mohd Radi

For updated version, please click on
<http://ocw.ump.edu.my>

Author Information

Nor Hadzfizah Binti Mohd Radi

Lecturer

FKEE, UMP

email

hadzfizah@ump.edu.my



Smith Chart by
Nor Hadzfizah Mohd Radi