

For updated version, please click on  
<http://ocw.ump.edu.my>

# Principles of Communication Systems

## Chapter 3 (part 2): FM Transmitter & Receiver

by

Nurulfadzilah Hasan

Faculty of Electrical & Electronics Engineering

[nurulfadzilah@ump.edu.my](mailto:nurulfadzilah@ump.edu.my)




# Lesson Outcomes

“ By the end of this topics students should be able to:

- . Explain how FM transmitters and receivers operate
- . Describe how FM overcomes noise

# FM Transmitter

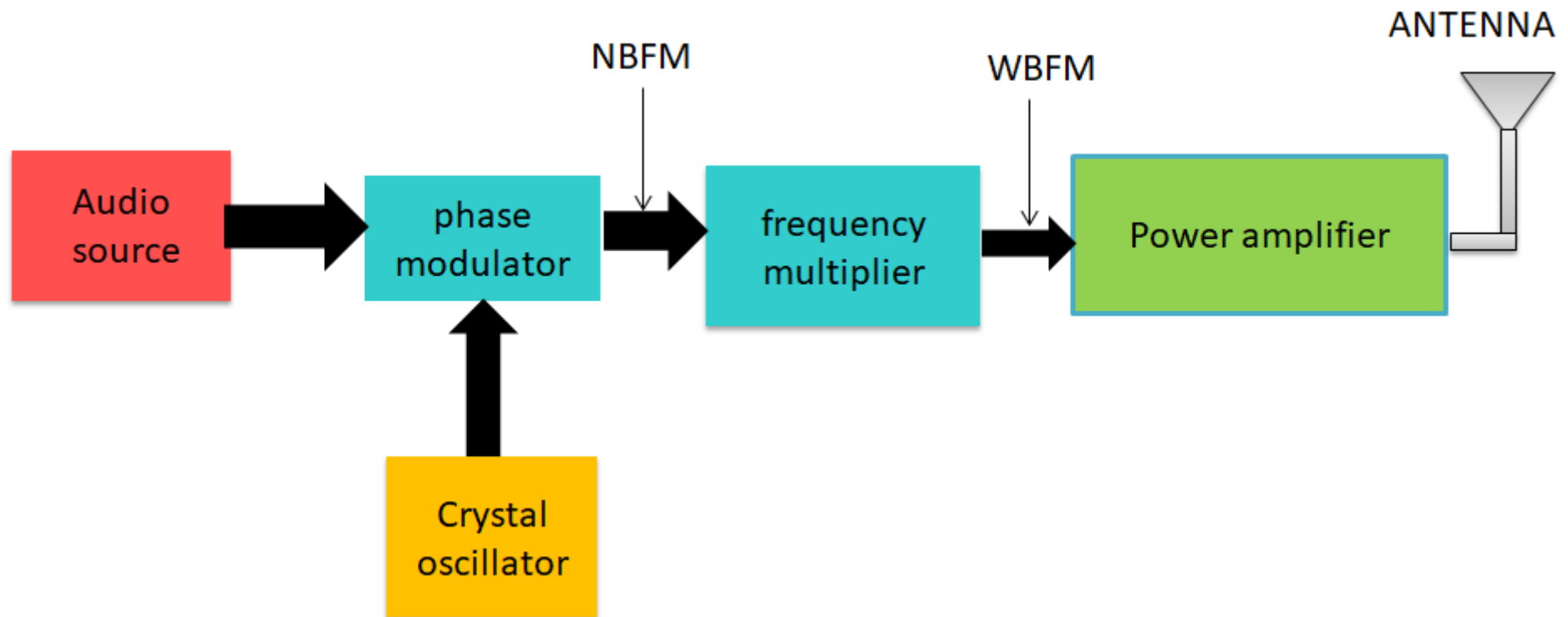

# Description


**Crystal oscillator:** Crystal oscillator generates carrier signal.

**Phase modulator:** Modulates carrier signal and input signal. The output is a narrowband FM signal.

**Frequency multiplier:** Increase frequency deviation and carrier signal frequency to the desired level.

**Power amplifier:** Increase the power level to the signal before passes through the antenna.

# FM Receiver

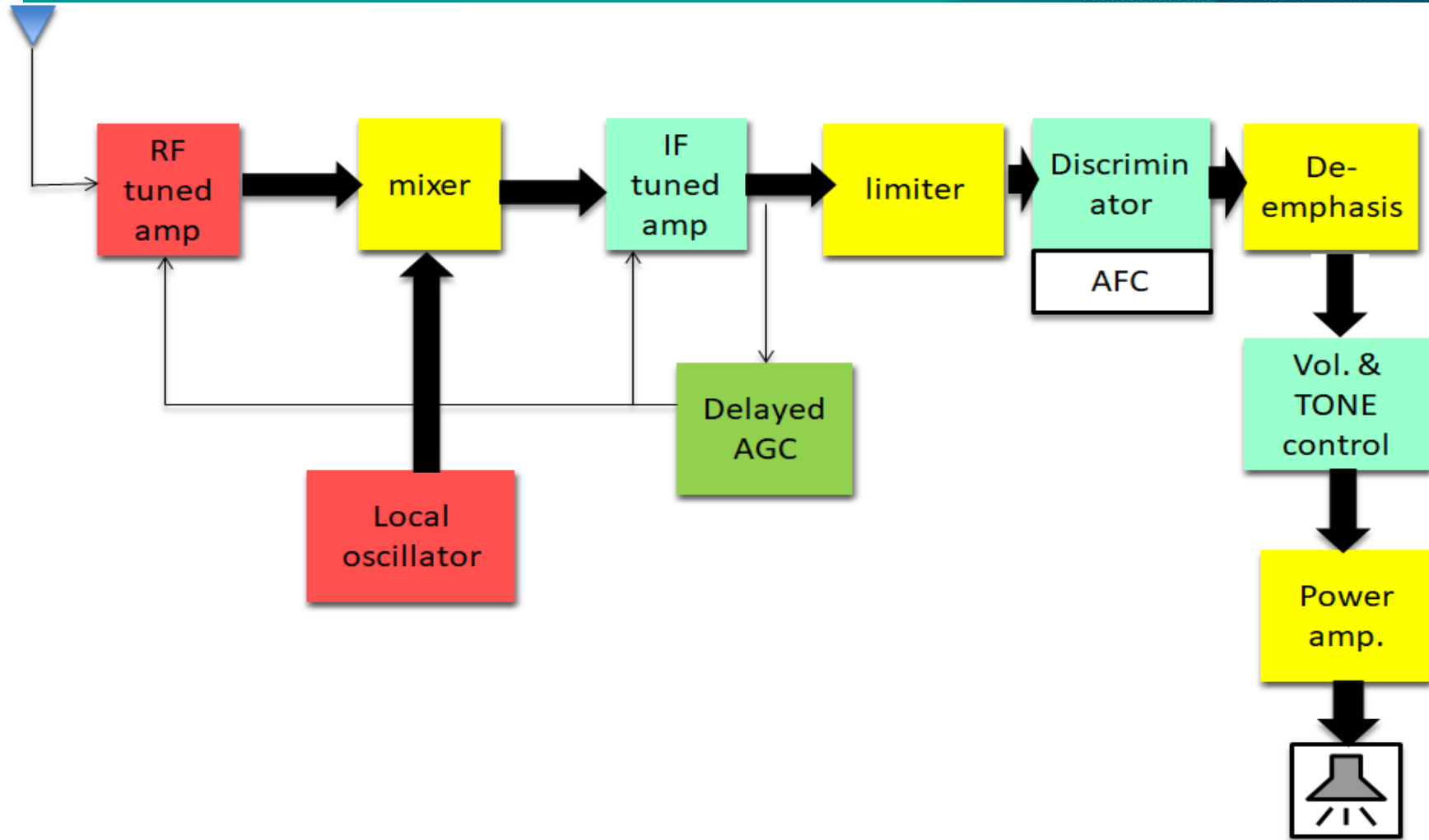

# Description (cont.)

**RF tuned amplifier:** Minimise noise level

**Mixers:** Mix the frequency modulated signal with signal generated by local oscillator. The central frequency are is change but deviation remains constant

**Intermediate frequency amplifier:** Provides most of the gain and bandwidth requirement of the receiver.

**Limiters:** Limiters allows certain frequency range to pass and block other signals

**Discriminator:** Converts FM into AM.


**De-emphasis:** The artificial boosting given to the higher modulating frequencies

**Vol & tone controller:** Controls the efficiency of audio signal.

**Power amplifier:** Gives the required power level to the signal which passes through the loudspeaker.
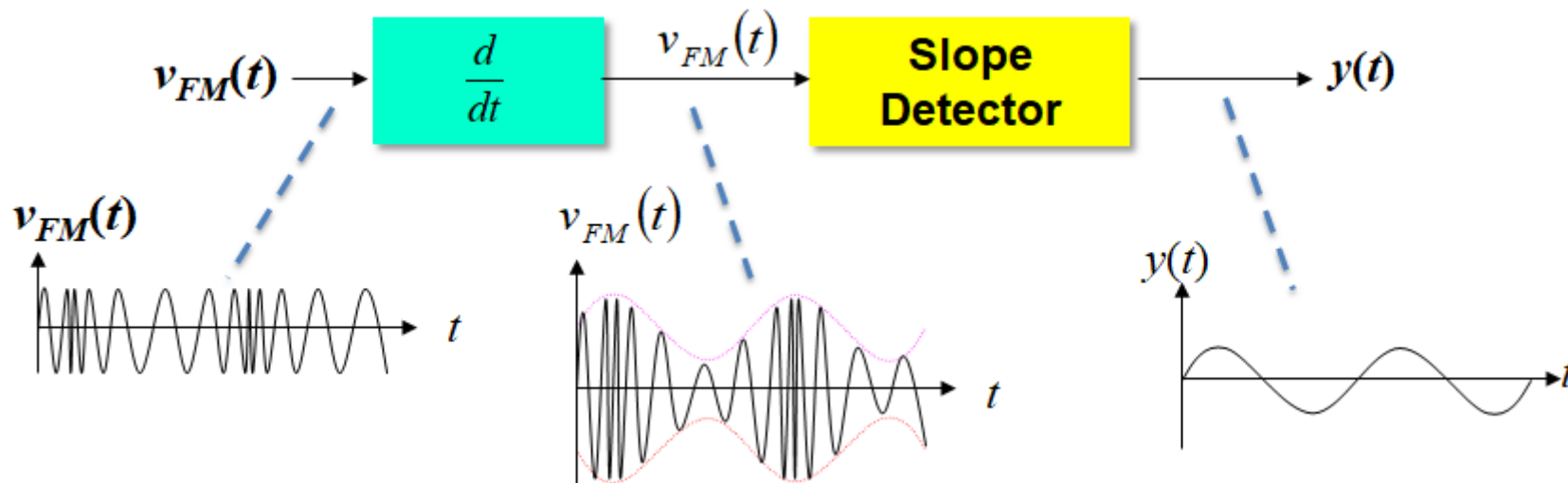
# Discriminator

*Discriminator (or slope detection)* converts FM signal to AM signal and then by using AM demodulation circuit is to get back the information signal.



# Frequency modulators

Two common types of frequency modulator

## Varactor modulator

- Uses either:
  - LC oscillator: the carrier frequency can be changed by varying either the inductance or capacitance.
  - Crystal Oscillator: the frequency is fixed by the crystal


## Reactance Modulator

- uses a transistor amplifier that acts like either a variable capacitor or an inductor.


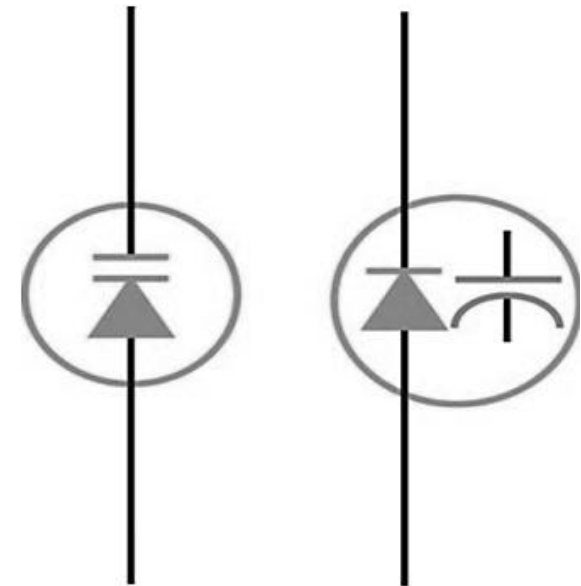
# Varactor Modulator

- All diodes exhibit variable capacitance.
- Varactors are designed to optimize this characteristic.
- Reverse-biased diode acts like a small capacitor:
  - The P- and N-type materials act as the two plates of the capacitor.
  - The depletion region acts as the dielectric material.
  - The width of the depletion layer determines the width of the dielectric and, therefore the amount of capacitance.



# Reactance Modulator

- “ **Reactance modulator** works by using transistor amplifier as variable capacitor or an inductor.
- “ When the circuit is connected across the tuned circuit of an oscillator, the oscillator frequency can be varied by applying the modulating signal to the amplifier.
- “ Reactance modulators can produce frequency deviation over a wide range.
- “ Reactance modulators are highly linear, so distortion is minimal.

# A Reactance Modulator

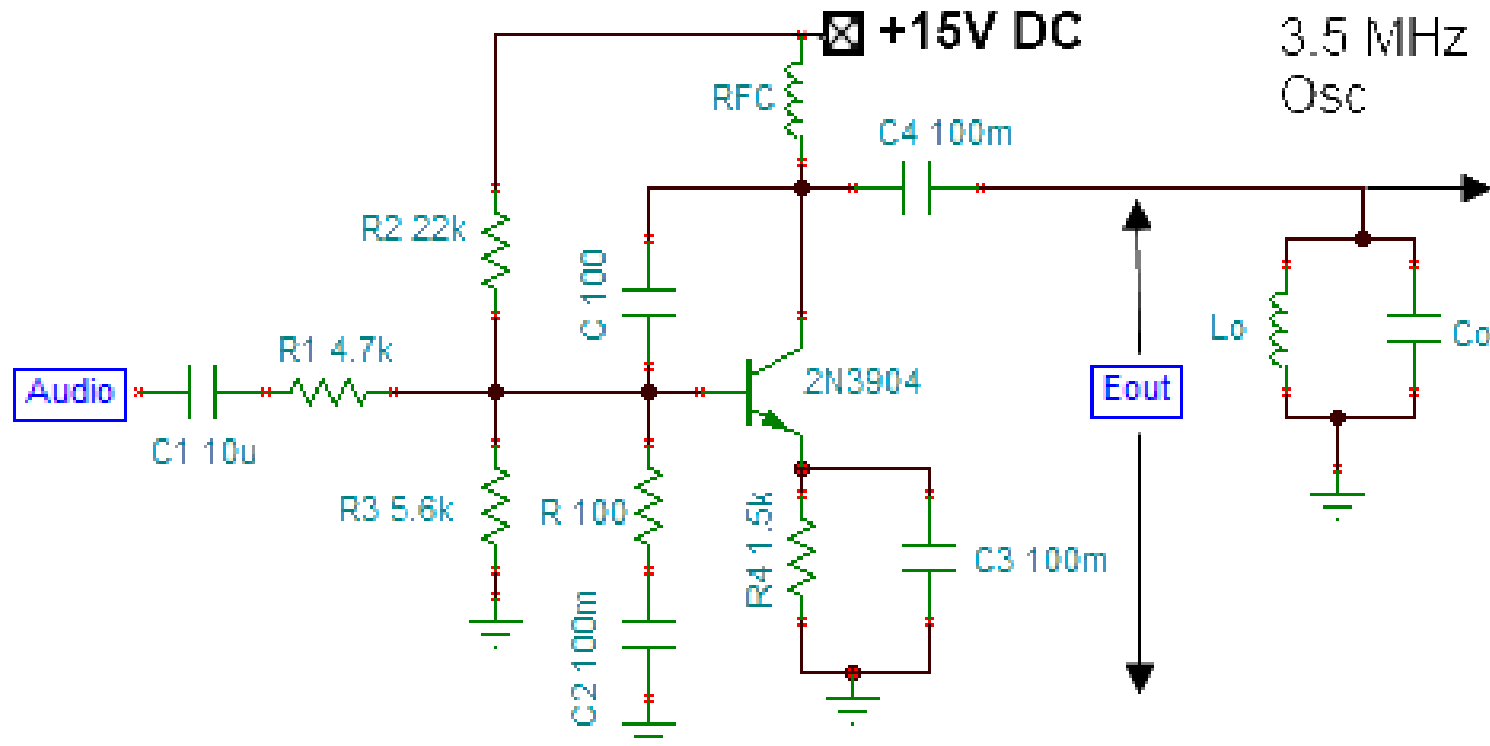


Image source: <https://et.wikipedia.org/wiki/Fail:Reaktiivmodulaator.png>




Principles of Communication System by N Hasan

Communitising Technology

# Frequency Demodulators

- Slope Detector
- Pulse-Averaging Discriminators
- Quadrature Detector
- Phase-Locked Loop Detector


# Slope Detector

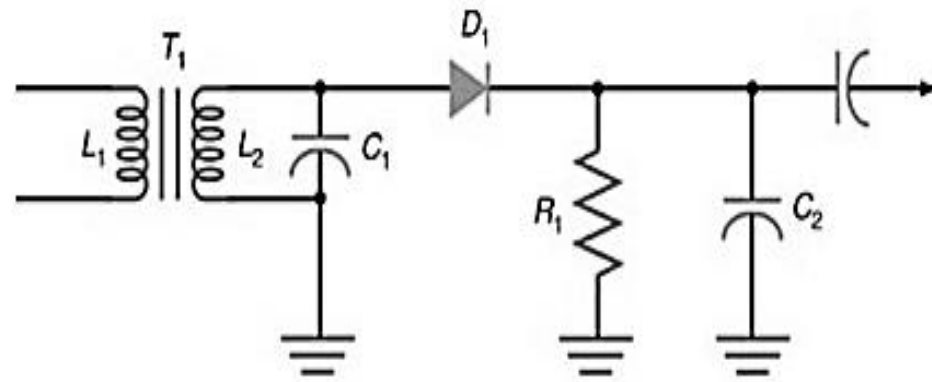

- “ **Slope detector** uses tuned circuit and a diode detector to convert frequency variations into voltage variations.
- “ The main difficulty with slope detectors is tuning them.

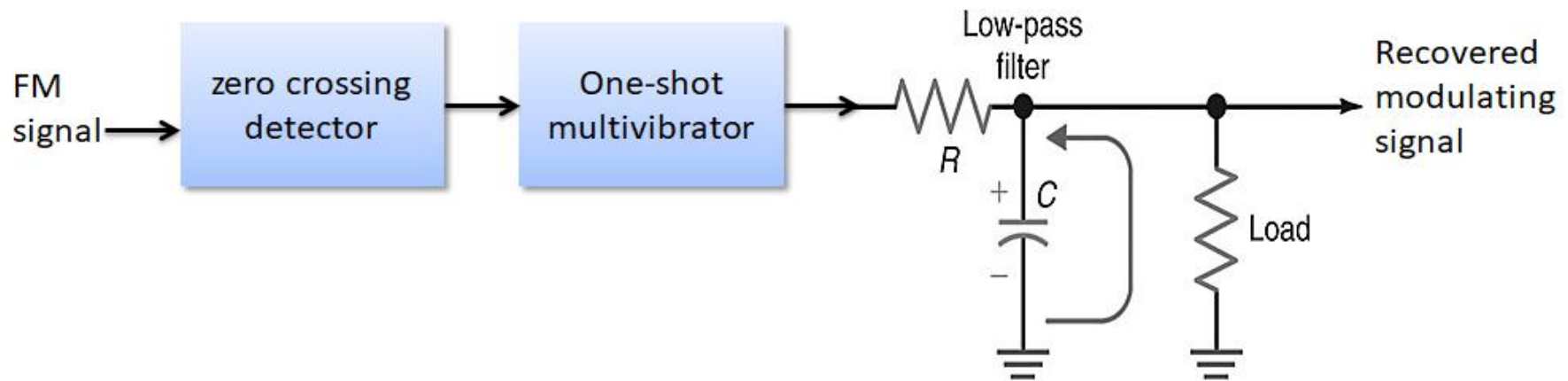
# Pulse-Averaging Discriminators

- “ Consists of a zero crossing detector, a one shot multi vibrator and a low-pass filter.
- “ A very high-quality frequency demodulator.
- “ This discriminator is used in many electronic products.



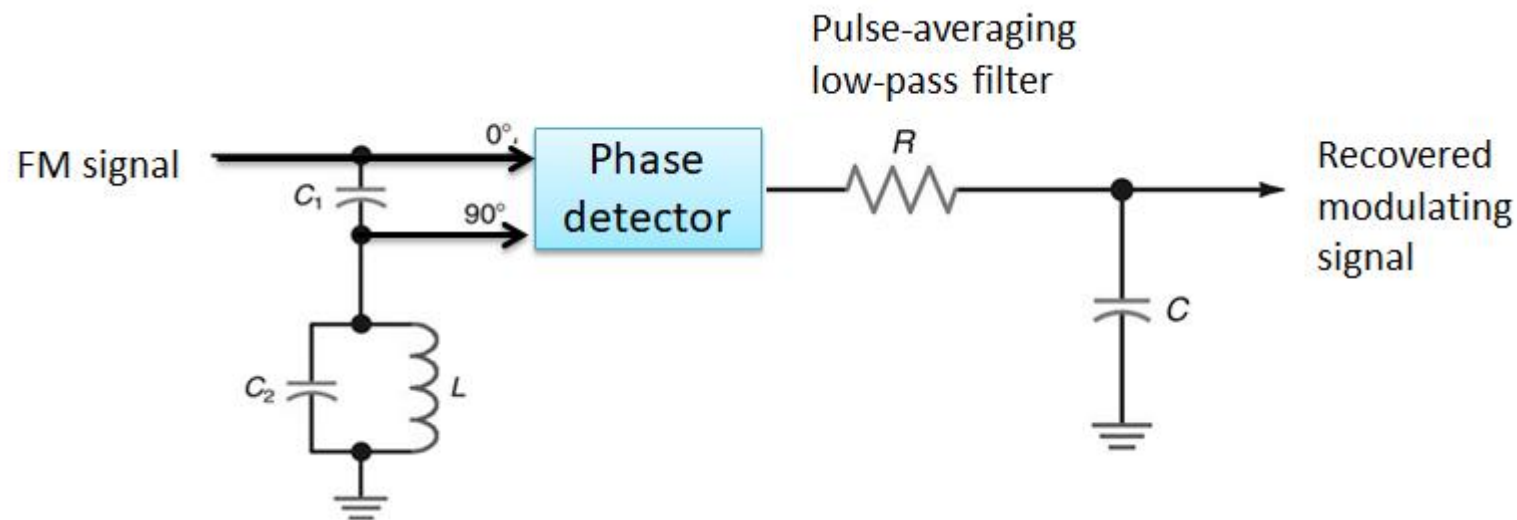
# Quadrature Detector

- “ Most widely used FM demodulator.
- “ Uses a phase-shift circuit to produce a phase shift of 90 degrees at the unmodulated carrier frequency.


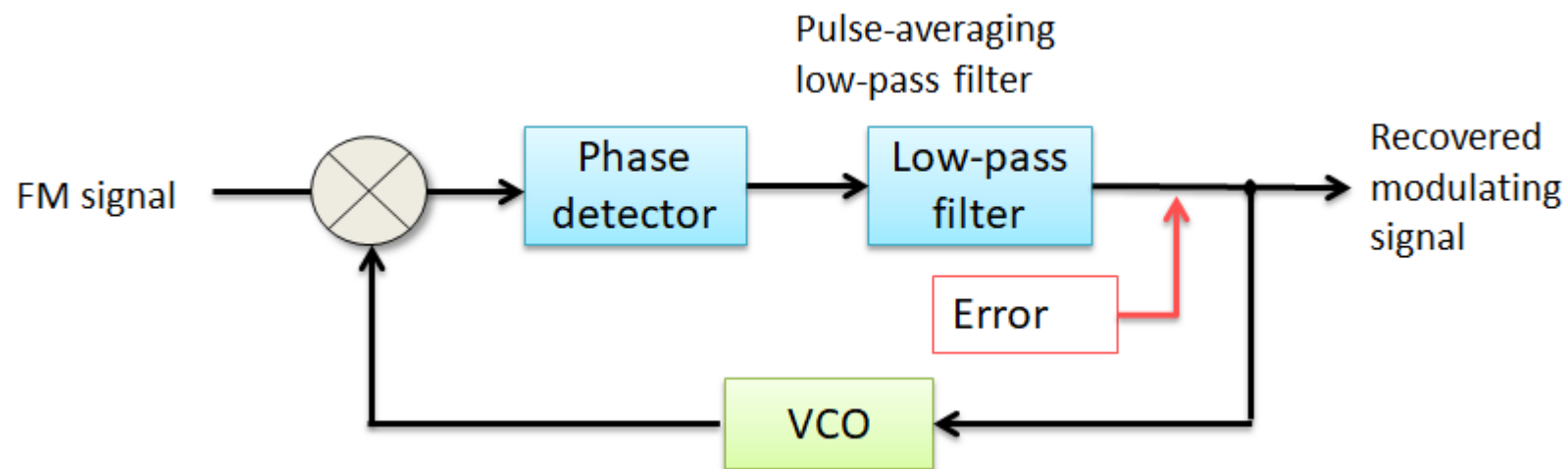
# Phase-Locked Loops

- “ Phase-locked loop (PLL) is a frequency-sensitive feedback control circuit used in frequency demodulation
- “ PLLs have three basic elements: Phase detector, Low-pass filter, Voltage-controlled oscillator (VCO)






# Noise in FM

- “ Noise is interference that affect information signal.
- “ In FM, modulated signals have a constant amplitude.
- “ At receiver, limiter circuits clipped any amplitude variations that may exist on the received signal.
- “ Information content of the FM signal is not affected since it is contained by the frequency variations, not amplitude of the received signal.
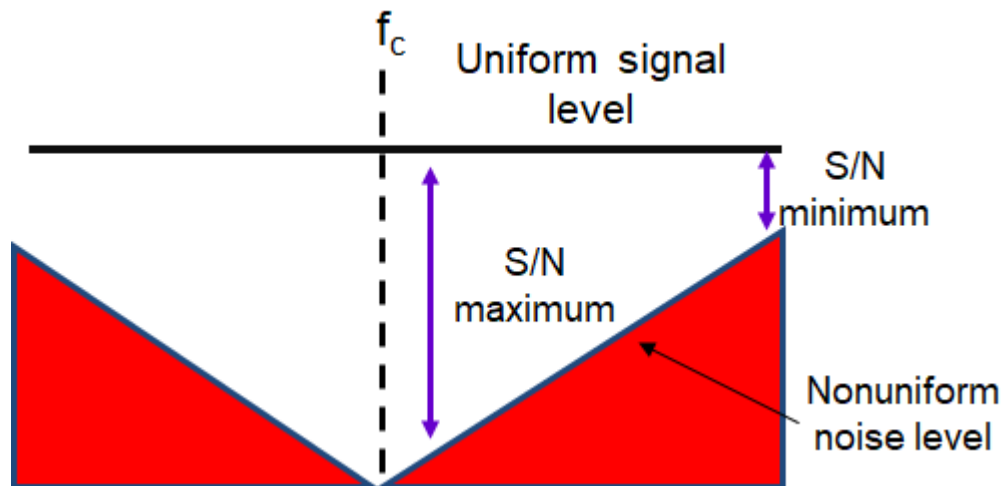
# Noise and Angle Modulation

- Noise distribution in FM is **non-uniform**.
- Higher frequencies suffers more noise than the lower frequencies.
- Higher frequencies also have lower amplitudes compared to lower frequencies.
- Consequently, the Signal to noise ratio is also **non-uniform**.
- The SNR for higher-modulating frequencies are lower than the SNR for the lower frequencies.




Without  
preemphasis


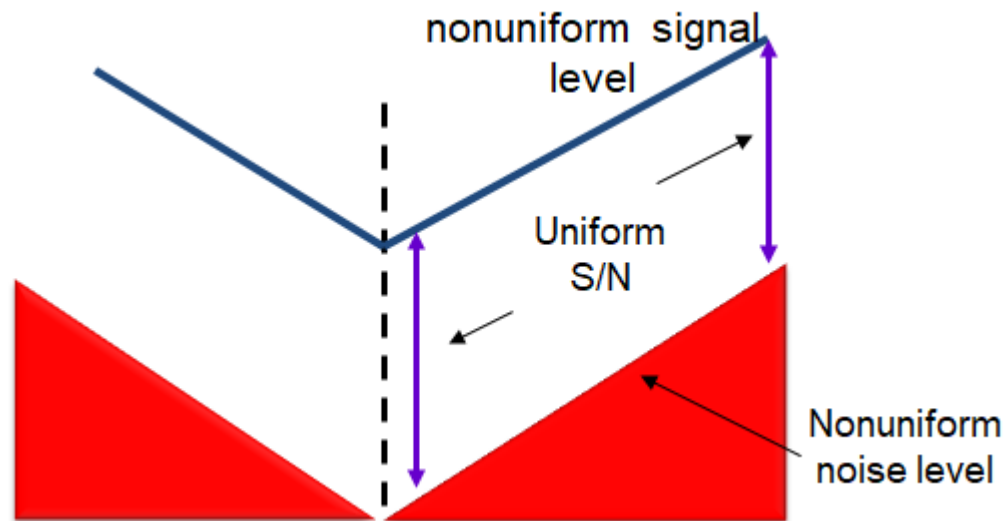
# Pre-emphasis & De-emphasis

- Solution: the high-frequency modulating signals are **emphasized** or boosted in amplitude of the transmitter prior to performing modulation and then **deemphasized** or attenuated during demodulation at receiver.



With  
preemphasis

# Pre-emphasis & De-emphasis

## PRE-EMPHASIS



- The amplitudes of higher frequencies components of input signal are increased before it modulate the carrier
- Therefore will be less affected to noise.
- Preemphasis Network → High-Pass Filter (Differentiator)

## DE-EMPHASIS

- Deemphasis – returns the frequency response to its normal flat level.
- Deemphasis Network → Low-Pass Filter (Integrator)

# Pre-emphasis & De-emphasis circuits

**Pre-emphasis**

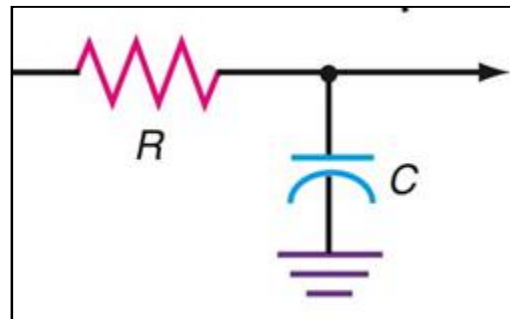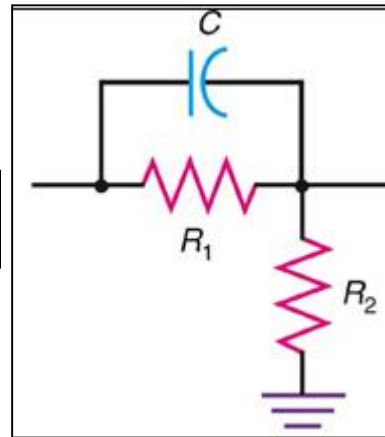

**De-emphasis**

# FM Application

---

Radio broadcasting

---

Two way mobile radio

---

Microwave communication

---

TV sound transmission

---

Cellular radio communication

---

Satellite communication



Collaborative authors:

Nurulfadzilah Binti Hasan  
Noor Zirwatul Ahlam Binti Naharuddin  
Norhadzfizah Binti Mohd Radi  
Mohd Hisyam Bin Mohd Ariff

Faculty of Electrical & Electronics Engineering,  
UMP

