

# **BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING**

## **Introduction**

Ismail Mohd Khairuddin , Zulkifil Md Yusof  
Faculty of Manufacturing Engineering  
Universiti Malaysia Pahang

# Introduction

## BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING




### Faculty of Manufacturing

Universiti Malaysia Pahang  
Kampus Pekan, Pahang Darul Makmur  
Tel: +609-424 5800  
Fax: +609-4245888

### Contents:

- Ohm' Law
- Electrical Circuits
- Systems of Units
- Charge and Current
- Voltage
- Switch
- Power and Energy
- Circuit Elements
- Nodes, Branches and Loops
- Basic Connection


# Outcomes

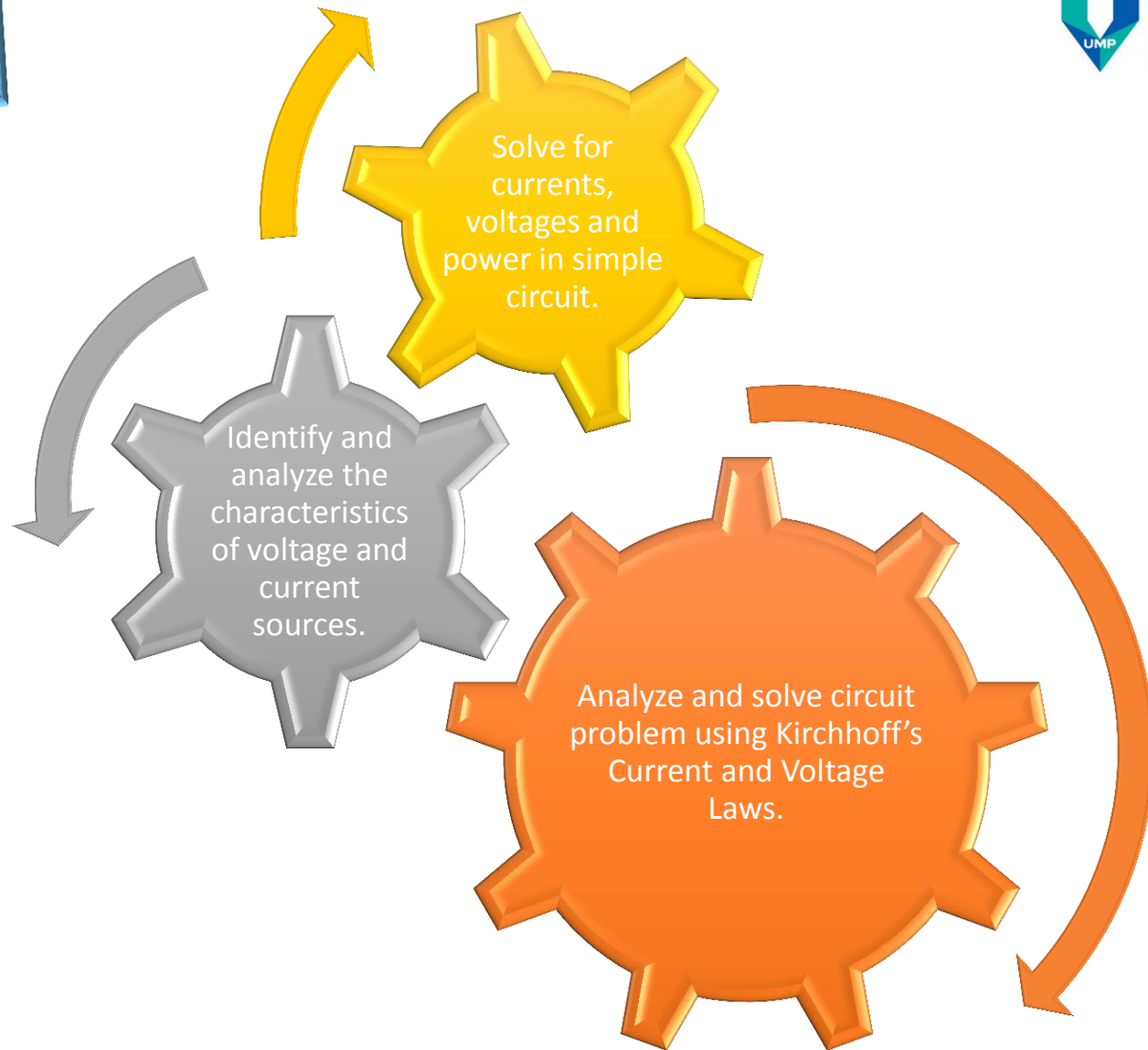

# Ohm's Law

- Most material have a characteristic behavior of **resisting** the flow of electric charge.
- The physical property to resist current known as **resistance** and is represented by the symbol  $R$ .
- The resistance of any material with a uniform cross-sectional area  $A$  depends on  $A$  and its length  $l$

$$R = \rho \frac{l}{A}$$


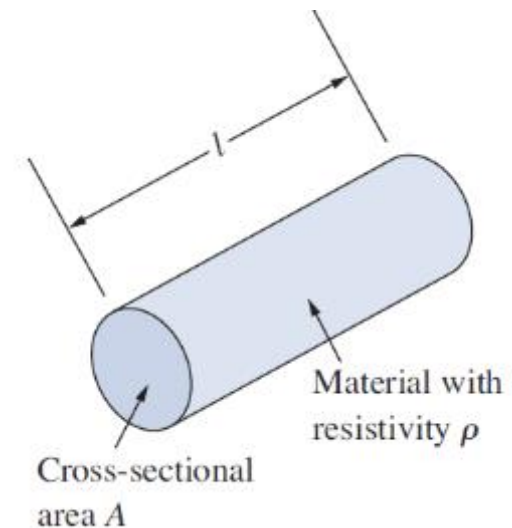


- ❑ An interconnection of electrical elements.
- ❑ Consists of various type of elements connected in closed path by conductors.
- ❑ The circuits elements consists of: resistance, inductance, capacitance and voltage sources.
- ❑ Charge flow easily through conductors
- ❑ Conductors correspond to connecting wire in physical circuits.






# Electrical Circuits

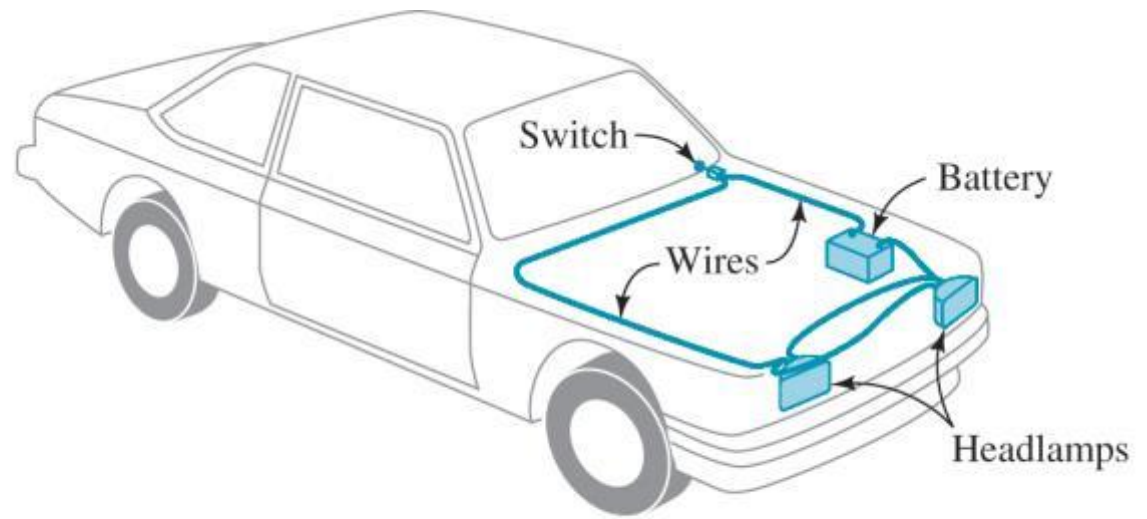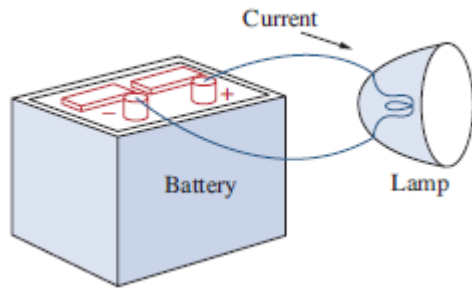

(a) Physical configuration

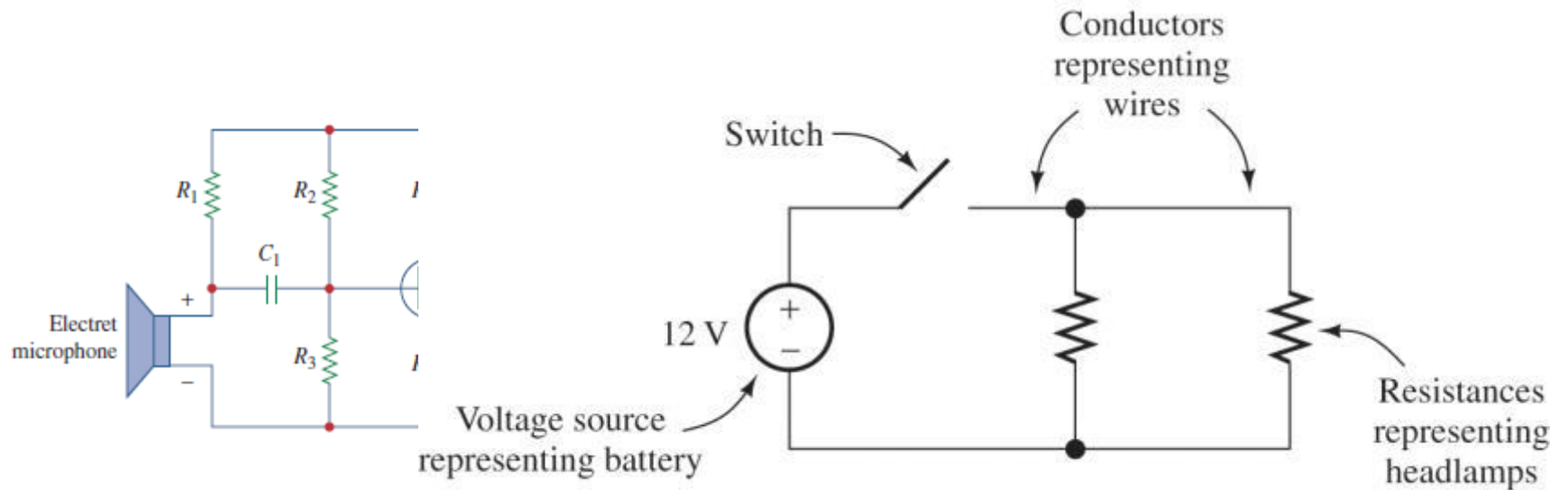

(b) Circuit diagram



## SI Fundamental Units

Quantity	Unit	Symbol
Length	Meter	m
Mass	Kilogram	kg
Time	Second	s
<b>Electric current</b>	<b>Ampere</b>	<b>A</b>
Temperature	Kelvin	K
Luminous intensity	Candela	cd
Amount of substance	Mole	mol



# Systems of Units

Quantity	Unit	Symbol
Current	Ampere	A
Charge	Coulomb	C
Voltage	Volt	V
Resistance	Ohm	$\Omega$
Power	Watt	W





- **Charge** is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.
- The charge  $e$  on an electron is **negative** and equal in magnitude to  $1.602 \times 10^{-19}$  C.
- The *law of conservation of charge* states that charge can neither be **created** nor **destroyed, only transferred**. Thus the algebraic sum of the electric charges in a system does not change.




**Electric Current** is the time rate of change of charge, measured in amperes (A).

1 ampere = 1 coulomb/second

Generally, there are 2 types of current

**direct current (dc)** – a current that remains constant with time. Symbol,  $I$

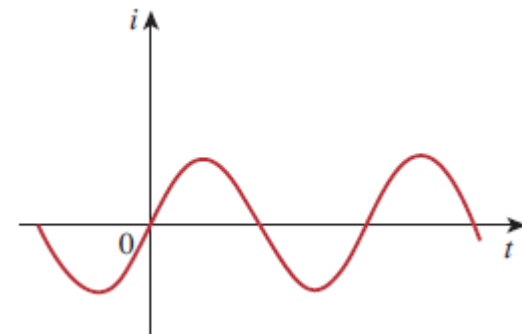
**alternating current (ac)** – a current that varies sinusoidal with time. Symbol,  $i$



# Charge and Current

$$i = \frac{dq}{dt}$$

$$Q = \int_{t_0}^t i dt$$

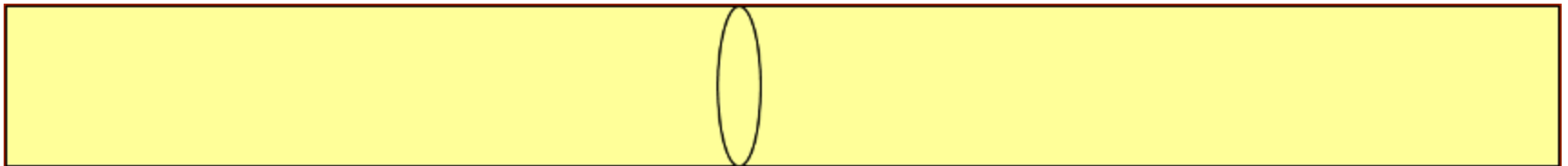

## Example #1

The total charge entering a terminal is given by

$$q(t) = 5t \sin 4\pi t$$

Calculate the current at  $t = 0.5s$

### Solution

$$i = \frac{dq}{dt}$$

$$= \frac{d}{dt}(5t \sin 4\pi t)$$

$$= (5 \sin 4\pi t + 20\pi t \cos 4\pi t)$$

$$i = 5 \sin 2\pi + 10\pi \cos 2\pi$$

$$i = 31.42 \text{ mA}$$



## Example #2

Determine the total charge entering a terminal between  $t = 1\text{ s}$  and  $t = 2\text{ s}$  if the current passing the terminal is

$$i = (3t^2 - t)\text{ A}$$

### Solution

$$\begin{aligned} Q &= \int_{t=1}^2 i \, dt = \int_1^2 (3t^2 - t) \, dt \\ &= \left( t^3 - \frac{t^2}{2} \right) \Big|_1^2 = (8 - 2) - \left( 1 - \frac{1}{2} \right) \\ &= 5.5\text{ C} \end{aligned}$$




# Voltage

- ❑ **Voltage** (or **potential difference**) – the energy required to move a unit charge through an element, measured in **volts (V)**.
- ❑ To move an electron in a conductor in a particular direction requires some work or energy transfer.
- ❑ This work is performed by an external **electromotive force (emf)** – i.e. battery
- ❑ This emf also known as **potential difference** or **voltage**.
- ❑ Voltage is a **measurement of potential** between **two points**.





# Voltage

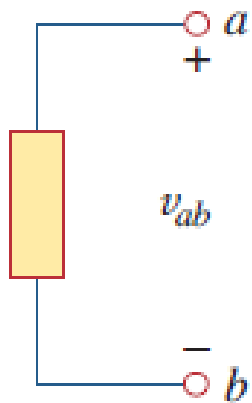

- ❑ Voltage  $v_{ab}$  the energy (or work) needed to move a unit charge from  $a$  to  $b$ .

- ❑  $1 \text{ volt} = 1 \text{ joule/coulomb} = 1 \text{ newton-meter/coulomb}$

- ❑ Plus (+) and minus (-) signs – voltage polarity or direction of charges being pushed.

- ❑ 2 type of voltages


- ❑ **dc voltage, (V)** – a constant voltage with time. i.e. battery.

- ❑ **ac voltage, (v)** – a voltage that varies **sinusoidally** with time. i.e. electric generator

$$v_{ab} = \frac{dw}{dq}$$



# Voltage

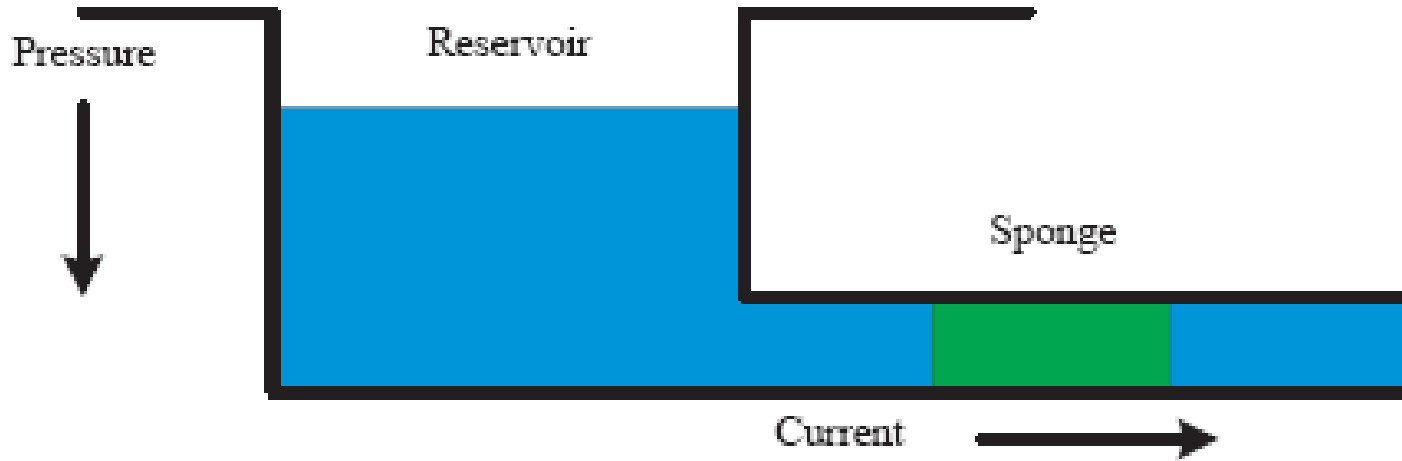

Pressure = Voltage

Water current = Electric current

Sponge porosity = Resistance



# Switches

- ❑ Control the current in circuits.
- ❑ When ideal switch is **open**, the **current through** it is **zero** the voltage across is determine by the remainder of the circuit.
- ❑ When ideal switch is **closed**, the **voltage across** it is **zero**, and the current through it determined by the remainder of the circuit.



- Time rate of **supplying** or **absorbing energy**, measured in **watts (W)** or **joules per second (J/s)**.

$$p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = vi \qquad p = vi$$

- Positive power – power is **absorb** by the element

$$p = +vi$$


- Negative power – power is **supplied** by the element

$$p = -vi$$

- How to identify positive and negative power? Based on the **direction of current flow and voltage polarity**.







# Power and Energy

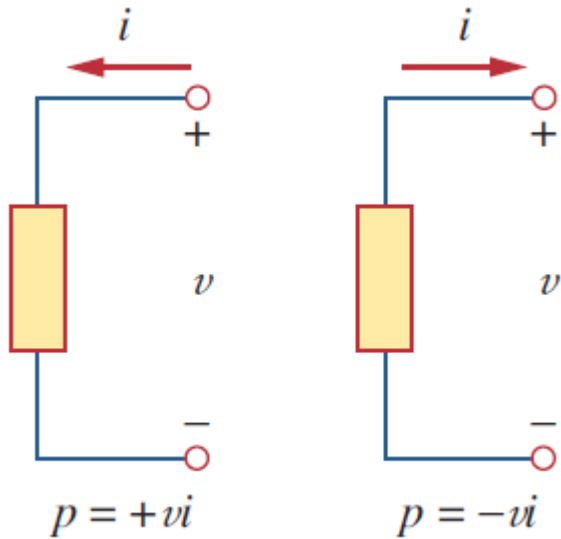

Note: focus on the direction of current entering an element. If enter at:

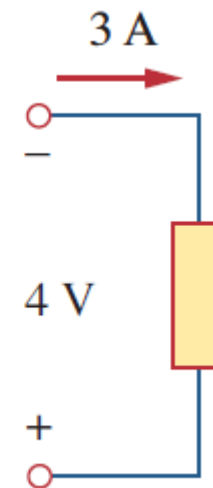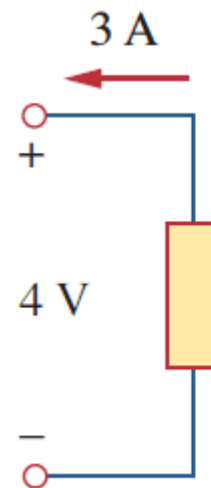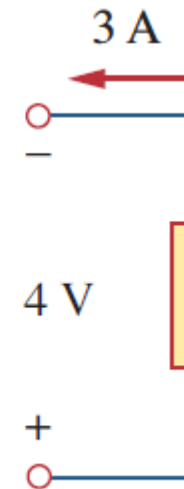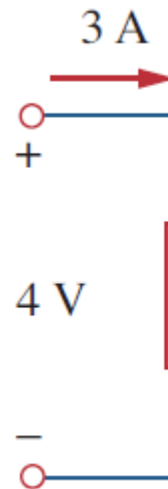- +ve terminal – power absorbed
- -ve terminal – power supplied



❏ **Law of conservation of energy** – the algebraic sum of power in a circuit, at any instant of time, must be zero.

$$\sum p = 0$$

❏ The total power supplied to the circuit must equal to the total power absorbed.

❏ **Energy** is the capacity to do work, measured in joules (J).


$$w = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$$




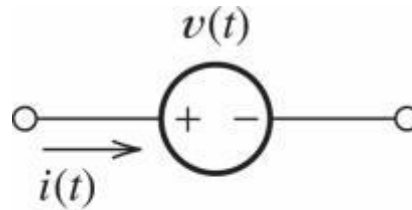
## Example #3

Find an expression for the power for the voltage source



$$v(t) = 12 \text{ V}$$

$$i(t) = 2e^{-t} \text{ A}$$

Copyright © 2011, Pearson Education, Inc.

Compute the energy for the interval from  $t_1 = 0$  to  $t_2 = \infty$

### Solution

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= 12 \times 2e^{-t} \\ &= 24e^{-t} \text{ W} \end{aligned}$$

$$\begin{aligned} w &= \int_0^{\infty} p(t) dt \\ &= \int_0^{\infty} 24e^{-t} dt \\ &= \left[ -24e^{-t} \right]_0^{\infty} = 24 \text{ J} \end{aligned}$$

- **Element** – basic building block of a circuit or electrical components of an electrical circuit.
  
- **Electric circuit** – an interconnection of electrical elements.
  
- **Circuit analysis** – process of determining voltages across (or the currents through) the elements of the circuit.
  
- 2 types of electrical circuits:
  - **Active elements**
  - **Passive elements**



- ❑ Active elements:- **capable of generating electrical energy** i.e. voltage source & current source.
  
- ❑ Passive elements :- **not capable of generating electrical energy** i.e. resistor, capacitor and inductors.
  
- ❑ Voltage and current source deliver power to the electrical circuit.
  
- ❑ 2 kinds of source
  - ❑ **Independent source**
  - ❑ **Dependent source**




## Ideal Independent Source

■ An active elements that provides a specified voltage or current that is completely independent of other circuit elements.

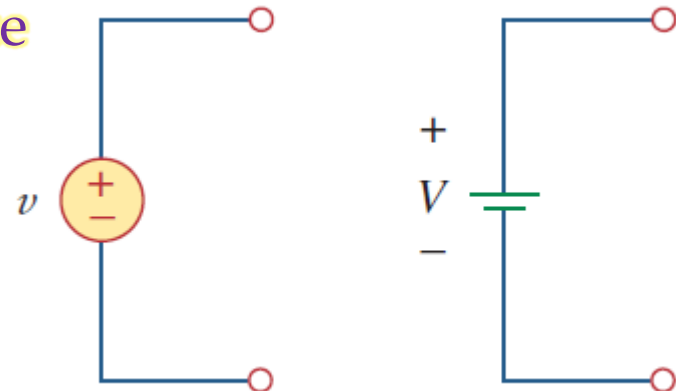
### i. Ideal Independent Voltage Source

■ Ideal independent voltage source delivers to the circuit **whatever current is necessary to maintain its terminal voltage.**


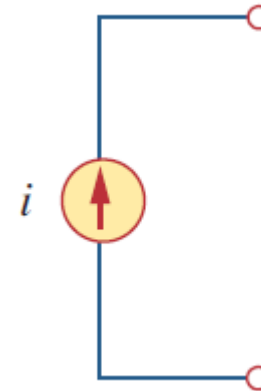
## ii. Ideal Independent Current Source

- Ideal independent current source delivers to the circuit **whatever voltage is necessary to maintain the designated current.**




## Ideal Dependent @ Controlled Source


- An active elements in which the source quantity is controlled by another voltage or current
- 4 types of dependent source
  - Voltage-Controlled Voltage Source (VCVS)
  - Current-Controlled Voltage Source (CCVS)
  - Voltage-Controlled Current Source (VCCS)
  - Current-Controlled Current Source (CCCS)




# Circuit Elements

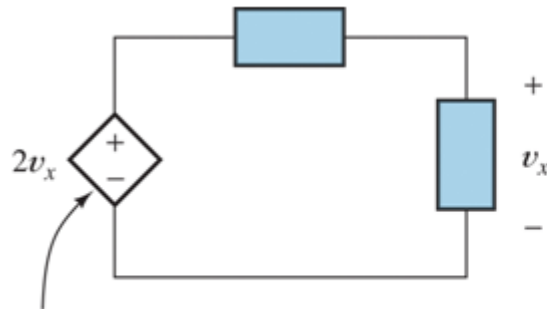


Voltage-controlled  
voltage source

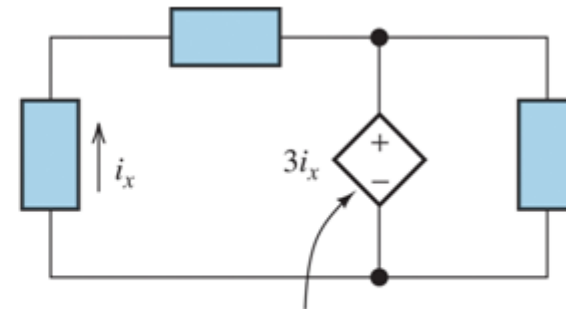

Current-controlled  
voltage source

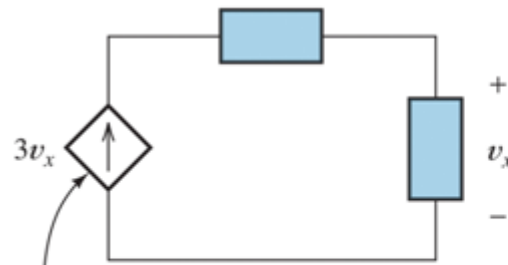

Voltage-controlled  
current source

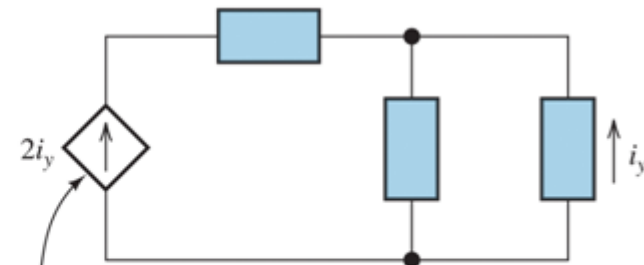


Current-controlled  
current source





## Example #4

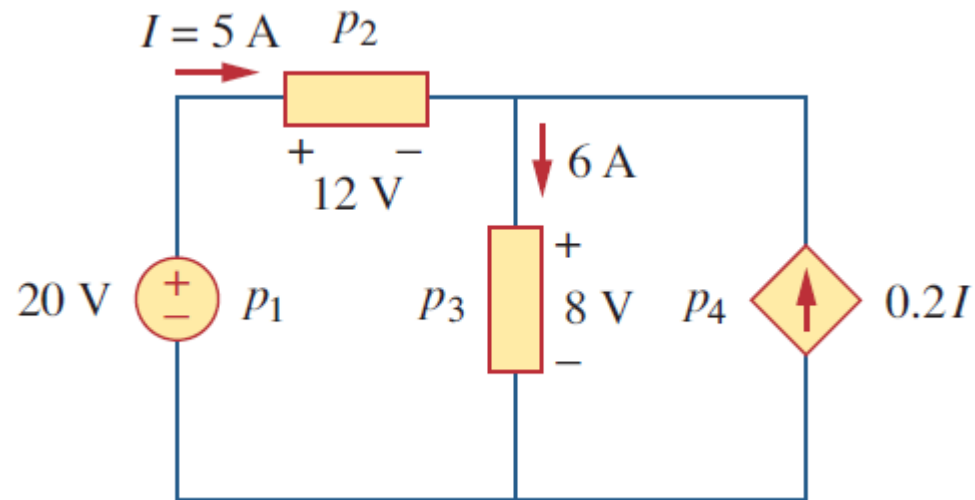

Calculate the power supplied or absorbed by each element in figure above

## Example #4

### Solution

$$p_1 = (20)(5) = 100 \text{ W}$$

Since the **current leaves** the positive terminal thus,  $p_1 = -100 \text{ W}$

$$p_2 = (12)(5) = 60 \text{ W} \text{ The } \mathbf{current \ enters} \text{ the positive terminal}$$

$$p_3 = (8)(6) = 48 \text{ W} \text{ The } \mathbf{current \ enters} \text{ the positive terminal}$$

Since the **current leaves** the positive terminal thus,  $p_4 = -8 \text{ W}$

$$p_4 = (8)(0.2I) = (8)(1) = 8 \text{ W}$$


Algebraic sum of power in  
the circuit

$$p_1 + p_2 + p_3 + p_4$$

$$-100 + 60 + 48 - 8 = 0 \text{ W}$$



## Example #5

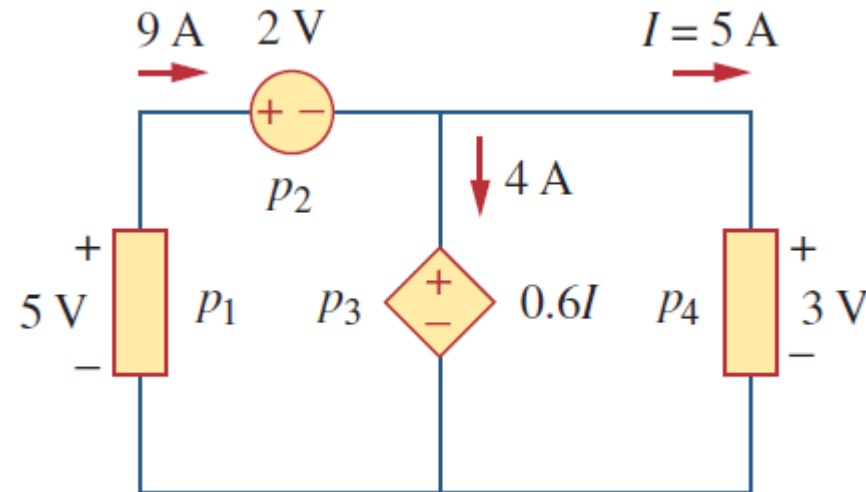

Calculate the power supplied or absorbed by each element in figure above

## Example #5

### Solution

$$p_1 = (5)(9) = 45 \text{ W}$$

Since the **current leaves** the positive terminal thus,  $p_1 = -45 \text{ W}$

$$p_2 = (9)(2) = 18 \text{ W} \quad \text{The **current enters** the positive terminal}$$

$$p_3 = (4)(0.6I) = (4)(3) = 12 \text{ W}$$

The **current enters** the positive terminal

$$p_4 = (3)(5) = 15 \text{ W} \quad \text{The **current enters** the positive terminal}$$

Algebraic sum of power in the  
circuit

$$\begin{aligned} p_1 + p_2 + p_3 + p_4 \\ -45 + 18 + 12 + 15 = 0 \text{ W} \end{aligned}$$

## Branch


Represents a single 2-terminal elements such as voltage source or a resistor.

## Node

A point of connection between 2 or more branches.  
If a short circuit (a connecting wire) connects between 2 nodes, this 2 nodes constitute a single node.
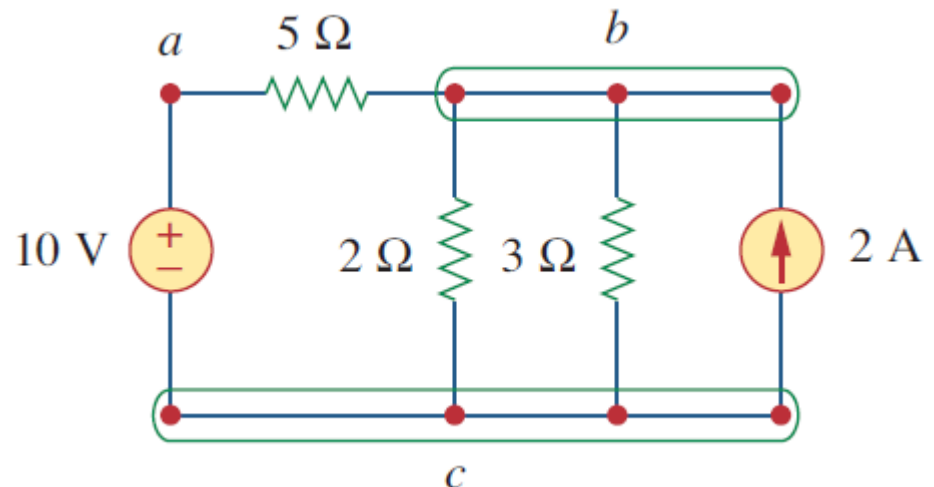
## Loop

A closed path formed by starting at a node, passing through a set of nodes and returning to the starting node without passing through any node more than once.



# Basic Connection


2 types of connections:

Series

Parallel



When **Series** connection – **2 elements** are joint at a **node** and no other element is connected to that node.

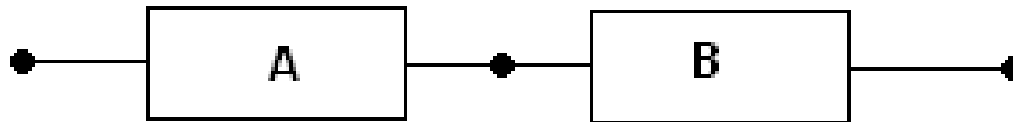Elements in series carry the **same current**.





# Basic Connection

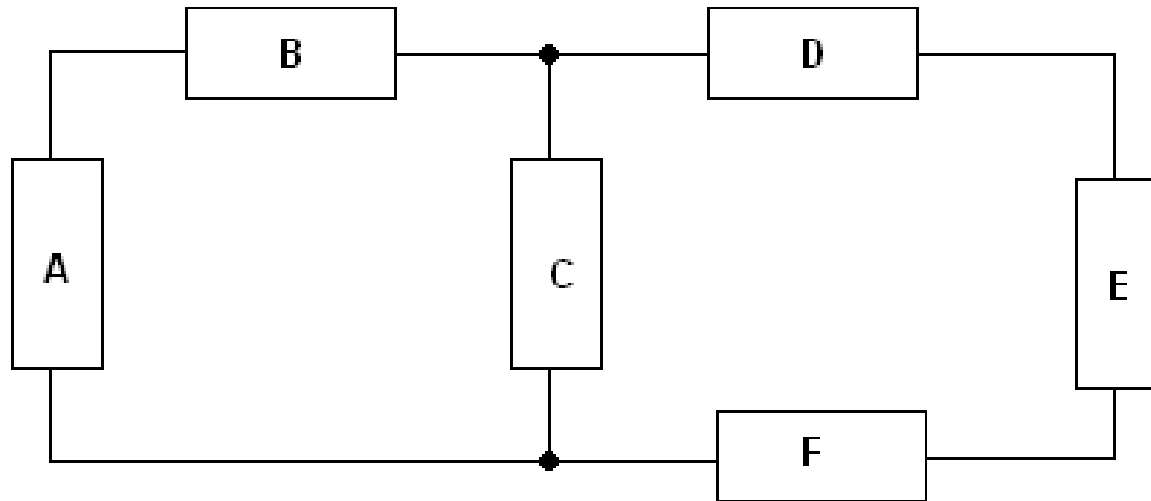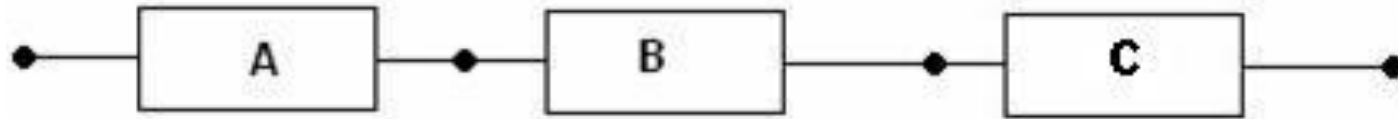

The series connection are:

■ A & B

■ D, E & F

6 branches.



5 nodes.

2 loops.




▣ **Parallel** connection – elements that are connected to the **same pair of terminals**.

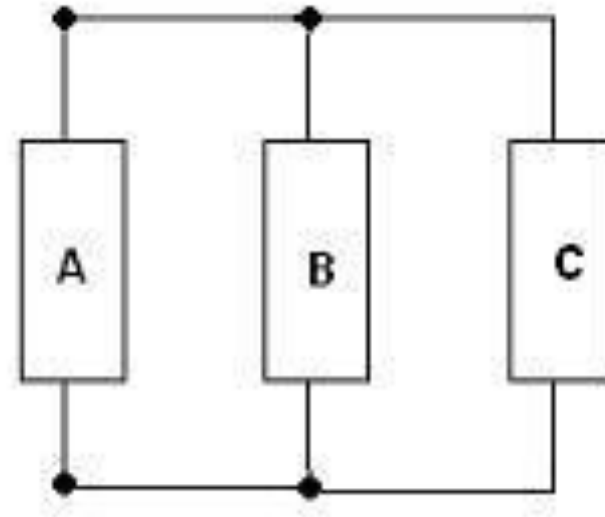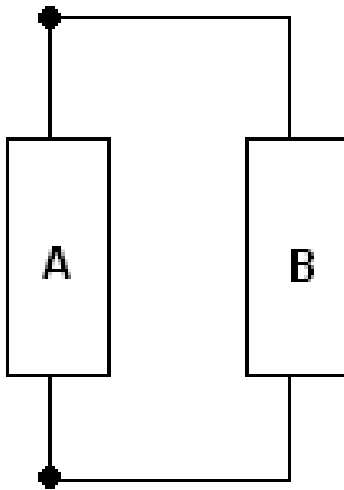▣ Elements in parallel have the **same voltage** across them.



# Basic Connection

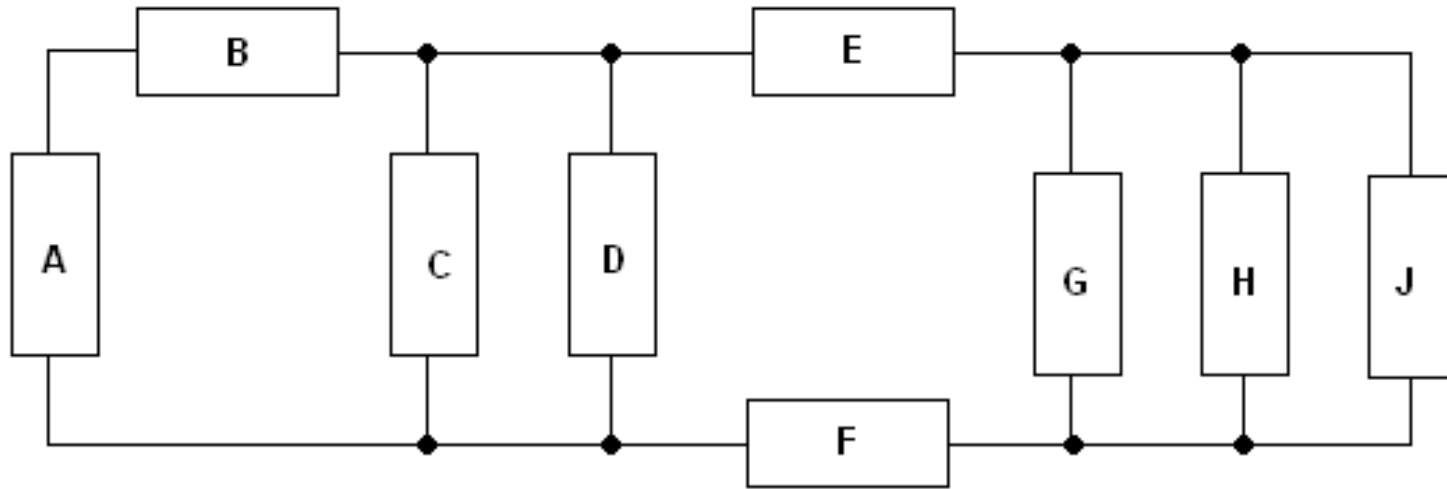

Parallel connections:

▣ C & D

▣ G, H & J

Series connection – A & B


9 branches.

5 nodes.

5 loops.



## Example #6

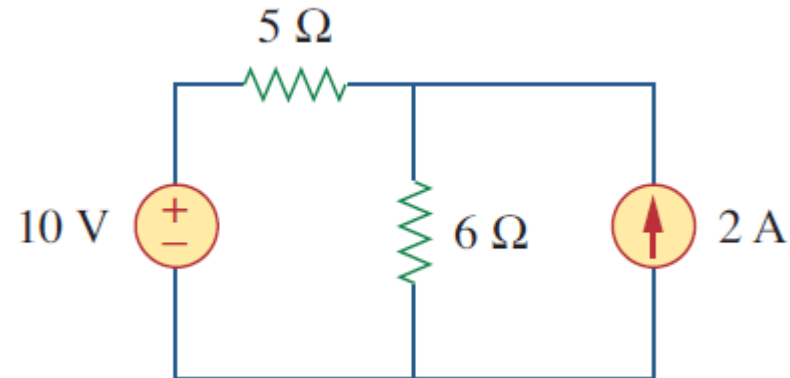

Determine the number of branches and nodes.  
Identify which elements are in series and parallel.



## Example #6


### Solution

Since there are 4 elements, the circuit has 4 branches:  
10 V, 5  $\Omega$ , 6  $\Omega$  and 2 A.


Has 3 nodes.

Series connection: 5  $\Omega$  resistor with 10 V voltage source.

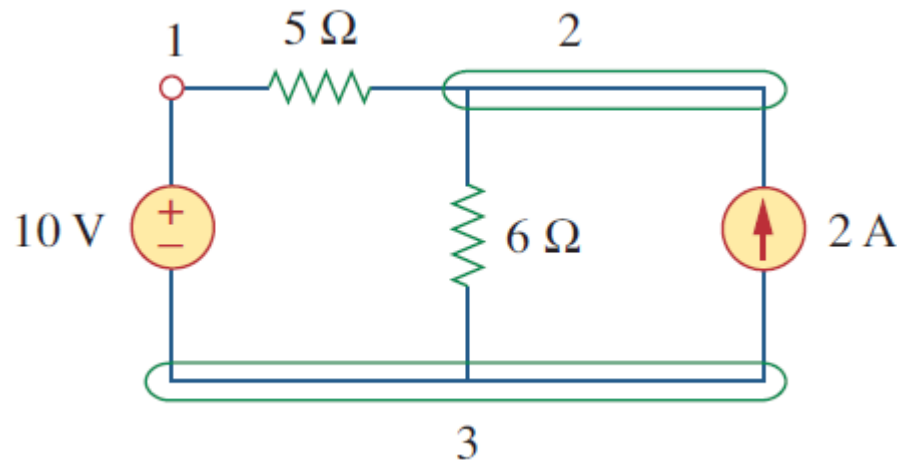Parallel connection: 6  $\Omega$  resistor with 2 A current source.



## Example #7

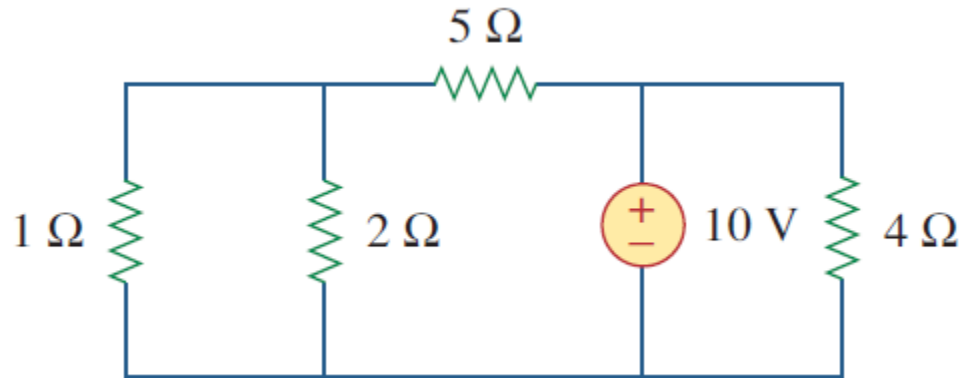

Determine the number of branches and nodes.  
Identify which elements are in series and parallel.



## Example #7

### Solution

Since there are 5 elements, the circuit has 5 branches:  
 $10\text{ V}$ ,  $5\ \Omega$ ,  $4\ \Omega$ ,  $2\ \Omega$  and  $1\ \Omega$ .

Has 3 nodes.

Parallel connection:  $1\ \Omega$  resistor with  $2\ \Omega$  resistor.  
 $4\ \Omega$  resistor with  $10\text{ V}$  source.

