

# **BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING**

## **Direct Current Circuits : Methods of Analysis**

Ismail Mohd Khairuddin , Zulkifil Md Yusof  
Faculty of Manufacturing Engineering  
Universiti Malaysia Pahang

# Direct Current Circuit (DC)- Methods of Analysis

**BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING**




## Faculty of Manufacturing

Universiti Malaysia Pahang  
Kampus Pekan, Pahang Darul Makmur  
Tel: +609-424 5800  
Fax: +609-4245888


### Contents:

- Outcomes
- Nodal Analysis
- Mesh Analysis

# Outcomes

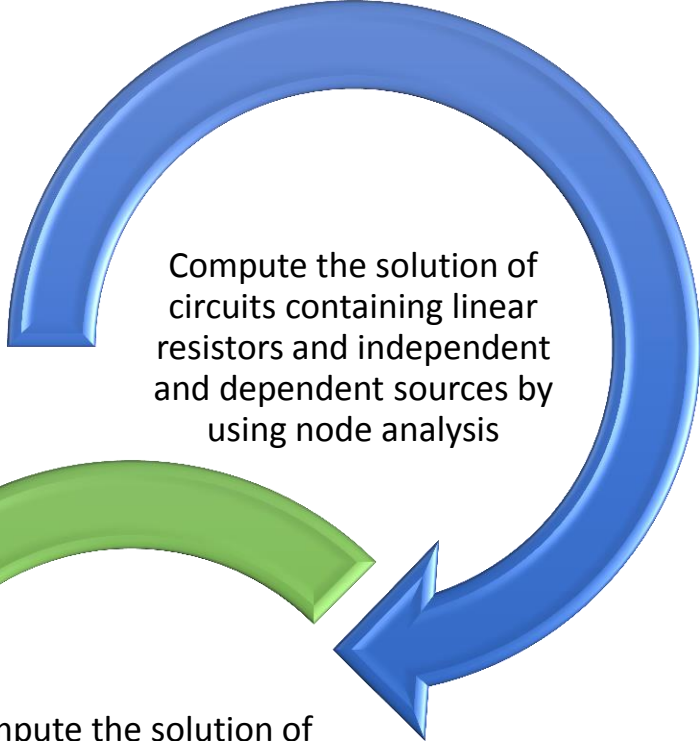

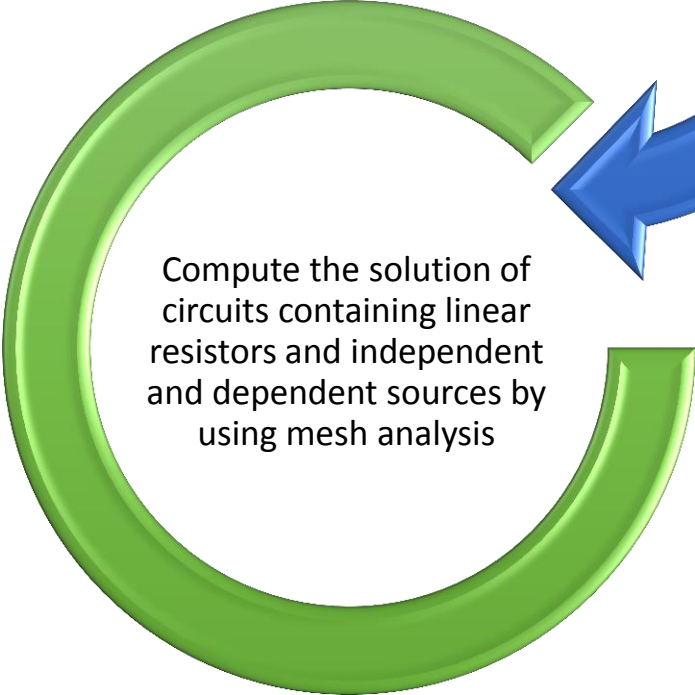Compute the solution of circuits containing linear resistors and independent and dependent sources by using node analysis



Compute the solution of circuits containing linear resistors and independent and dependent sources by using mesh analysis

# Nodal Analysis

There is another method to solve for currents and voltages.

Easier

More methodical

Still based on **Ohm's Law**, **KVL** and **KCL**

The methods are the **nodal** and **mesh** analysis.

**Nodal** analysis is based on the **KCL**.

**Mesh** analysis is based on the **KVL**.




## WITHOUT VOLTAGE SOURCE

- ❑ Analyze the circuit using node voltages as the circuit variables.
- ❑ The node voltages is chosen instead of the elements voltages.
- ❑ To simplify matters, it is first assumed that the circuits **do not** contain voltage sources.




## Steps to determine node voltages:

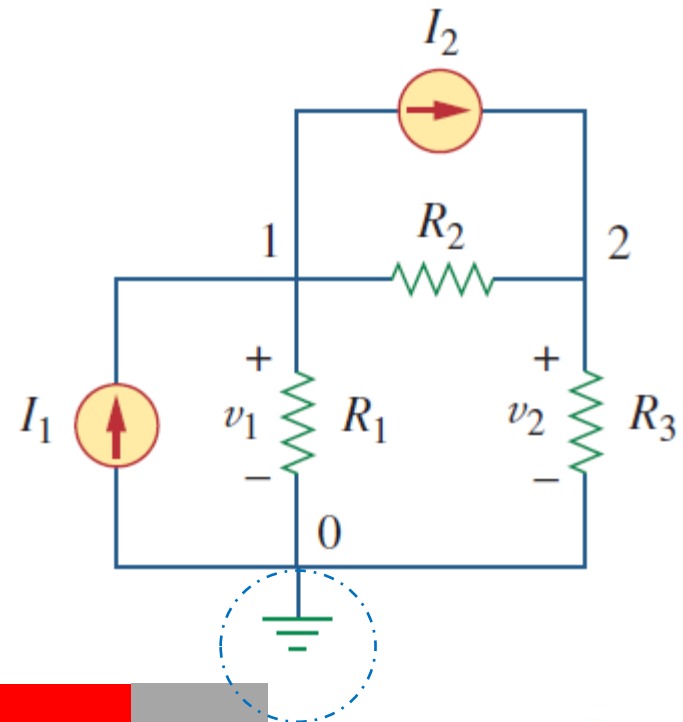- i. Select a node as a **reference node** – This reference node also called the **ground**, have **zero potential**.




# Nodal Analysis

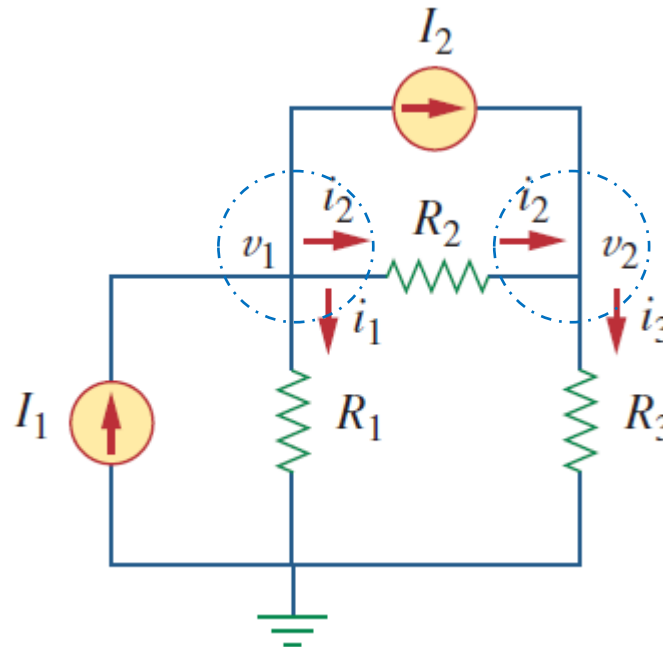- ii. The other node (**nonreference nodes**) will be assigned as  $v_1, v_2, \dots$



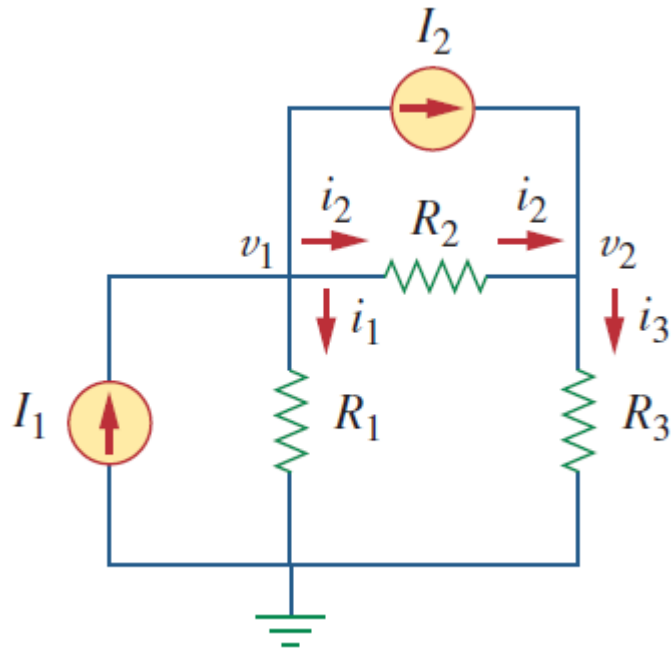iii. Apply **KCL** to each of the **nonreference** node.



At node  $v_1$ :

$$I_1 = I_2 + i_1 + i_2$$

At node  $v_2$ :

$$i_3 = I_2 + i_2$$






- iv. Apply the **Ohm's law** to express the unknown current  $i_1$ ,  $i_2$  and  $i_3$  in terms of node voltages.

$$i = \frac{V_{\text{higher}} - V_{\text{lower}}}{R}$$

Note: Current flows from a **higher potential** (positive terminal) to a **lower potential** (negative terminal) in resistor.



# Nodal Analysis

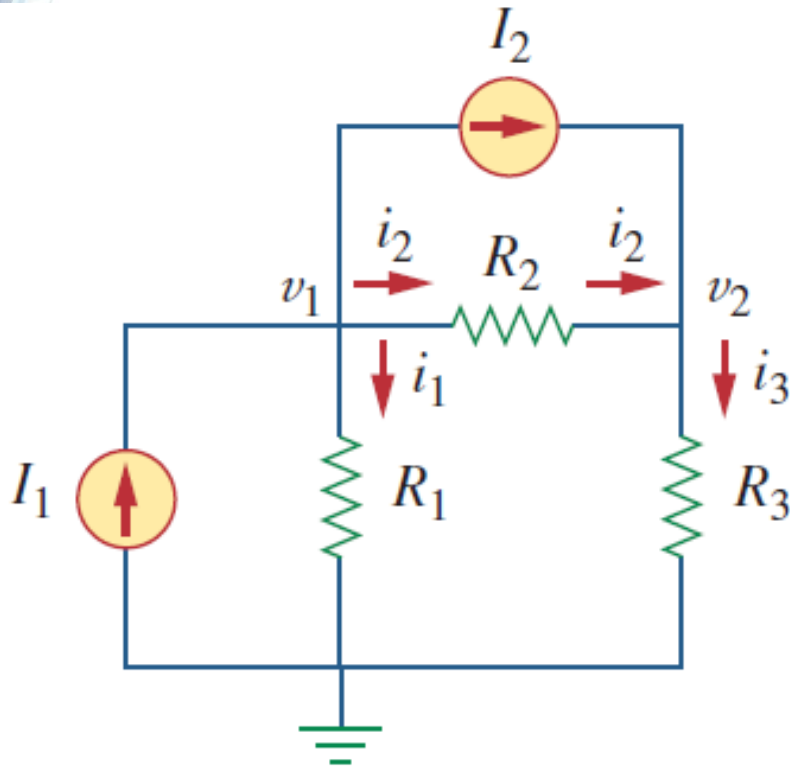

$$i_1 = \frac{v_1 - 0}{R_1} \quad i_2 = \frac{v_1 - v_2}{R_2}$$


$$i_3 = \frac{v_2 - 0}{R_3}$$

$$I_1 = I_2 + \frac{v_1 - 0}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$\frac{v_2 - 0}{R_3} = I_2 + \frac{v_1 - v_2}{R_2}$$
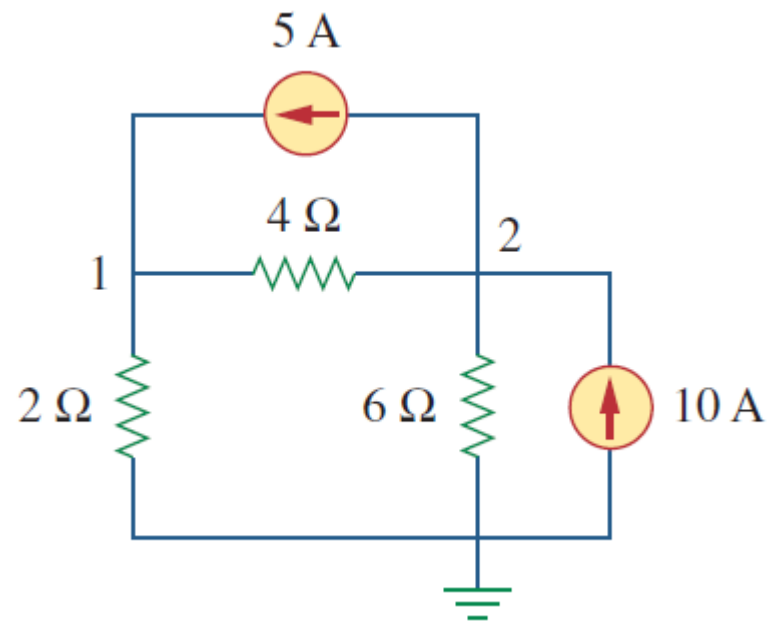
## Example #1


Obtain the node voltages for the following circuit



# Example #1

## Solution

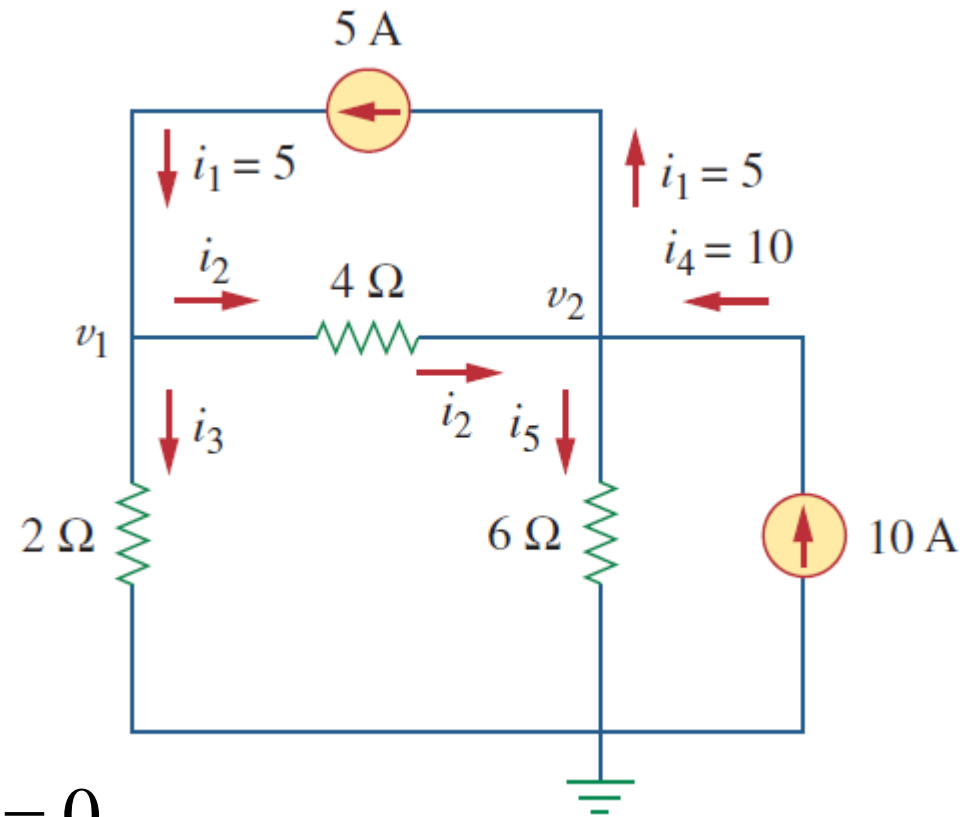- i. Select a node as a **reference node**
- ii. The other node (**nonreference nodes**) will be assigned as  $v_1, v_2 \dots$
- iii. Apply **KCL** to each of the **nonreference** node.



At node  $v_1$ :

$$i_1 - i_2 - i_3 = 0$$

$$i_1 = i_2 + i_3$$

At node  $v_2$ :

$$i_2 + i_4 - i_1 - i_5 = 0$$

$$i_2 + i_4 = i_1 + i_5$$



## Example #1

iv. Express the currents in term of node voltages.

$$i_2 = \frac{v_1 - v_2}{4}$$

$$i_3 = \frac{v_1 - 0}{2}$$

$$i_5 = \frac{v_2 - 0}{6}$$

$$5 = \frac{v_1 - v_2}{4} + \frac{v_1}{2}$$

$$\frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2}{6}$$

Rearrange the equation

$$3v_1 - v_2 = 20$$

$$-3v_1 + 5v_2 = 60$$



## Example #1

Then in matrix form

$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

By using Cramer's Rule


$$\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix} = 15 - 3 = 12$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} 20 & -1 \\ 60 & 5 \end{bmatrix}}{\Delta} = \frac{100 + 60}{12} = 13.333 \text{ V}$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 3 & 20 \\ -3 & 60 \end{bmatrix}}{\Delta} = \frac{180 + 60}{12} = 20 \text{ V}$$
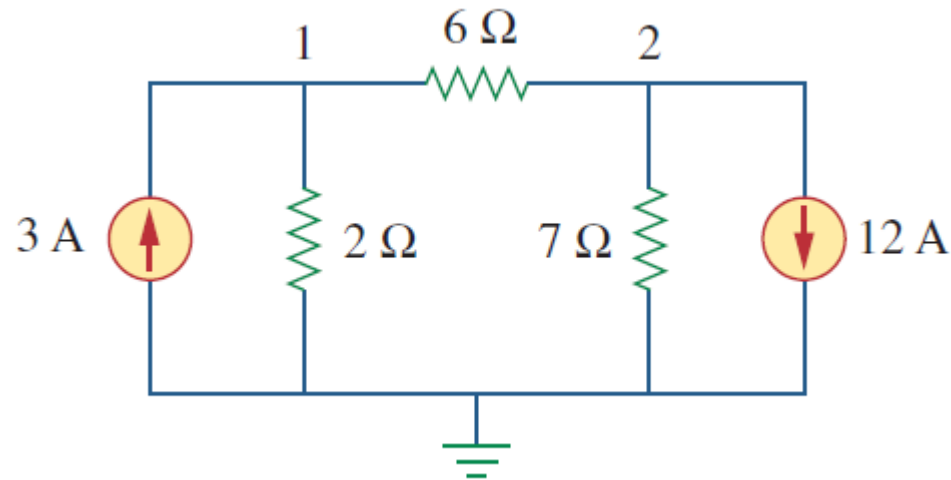
## Example #2

In the given circuit, obtain the node voltages



Answer


$$v_1 = -6 \text{ V}$$

$$v_2 = -42 \text{ V}$$


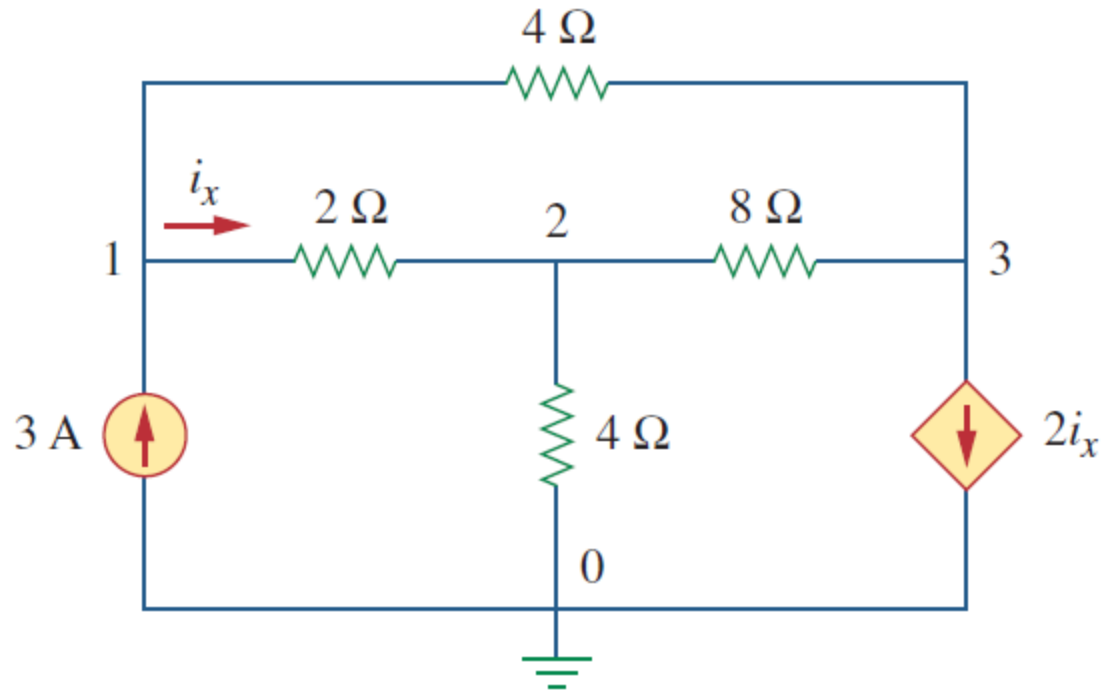
### Example #3

For the given circuit, determine the voltages at the nodes



Answer

$$v_1 = 4.8 \text{ V}$$

$$v_2 = 2.4 \text{ V}$$

$$v_3 = -2.4 \text{ V}$$



Review of steps for nodal analysis **without** voltage sources:

- i. Select a node as a **reference node** – This reference node also called the **ground**, have **zero potential**.
- ii. The other node (**nonreference nodes**) will be assigned as  $v_1, v_2, \dots$
- iii. Apply **KCL** to each of the **nonreference** node.
- iv. Apply the **Ohm's law** to express the unknown current  $i_1, i_2$  and  $i_3$  in terms of node voltages.

$$i = \frac{V_{\text{higher}} - V_{\text{lower}}}{R}$$




## WITH VOLTAGE SOURCE

### Case 1


If a voltage source is connected **between** the reference node and a nonreference node. The voltage at the nonreference node **equal to** the voltage source.

$$v_1 = 10 \text{ V}$$

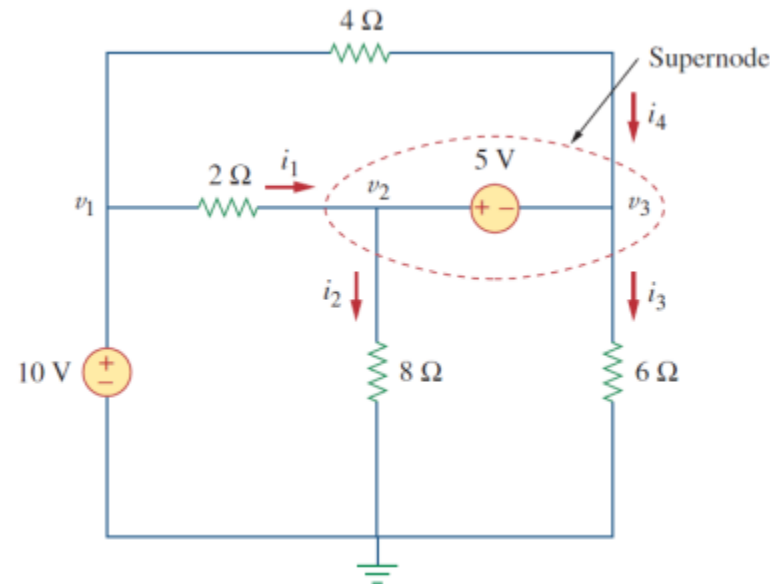

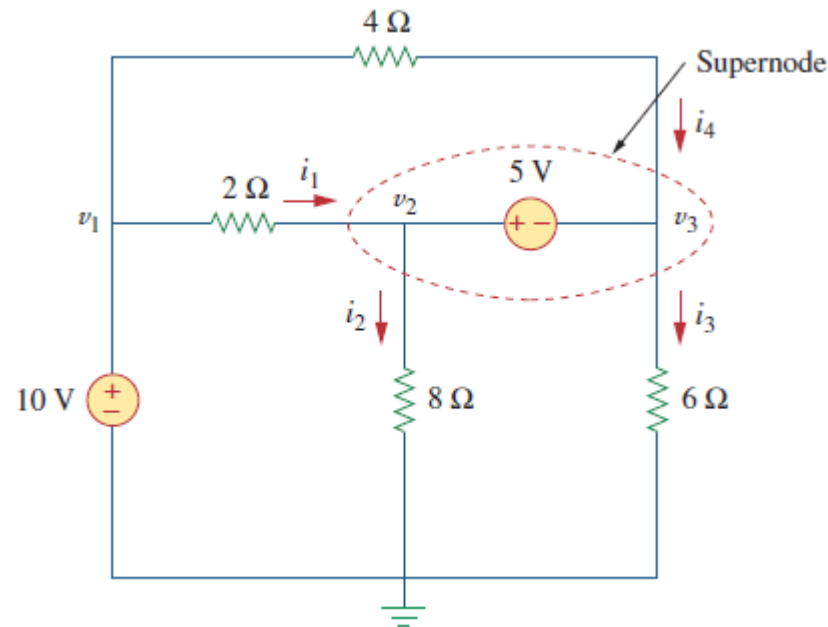
## Case 2

If the voltage source (dependent or independent) is connected between two nonreference nodes, the two nonreference nodes form a generalized node or **supernode**.


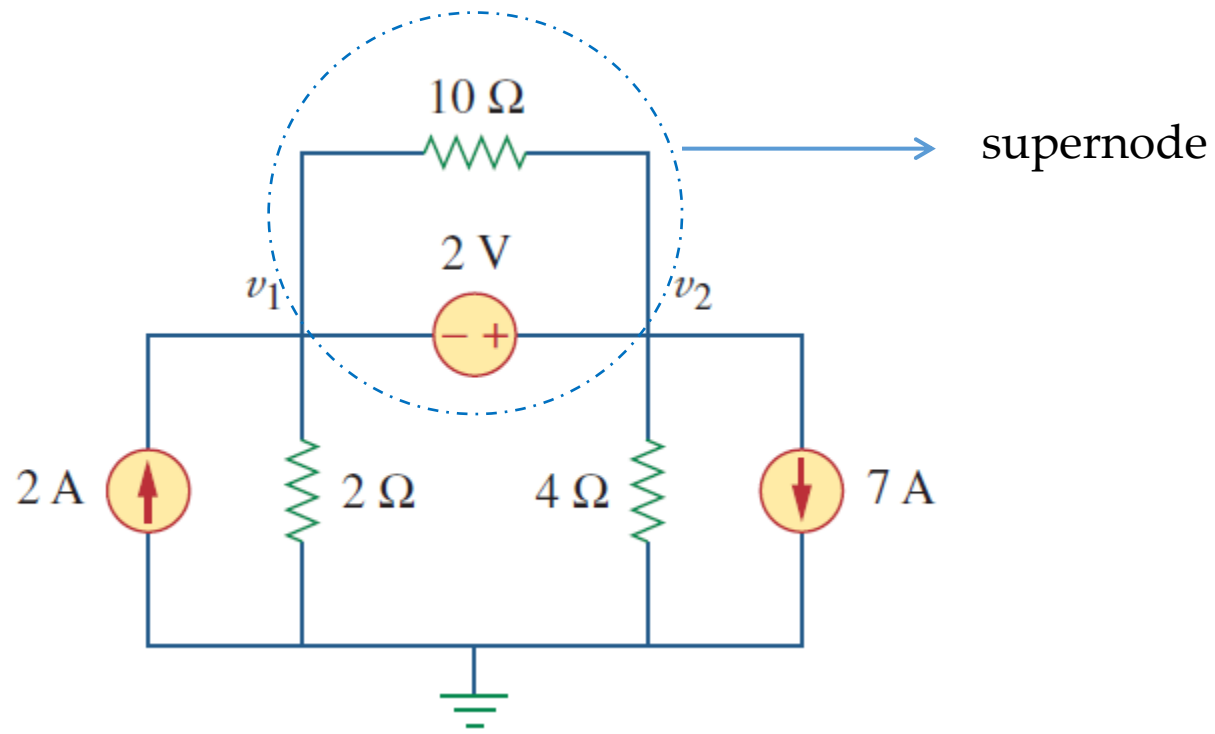
# Nodal Analysis

A supernode is formed by **enclosing a** (dependent or independent) **voltage source** connected between two nonreference nodes and **any elements** connected in **parallel** with it.



# Nodal Analysis


- ❑ A supernode requires the applications of both **KCL** and **KVL**.
- ❑ A supernode has no voltage of its own.
- ❑ A supernode can be assumed as one big node.



## Steps for nodal analysis with voltage source:

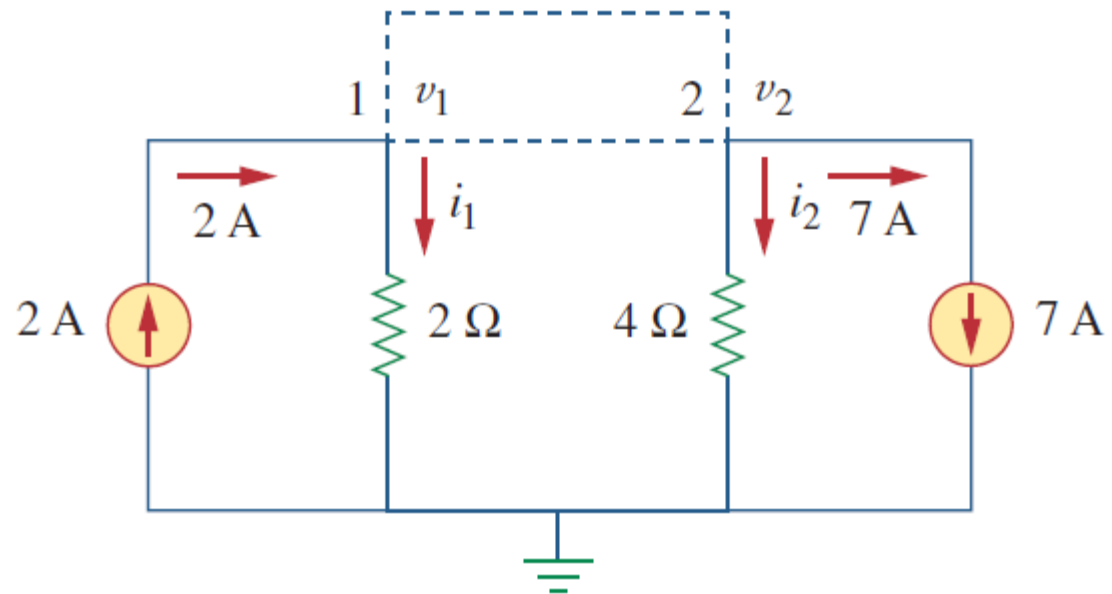- i. Select a node as a **reference node** – This reference node also called the **ground**, have **zero potential**.
- ii. Assign the other nodes (**nonreference nodes**) as  $v_1, v_2, \dots$  and identify the **supernode**.
- iii. Apply **KCL** to each of the **nonreference** node and the **supernode**.

Note: For supernode, apply the KCL **around** the supernode. Assume the supernode as one big node




# Nodal Analysis

iv. Express the currents in term of node voltages.


$$i = \frac{V_{\text{higher}} - V_{\text{lower}}}{R}$$

v. Apply **KVL** around the supernode.

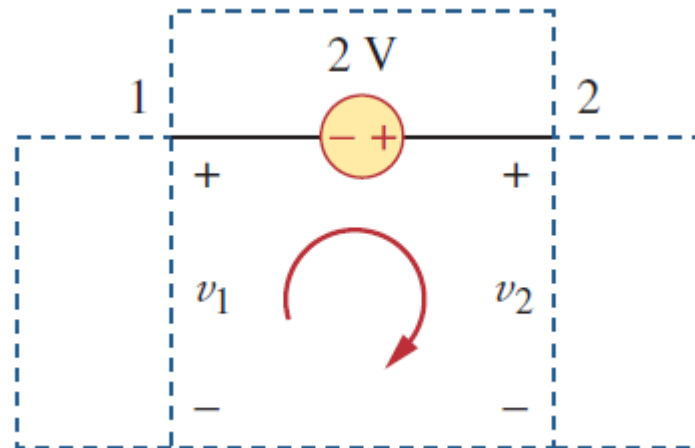
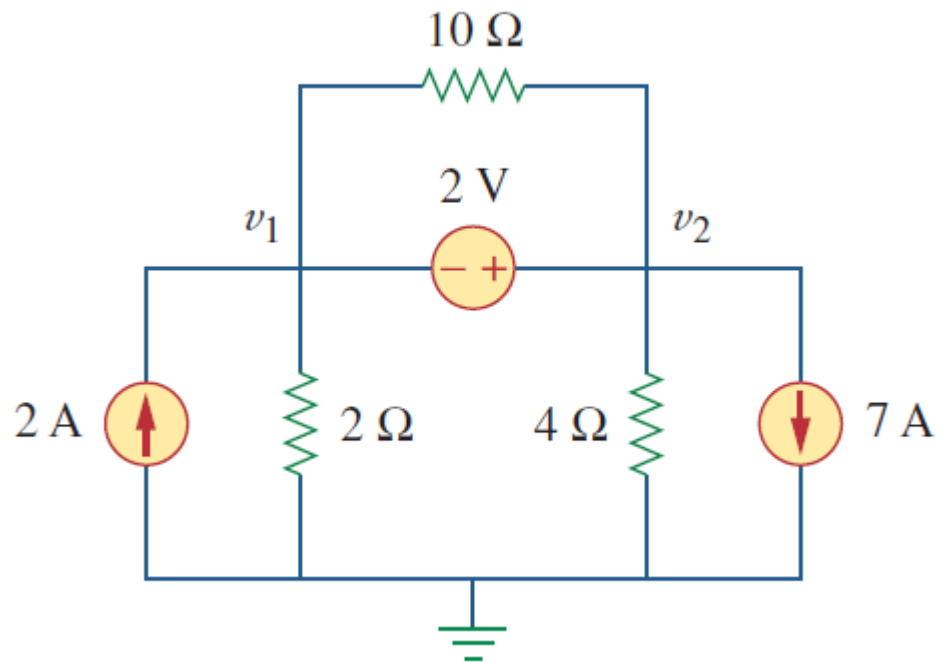
## Example #4

Obtain the node voltages for the following circuit







# Example #4

## Solution

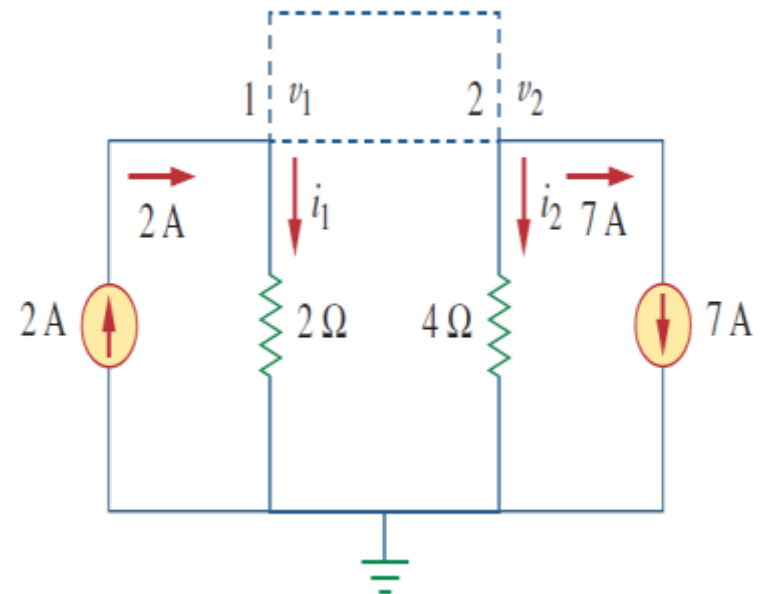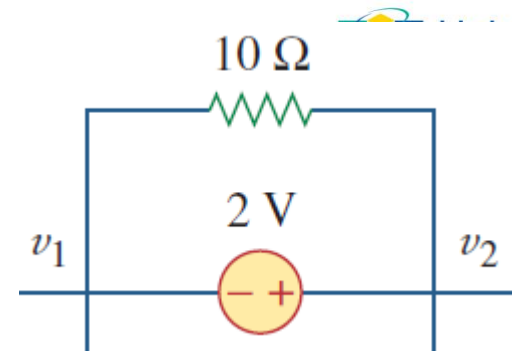- i. Select a node as a **reference node**
- ii. Assign the other node (**nonreference nodes**) as  $v_1, v_2 \dots$  and identify the **supernode**
- iii. Apply **KCL** to each of the **nonreference node** and the **supernode**.



At node  $v_1@1$ :

$$i_1 - 2 = 0$$

$$i_1 = 2 \text{ A}$$

At node  $v_2@2$ :

$$i_2 + 7 = 0$$

$$i_2 = -7 \text{ A}$$

At supernode

$$2 - i_1 - i_2 - 7 = 0$$

$$2 = i_1 + i_2 + 7$$



## Example #4

iv. Express the currents in term of node voltages.

$$i_1 = \frac{v_1 - 0}{2}$$

$$i_2 = \frac{v_2 - 0}{4}$$

$$2 = \frac{v_1}{2} + \frac{v_2}{4} + 7$$

Rearrange the equation


$$8 = 2v_1 + v_2 + 28$$

$$v_2 = -20 - 2v_1$$

v. Apply **KVL** around the supernode.

$$-v_1 - 2 + v_2 = 0$$

$$v_2 = v_1 + 2$$

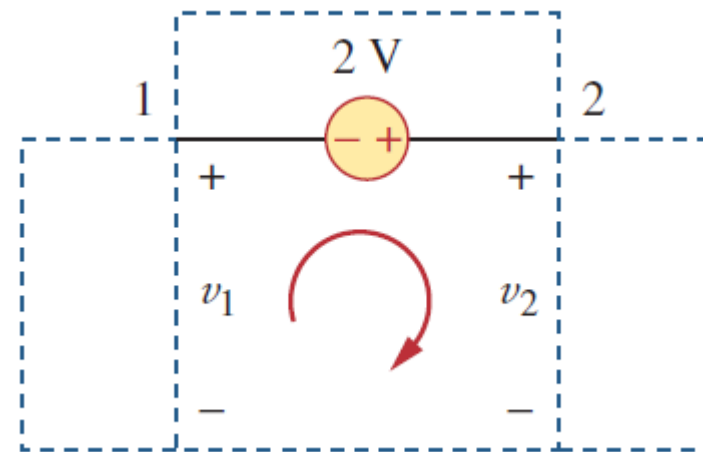

## Example #4

Then in matrix form

$$\begin{bmatrix} 2 & 1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -20 \\ 2 \end{bmatrix}$$

By using Cramer's Rule


$$\Delta = \begin{vmatrix} 2 & 1 \\ -1 & 1 \end{vmatrix} = 2 + 1 = 3$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} -20 & 1 \\ 2 & 1 \end{bmatrix}}{\Delta} = \frac{-20 - 2}{3} = -7.333 \text{ V}$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 2 & -20 \\ -1 & 2 \end{bmatrix}}{\Delta} = \frac{4 - 20}{3} = -5.333 \text{ V}$$
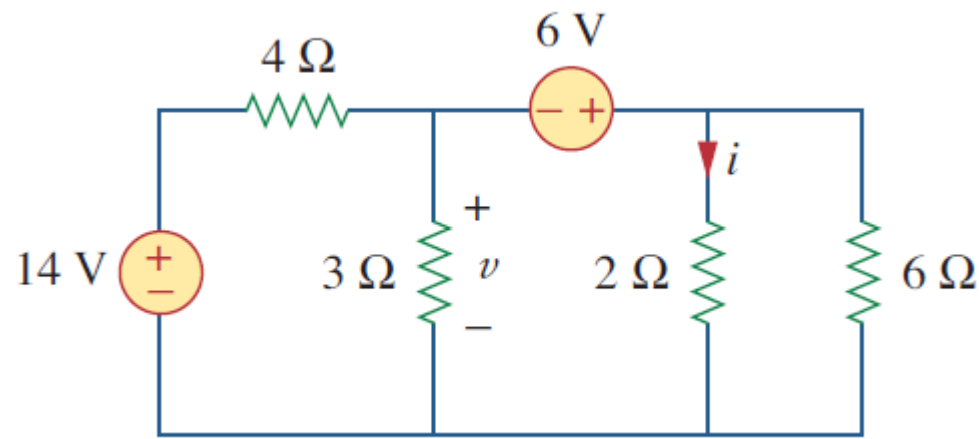
## Example #5

Find  $v$  and  $i$  for the given circuit




Answer

$$v = -400 \text{ mV} \quad i = 2.8 \text{ A}$$




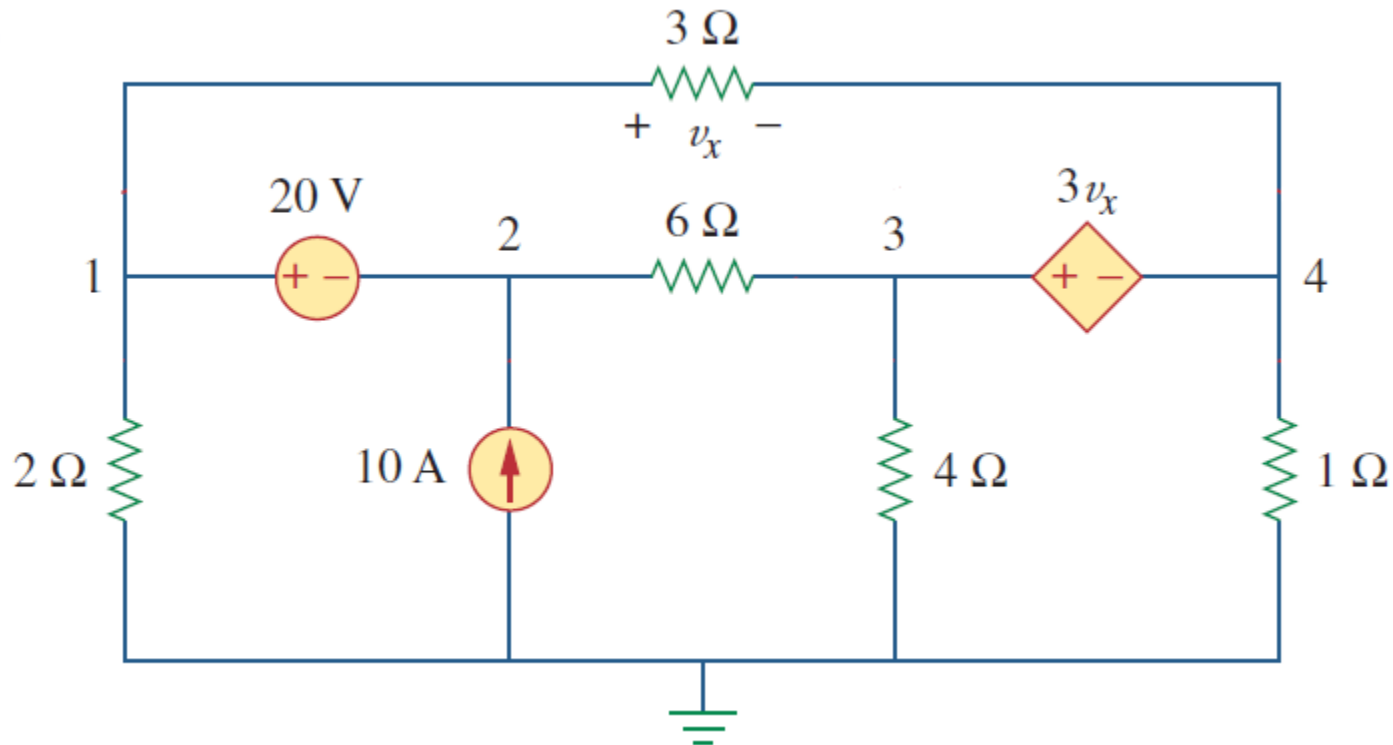
## Example #6

Obtain the node voltages for the following circuit




# Example #6

## Solution

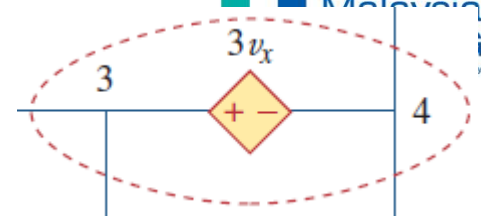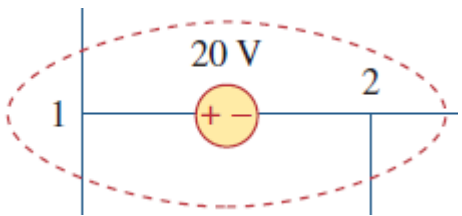

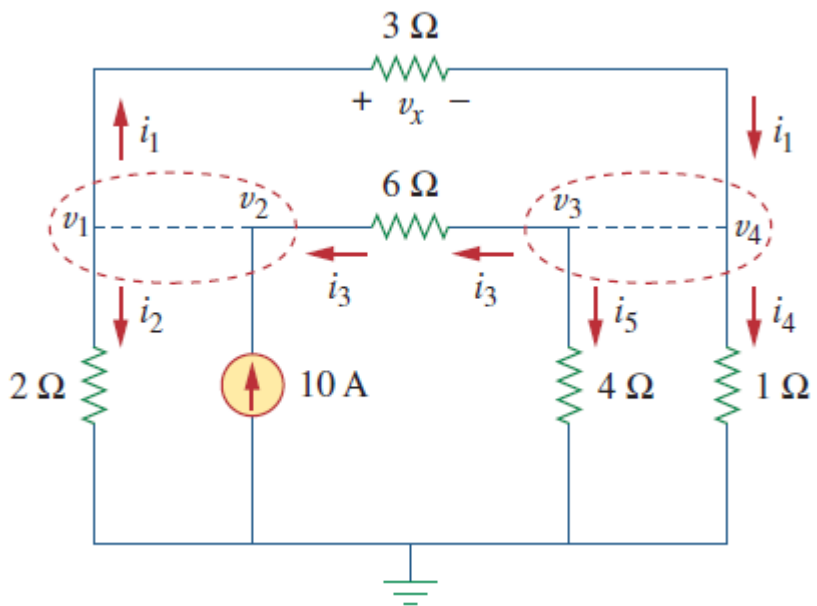- i. Select a node as a **reference node**
- ii. Assign the other node (**nonreference nodes**) as  $v_1, v_2 \dots$  and identify the **supernode**
- iii. Apply **KCL** to each of the **nonreference node** and the **supernode**.



At supernode 1-2:

$$i_3 + 10 - i_1 - i_2 = 0$$

$$i_3 + 10 = i_1 + i_2$$

At supernode 3-4:

$$i_1 - i_3 - i_4 - i_5 = 0$$

$$i_1 = i_3 + i_4 + i_5$$



## Example #6

iv. Express the currents in term of node voltages.

$$i_1 = \frac{v_1 - v_4}{3} \quad i_2 = \frac{v_1 - 0}{2} \quad i_3 = \frac{v_3 - v_2}{6}$$

$$i_4 = \frac{v_4 - 0}{1} \quad i_5 = \frac{v_3 - 0}{4}$$

$$\frac{v_3 - v_2}{6} + 10 = \frac{v_1 - v_4}{3} + \frac{v_1}{2}$$

$$\frac{v_1 - v_4}{3} = \frac{v_3 - v_2}{6} + \frac{v_4}{1} + \frac{v_3}{4}$$

$$5v_1 + v_2 - v_3 - 2v_4 = 60$$

$$4v_1 + 2v_2 - 5v_3 - 16v_4 = 0$$

## Example #6

- v. Apply **KVL** around the supernode.

At loop 1

$$-v_1 + 20 + v_2 = 0$$


$$v_1 - v_2 = 20$$

At loop 2

$$-v_3 + 3v_x + v_4 = 0$$

and  $v_x = v_1 - v_4$

$$3v_1 - v_3 - 2v_4 = 0$$

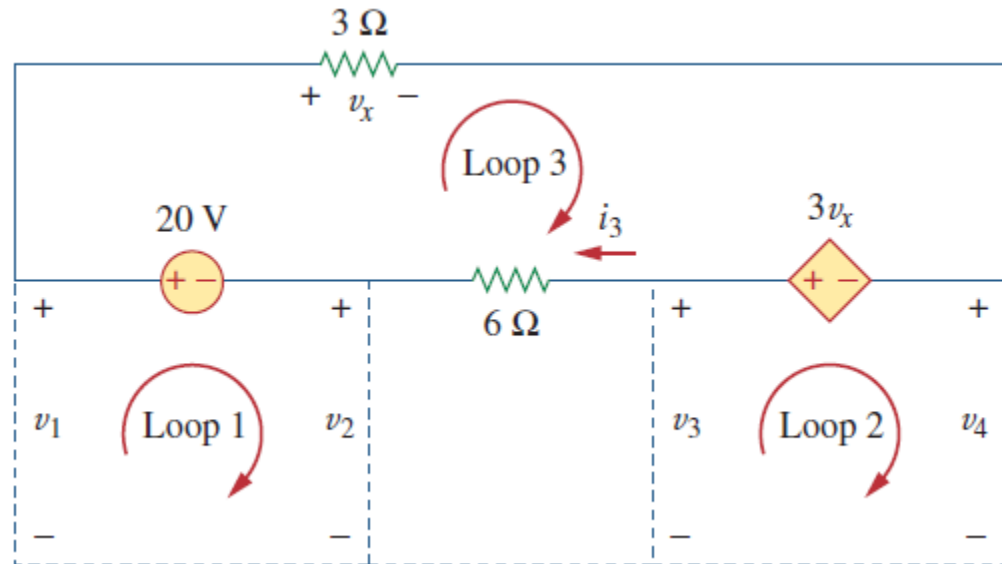

At loop 3

$$v_x - 3v_x + 6i_3 - 20 = 0$$

$$-2v_1 - v_2 + v_3 + 2v_4 = 20$$

and

$$v_x = v_1 - v_4$$

$$6i_3 = v_3 - v_2$$



## Example #6

$$\text{From loop 1 } v_2 = v_1 - 20$$

and subs this Eq. into

$$5v_1 + v_2 - v_3 - 2v_4 = 60$$

and

$$4v_1 + 2v_2 - 5v_3 - 16v_4 = 0$$

$$6v_1 - v_3 - 2v_4 = 80$$

$$6v_1 - 5v_3 - 16v_4 = 40$$

Then in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{bmatrix} \begin{bmatrix} v_1 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 80 \\ 40 \end{bmatrix}$$

## Example #6

By using Cramer's Rule

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{vmatrix} = -18$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} 0 & -1 & -2 \\ 80 & -1 & -2 \\ 40 & -5 & -16 \end{bmatrix}}{\Delta} = \frac{-480}{-18} = 26.667 \text{ V}$$



## Example #6

$$v_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{bmatrix} 3 & -0 & -2 \\ 6 & 80 & -2 \\ 6 & 40 & -16 \end{bmatrix}}{\Delta} = \frac{-3120}{-18} = 173.333 \text{ V}$$

$$v_4 = \frac{\Delta_4}{\Delta} = \frac{\begin{bmatrix} 3 & -1 & 0 \\ 6 & -1 & 80 \\ 6 & -5 & 40 \end{bmatrix}}{\Delta} = \frac{840}{-18} = -46.667 \text{ V}$$


$$v_2 = v_1 - 20$$

$$v_2 = 26.667 - 20 = 6.667 \text{ V}$$


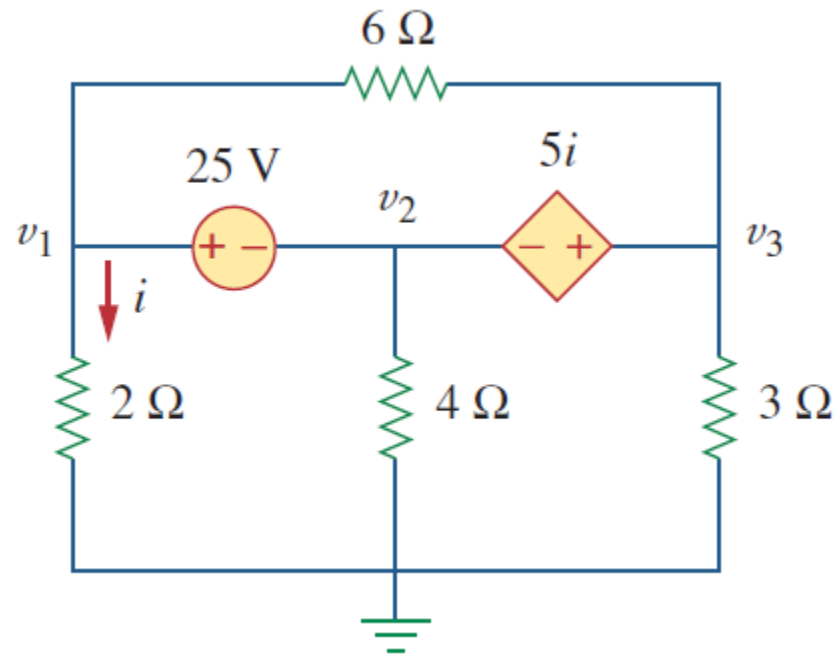
## Example #7

By using nodal analysis obtain the node voltages for the following circuit



Answer

$$v_1 = 7.608 \text{ V}$$

$$v_2 = -17.39 \text{ V}$$

$$v_3 = 1.6305 \text{ V}$$




## WITHOUT CURRENT SOURCE

- ❑ Mesh analysis use the **mesh currents** as the circuit variables.
- ❑ Recall: nodal analysis use the node voltages as the circuit variables.
- ❑ Recall: a loop is a closed path with no node passed more than once.
- ❑ A **mesh** is a loop that does not contain any other loop within it.


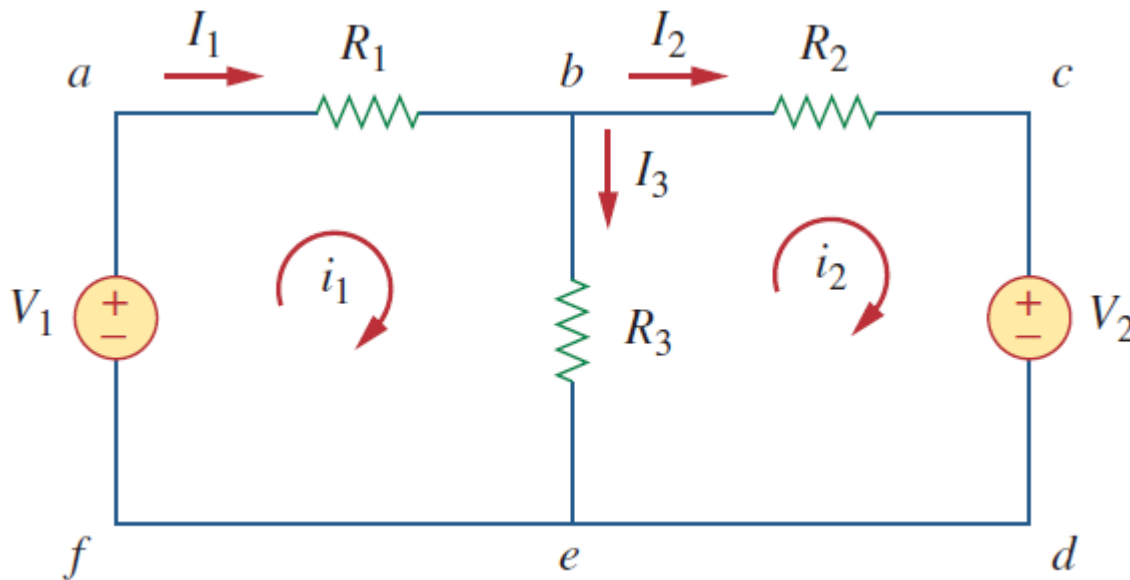
# Mesh Analysis

- Recall: nodal analysis applies **KCL** to find unknown voltages.
- Mesh analysis applies **KVL** to find unknown currents.




abefa & bcdeb are meshes.

abcdefa is not a mesh.

- The current through a mesh is known as **mesh current**.
- First, the analysis will concentrate on circuit with no current source.
- Steps to determine mesh currents:
  - i. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes. The flow of the mesh currents is conventionally assume in **clockwise direction**.
  - ii. Determine the **polarity & the direction** of current flow through each element.
  - iii. Apply **KCL for each node** in term of mesh current.
  - iv. Apply **KVL to each of the  $n$  meshes**. Use Ohm's law to express the voltages in terms of the mesh currents.



# Mesh Analysis

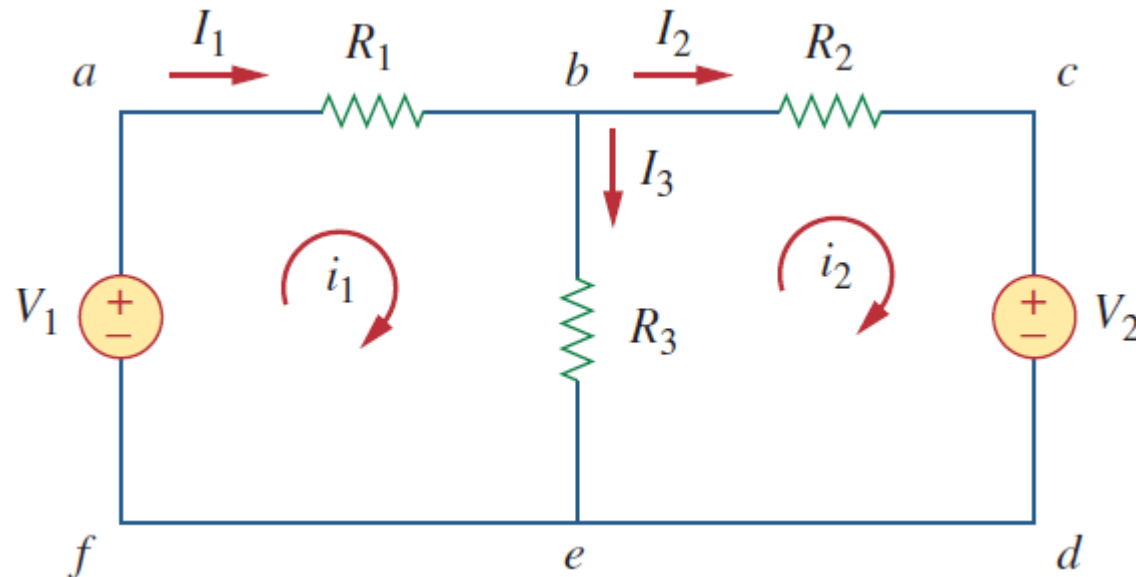

- i. Assign the mesh currents:  $i_1$  and  $i_2$
- ii. Determine the polarity & the direction of current.

*Note: let the direction of current at the outside branch = direction of the mesh current*





iii. Apply KCL.

$$I_3 = I_1 - I_2$$

since  $I_1 = i_1$   
 $I_2 = i_2$

$$I_3 = i_1 - i_2$$

Note:  $I$  for branch current,  $i$  for mesh current

iv. Apply KVL to each mesh.

Mesh 1  $-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$

$$3i_1 - 2i_2 = 1 \quad \rightarrow (1)$$



Mesh 2

$$6i_2 + 4i_2 - 10(i_1 - i_2) - 10 = 0$$

$$i_1 - 2i_2 = -1$$

→ (2)

Then in matrix form

By using Cramer's Rule

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -2 \\ -1 & 2 \end{vmatrix} = 6 - 2 = 4$$


$$i_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix}}{\Delta} = \frac{2 + 2}{4} = 1 \text{ A}$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix}}{\Delta} = \frac{3 + 1}{4} = 1 \text{ A}$$


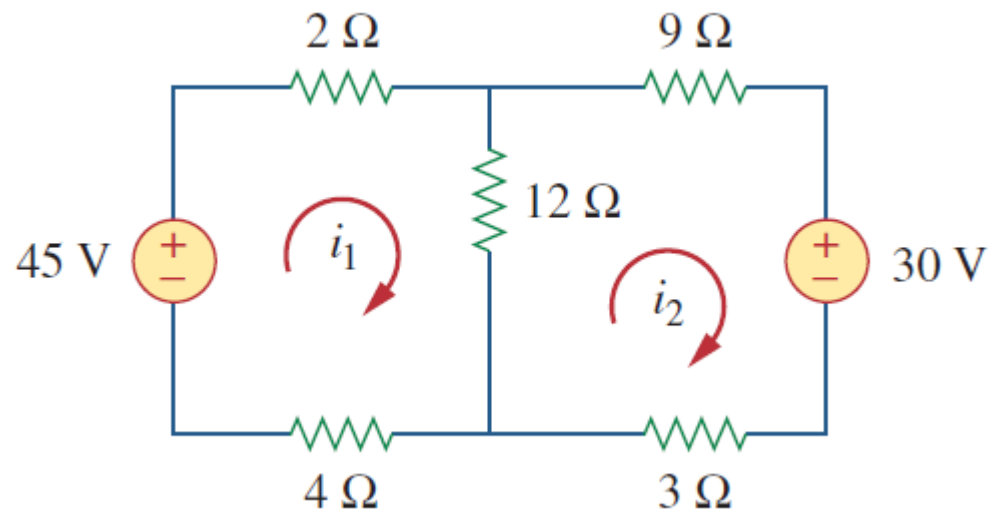
## Example #8

Calculate the mesh current  $i_1$  and  $i_2$  for the following circuit




Answer

$$i_1 = 2.5\ \text{A} \quad i_2 = 0\ \text{A}$$


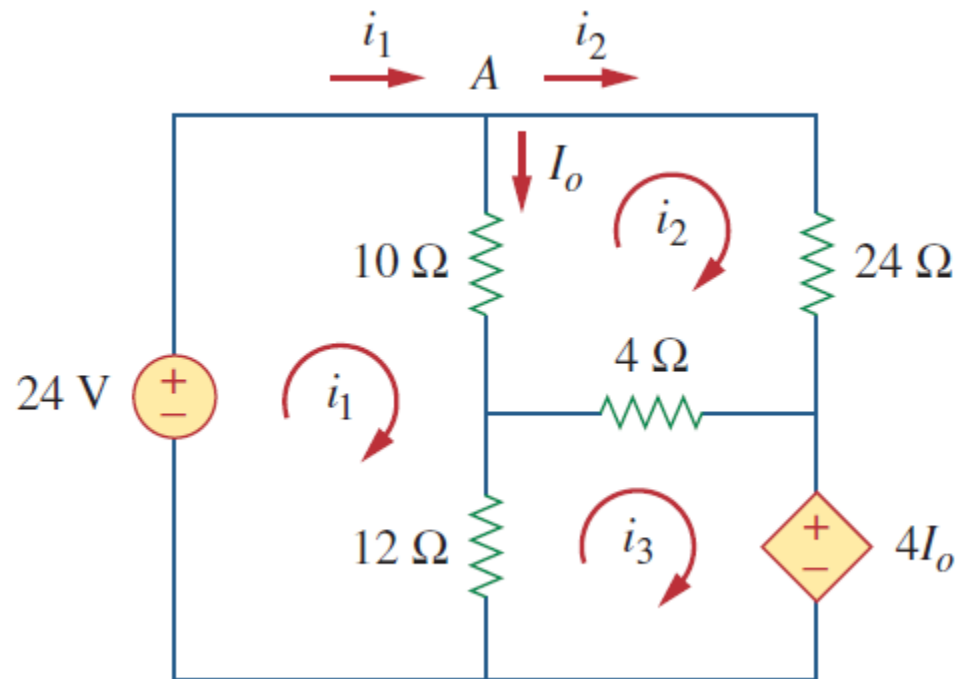
## Example #9

Use mesh analysis to find  $I_o$  for the following circuit



# Mesh Analysis

- i. Assign the mesh currents:  $i_1$  and  $i_2$ .
- ii. Determine the polarity & the direction of current.
- iii. Apply KCL.

$$I_o = i_1 - i_2$$

- iv. Apply KVL to each mesh.

Mesh 1

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$11i_1 - 5i_2 - 6i_3 = 12 \quad \rightarrow (1)$$



Mesh 2

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$-5i_1 + 19i_2 - 2i_3 = 0 \quad \rightarrow (2)$$

Mesh 3

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$-i_1 - i_2 + 2i_3 = 0 \quad \rightarrow (3)$$

Then in matrix form



# Mesh Analysis

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

By using Cramer's Rule

$$\Delta = 192$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{432}{192} = 2.25 \text{ A} \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{144}{192} = 0.75 \text{ A}$$


$$i_3 = \frac{\Delta_3}{\Delta} = \frac{288}{192} = 1.5 \text{ A}$$

Thus,  $I_o = i_1 - i_2 = 1.5 \text{ A}$


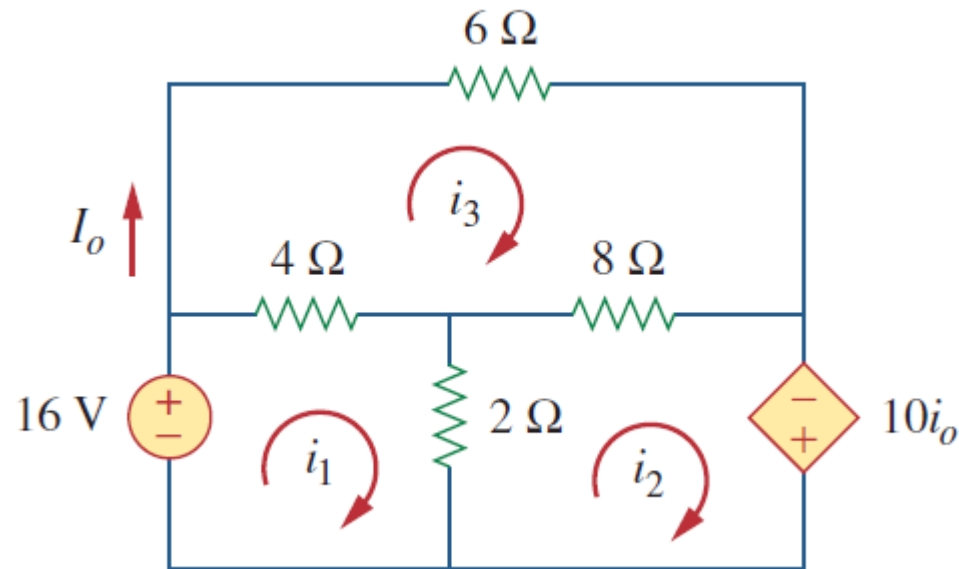
## Example #10

By using mesh analysis find  $I_o$  in the following circuit



Answer

$$I_o = -4 \text{ A}$$






## WITH CURRENT SOURCE
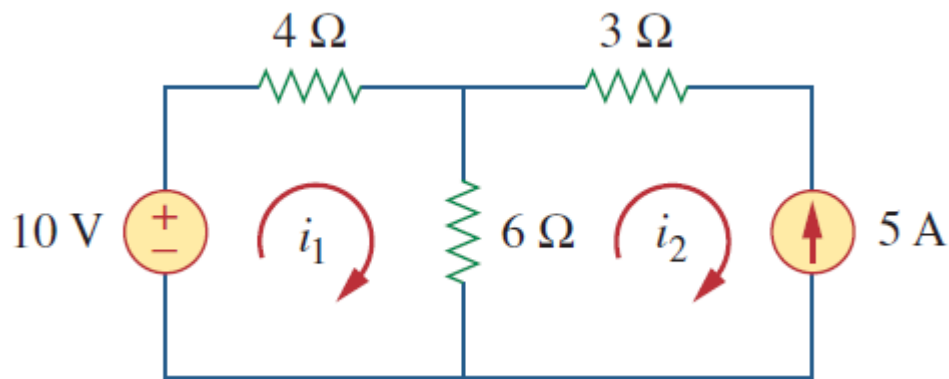
### Case 1

When the current source exist only in **one mesh**



Set the value of  $i_2 = -5$  A and write a mesh equation for the other mesh in the usual way.


$$-10 + 4i_1 + 6(i_1 - i_2) = 0 \quad \Rightarrow \quad i_1 = -2 \text{ A}$$



# Mesh Analysis
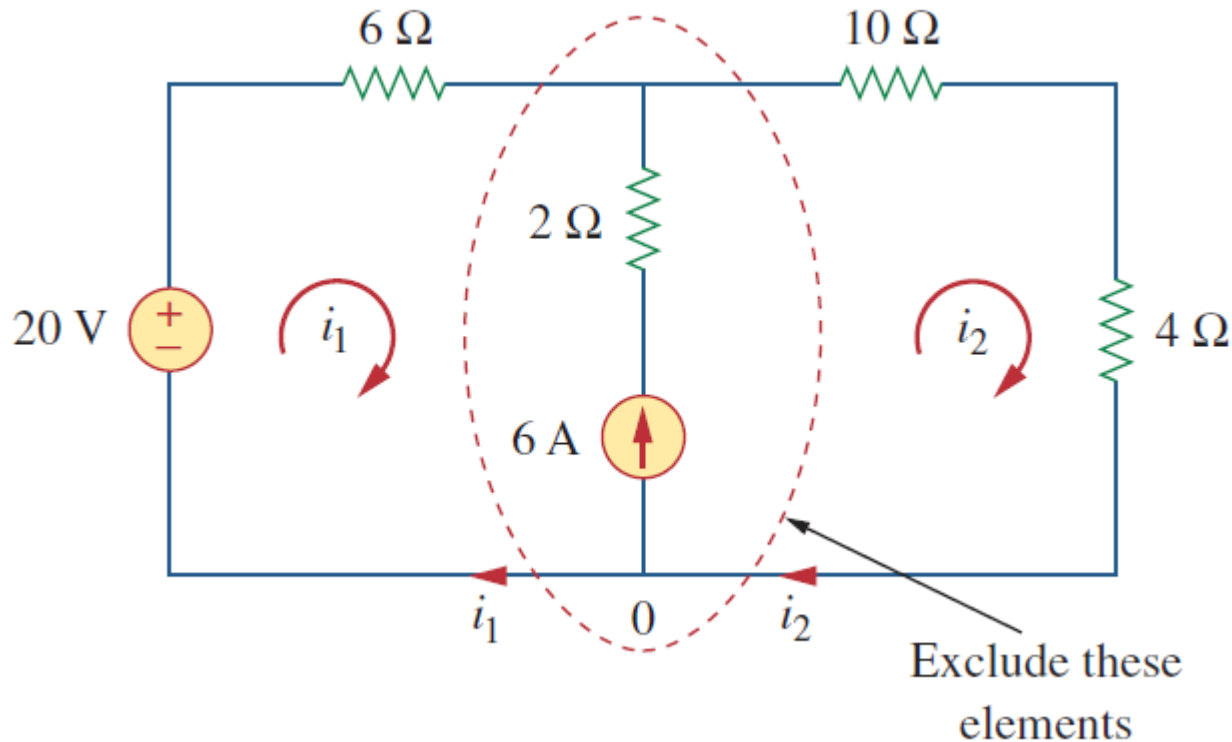
## Case 2


When the current source exist between **two meshes**.



need to create a **supermesh** by excluding the current source and any elements connected in series with it.



# Mesh Analysis

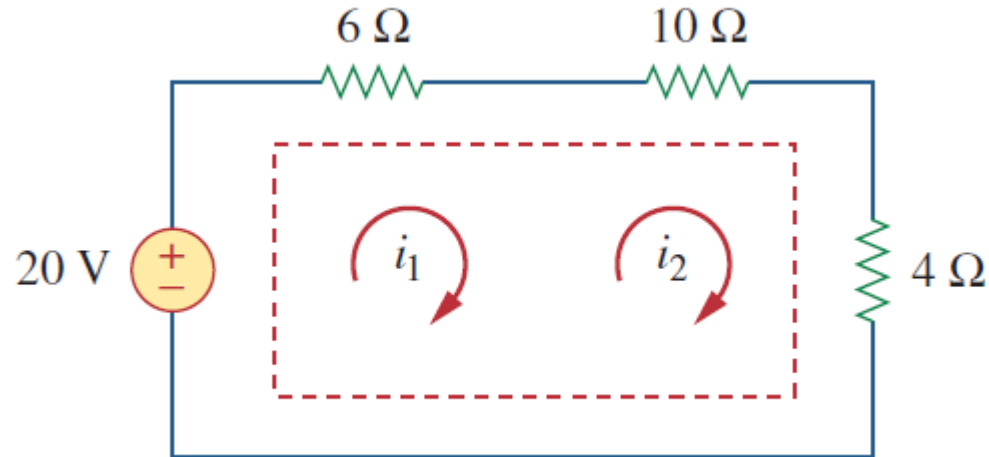

*NOTE:* A **supermesh** results when **two meshes** have a (dependent or independent) **current source** in common.

Applying KVL to the supermesh

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$


$$6i_1 + 14i_2 = 20 \quad \rightarrow (1)$$



# Mesh Analysis

Applying KCL to the circuit

$$i_2 = i_1 + 6 \rightarrow (2)$$

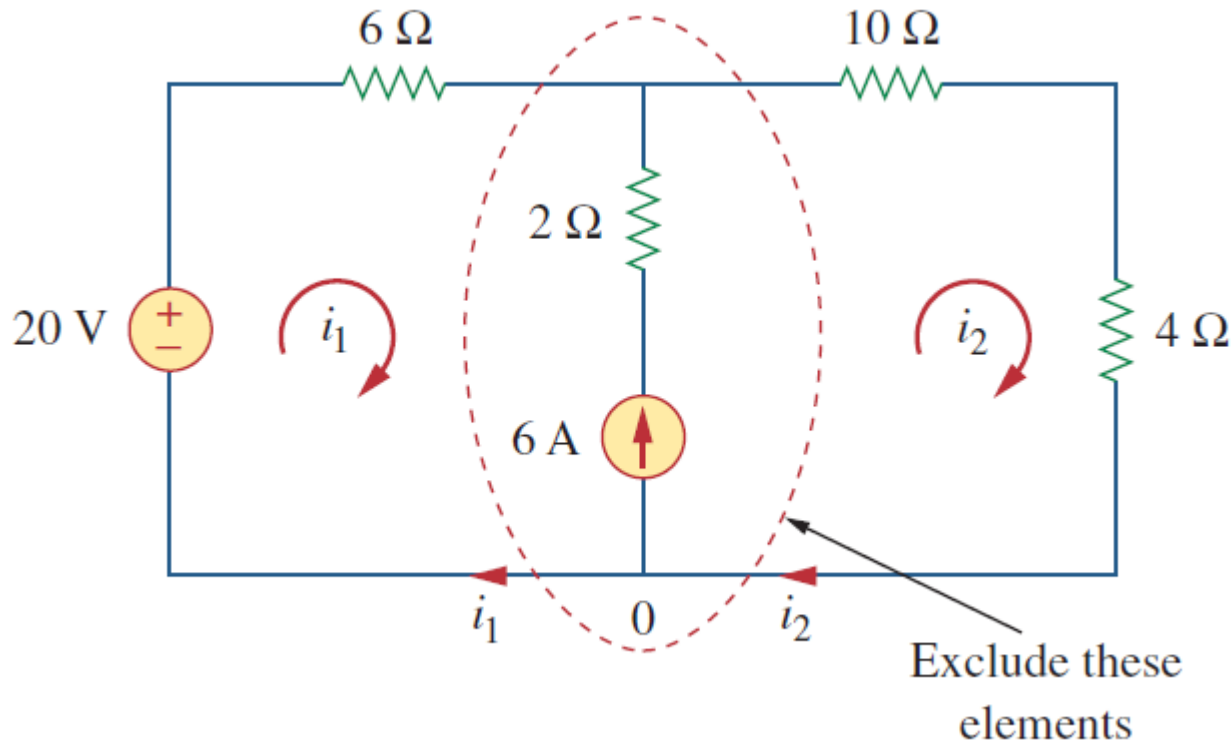

Then solve the  
Eq. (1) and (2)

$$i_1 = -3.2 \text{ A} \quad i_2 = 2.8 \text{ A}$$




- ❑ The current source in the supermesh provides the **constraint equation** necessary to solve for the mesh currents.
- ❑ A supermesh has **no current of its own**.
- ❑ A supermesh requires the application of both **KVL** and **KCL**.


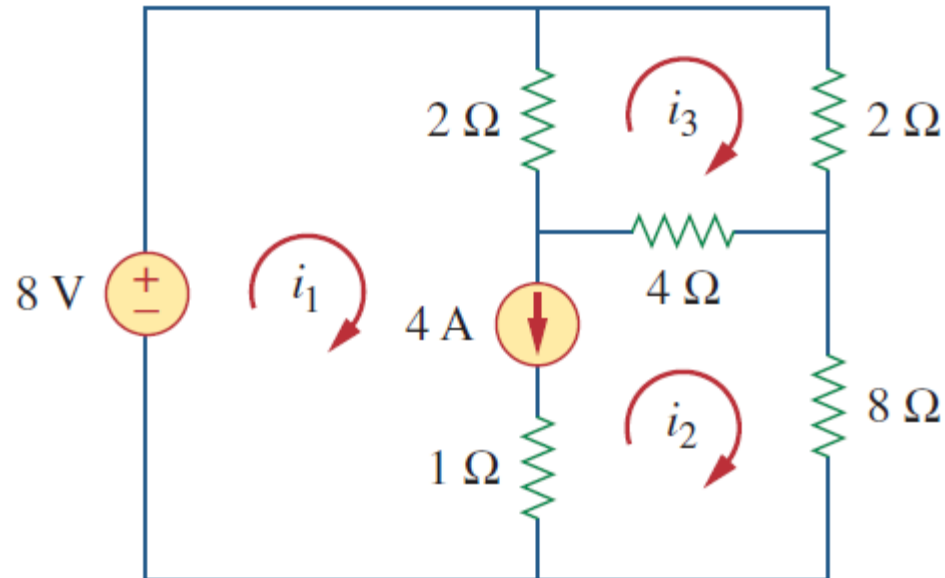
## Example #11

By using mesh analysis find  $i_1$ ,  $i_2$  and  $i_3$  in the following circuit




## Example #11

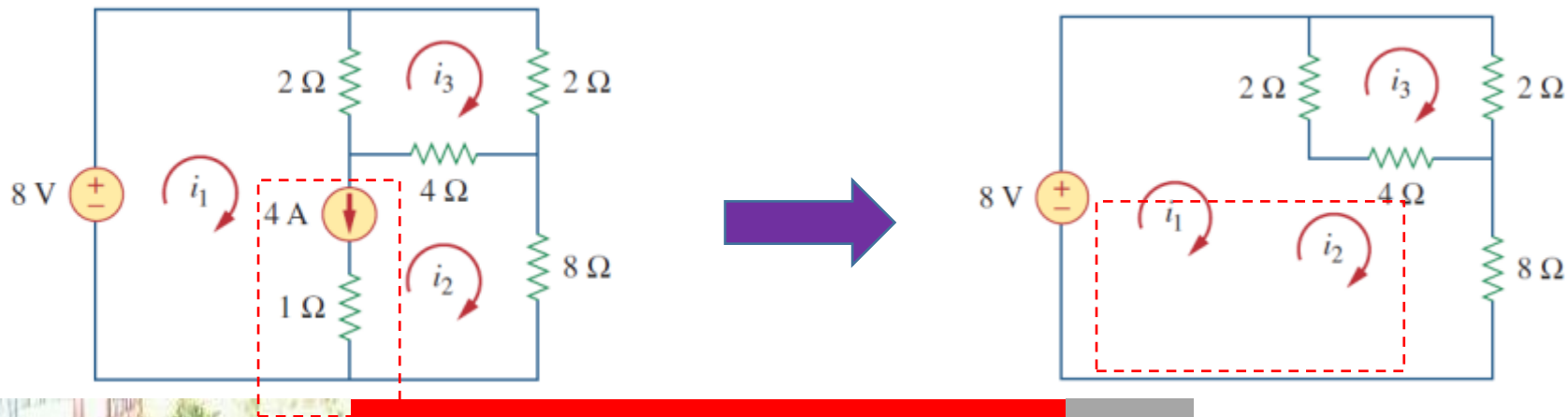- i. Assign the mesh currents:  $i_1$ ,  $i_2$  and  $i_3$ .
- ii. Determine the polarity & the direction of current.
- iii. Applying KCL to supermesh.

$$i_1 = 4 + i_2 \quad \rightarrow (1)$$

Notice that meshes (1) and (2) form a supermesh since they have independent current source in common



## Example #11

iv. Apply KVL to supermesh.

$$-8 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$

$$2i_1 + 12i_2 - 6i_3 = 8 \quad \rightarrow (2)$$

Applying KVL in Mesh 3

$$2i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0$$

$$-2i_1 - 4i_2 + 8i_3 = 0 \quad \rightarrow (3)$$

Then in matrix form





## Example #11

$$\begin{bmatrix} 1 & -1 & 0 \\ 2 & 12 & -6 \\ -2 & -4 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 8 \\ 0 \end{bmatrix}$$

By using Cramer's Rule  $\Delta = 76$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{352}{76} = 4.3516 \text{ A}$$


$$i_2 = \frac{\Delta_2}{\Delta} = \frac{48}{76} = 0.6316 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{112}{76} = 1.4737 \text{ A}$$


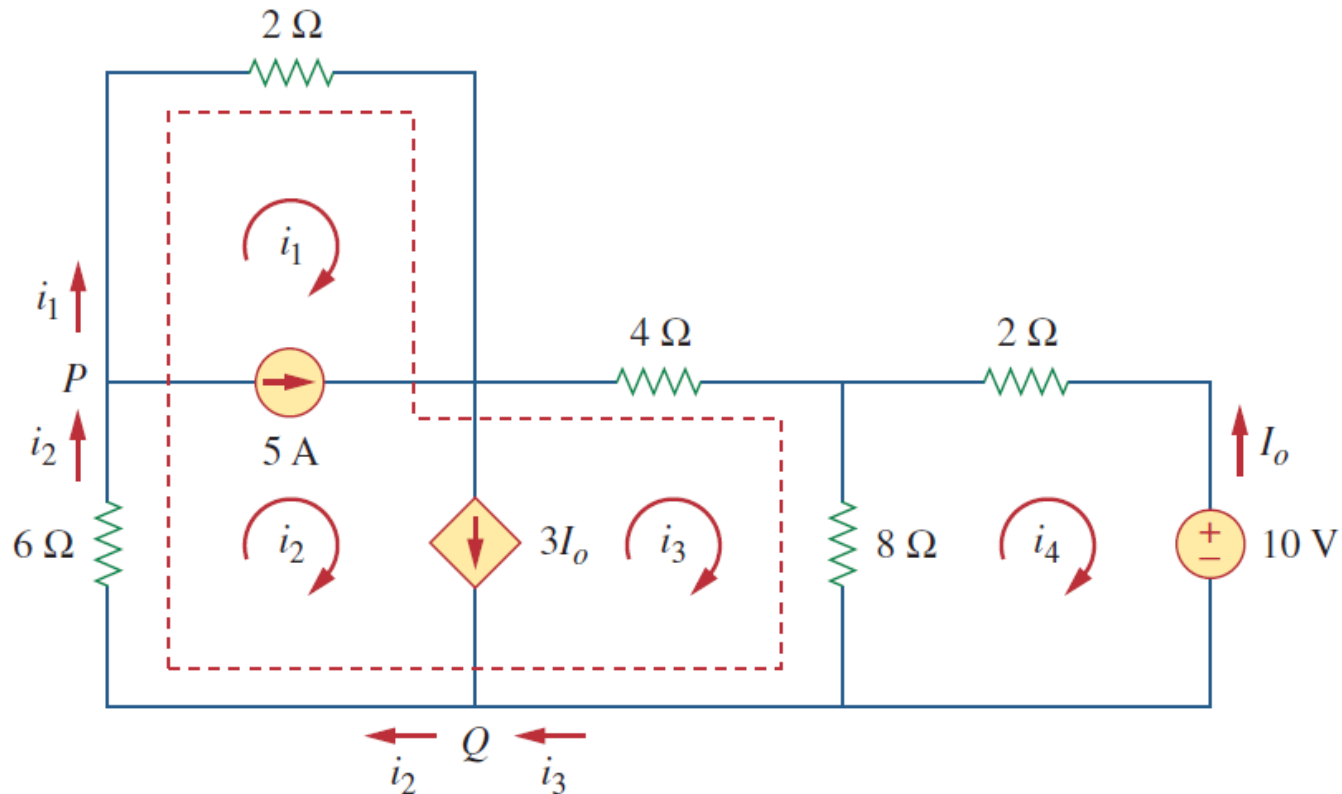
# Example #12

By using mesh analysis find  $i_1$ , to  $i_4$  in the following circuit



**Answer**  $i_1 = -7.5 \text{ A}$     $i_2 = -2.5 \text{ A}$     $i_3 = 3.93 \text{ A}$     $i_4 = 2.143 \text{ A}$

