

BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING

Direct Current Circuits : Circuits Theorems

Ismail Mohd Khairuddin , Zulkifil Md Yusof
Faculty of Manufacturing Engineering
Universiti Malaysia Pahang

Direct Current Circuit (DC)- Circuit Theorems

BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING




Faculty of Manufacturing

Universiti Malaysia Pahang
Kampus Pekan, Pahang Darul Makmur
Tel: +609-424 5800
Fax: +609-4245888

Contents:

- Outcomes
- Superposition
- Source Transformation
- Thevenin's Theorem
- Norton's Theorem
- Maximum Power Transfer

Outcomes

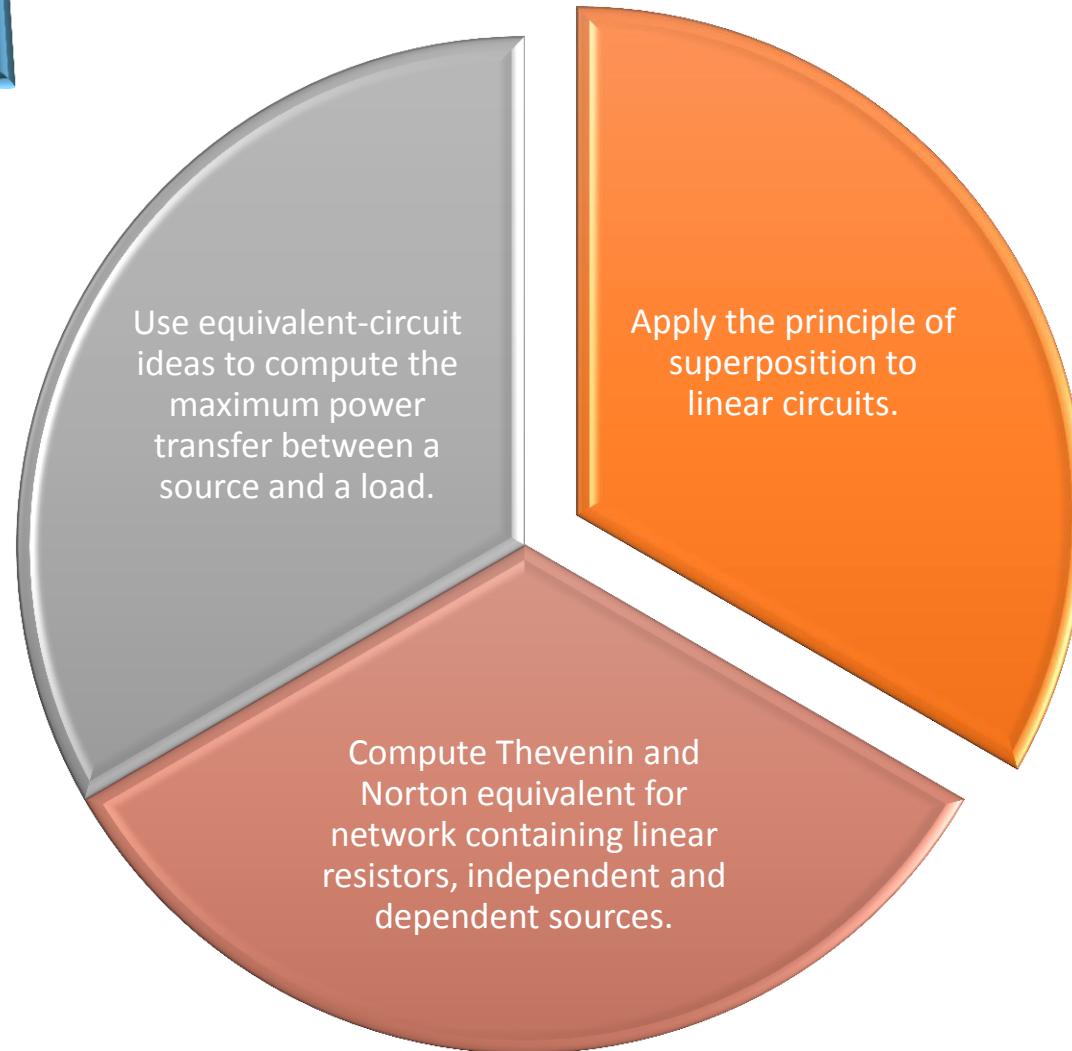


- The **superposition principle** states that the voltage across (or current through) an element in a linear circuit is the **algebraic sum** of the voltage across (or current through) that element due to each **independent source** acting alone.
- To apply the principle, two things should keep in mind:
 - Consider **only one independent source at a time** while all other independent sources are **turned off**. This implies that replacing every **voltage source by 0 V (or short circuit)** and every **current source by 0 A (or an open circuit)**.
 - Dependent sources are left intact because they are **controlled** by circuit variables.



Steps to apply superposition principle:


- i. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using the techniques previously covered.
- ii. Repeat step 1 for each of the other independent sources.
- iii. Find the total contribution by adding algebraically all the contributions due to the independent sources.

 **Disadvantage:** may involve more work but help reduce a complex circuit to simpler circuits.



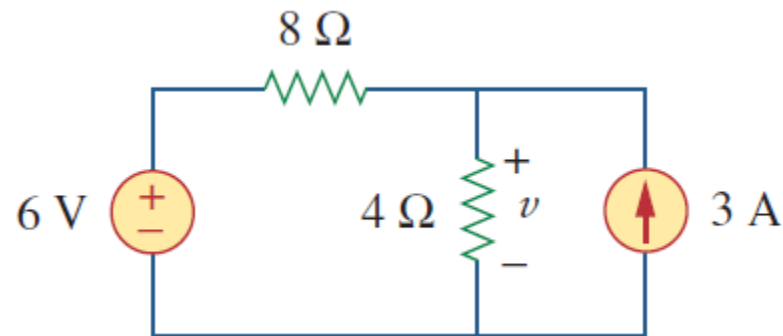Example #1

Use the superposition principle to find v , in the circuit given



Solution


Since there are two sources, let

$$v = v_1 + v_2 \quad \text{where} \quad \begin{aligned} v_1 &= \text{due to the 6 V voltage source} \\ v_2 &= \text{due to the 3 A current source} \end{aligned}$$



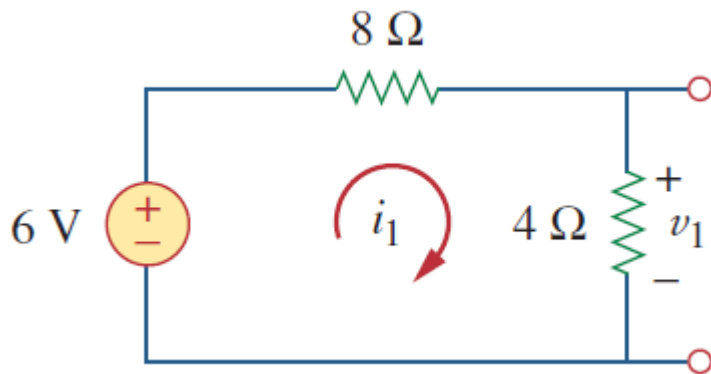Example #1

To obtain v_1 set the **current source to zero (open circuit)**



Applying KVL to the loop

$$-6 + 12i_1 = 0$$

$$i_1 = 0.5 \text{ A}$$


Thus, give the value $v_1 = 4i_1 = 2 \text{ V}$

$$v_1 = \left(\frac{4}{4+8} \right) 6 = 2 \text{ V}$$



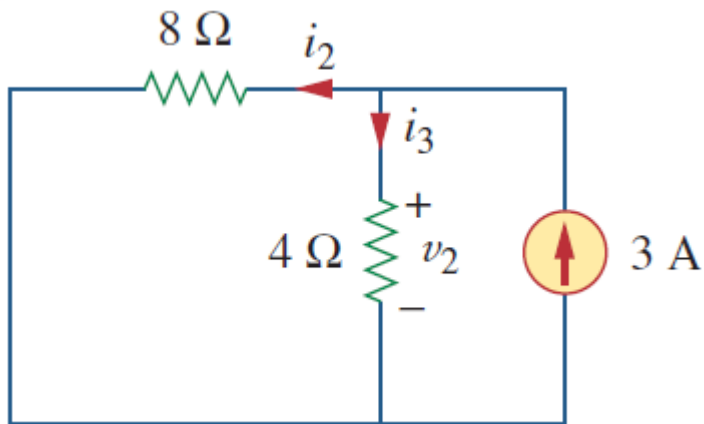Example #1

To obtain v_2 set the **voltage source to zero (short circuit)**



By using current division

$$i_3 = \left(\frac{8}{4 + 8} \right) 3 = 2 \text{ A}$$


$$\text{Hence, } v_2 = 4i_3 = 8 \text{ V}$$

$$\text{Thus, } v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$



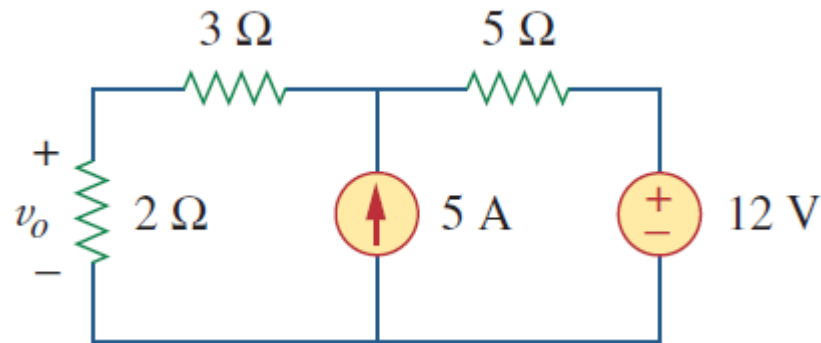Example #2

By using the superposition principle find v_o , in the circuit given




Answer

$$v_o = 7.4 \text{ V}$$



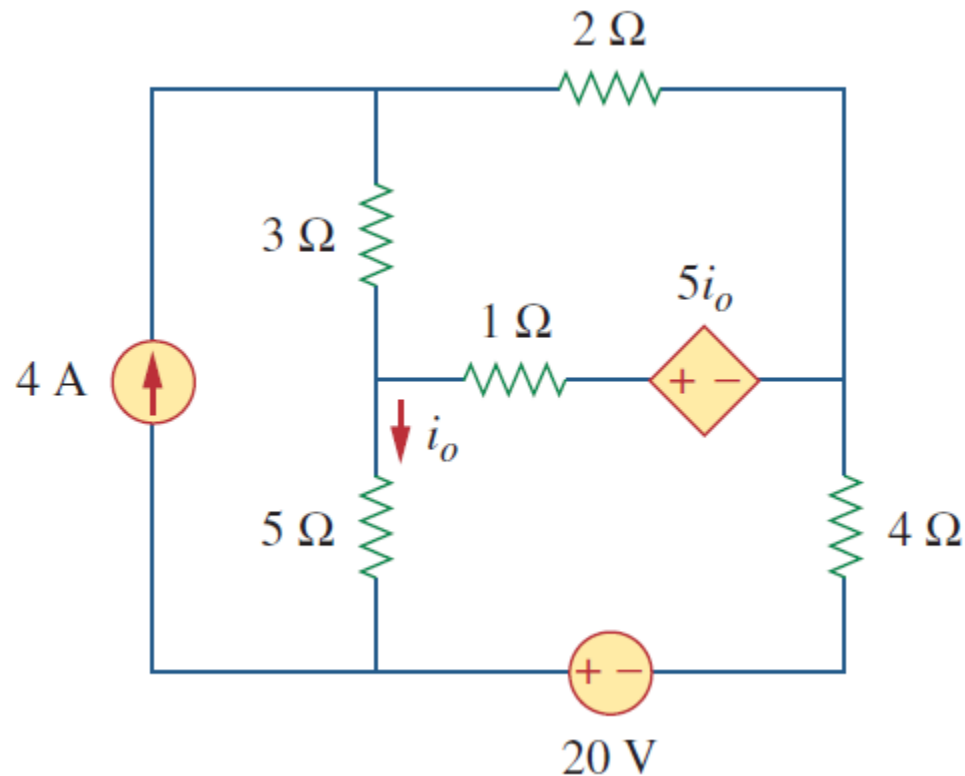Example #3

Find i_o , in the circuit given using the superposition principle



Example #3

Solution

Since the circuit involves a dependent source, which must be left intact

$$i_o = i_o' + i_o'' \quad \text{where} \quad \begin{aligned} i_o' &= \text{due to the 4 A current source} \\ i_o'' &= \text{due to the 20 V voltage source} \end{aligned}$$

To obtain i_o' set the **voltage source to zero (short circuit)**



Example #3

Apply mesh analysis to the loop

For mesh/loop 1

$$i_1 = 4 \text{ A}$$

For mesh/loop 2


$$-3i_1 + 6i_2 - i_3 - 5i_o' = 0$$

$$6i_2 - i_3 - 5i_o' = 12 \text{ A}$$

For mesh/loop 3

$$-5i_1 - i_2 + 10i_3 + 5i_o' = 0$$

$$-i_2 + 10i_3 + 5i_o' = 20 \text{ A}$$

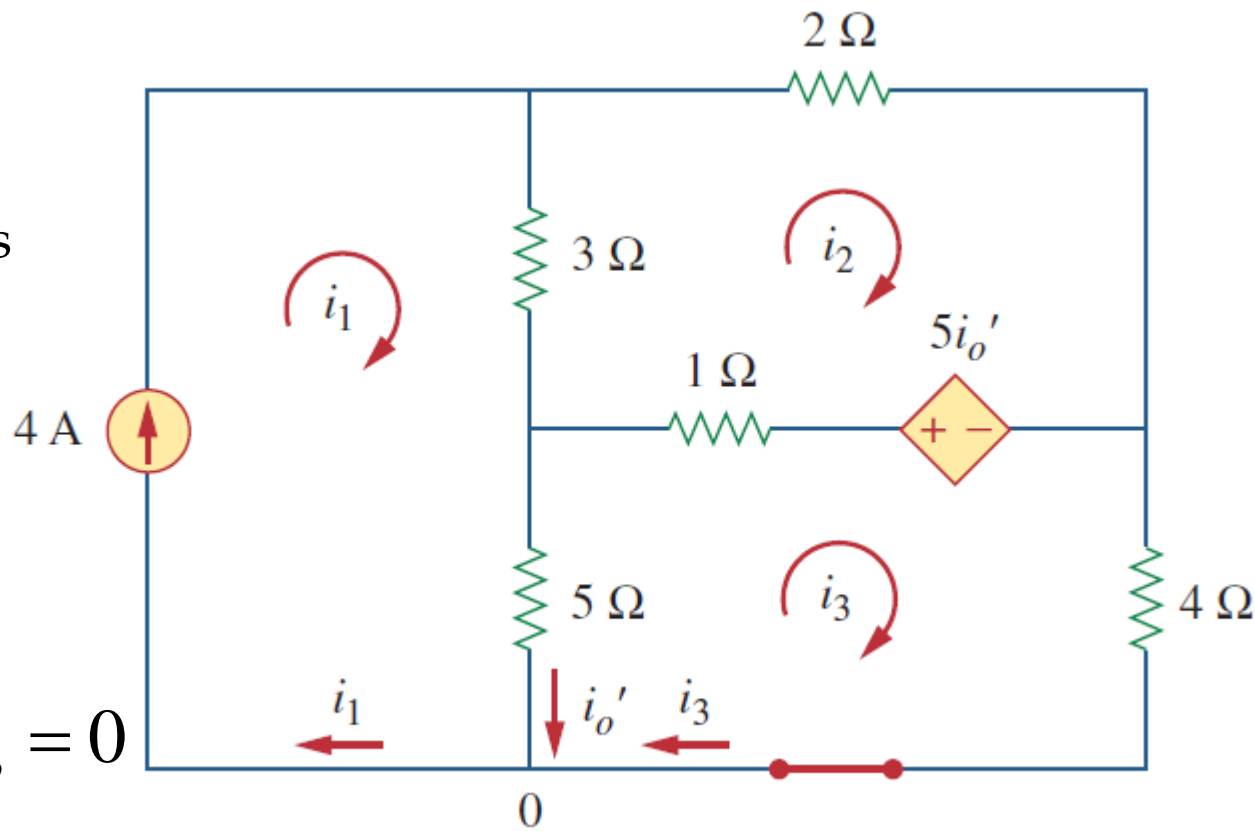

KCL at node 0

$$i_3 = i_1 - i_o' = 4 - i_o'$$



Example #3

Then, in matrix form

$$\begin{bmatrix} 6 & -1 & -5 \\ -1 & 10 & 5 \\ 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_2 \\ i_3 \\ i_0' \end{bmatrix} = \begin{bmatrix} 12 \\ 20 \\ 4 \end{bmatrix}$$

By using Cramer's rule

$$i_0' = \frac{\Delta_1}{\Delta} = \frac{104}{34} = 3.0588 \text{ A}$$

To obtain i_0'' set the **current source to zero (open circuit)**



Example #3

Apply mesh analysis to the loop


Mesh/loop 4

$$6i_4 - i_5 - 5i_o'' = 0$$

Mesh/loop 5

$$-i_4 + 10i_5 - 20 + 5i_o'' = 0$$

and $i_5 = -i_o''$

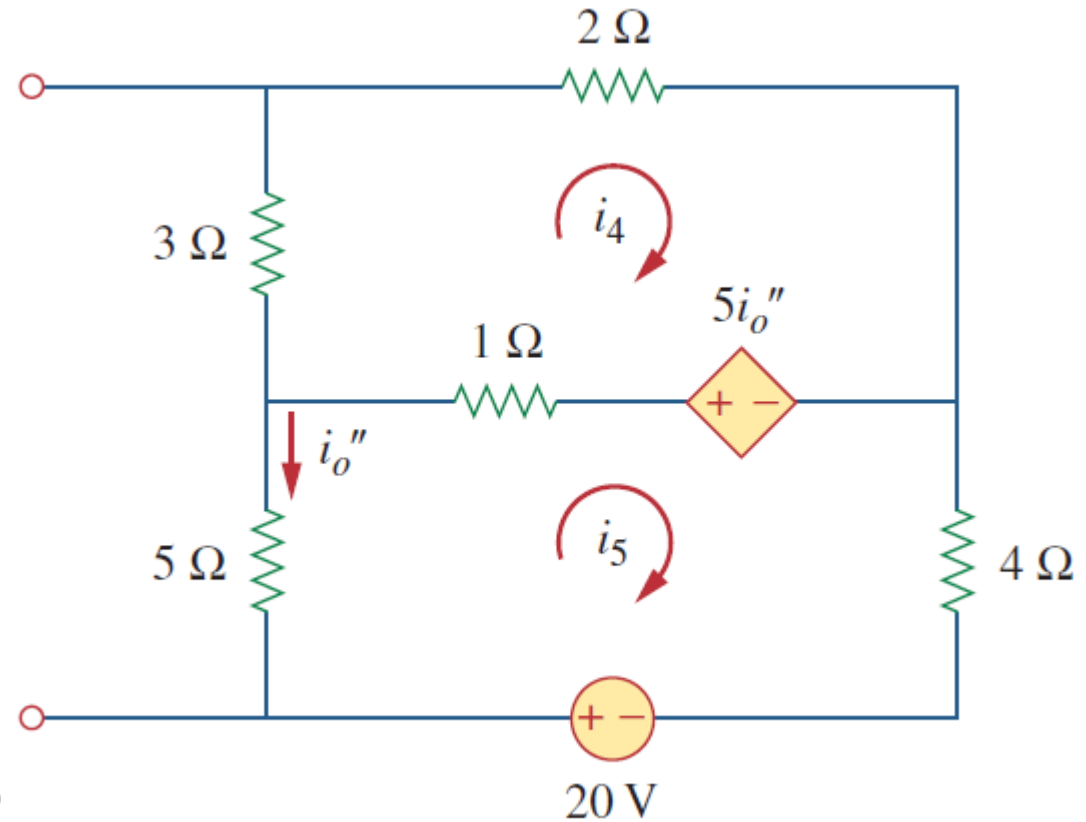

$$6i_4 - 4i_o'' = 0$$

$$i_4 + 5i_o'' = -20$$

Example #3

Then, in matrix form

$$\begin{bmatrix} 6 & -4 \\ 1 & 5 \end{bmatrix} \begin{bmatrix} i_2 \\ i_0'' \end{bmatrix} = \begin{bmatrix} 0 \\ -20 \end{bmatrix}$$

By using Cramer's rule

$$i_0'' = \frac{\Delta_1}{\Delta} = \frac{-120}{34} = -3.5294 \text{ A}$$


Thus,

$$i_o = i_o' + i_o'' = 3.0588 - 3.5294 = -0.4706 \text{ A}$$



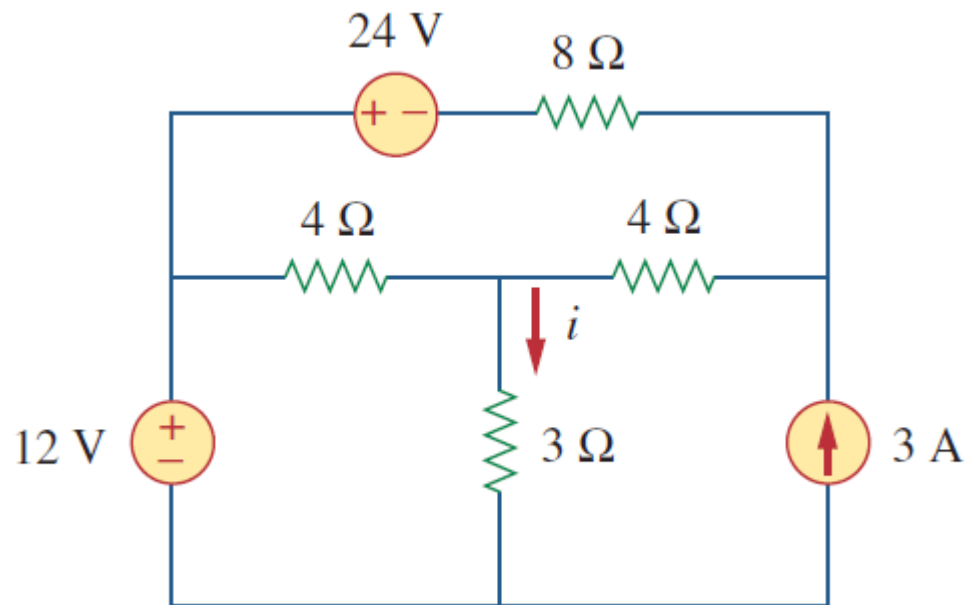Example #4

For the circuit given use the superposition principle to find i




Answer

$$i = 2 \text{ A}$$



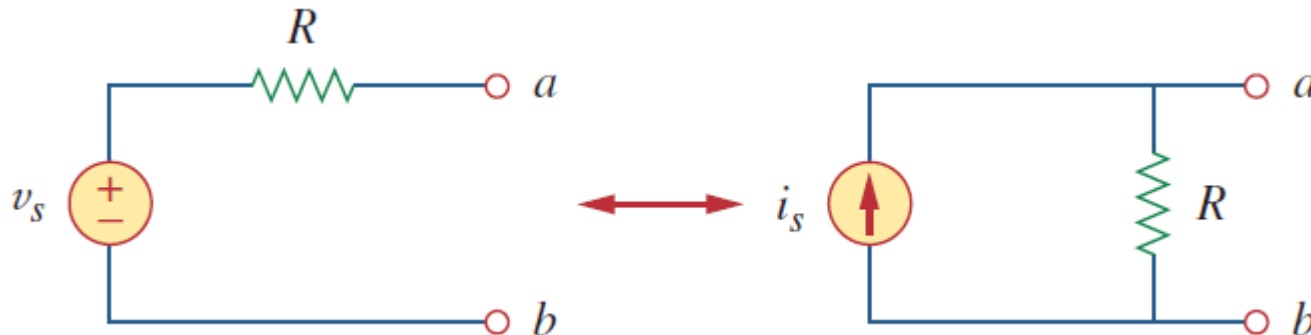- Another tool for simplifying circuit.
- Basic to these tools is the concept of equivalence.
- A **source transformation** is the process of replacing a voltage source v_s in **series** with a resistor R by a current source i_s in **parallel** with a resistor R , or vice versa.




- Since the circuit are equivalent, there have the same voltage-current relation at terminals $a - b$.
- If the sources are turned off, the equivalent resistance at terminals $a - b$ in both circuits is R .

$$v_s = i_s R$$


$$i_s = \frac{v_s}{R}$$

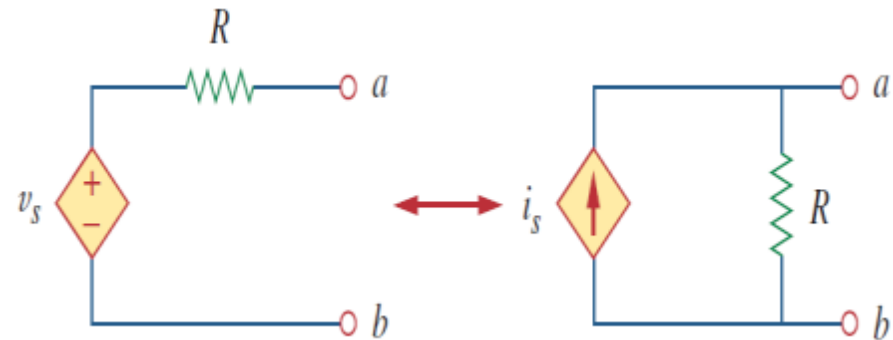- Source transformation also applies to dependent sources, provided we carefully handle the dependent variable.



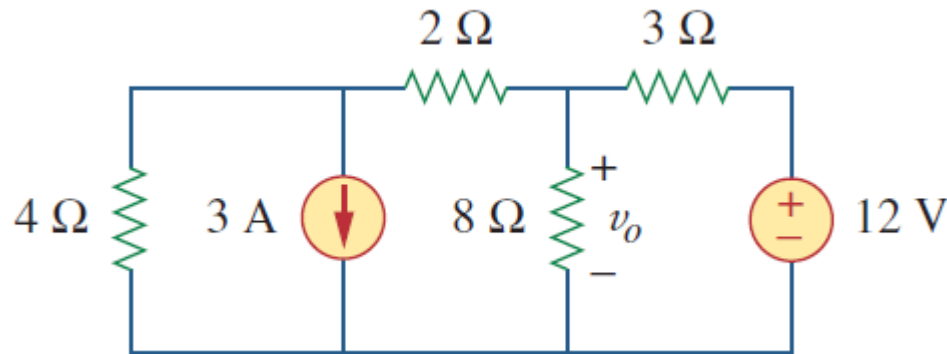Example #5

Use source transformation to find v_o , in the circuit given



Solution


First transform the current and voltage sources to obtain the circuit

$$v_s = 4 \times 3 = 12 \text{ V}$$


$$i_s = \frac{12}{3} = 4 \text{ A}$$



Example #5

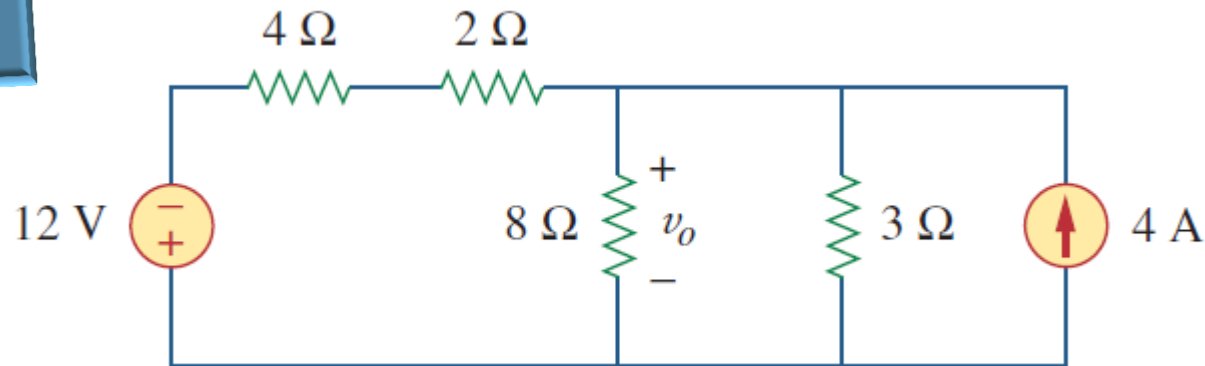

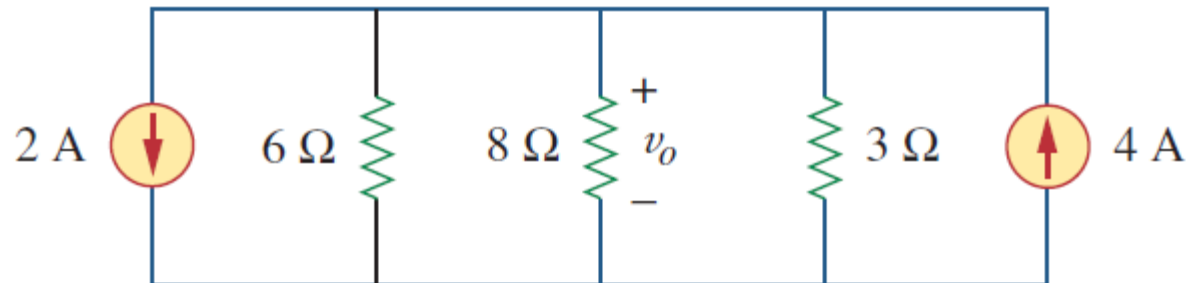
Combining the 4 Ω and 2 Ω in series and transforming 12 V voltage source



Combining the 2 A and 4 A and repeating the source transformation



Example #5

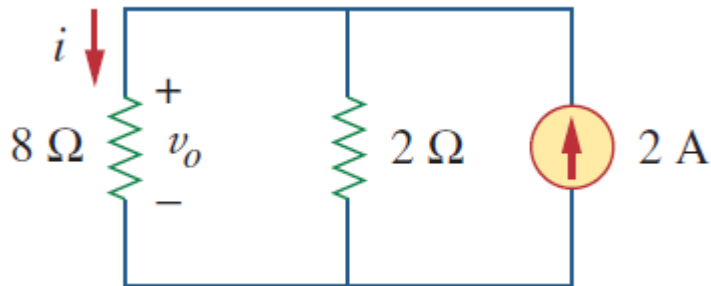

By using current divider


$$i = \left(\frac{2}{10} \right) 2 = 0.4\ \text{A}$$

and $v_o = 8i = 8(0.4) = 3.2\ \text{V}$



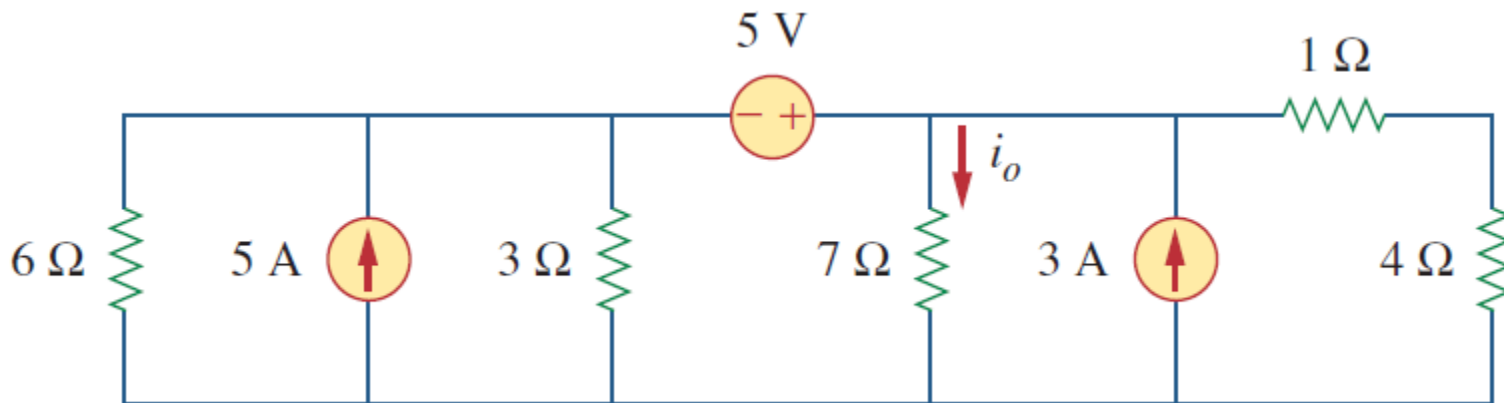Example #6

Use source transformation to find i_o , in the circuit given




Answer

$$i_o = 1.78 \text{ A}$$



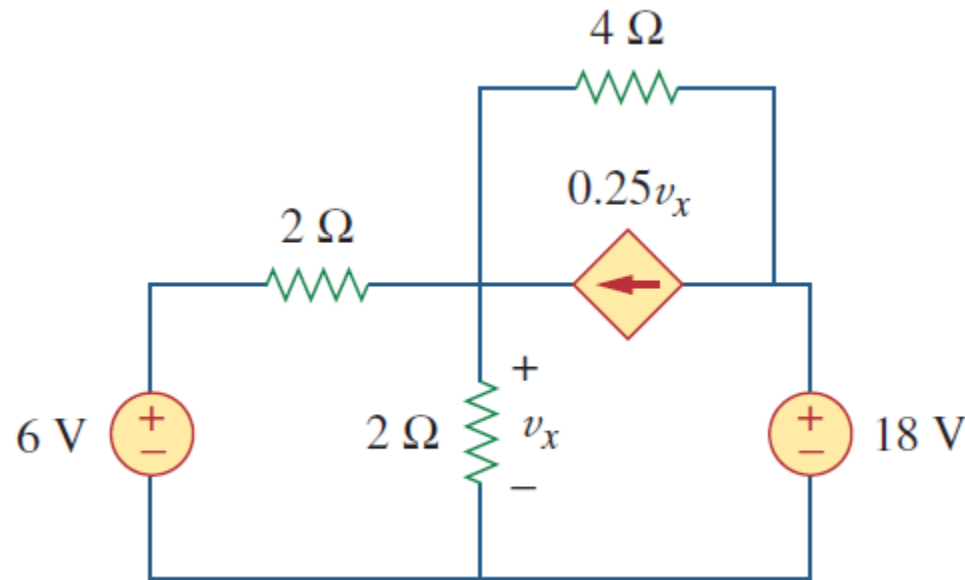Example #7

Find v_x in the circuit given using source transformation




Solution

First transform the dependent current source and voltage sources

$$v_s = 4 \times 0.25 = 1 \text{ V}$$


$$i_s = \frac{6}{2} = 3 \text{ A}$$

Example #7

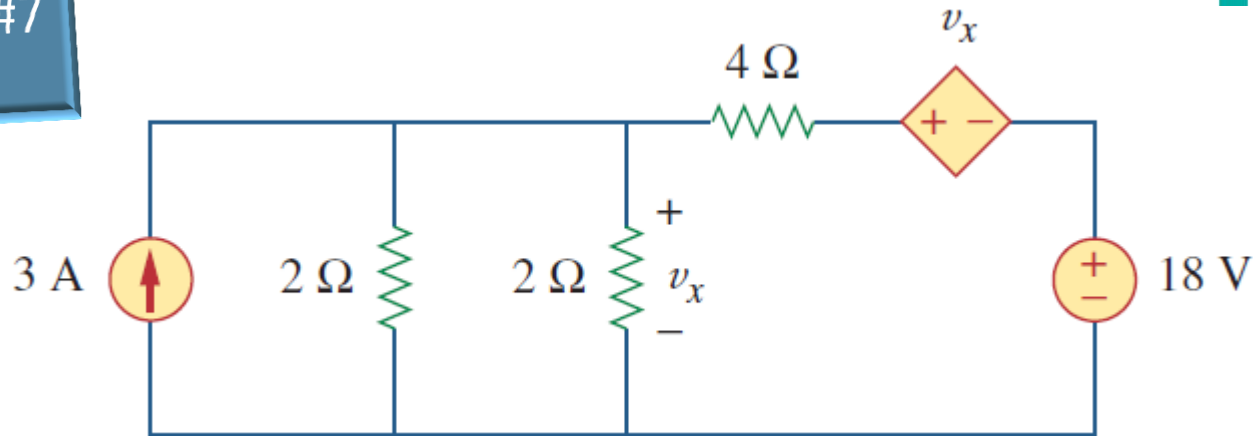



since the 2Ω and 2Ω in parallel $2 \square 2 = \frac{2 \times 2}{2 + 2} = 1 \Omega$

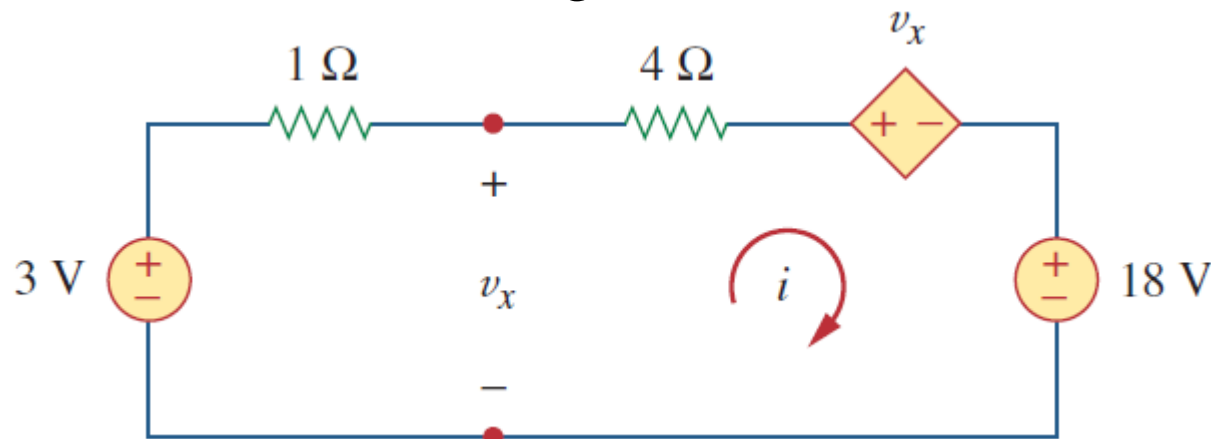Transform the 2Ω and $3A$ will give $v = 3 \times 2 = 6 V$



Example #7

Applying KVL around the loop

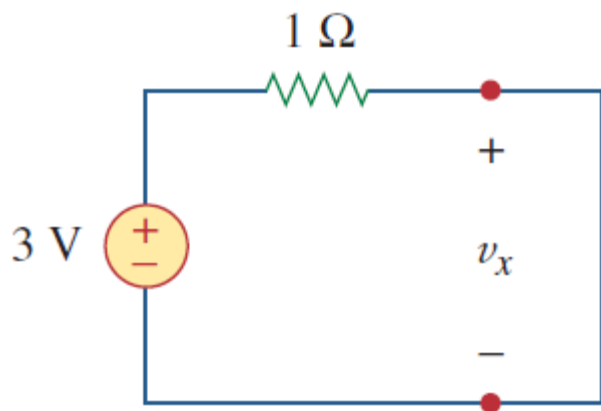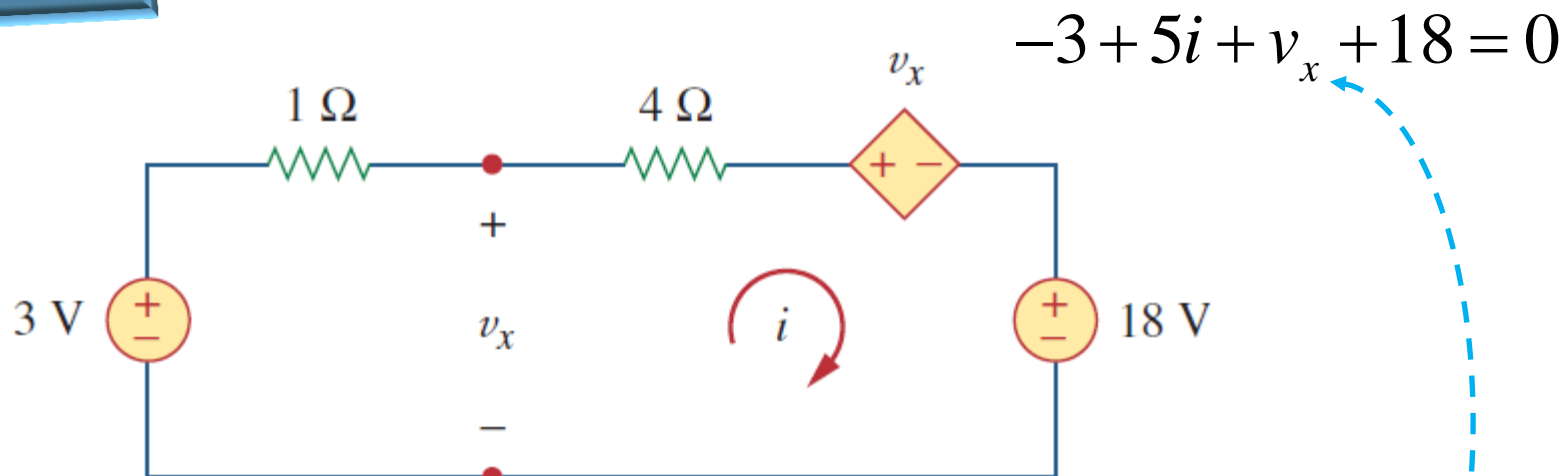

Applying KVL to the circuit

$$-3 + i + v_x = 0 \quad \Rightarrow v_x = 3 - i$$

$$15 + 5i + 3 - i = 0 \quad \Rightarrow i = 4.5 \text{ A}$$

Thus $v_x = 3 + 4.5 = 7.5 \text{ V}$

Thevenin's Theorem

▣ Provides a technique by which the fixed part of the circuit replaced by the equivalent circuit.


▣ **Thevenin's theorem**: a linear 2-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{TH} in **series** with resistor R_{TH} .

V_{TH} **open-circuit voltage** at terminal


R_{TH} input or **equivalent resistance** at the terminals when the **independent source are turned off**



Thevenin's Theorem

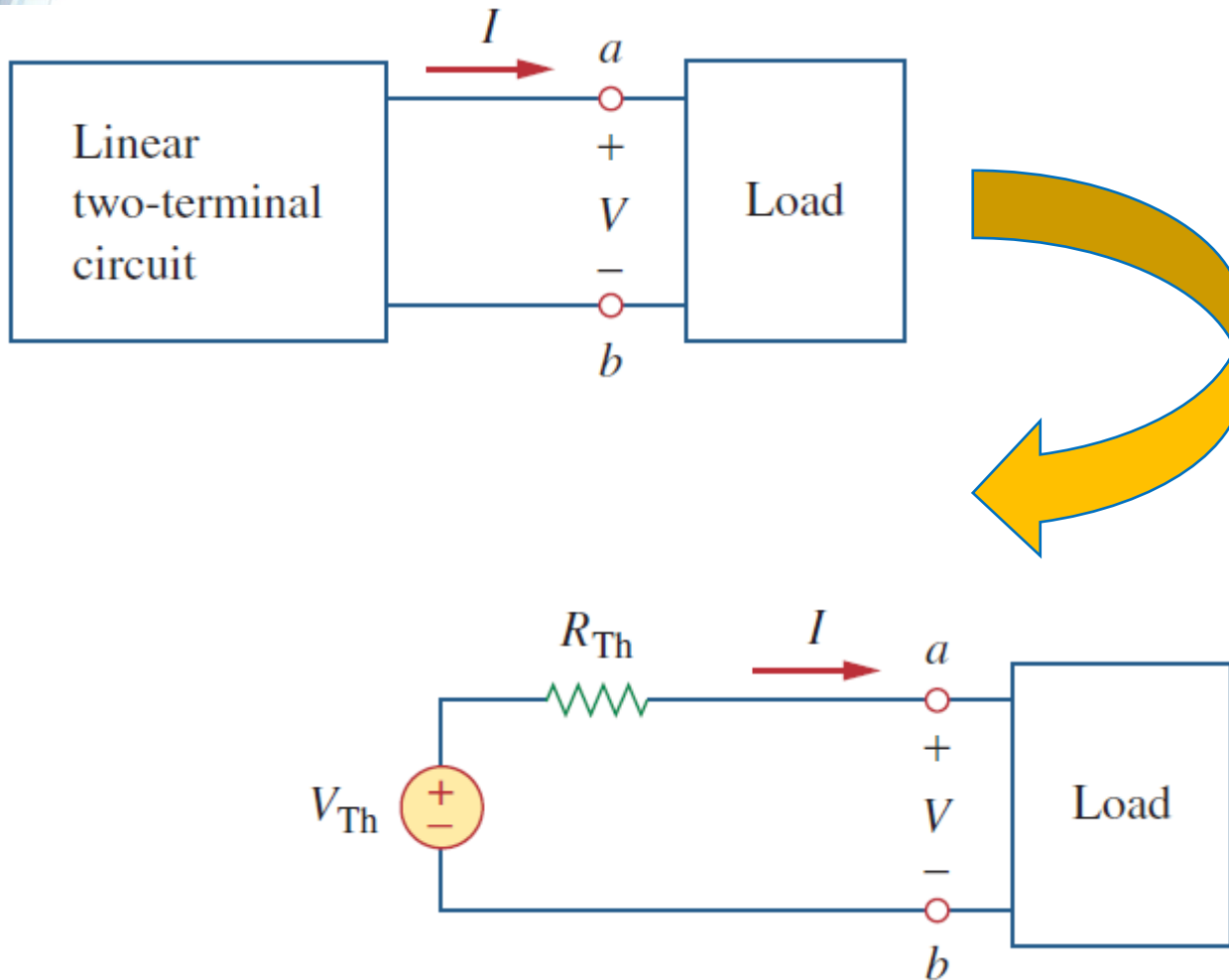

Thevenin's Theorem

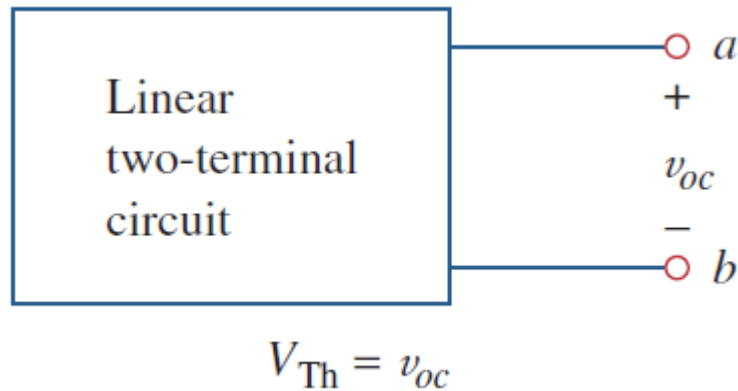


- By removing the load, there is no **current flows**, so that the **open-circuit voltage across** to terminal $a - b$
- The open-circuit voltage is **equal** to the V_{TH}

$$V_{TH} = v_{oc}$$

- With the load disconnected and we turn off all the independent sources the input/equivalent resistance must be equal to the R_{TH}

$$R_{TH} = R_{in}$$

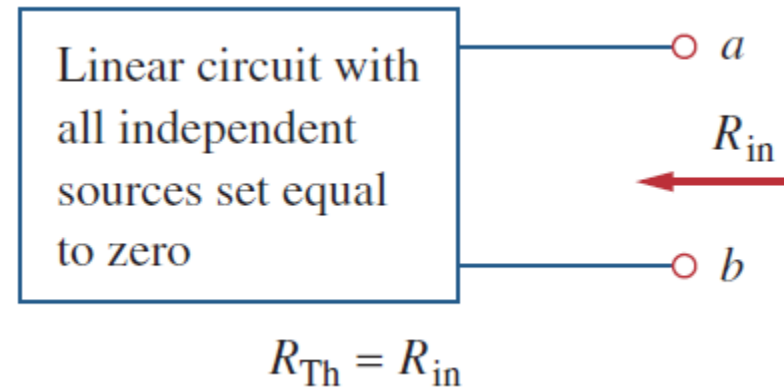


Thevenin's Theorem

■ To find the Thevenin resistance, R_{TH} we need to consider 2 cases.

■ Case 1

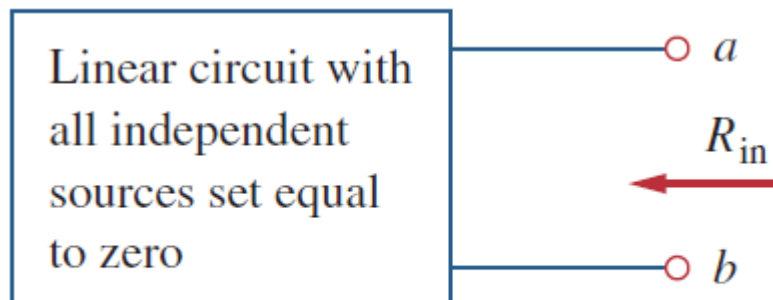If the network has no dependent sources, we turn off all independent sources. R_{TH} is the input resistance of the network looking between terminals a and b





$$R_{Th} = R_{in}$$

$$R_{Th} = R_{in}$$

Thevenin's Theorem

Case 2

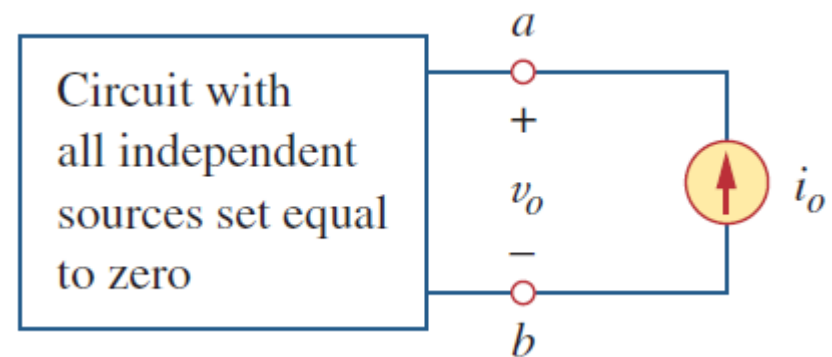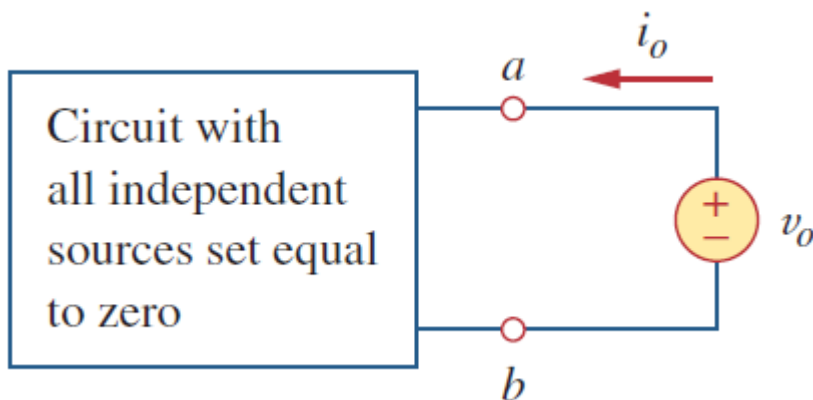If the network has dependent sources, we turn off all independent sources and need to apply v_o at terminal a and b and determine the resulting i_o




$$R_{Th} = \frac{v_o}{i_o}$$



Thevenin's Theorem

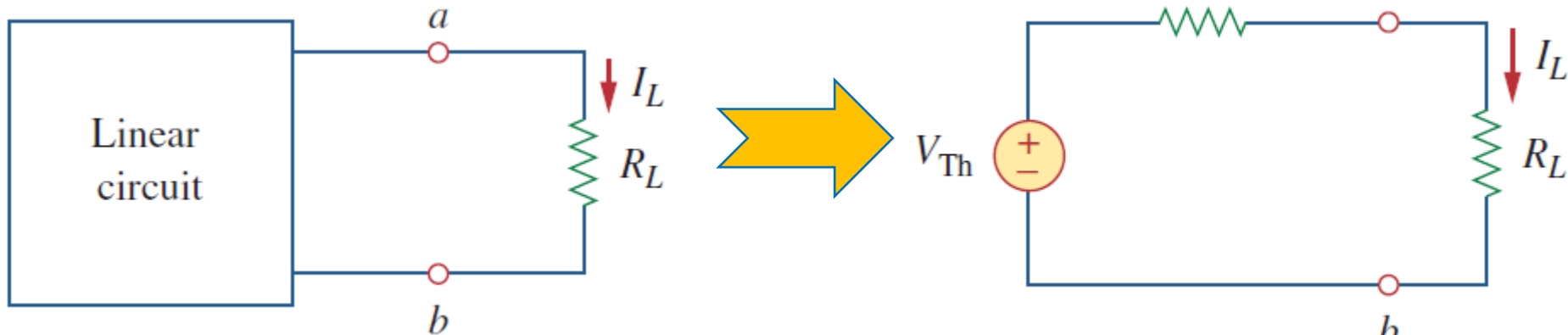- A linear circuit with a variable load can be replaced by the Thevenin equivalent, exclusive of the load.
- The equivalent network behaves the same way externally as the original circuit



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \left(\frac{R_L}{R_{Th} + R_L} \right) V_{Th}$$




Thevenin's Theorem

- A linear circuit with a variable load can be replaced by the Thevenin equivalent, exclusive of the load.
- The equivalent network behaves the same way externally as the original circuit



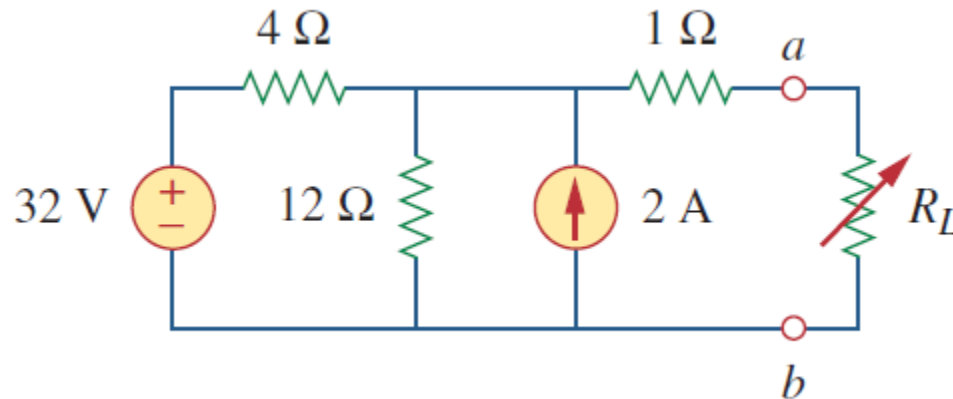Example #8

Find the Thevenin equivalent circuit of the circuit shown in following figure to the left of the terminal $a - b$. then find the current through $R_L = 6, 16$ and 36Ω




Solution


To find R_{Th} turn off the voltage source (short circuit) and current source (open circuit).



Example #8

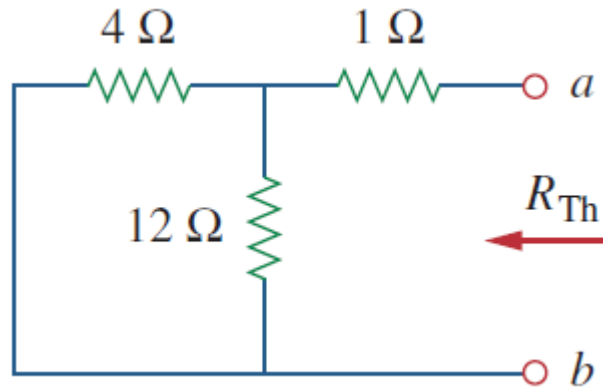
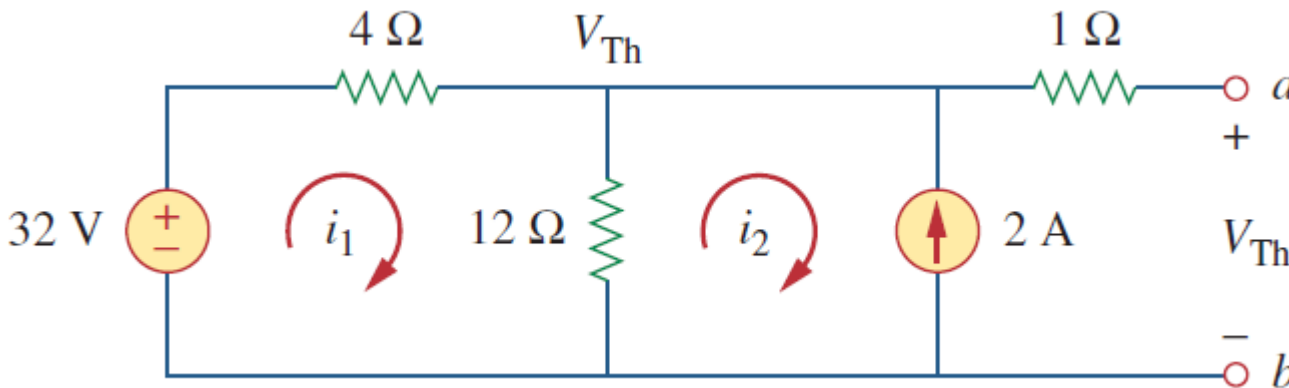
$$R_{Th} = (4 \parallel 12) + 1 = \left(\frac{48}{16} \right) + 1 = 4 \Omega$$



To find V_{Th} apply mesh analysis to the two loops



Example #8

$$\text{Loop 1} \quad -32 + 4i_1 + 12(i_1 - i_2) = 0$$

$$\text{Loop 2} \quad i_2 = -2 \text{ A}$$

$$\text{Solving for } i_1 \quad i_1 = 0.5 \text{ A}$$

Thus

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$

Then the current through R_L


$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

when $R_L = 6$ when $R_L = 16$ when $R_L = 36$

$$I_L = 3 \text{ A}$$


$$I_L = 1.5 \text{ A}$$

$$I_L = 0.75 \text{ A}$$

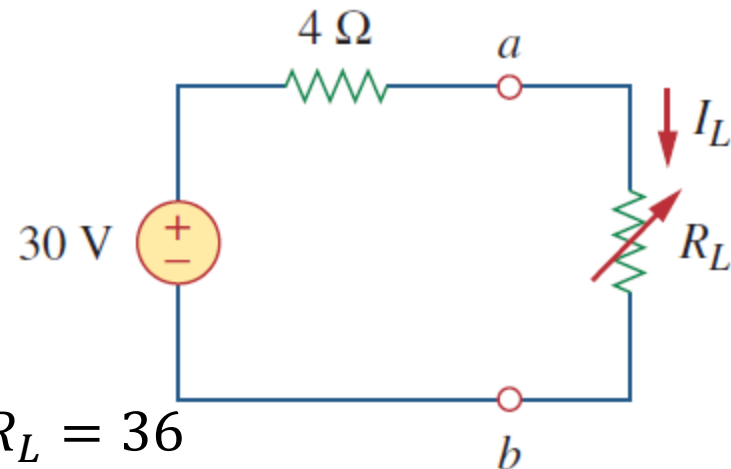

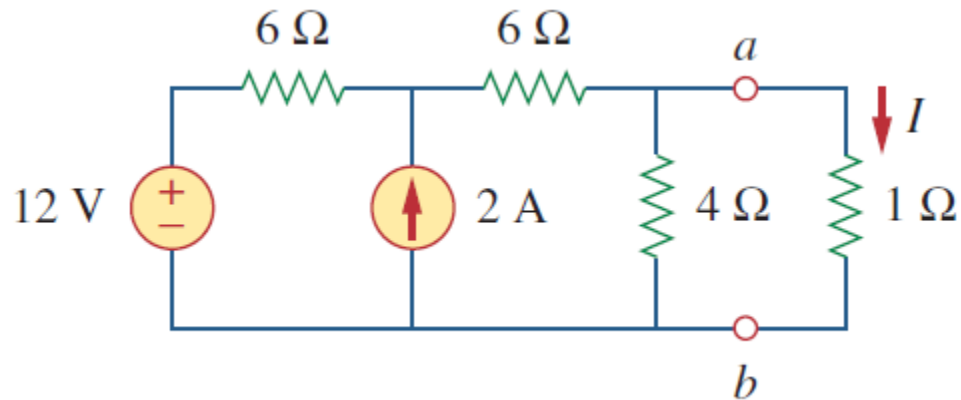Example #9

Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown. Then find I



Answer

$$V_{Th} = 6\text{ V}, \quad R_{Th} = 3\Omega, \quad I = 1.5\text{ A}$$




Norton's Theorem

Norton's theorem: a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in **parallel** with a resistor R_N .


I_N **short-circuit current** through the terminal

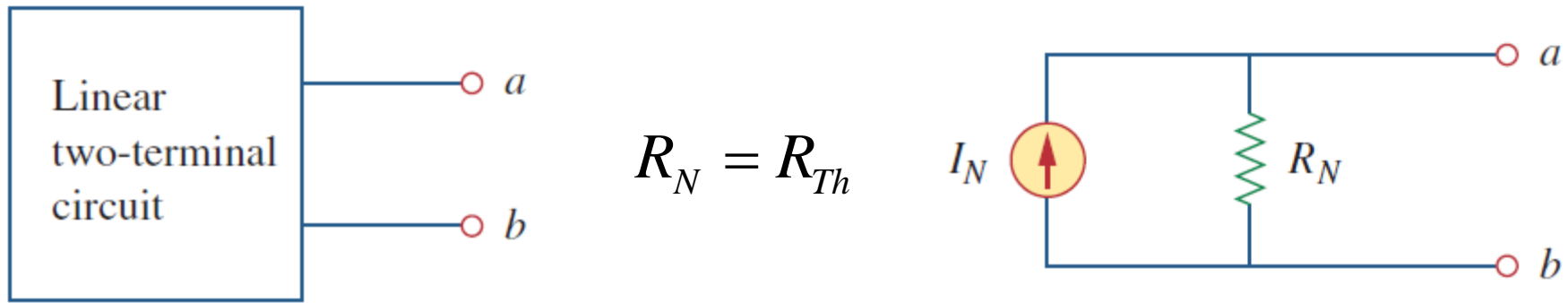R_N input or **equivalent resistance** at the terminals when the **independent source are turned off**



Norton's Theorem

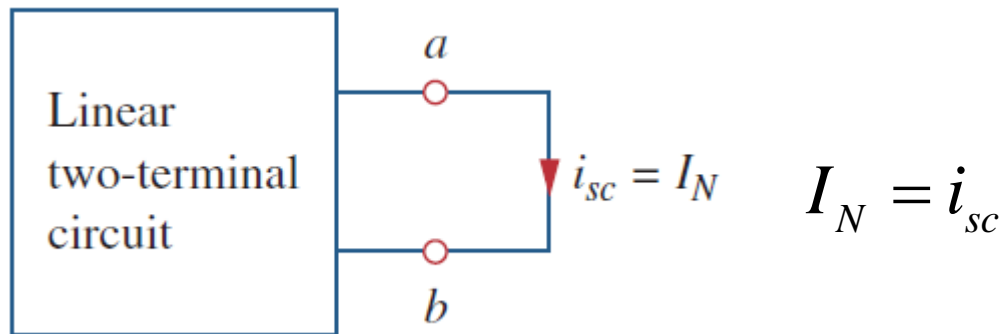- To find the value of I_N we determine the short circuit current following from terminal a to b



Since

$$R_N = R_{Th}$$

Then

$$I_N = \frac{V_{Th}}{R_{Th}}$$



Norton's Theorem

To determine the Thevenin or Norton equivalent circuit requires that we find:

- ❑ The open circuit voltage v_{oc} across terminal a and b .
- ❑ The short circuit current i_{sc} at terminal a and b .
- ❑ The equivalent or input resistance R_{in} at terminal a and b when all independent sources are turned off.

$$V_{Th} = v_{oc}$$


$$I_N = i_{sc}$$

$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$



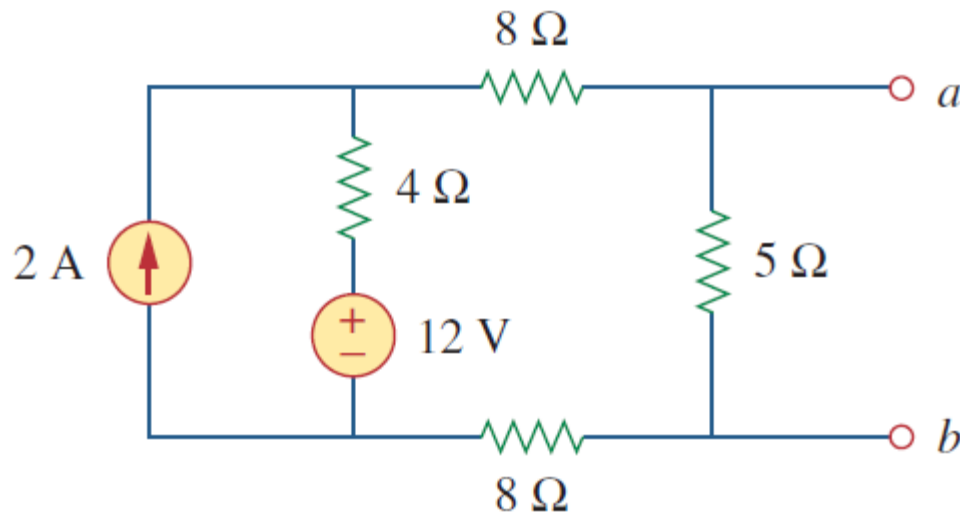Example #10

Find the Norton equivalent circuit of the circuit in figure shown at terminals $a - b$




Solution

We find R_N in the same way we find R_{Th} in the Thevenin equivalent circuit. Set the independent sources equal to zero.




Example #10

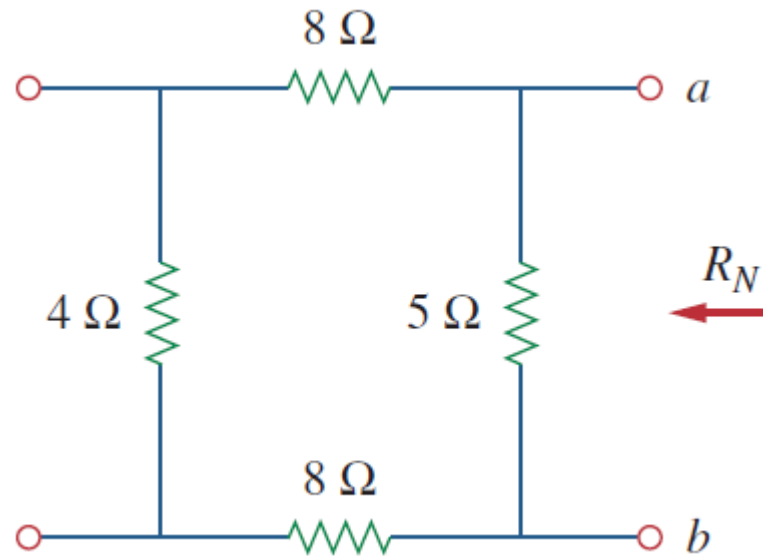

$$R_N = 5 \parallel (8 + 4 + 8)$$

$$R_N = 5 \parallel 20 = 4 \Omega$$

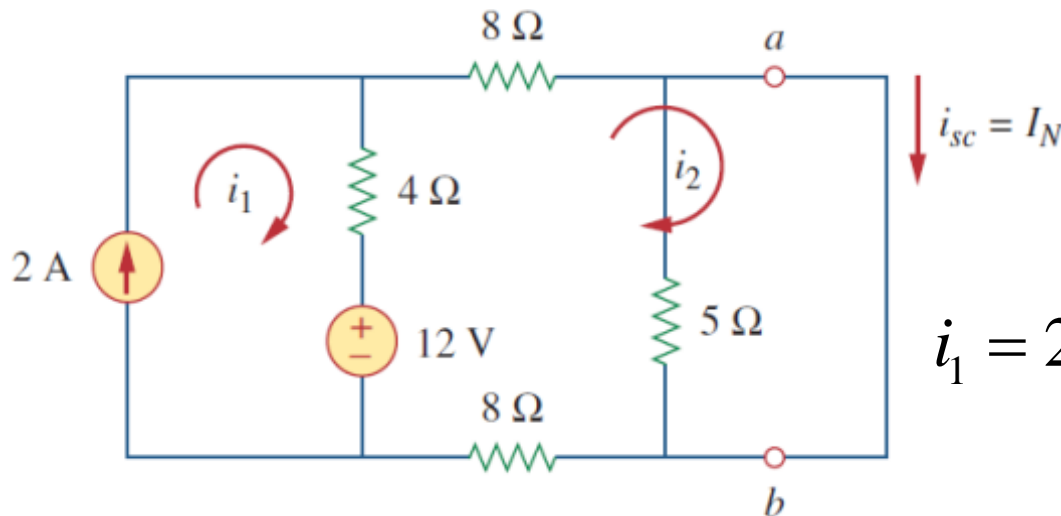To find the value of I_N we short circuit terminals a to b




we ignored the 5Ω resistor because it has been short circuit

$$i_1 = 2 \text{ A} \quad 20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

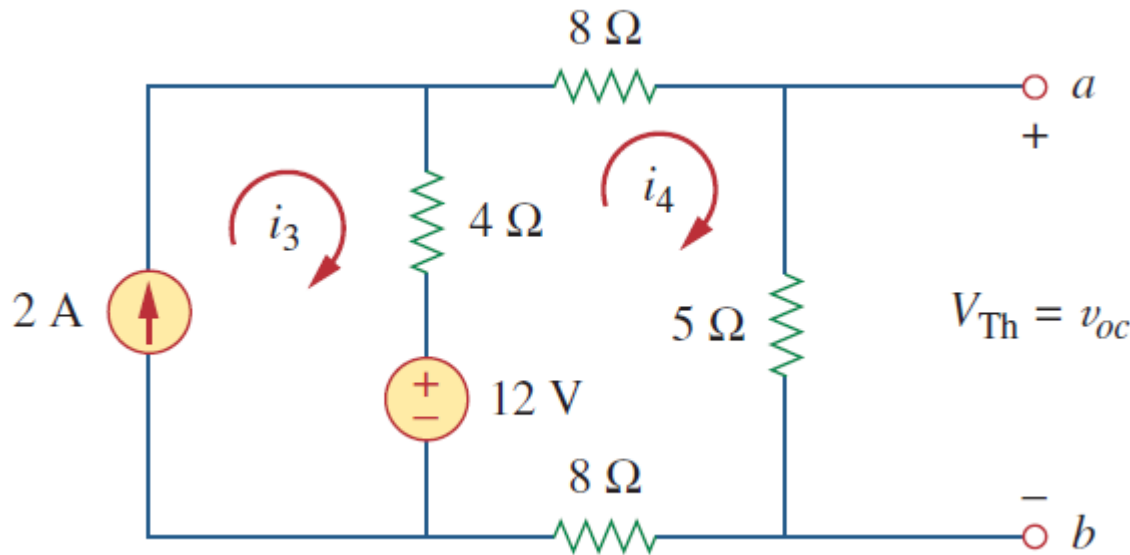Example #10

We obtain V_{Th} as the open circuit voltage across terminal $a - b$



By using mesh analysis

$$i_3 = 2 \text{ A}$$

$$25i_4 - 4i_3 - 12 = 0$$

$$i_4 = 0.8 \text{ A}$$


$$v_{oc} = V_{Th} = 5i_4 = 4 \text{ V}$$

$$\therefore I_N = \frac{V_{Th}}{R_N} = 1 \text{ A}$$



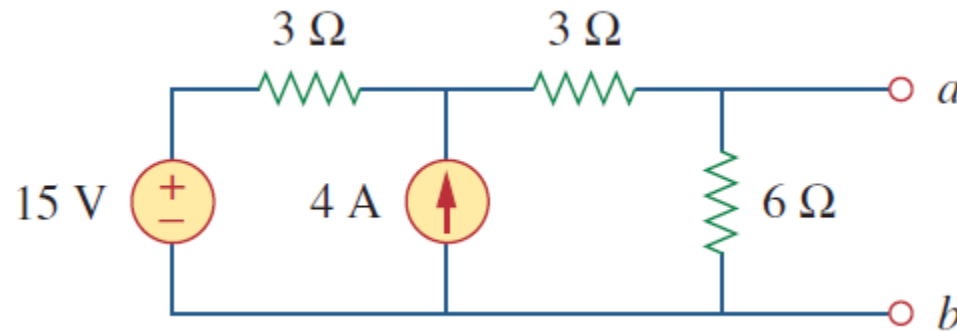Example #11

Find the Norton equivalent circuit of the circuit in figure shown at terminals $a - b$





Answer

$$R_N = 3\Omega, \quad I_N = 4.5\text{ A}$$



Maximum Power Transfer

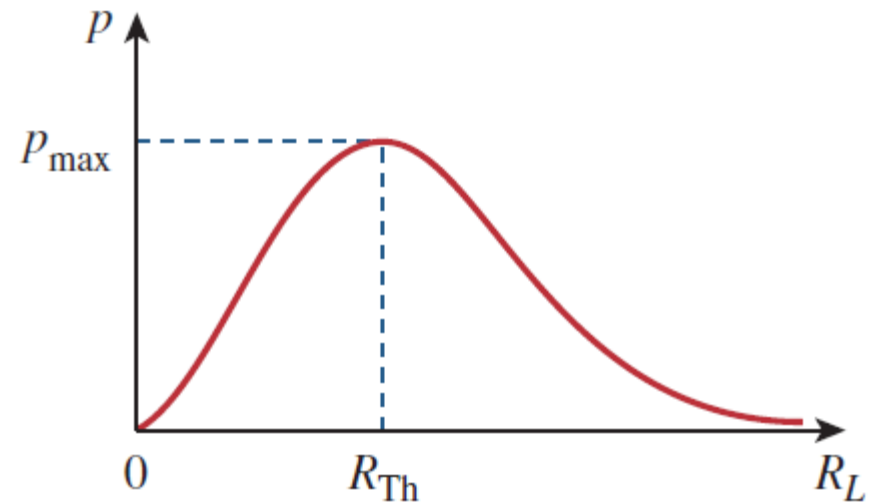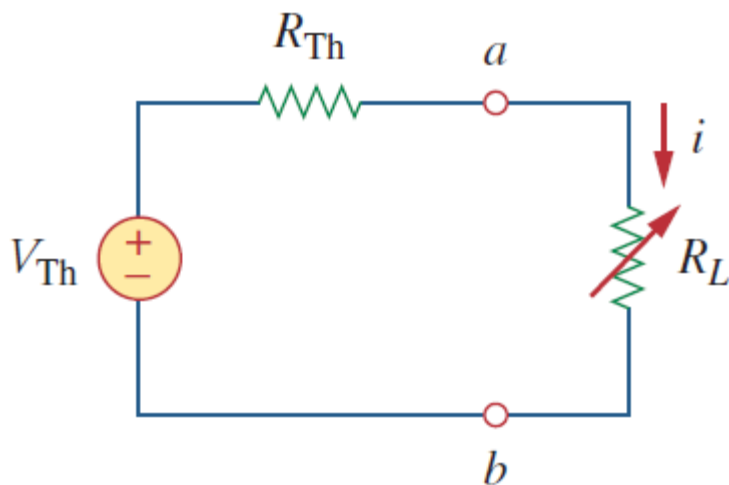- ❑ In many practical situations, a circuit is designed to **provide power to a load**.
- ❑ There are applications in areas such as communications where it is desirable to maximize the power delivered to a load.
- ❑ The Thevenin equivalent is useful in **finding** the maximum power a linear circuit can deliver to a load.



$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$


Maximum Power is transferred to the load when the load resistance equal the Thevenin resistance as seen from the load

$$R_L = R_{Th} \qquad p_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$



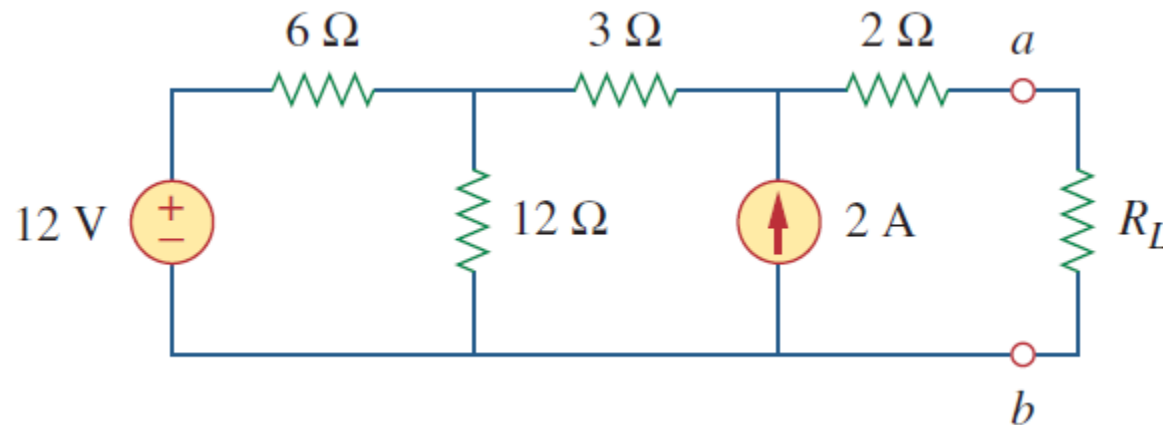Example #12

Find the value of R_L for the maximum power transfer for the circuit shown and give the maximum power transfer.




Solution

We find R_{Th} by set the independent sources equal to zero.




Example #12

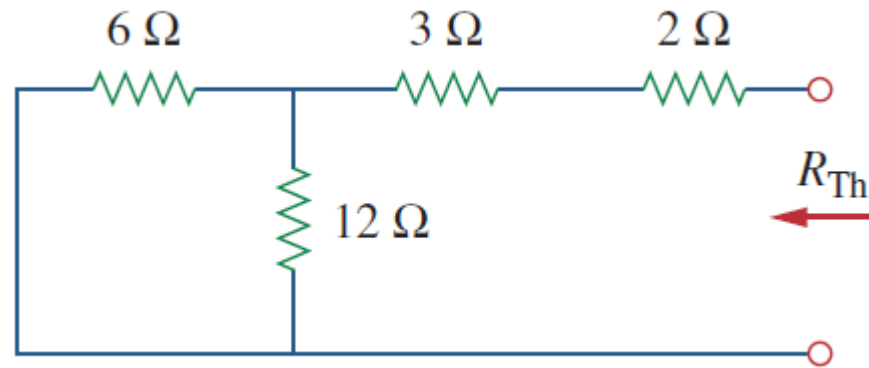

$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{72}{18}$$

$$R_{Th} = 9 \Omega$$

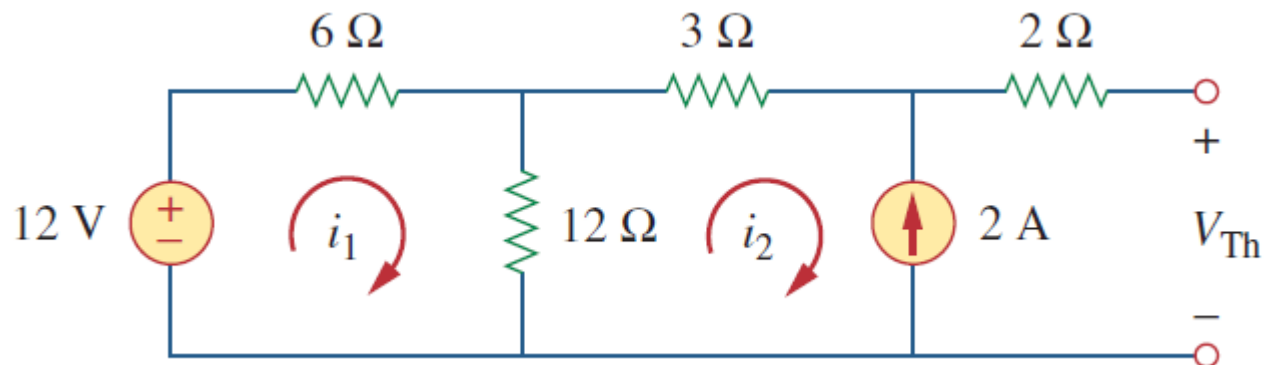

Example #12

By using mesh analysis

$$-12 + 18i_1 - 12i_2 = 0$$

$$i_2 = -2 \text{ A}$$

$$\text{Then } i_1 = -\frac{2}{3} \text{ A}$$

Applying KVL around the outer loop in order to find V_{Th}

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0$$

$$V_{Th} = 22 \text{ V}$$

For maximum power transfer

$$R_L = R_{Th} = 9 \Omega$$

the maximum power transfer

$$P_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{(22)^2}{36} = 13.44 \text{ W}$$

