

BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING

Alternating Current Circuits : Basic Law

Ismail Mohd Khairuddin , Zulkifil Md Yusof
Faculty of Manufacturing Engineering
Universiti Malaysia Pahang

Alternating Current Circuit (AC)-Basic Laws & Circuit Techniques

BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING



Faculty of Manufacturing

Universiti Malaysia Pahang
Kampus Pekan, Pahang Darul Makmur
Tel: +609-424 5800
Fax: +609-4245888

Contents:

- Outcome
- Kirchhoff's Law
- Series Impedances and Voltage Division
- Parallel Impedances and Current Division
- Nodal Analysis
- Mesh Analysis
- Superposition
- Source Transformation
- Thevenin and Norton Equivalent Circuit

Outcomes


Draw the power triangle, and compute the capacitor size required to perform power factor correction on a load.

Convert time-domain sinusoidal voltages and currents to phasor notation, and vice versa; represent circuit using impedance



Learn complex power notation; compute apparent power, real, and reactive power for complex load.

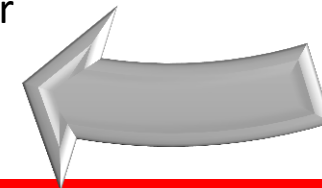Solve steady-state ac circuits, using phasors and complex impedances.



Kirchhoff's Law


- This principles used in dc analysis, are also applicable in the phasor domain.
- The difference is simply the voltages, currents and resistance/inductance/capacitance are converted to phasor and impedance.
- Kirchhoff's current law (KCL) – that the algebraic sum of phasor currents entering a node (or a closed boundary) is zero.
- Kirchhoff's voltage law (KVL) – the algebraic sum of all phasor voltages around a closed path (or loop) is zero.

$$\sum_{n=1}^N \mathbf{I}_n = 0$$

$$\sum_{m=1}^M \mathbf{V}_m = 0$$



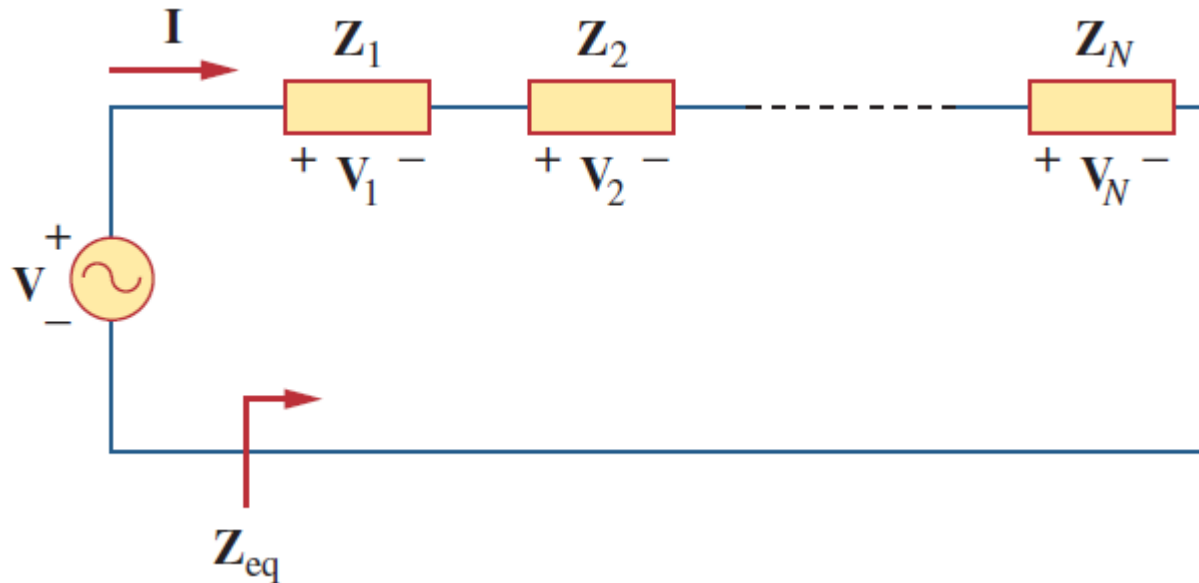- Consider the following figure, the **same current I** flow through the impedance



- Applying **KVL** around the loop




- The equivalent impedance at the input terminals

$$\mathbf{Z}_{eq} = \frac{\mathbf{V}}{\mathbf{I}} = (\mathbf{Z}_1 + \mathbf{Z}_2 + \dots + \mathbf{Z}_N)$$

- Any number of impedances connected in series is the **sum of the individual impedances**.

- If $N = 2$

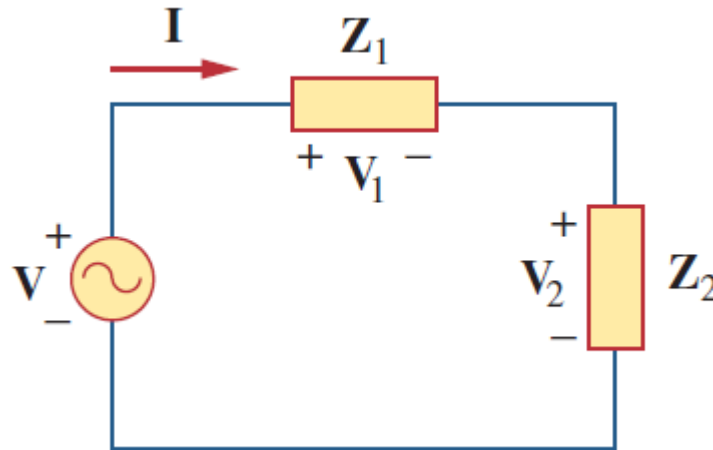

- The current through impedances

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

Since

$$\mathbf{V}_1 = \mathbf{Z}_1 \mathbf{I}$$

$$\mathbf{V}_2 = \mathbf{Z}_2 \mathbf{I}$$

Then

$$\mathbf{V}_1 = \left(\frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \right) \mathbf{V}, \quad \mathbf{V}_2 = \left(\frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \right) \mathbf{V}$$




Principle of **voltage division**.



Parallel Resistors and Current Division

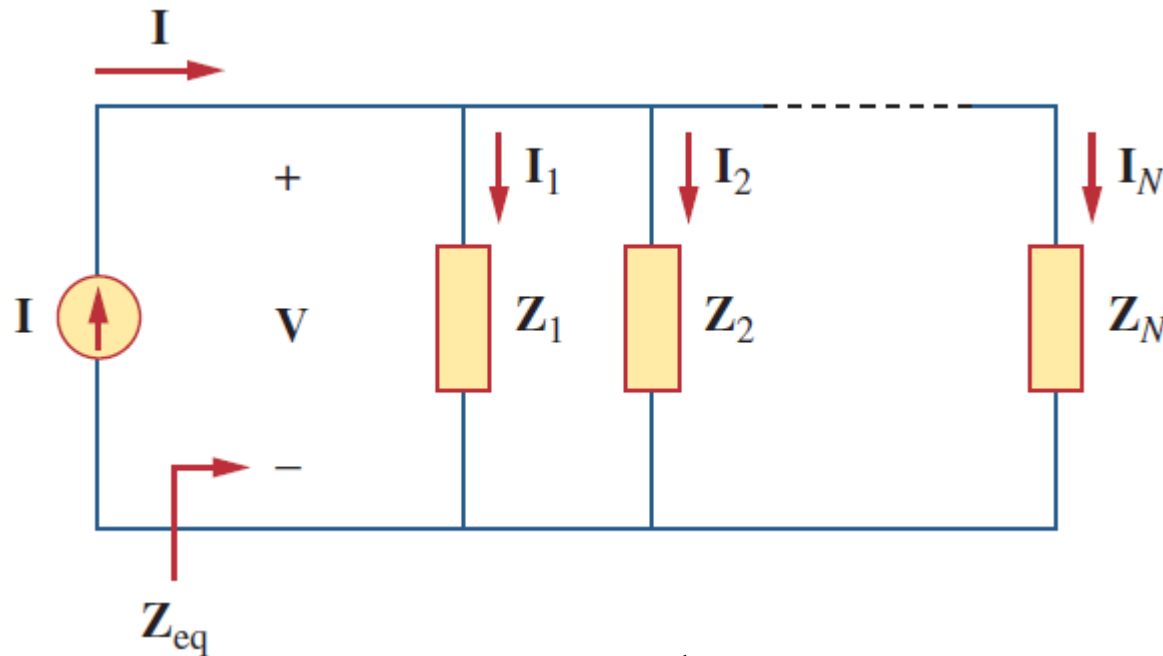- The **voltage across** each **impedance** is the **same**. Applying **KCL** at top node




$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

■ The equivalent impedance

$$\frac{1}{\mathbf{Z}_{eq}} = \frac{1}{\mathbf{V}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_N}$$

■ When $N = 2$

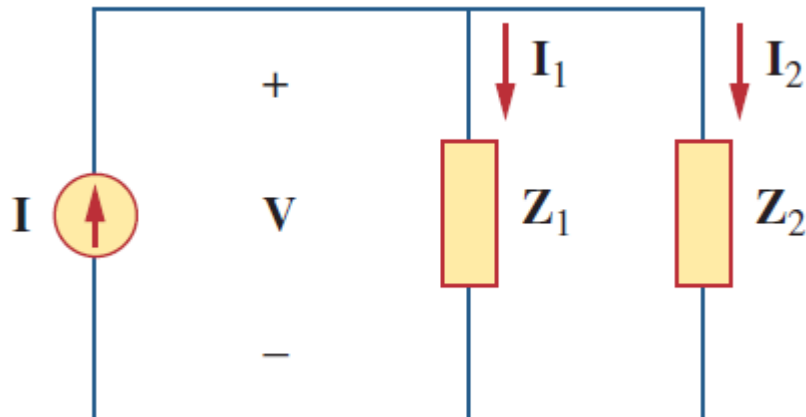


$$\mathbf{Z}_{eq} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2}} = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$



Since

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = \mathbf{I}_1\mathbf{Z}_1 = \mathbf{I}_2\mathbf{Z}_2$$


The current in the impedances are
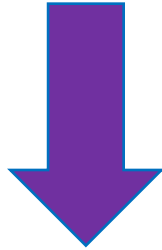
$$\mathbf{I}_1 = \left(\frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \right) \mathbf{I}, \quad \mathbf{I}_2 = \left(\frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \right) \mathbf{I}$$



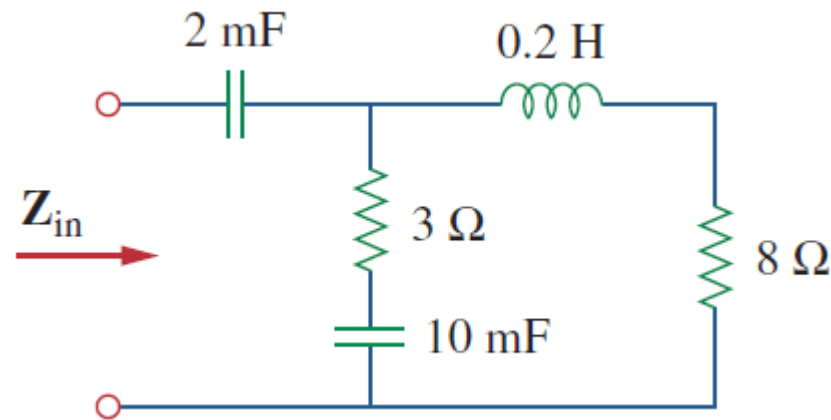
Example #1

Find the input impedance of the circuit shown. Assume that the circuit operates at $\omega = 50$ rad/s



Solution

To get Z_{in} , we combine resistors, resistor-capacitor and resistor-inductor in series and in parallel.

Example #1

Let

\mathbf{Z}_1 Impedance of the 2 mF capacitor

\mathbf{Z}_2 Impedance of the 3 Ω resistor in series with the 10 mF capacitor

\mathbf{Z}_3 Impedance of the 0.2 H inductor in series with the 8 Ω resistor

$$\mathbf{Z}_1 = \frac{1}{j\omega C} = -j10 \Omega$$

Then

$$\mathbf{Z}_2 = 3 + \frac{1}{j\omega C} = 3 - j2 \Omega$$

$$\mathbf{Z}_3 = 8 + j\omega L = 8 + j10 \Omega$$



Example #1

The input impedance

$$\mathbf{Z}_{in} = \mathbf{Z}_1 + (\mathbf{Z}_2 \square \mathbf{Z}_3)$$


$$\mathbf{Z}_{in} = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8}$$

$$\mathbf{Z}_{in} = 3.22 - j11.07 \Omega = 11.52 \angle -73.78^\circ \Omega$$



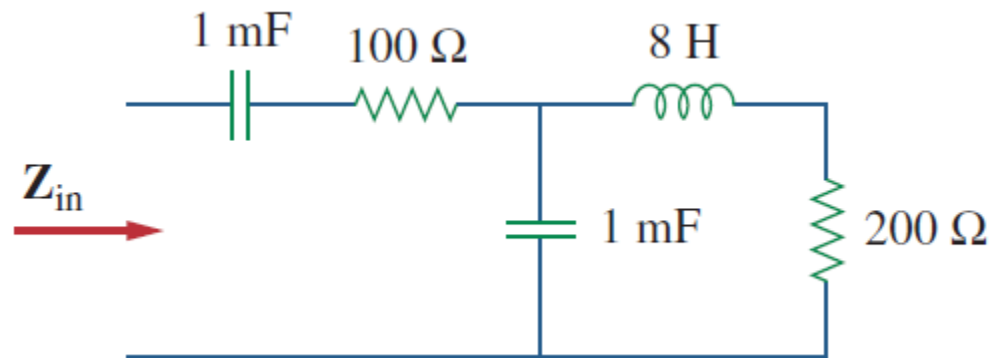Example #2

Determine the input impedance of the circuit in figure shown at $\omega = 10 \text{ rad/s}$.




Answer

$$\mathbf{Z}_{in} = 149.52 - j195 \ \Omega = 245.73 \angle 52.52^\circ \ \Omega$$



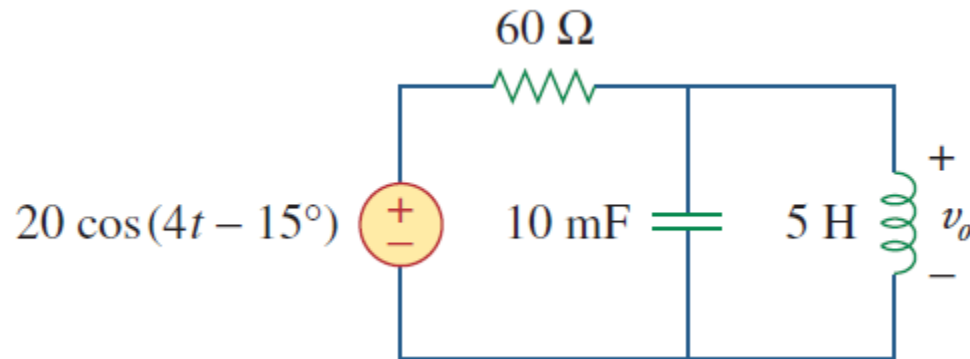Example #3

Determine $v_o(t)$ for the given circuit.




Solution

Transform the time domain equivalent to phasor form

$$\mathbf{V}_s = 20 \angle -15^\circ \text{ V} \quad \mathbf{Z}_C = \frac{1}{j\omega C} = -j25 \Omega \quad \mathbf{Z}_L = j\omega L = j20 \Omega$$



Example #3

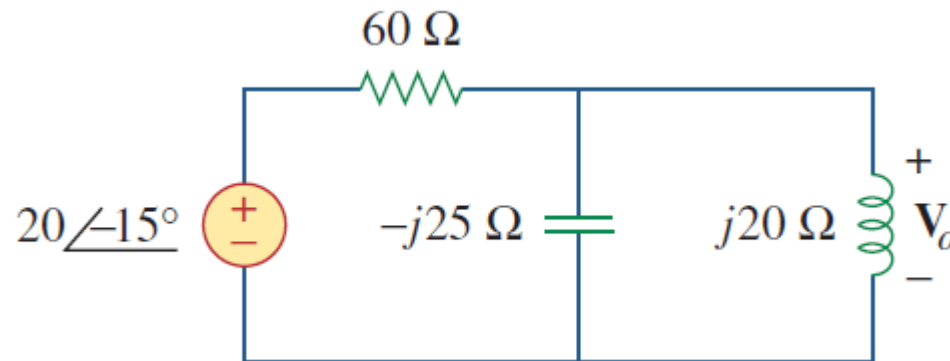

Let

\mathbf{Z}_1 Impedance of the 60Ω resistor

\mathbf{Z}_2 Impedance of the parallel combination of the 10 mF capacitor and the 5 H inductor

$$\mathbf{Z}_1 = 60 \Omega$$

$$\mathbf{Z}_2 = \mathbf{Z}_C \parallel \mathbf{Z}_L = j100 \Omega$$

Example #3

By using voltage divider

$$\mathbf{V}_o = \left(\frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \right) \mathbf{V}$$

$$\mathbf{V}_o = \left(\frac{j100}{60 + j100} \right) 20 \angle -15^\circ$$

$$\mathbf{V}_o = 17.15 \angle 15.96^\circ \text{ V}$$


In time domain

$$v_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$



Example #4

Find $v_o(t)$ in the given circuit

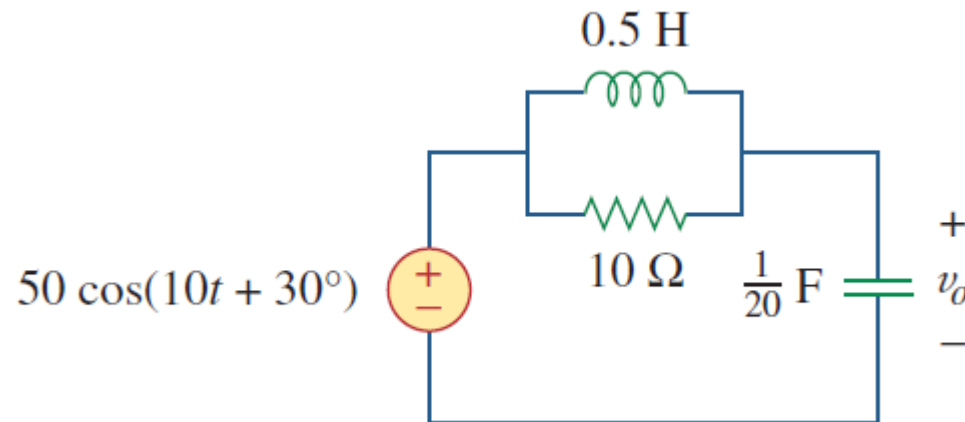

Answer

$$v_o(t) = 35.36 \cos(10t - 105^\circ) \text{ V}$$




Nodal Analysis

- The basis of nodal analysis is **Kirchhoff's Current Law**.
- Since KCL is valid for phasors, we can analyze ac circuit by nodal analysis.



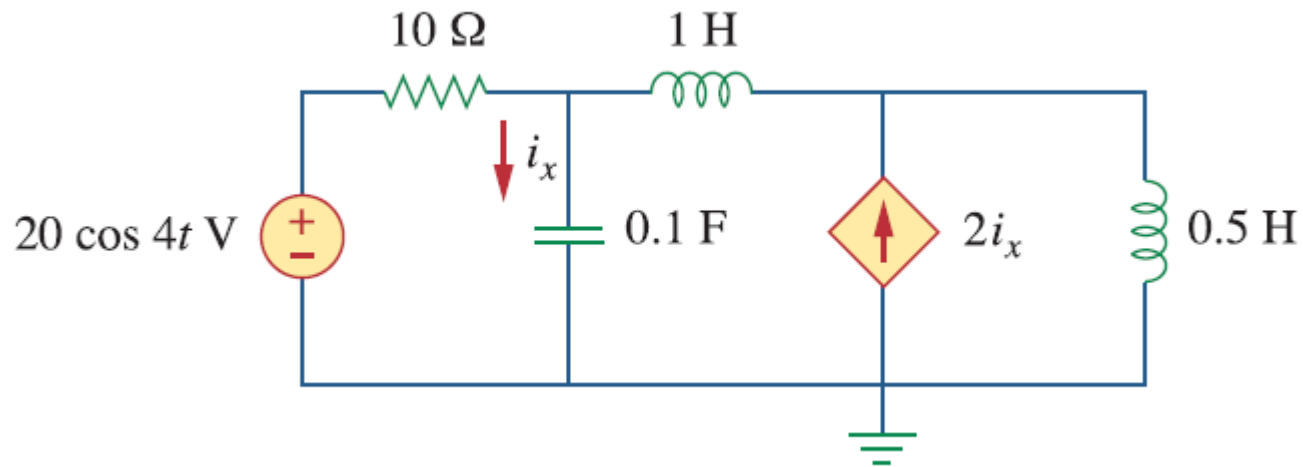Example #5

Find i_x in the given circuit using nodal analysis



Solution

Convert the circuit to phasor form




Example #5

$$20 \cos 4t \Rightarrow 20 \angle 0^\circ$$

$$1\text{H} \Rightarrow j\omega L = j4$$

$$0.5\text{H} \Rightarrow j\omega L = j2$$
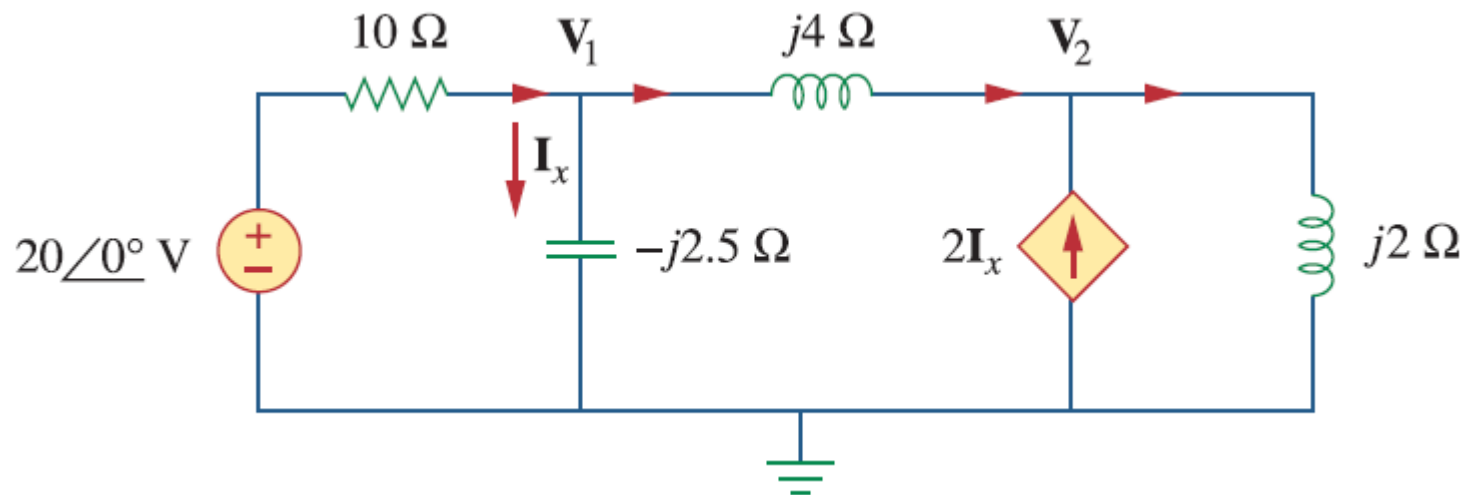
$$0.1\text{F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$



Example #5

Applying KCL at node V_1

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$(1 + j1.5)V_1 + j2.5V_2 = 20$$

$$\text{And } I_x = V_1 / -j2.5$$

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j}$$

$$11V_1 + 15V_2 = 0$$

Then in matrix form

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

Applying KCL at node V_2

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j}$$



Example #5

Then by using Cramer's Rule

$$\mathbf{V}_1 = \frac{\begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix}}{\begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix}} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$\mathbf{V}_2 = \frac{\begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix}}{\begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix}} = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$



Example #5

Then \mathbf{I}_x

$$\mathbf{I}_x = \frac{\mathbf{V}_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle 90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$


In time domain

$$i_x(t) = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



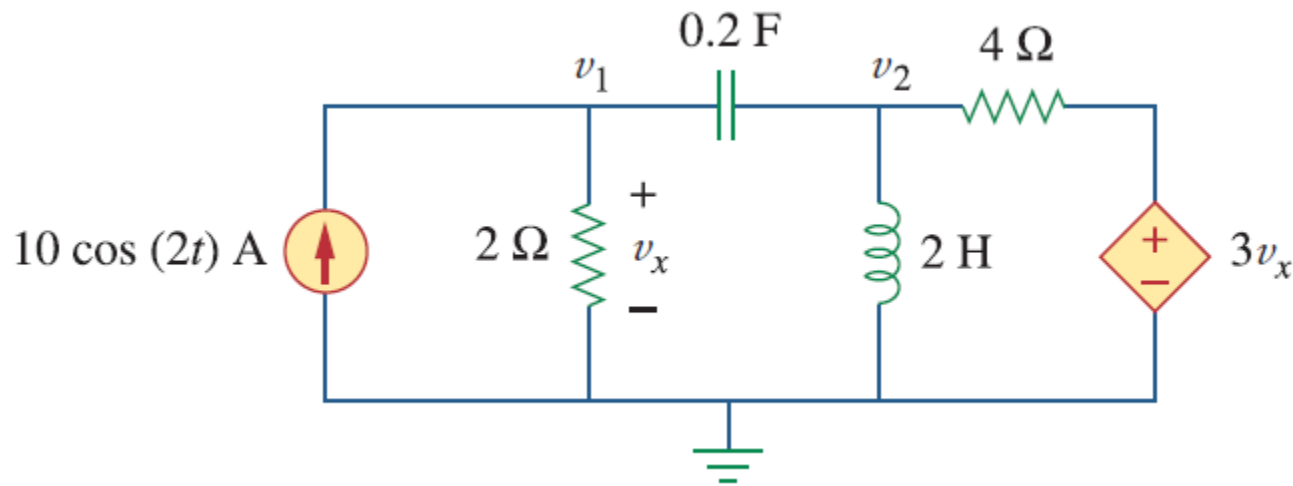Example #6

Find v_1 and v_2 in the given circuit using nodal analysis




Answer

$$v_1(t) = 11.325 \cos(2t + 60.01^\circ) \text{ V}$$

$$v_2(t) = 33.02 \cos(2t + 57.12^\circ) \text{ V}$$

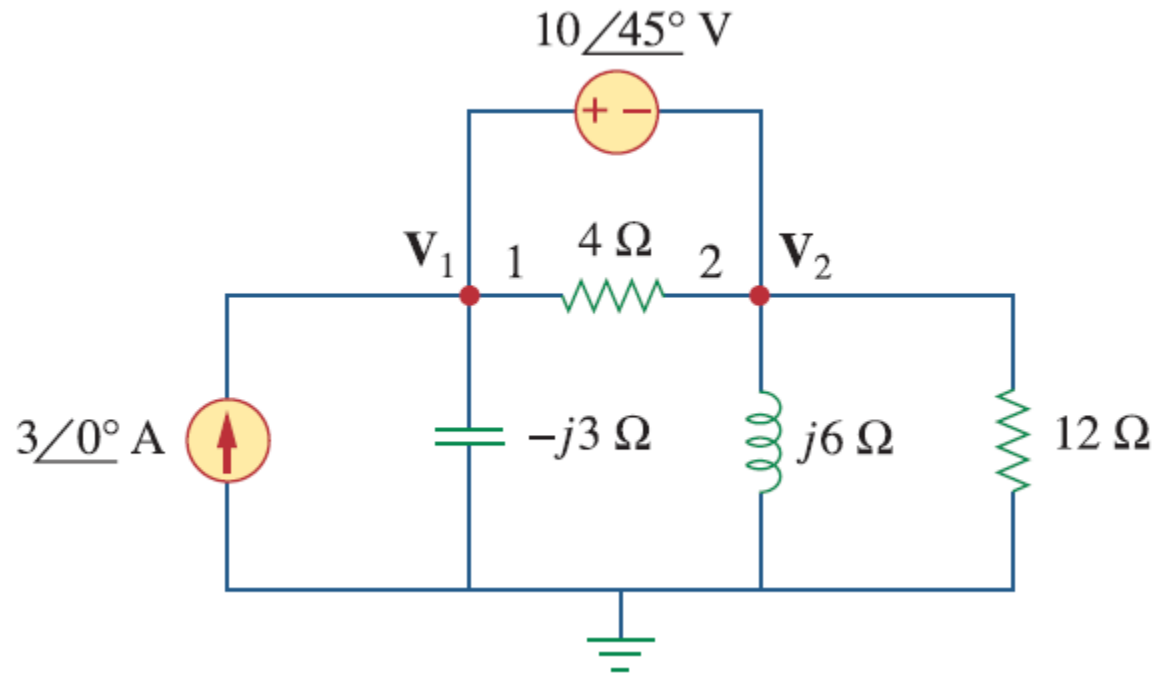Example #7

Compute V_1 and V_2 in the following circuit



Answer

$$V_1 = 25.78\angle -70.48^\circ \text{ V}$$

$$V_2 = 31.41\angle -87.18^\circ \text{ V}$$


Mesh Analysis

- **Kirchhoff's Voltage Law** form the basis of mesh analysis.
- Since KVL is valid for phasors, we can analyze ac circuit by mesh analysis.



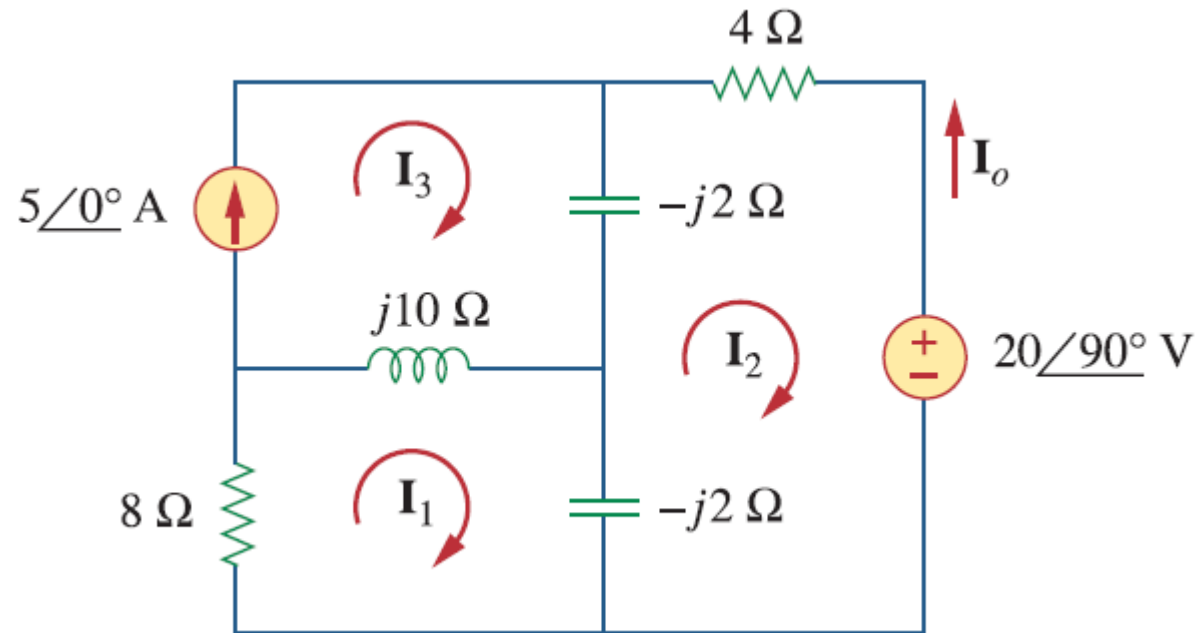Example #8

Determine I_o for the given circuit by using mesh analysis.



Solution

Apply KVL to mesh 1



Example #8

$$(8 + j10 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - (j10)\mathbf{I}_3 = 0$$

Apply KVL to mesh 2

$$(4 - j2 - j2)\mathbf{I}_2 - (-j2)\mathbf{I}_1 - (-j2)\mathbf{I}_3 + 2\angle 90^\circ = 0$$

For mesh 3 $\mathbf{I}_3 = 5$

Then

$$(8 + j8)\mathbf{I}_1 + j2\mathbf{I}_2 = j50$$

$$j2\mathbf{I}_1 + (4 - j4)\mathbf{I}_2 = -j30$$



Example #8

In matrix form

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

By using Cramer's Rule

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix}}{\begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix}} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ \text{ A}$$


The desired current

$$\mathbf{I}_o = -\mathbf{I}_2 = 6.12 \angle 144.78^\circ \text{ A}$$



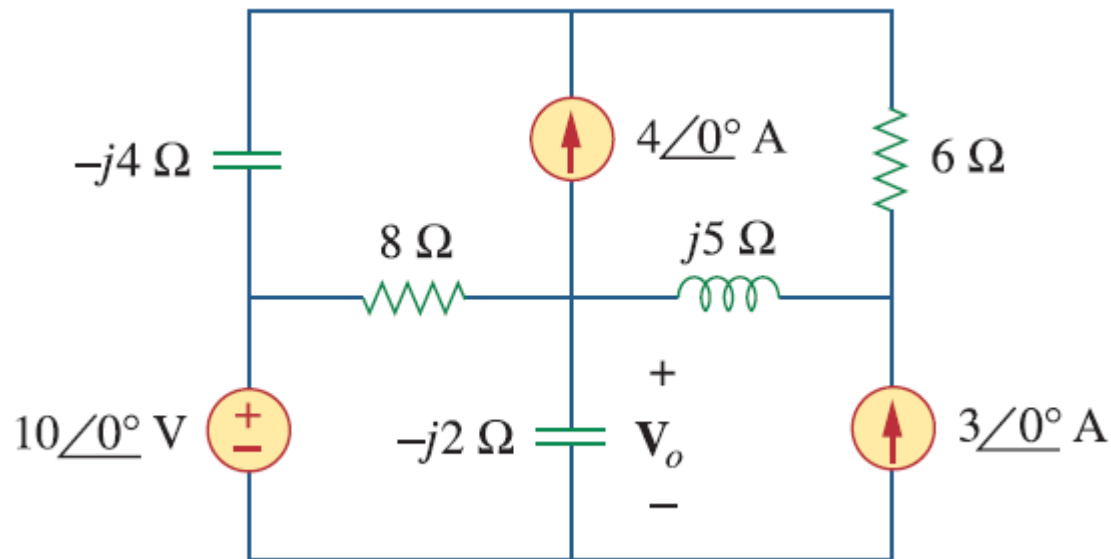Example #9

Solve for V_o in the following circuit using mesh analysis



Answer


$$V_o = 9.756 \angle 222.32^\circ \text{ V}$$



- Thevenin and Norton theorem are applied to AC circuit in the same way as they are to DC circuits.
- The only additional effort arises from the need to manipulate complex number.
- If the circuit has sources operating at different frequencies the Thevenin or Norton equivalent circuit must be determined at each frequency.



Thevenin and Norton Equivalent Circuit

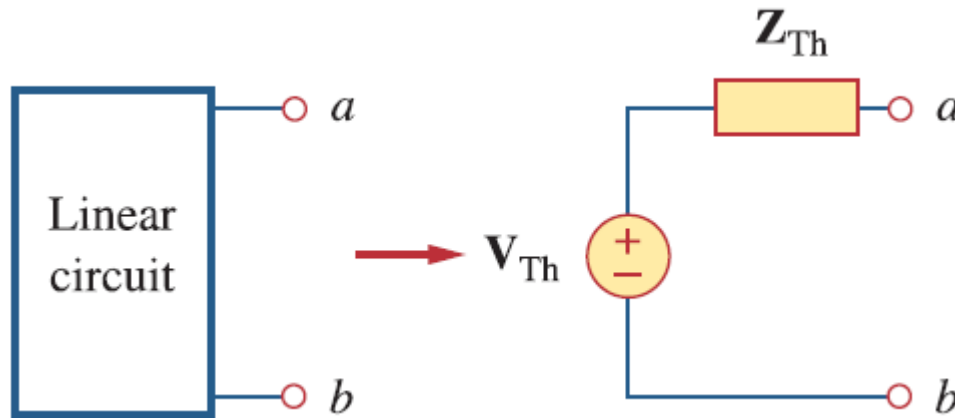

$$V_{Th} = Z_N I_N$$

$$Z_{Th} = Z_N$$

