

# **BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING**

## **Analog Electronics: Rectifier**

Ismail Mohd Khairuddin , Zulkifil Md Yusof  
Faculty of Manufacturing Engineering  
Universiti Malaysia Pahang

# Semiconductor Diodes & Circuits

**BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING**



## Faculty of Manufacturing

Universiti Malaysia Pahang  
Kampus Pekan, Pahang Darul Makmur  
Tel: +609-424 5800  
Fax: +609-4245888

### Contents:

- Outcomes
- Rectifier Circuit
- Zener Diode

# Outcomes

Understand the diode characteristics and its model

Learn the types of diodes

Learn the series and parallel operation of diodes

Analyze and design simple voltage-regulator circuits.




Understand various rectifiers and wave-shaping circuits

# Rectifier Circuit

- ❑ Convert AC power into DC power.
- ❑ The basis for power supply and battery charging.
- ❑ For signal processing such as demodulation of signal radio.
- ❑ For precision control of an AC voltage to DC in an electronic voltmeter.




## Half-Wave Rectifier

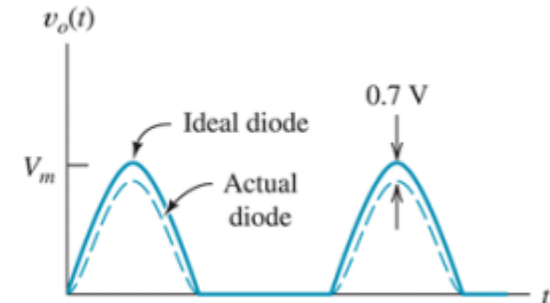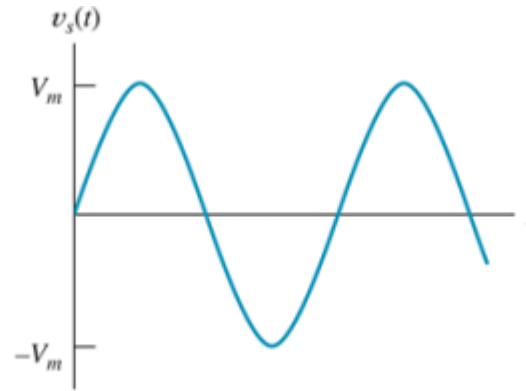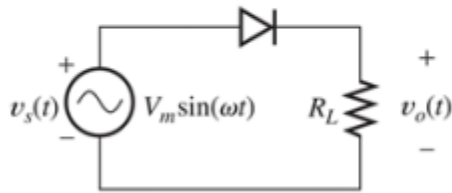


- Over 1 full cycle, the average value of areas (voltage) is zero.
- The output waveform,  $v_o$  that generated by the circuit will give an average value that will be use in AC to DC conversion.
- The power and current rating are typically much higher than those of diode employed in other applications.

# Rectifier Circuit

## Half-Wave Rectifier

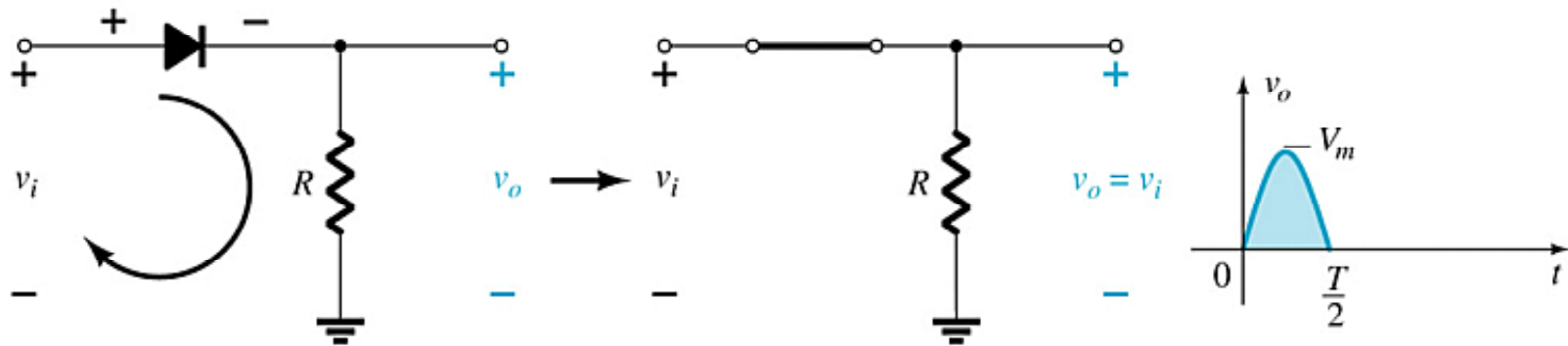

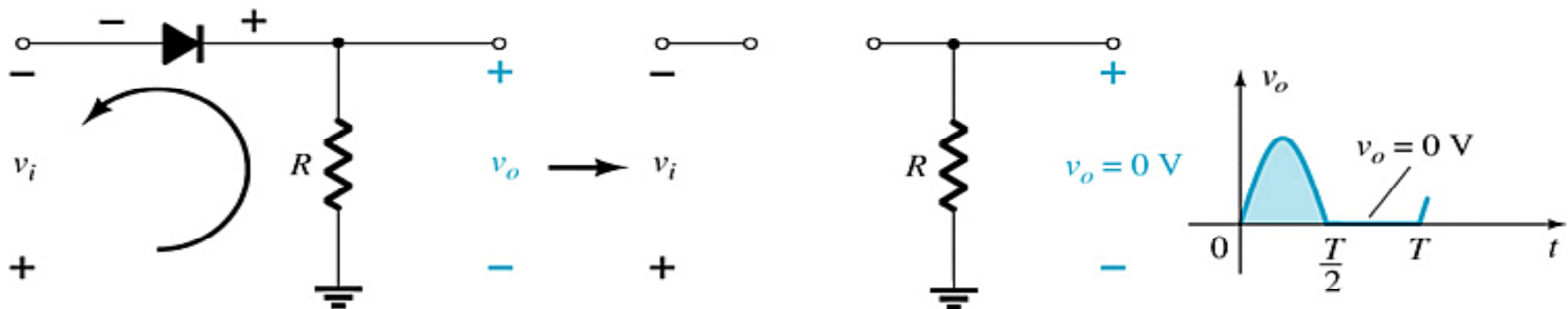
The DC output voltage is  $0.318V_m$ , where  $V_m$  = the peak AC voltage.




## PIV (PRV)

- Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.
- It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.

$$\text{PIV (PRV)} \geq V_m$$

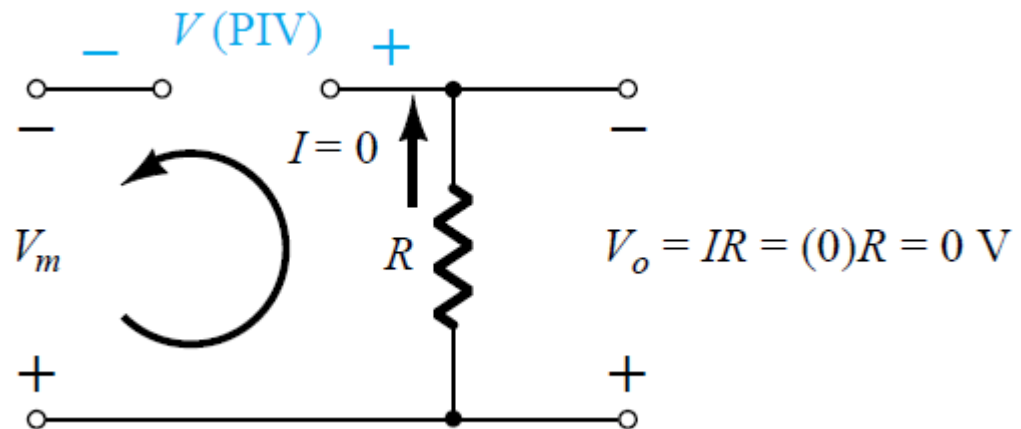


## Full-Wave Rectifier

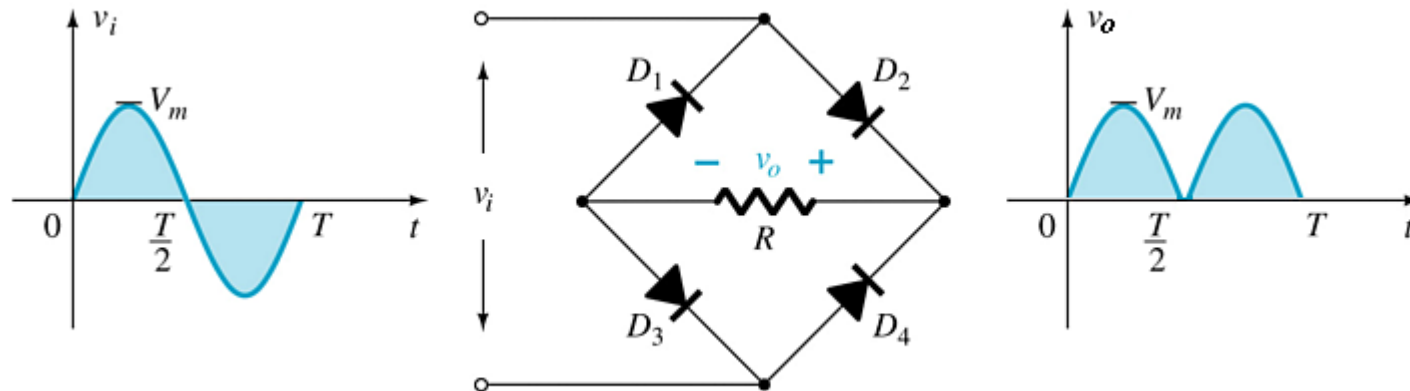

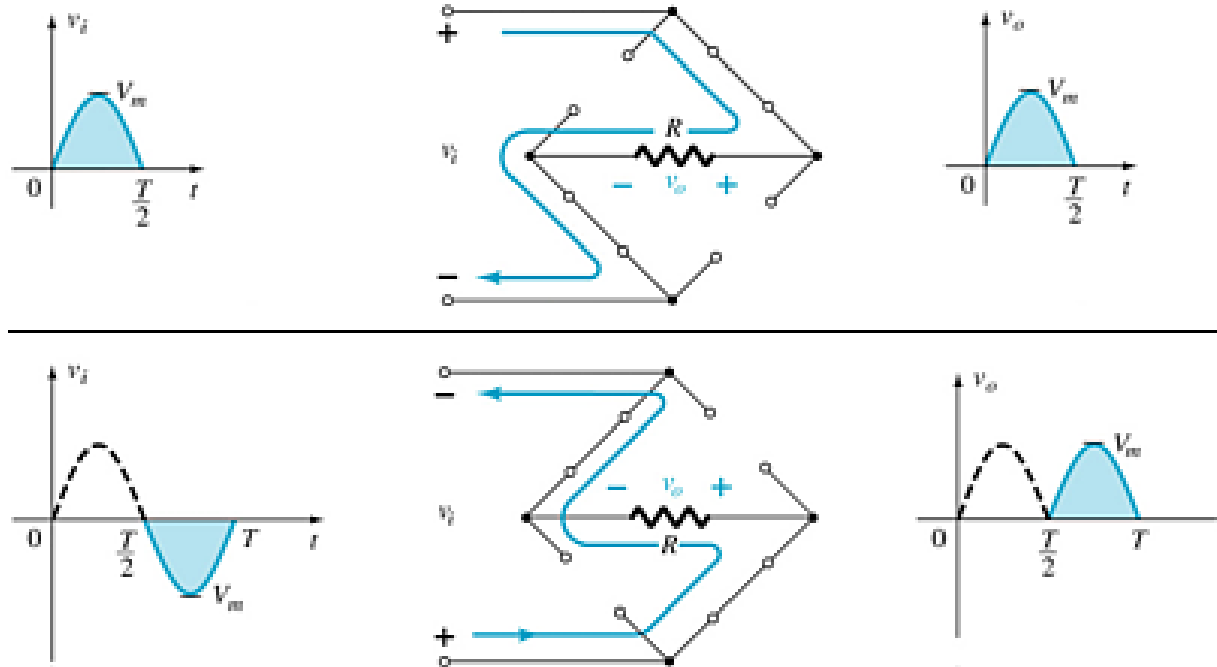- ❑ The rectification process can be improved by using a full-wave rectifier circuit.
- ❑ Full-wave rectification produces a greater DC output:
  - ❑ Half-wave:  $V_{dc} = 0.318V_m$
  - ❑ Full-wave:  $V_{dc} = 0.636V_m$










Four diodes are connected in a bridge configuration



# Rectifier Circuit
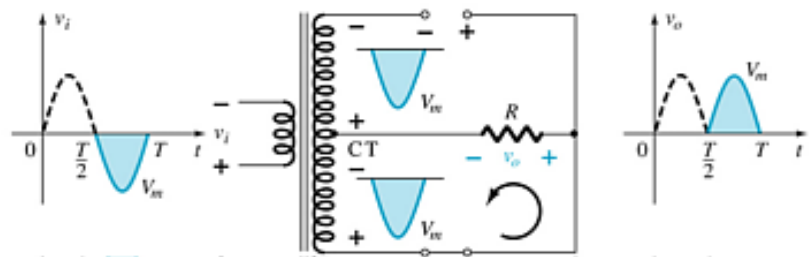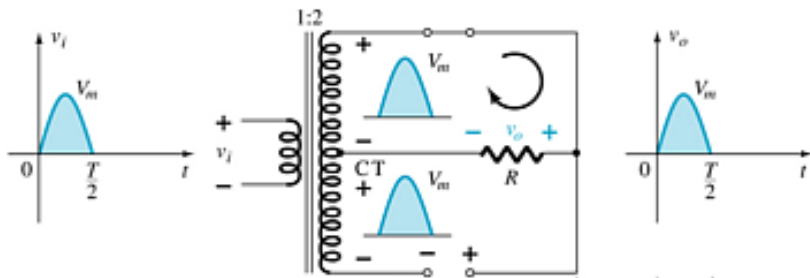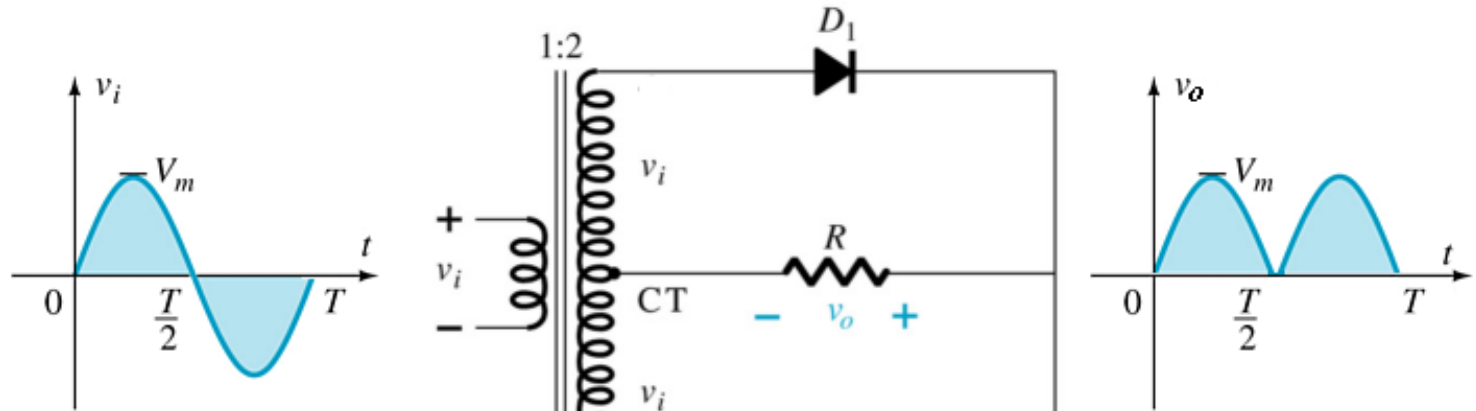
## Full-Wave Rectifier (Center-Tapped Transformer)



## Summary of Rectifier Circuit

### Rectifier

- Half Wave Rectifier
- Bridge Rectifier
- Center-Tapped Transformer Rectifier

### Ideal $V_{DC}$

- $V_{DC} = 0.318V_m$
- $V_{DC} = 0.636V_m$
- $V_{DC} = 0.636V_m$

### Realistic $V_{DC}$

- $V_{DC} = 0.318V_m - 0.7$
- $V_{DC} = 0.636V_m - 2(0.7 \text{ V})$
- $V_{DC} = 0.636V_m - 0.7 \text{ V}$

# Zener Diode



The Zener is a diode operated in **reverse bias** at the Zener Voltage  $V_Z$ .

When  $V \geq V_Z$

- The Zener is on
- Voltage across the Zener is  $V_Z$
- Zener current:  $I_Z = I_R - I_{RL}$
- The Zener Power:  $P_Z = V_Z I_Z$

When  $V < V_Z$

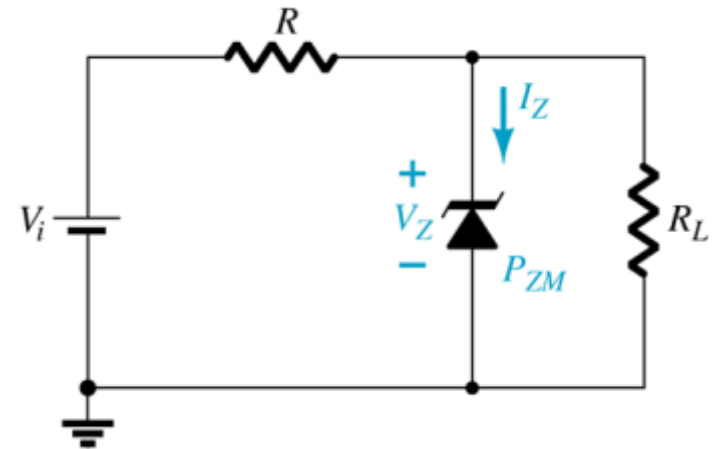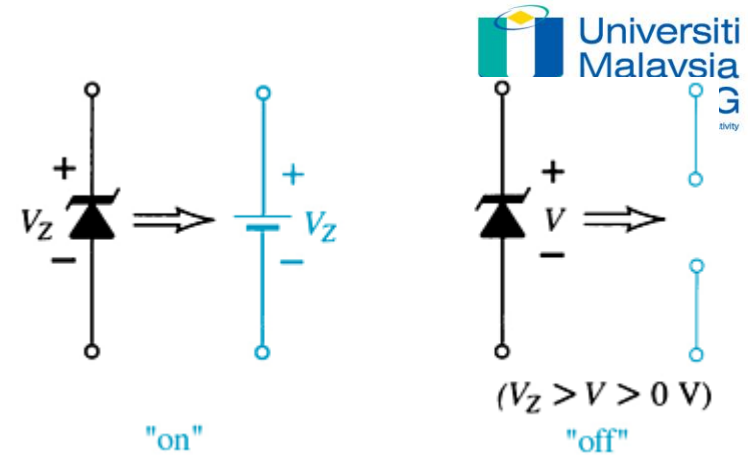
- The Zener is off
- The Zener acts as an open circuit



# Zener Diode


- To use of the Zener diode as a regulator we must considered 3 cases

## i. $V_i$ and $R$ fixed

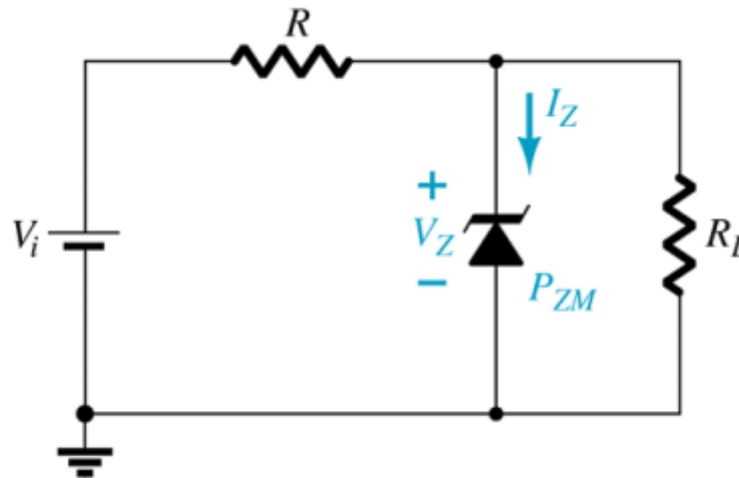

**Step #1:** Determine the state of Zener diode by removing it from the network and calculating the voltage across the resulting open circuit.

# Zener Diode

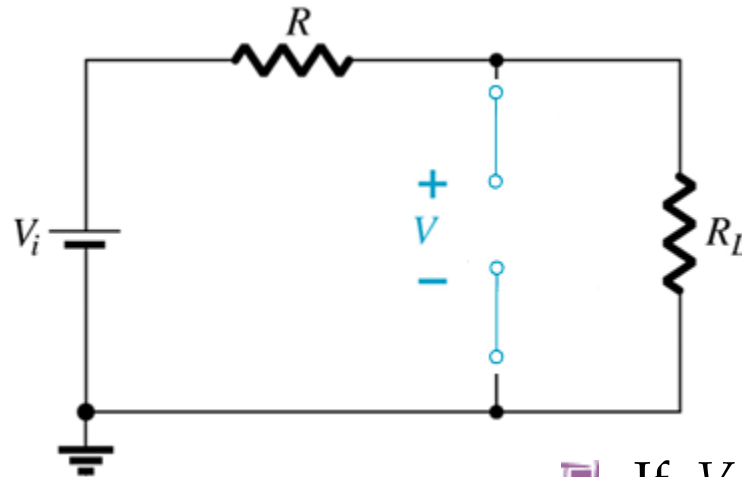


$$V = V_L = \frac{R_L V_i}{R + R_L}$$

- If  $V \geq V_Z$  the Zener is on and appropriate model can be substituted.
- If  $V < V_Z$  the Zener is off open circuit is substituted.

**Step #2:** Substitute the appropriate equivalent circuit and solve for the desired unknown



# Zener Diode

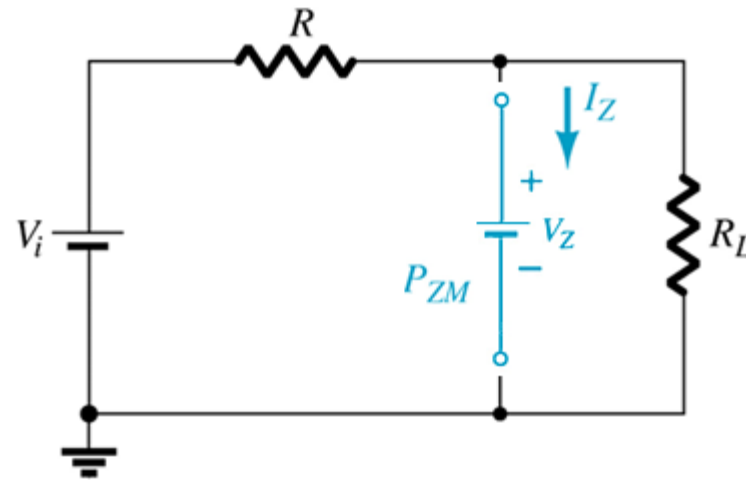

$$V_L = V_Z$$

where

$$I_R = I_Z + I_L$$


$$I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$

$$I_L = \frac{V_L}{R_L}$$

$$P_Z = V_Z I_Z$$



## ii. Fixed $V_i$ and variable $R_L$

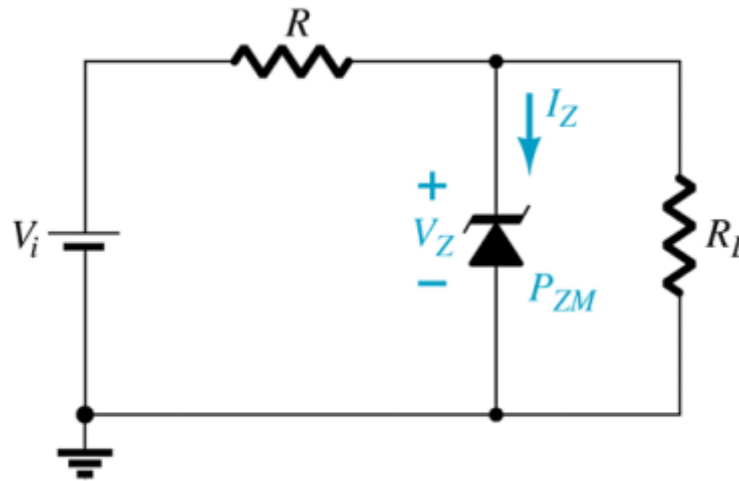

- Due to the offset voltage  $V_Z$ , there is a specific range of resistor values and load current that will ensure that Zener is in the on state.
- Too **small a load resistance**  $R_L$  will result in a voltage  $V_L$  across the load resistor less than  $V_Z$ , and the Zener device will be in the off state

$$V_L = V_Z = \frac{R_L V_i}{R + R_L}$$





$$R_{L\min} = \frac{RV_Z}{V_i - V_Z}$$

- Any load resistance value greater than the  $R_L$  will ensure that the Zener diode is in the on state and the diode can be replaced by its  $V_Z$  source equivalent.
- For minimum  $R_L$  the **Zener current exceeds the maximum current rating**,  $I_{ZM}$ . The maximum current for the circuit is given by:

$$I_{L\max} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L\min}}$$



# Zener Diode

Once the diode is in on state, the voltage across  $R$  remains fixed at

$$V_R = V_i - V_Z \quad \text{and} \quad I_R = \frac{V_R}{R}$$

Zener current  $I_Z = I_R - I_L$


$I_Z$  is **minimum** when  $I_L$  is a **maximum**  
 $I_Z$  is **maximum** when  $I_L$  is a **minimum** } Since  $I_R$  is constant

$$I_{L\min} = I_R - I_{Z\max} \qquad R_{L\max} = \frac{V_Z}{I_{L\min}}$$



# Zener Diode

## iii. Fixed $R_L$ and variable $V_i$

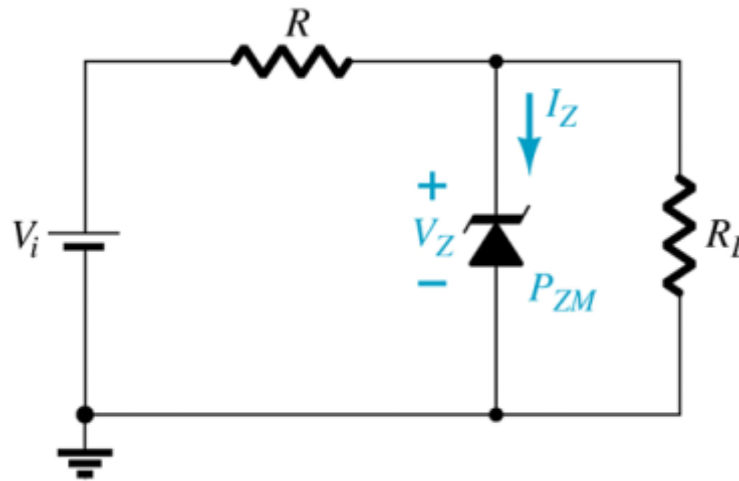

- For a fixed value of  $R_L$ , the voltage  $V_i$  must be sufficiently large to turn the Zener diode on.

The minimum turn on voltage

$$V_{i \min} = \frac{(R + R_L) V_Z}{R_L}$$



# Zener Diode

- The maximum value of  $V_i$  is limited by the maximum Zener current


$$I_{R\max} = I_{Z\max} + I_L$$

$$V_{i\max} = I_{R\max} R + V_Z$$


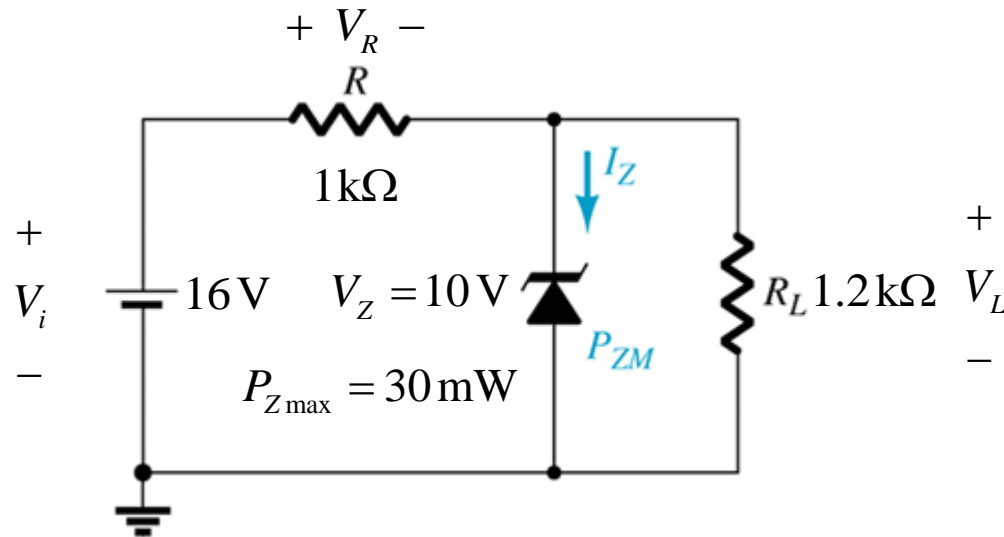
## Example #1

For the Zener diode network of figure below, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ .



## Solution

Since  $V_i$  and  $R$  is fixed, then


$$V = V_L = \frac{R_L V_i}{R + R_L}$$

$$V = \frac{1.2\text{k}(16)}{1\text{k} + 1.2\text{k}} = 8.73\text{V}$$


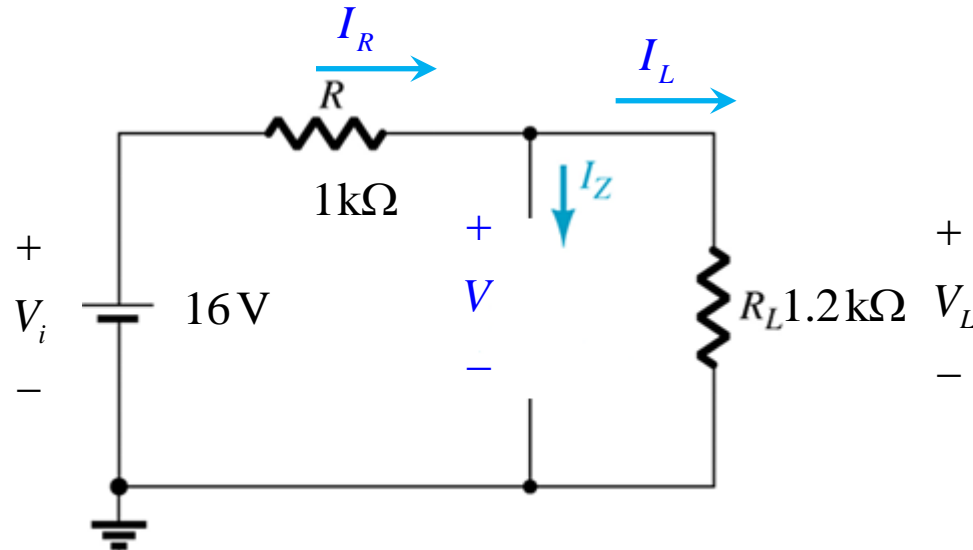
## Example #1

Since  $V < V_Z$  the Zener is off state and open circuit is substituted.



$$V_L = V$$

$$V_L = 8.73 \text{ V}$$

$$V_R = V_i - V_L$$

$$V_R = 16 - 8.73$$

$$V_R = 7.27 \text{ V}$$

$$I_Z = 0 \text{ A}$$


$$P_Z = V_Z I_Z$$

$$P_Z = 0 \text{ W}$$


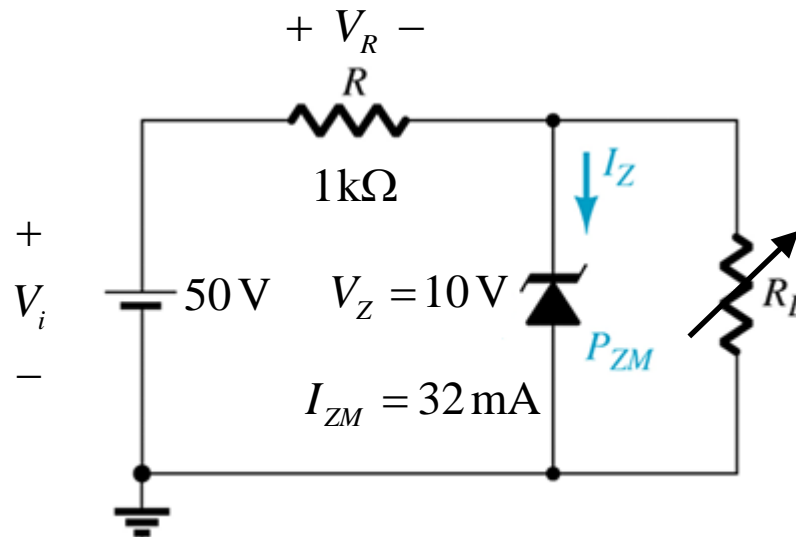
## Example #2

For the network of figure below, determine the range  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10 V. Then determine the maximum wattage rating of the diode



## Example #2

## Solution

Since  $V_i$  is fixed for the circuit shown and  $R_L$  is a variable

To turn on the Zener diode, we need a small load resistance, then

$$R_{L\min} = \frac{RV_Z}{V_i - V_Z}$$

$$V_R = V_i - V_Z$$

$$I_R = \frac{V_R}{R}$$

$$V_R = 40 \text{ V}$$

$$R_{L\min} = 250 \Omega$$

$$I_R = 40 \text{ mA}$$

$$I_{L\min} = I_R - I_{Z\max}$$

$$I_{L\min} = 40 \text{ m} - 32 \text{ m}$$

$$I_{L\min} = 8 \text{ mA}$$

$$R_{L\max} = \frac{V_Z}{I_{L\min}}$$

$$R_{L\max} = 1.25 \text{ k}\Omega$$

$$P_{\max} = V_Z I_{Z\max}$$


$$P_{\max} = 320 \text{ mW}$$




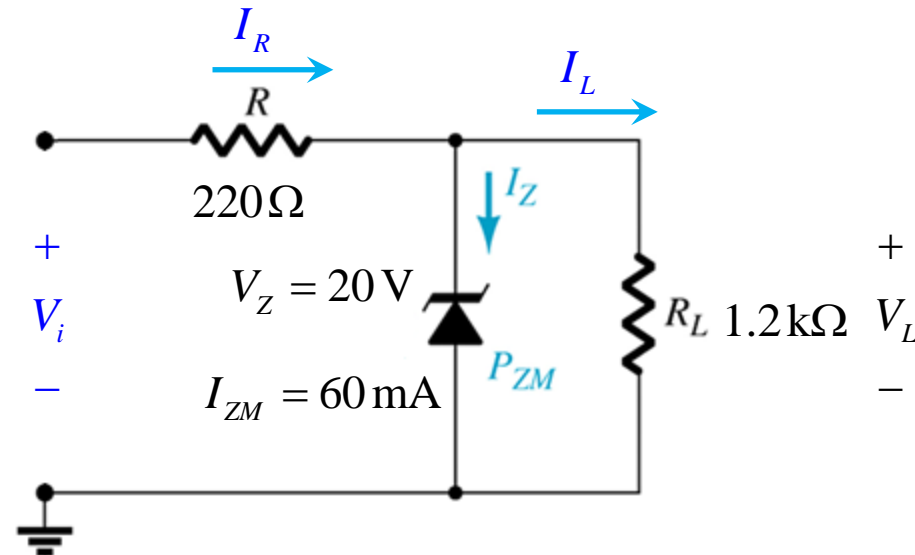
## Example #3

Determine the range of values of  $V_i$  that will maintain the Zener diode of figure shown in the on state



### Solution

Since  $V_i$  is a variable, then

$$V_{i \min} = \frac{(R + R_L) V_Z}{R_L} \quad I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$$

$$V_{i \min} = 23.67 \text{ V}$$

$$I_L = 16.67 \text{ A}$$

## Example #3

$$I_{R_{\max}} = I_{Z_{\max}} + I_L$$

$$I_{R_{\max}} = 76.67 \text{ mA}$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z$$

$$V_{i_{\max}} = 36.87 \text{ V}$$

