

# **BFF1303: ELECTRICAL / ELECTRONICS ENGINEERING**

## **Analog Electronics: Bipolar Junction Transistors**

Ismail Mohd Khairuddin , Zulkifil Md Yusof  
Faculty of Manufacturing Engineering  
Universiti Malaysia Pahang

# Bipolar Junction Transistor

**BFF1303 ELECTRICAL/ELECTRONICS ENGINEERING**



## Faculty of Manufacturing

Universiti Malaysia Pahang  
Kampus Pekan, Pahang Darul Makmur  
Tel: +609-424 5800  
Fax: +609-4245888

### Contents:

- Outcomes
- Introduction
- Transistor Construction
- Transistor Operation
- Common-Base Configuration
- Common-Emitter Configuration
- Common-Collector Configuration
- Limits Of Operation
- Transistor Specification Sheet

# Outcomes


Understand the physical operation of bipolar transistor

Select the operating point of a bipolar transistor circuit

Compute performance of several important amplifier configurations.

Select an amplifier configuration appropriate for a given application.

## Bardeen, Brattain and Shockley

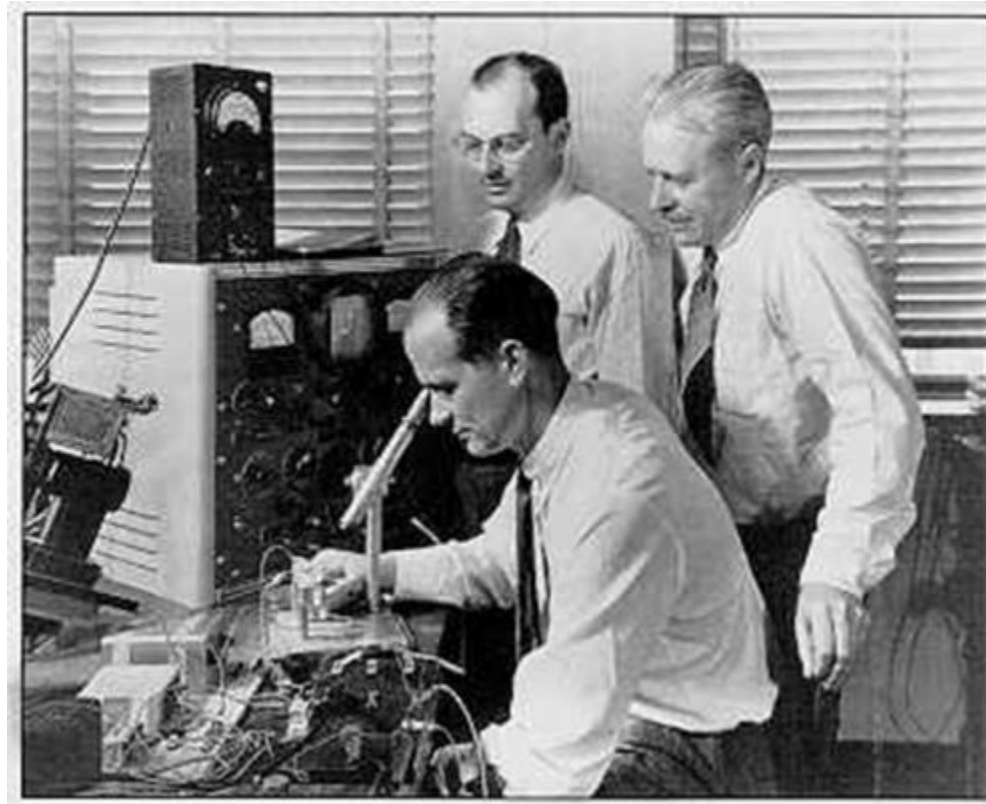

Discovery of the transistor in 1947

# Transistor Construction

There are two types of transistors:

*pnp*



*npn*

The terminals are labeled:

**E - Emitter**


**B - Base**

**C - Collector**

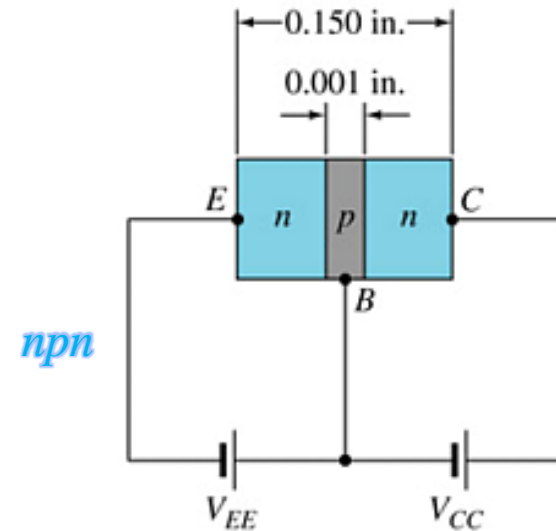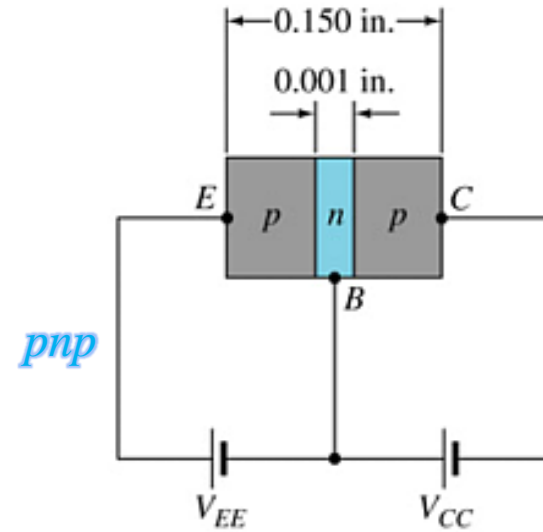
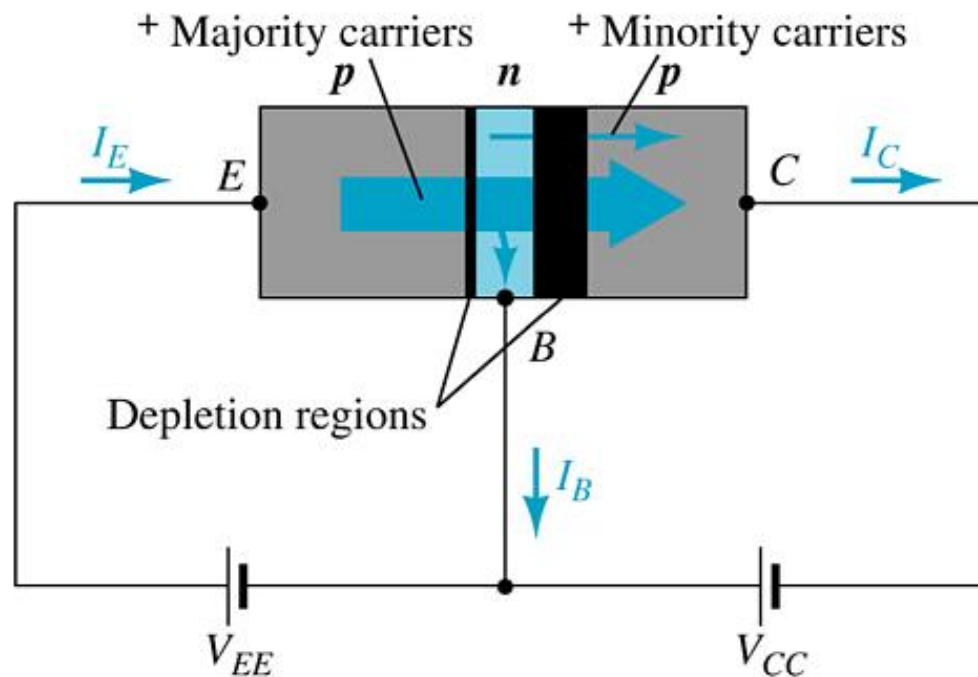
# Transistor Operation

- With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:
  - The emitter-base junction is **forward biased**
  - The base-collector junction is **reverse biased**




## Currents in a Transistor

- Emitter current is the sum of the collector and base currents:


$$I_E = I_C + I_B$$

- The collector current is comprised of two currents:
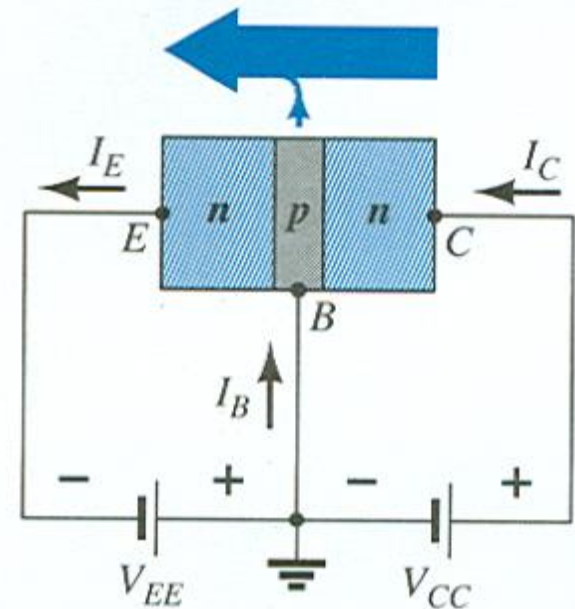
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



# Common-Base Configuration

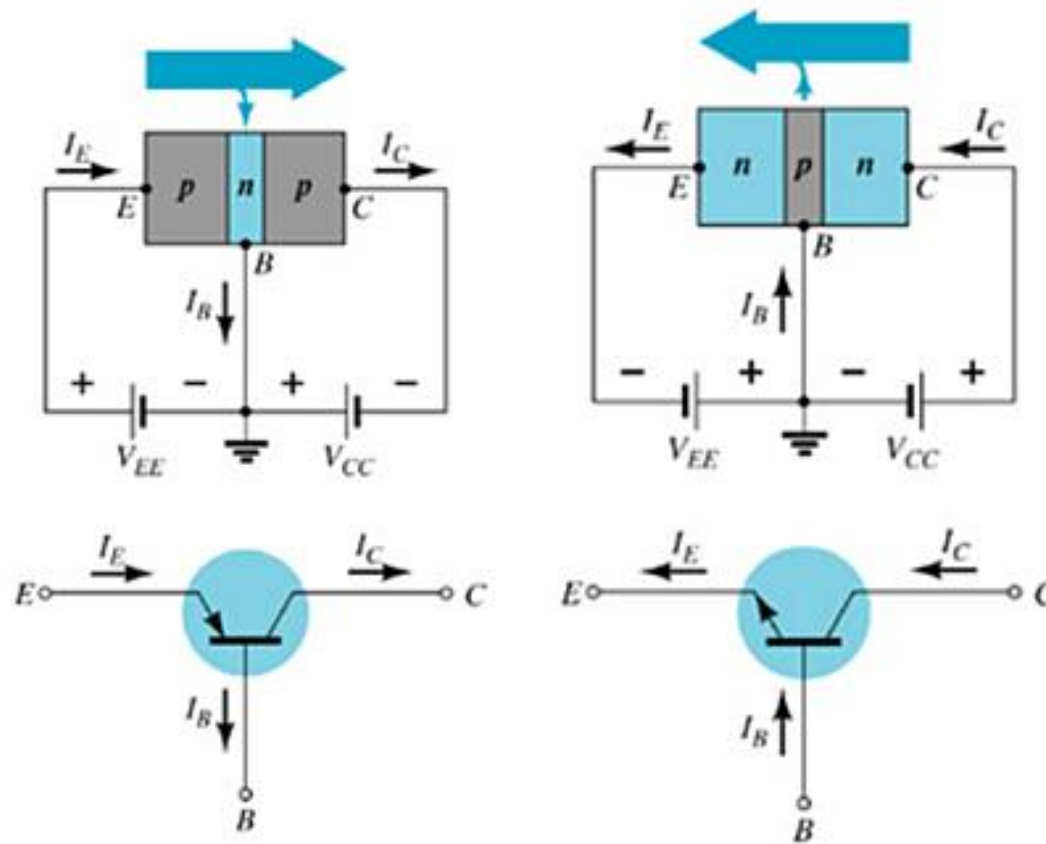

- The base is common to both input (emitter–base) and output (collector–base) of the transistor.






# Common-Base Amplifier
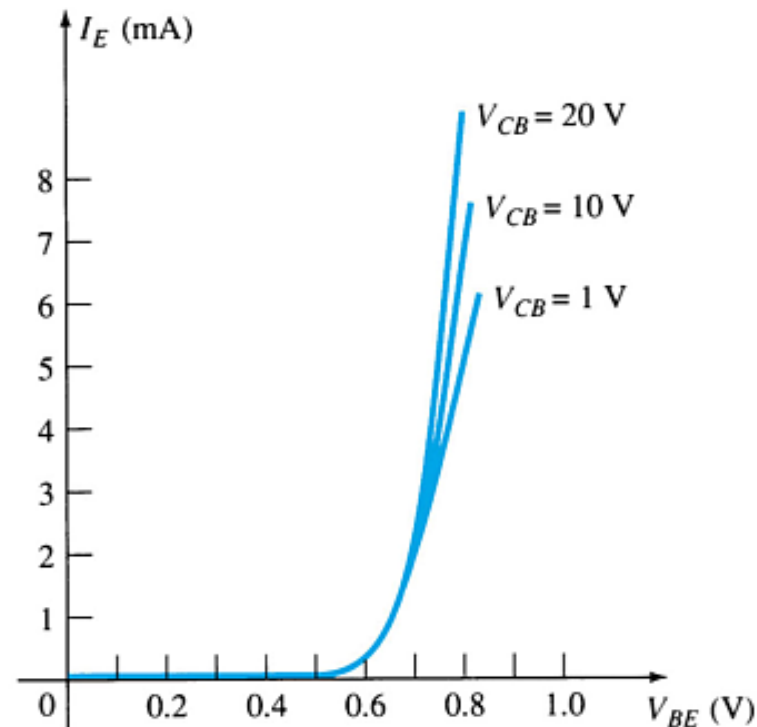
## Input Characteristics


- This curve shows the relationship between of input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.



# Common-Base Amplifier
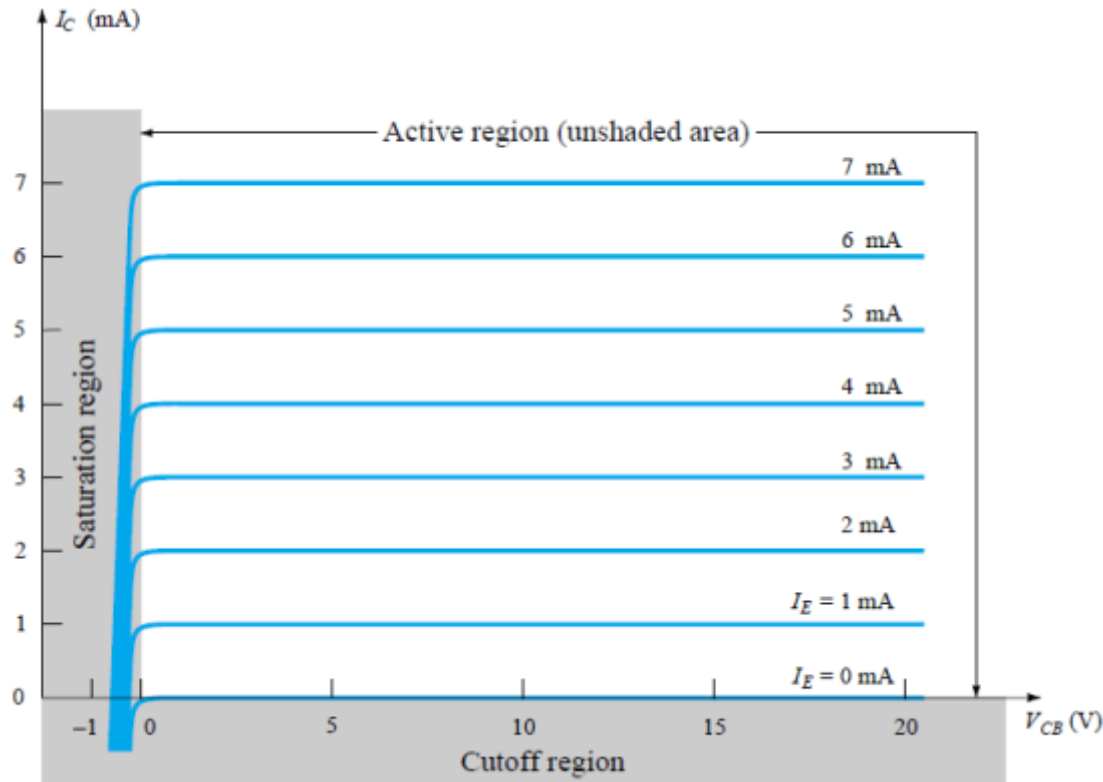
## Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).



## Operating Regions

- ❑ **Active** – Operating range of the amplifier.
- ❑ **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- ❑ **Saturation** – The amplifier is full on. There is current, but little voltage.

## Approximations

- ❑ Emitter and collector currents:

$$I_C \cong I_E$$

- ❑ Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$



## Alpha ( $\alpha$ )

- Ratio of  $I_C$  to  $I_E$  :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

- Ideally:  $\alpha = 1$
- In reality:  $\alpha$  is between 0.9 and 0.998
- Alpha ( $\alpha$ ) in the AC mode:



$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$


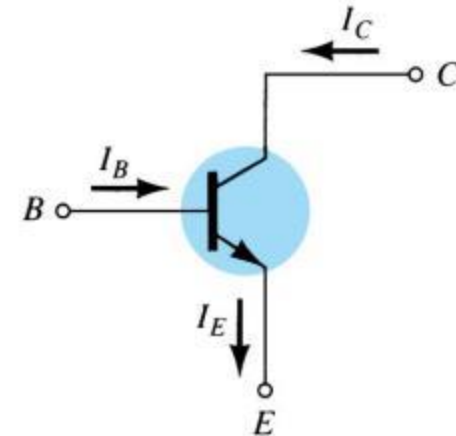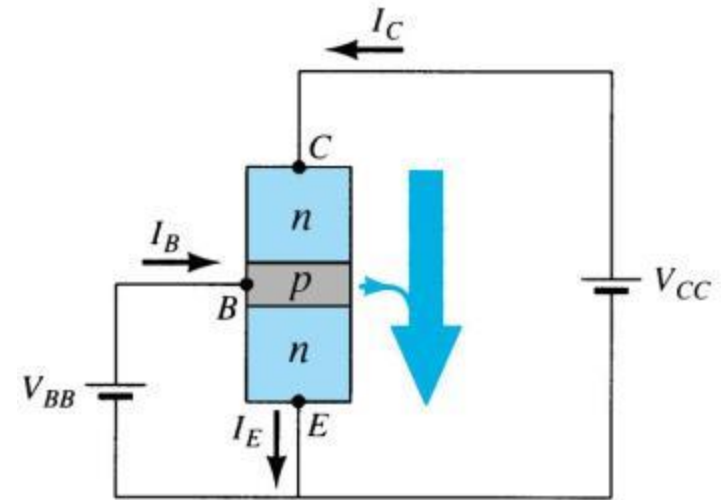
# Common-Emitter Configuration

❑ The emitter is common to both input (base-emitter) and output (collector-emitter).

❑ The input is on the base and the output is on the collector.




(a)




# Common-Emitter Configuration

## Common-Emitter Characteristics

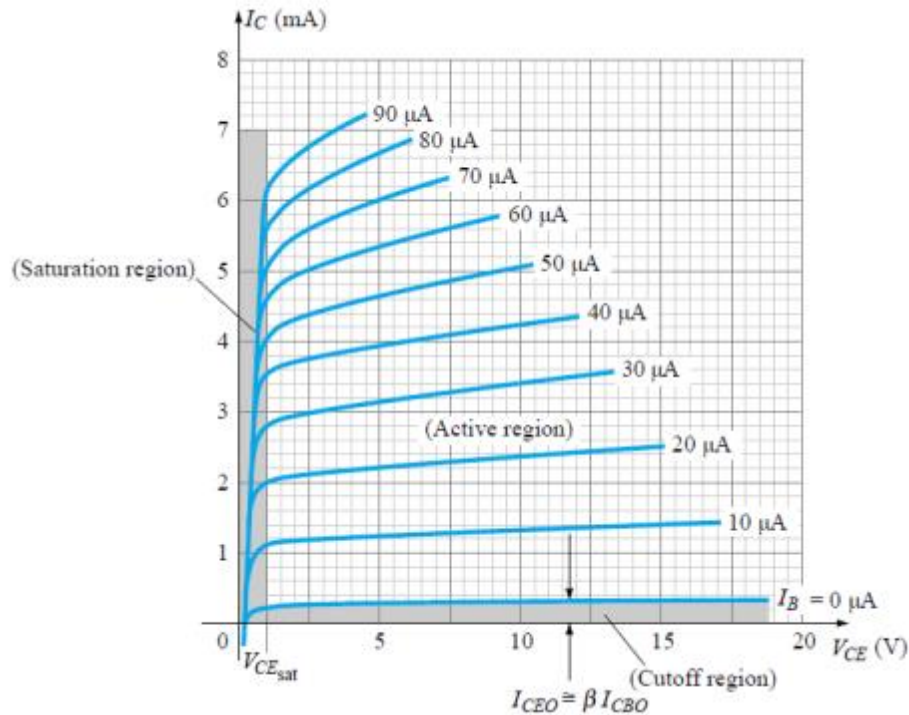

Collector Characteristics

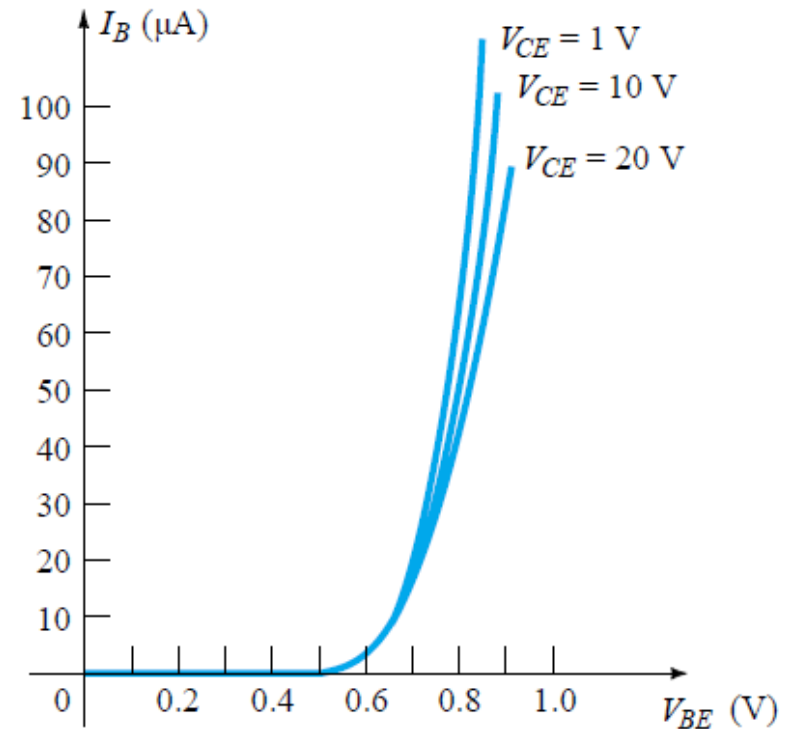

Base Characteristics



## Common-Emitter Amplifier Currents

### Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

### Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

$I_{CBO}$  is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When  $I_B = 0 \mu\text{A}$  the transistor is in cutoff, but there is some minority current flowing called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$



## Beta ( $\beta$ )

- $\beta$  represents the amplification factor of a transistor. ( $\beta$  is sometimes referred to as  $h_{fe}$ , a term used in transistor modeling calculations)
- In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

- In AC mode:

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE} = \text{constant}}$$





# Common-Emitter Configuration

## Beta ( $\beta$ )

Determining  $\beta$  from a Graph


$$\beta_{AC} = \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu\text{A} - 20 \mu\text{A})}$$

$$= \frac{1 \text{ mA}}{10 \mu\text{A}} \Big|_{V_{CE}=7.5}$$

$$= 100$$

$$\beta_{DC} = \frac{2.7 \text{ mA}}{25 \mu\text{A}} \Big|_{V_{CE}=7.5}$$

$$= 108$$

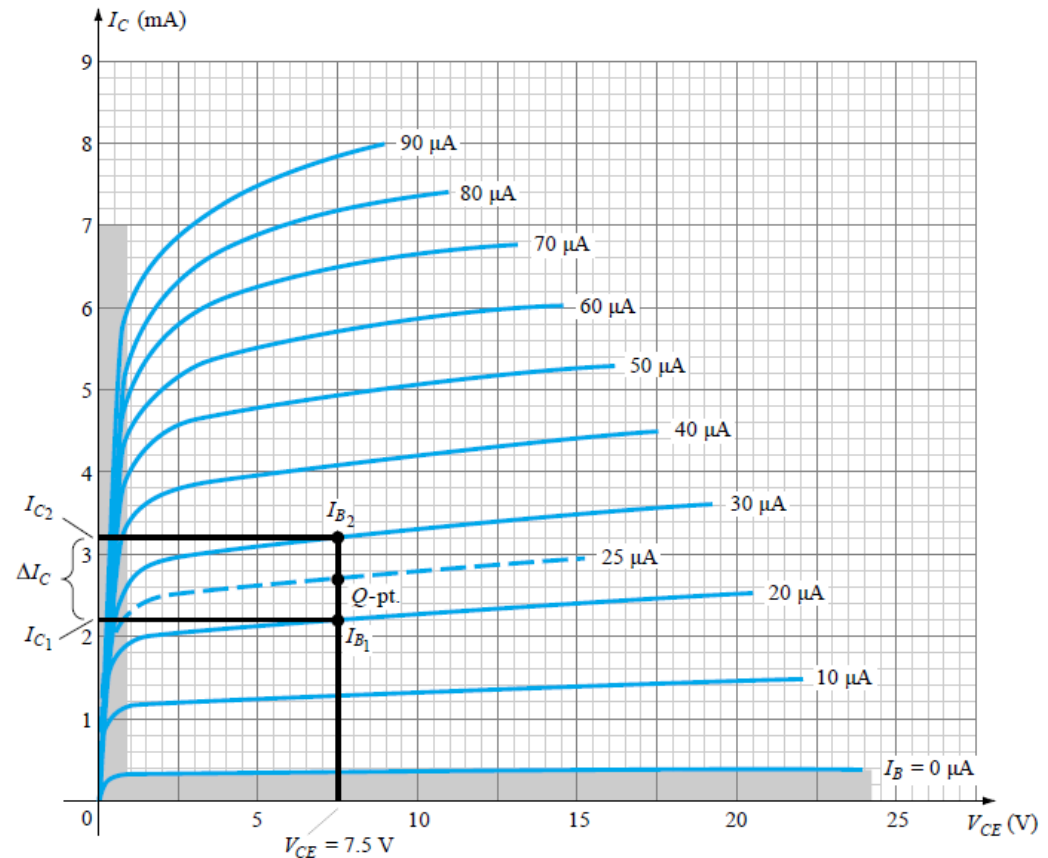

## Beta ( $\beta$ )

- Relationship between amplification factors  $\beta$  and  $\alpha$

$$\alpha = \frac{\beta}{\beta + 1} \qquad \beta = \frac{\alpha}{\alpha - 1}$$


- Relationship Between Currents

$$I_C = \beta I_B \qquad I_E = (\beta + 1) I_B$$






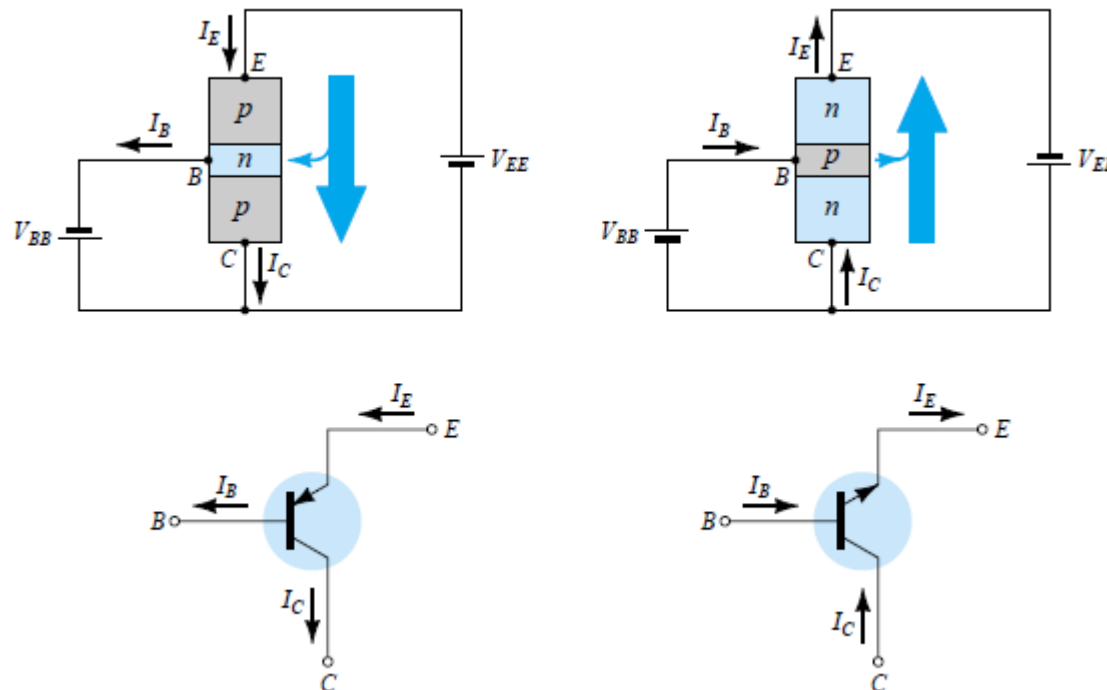
# Common-Collector Configuration

The input is on the base and the output is on the emitter.



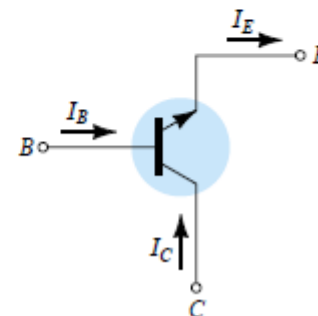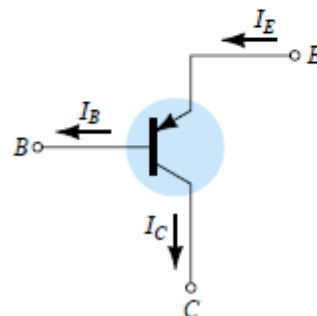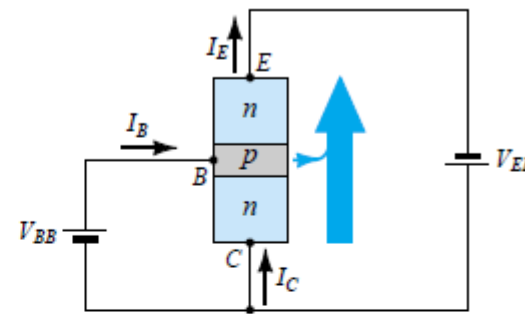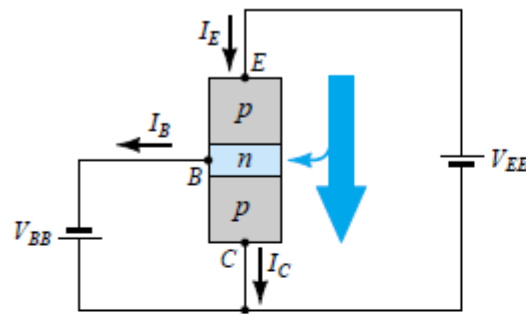
# Common-Collector Configuration

The input is on the base and the output is on the emitter.



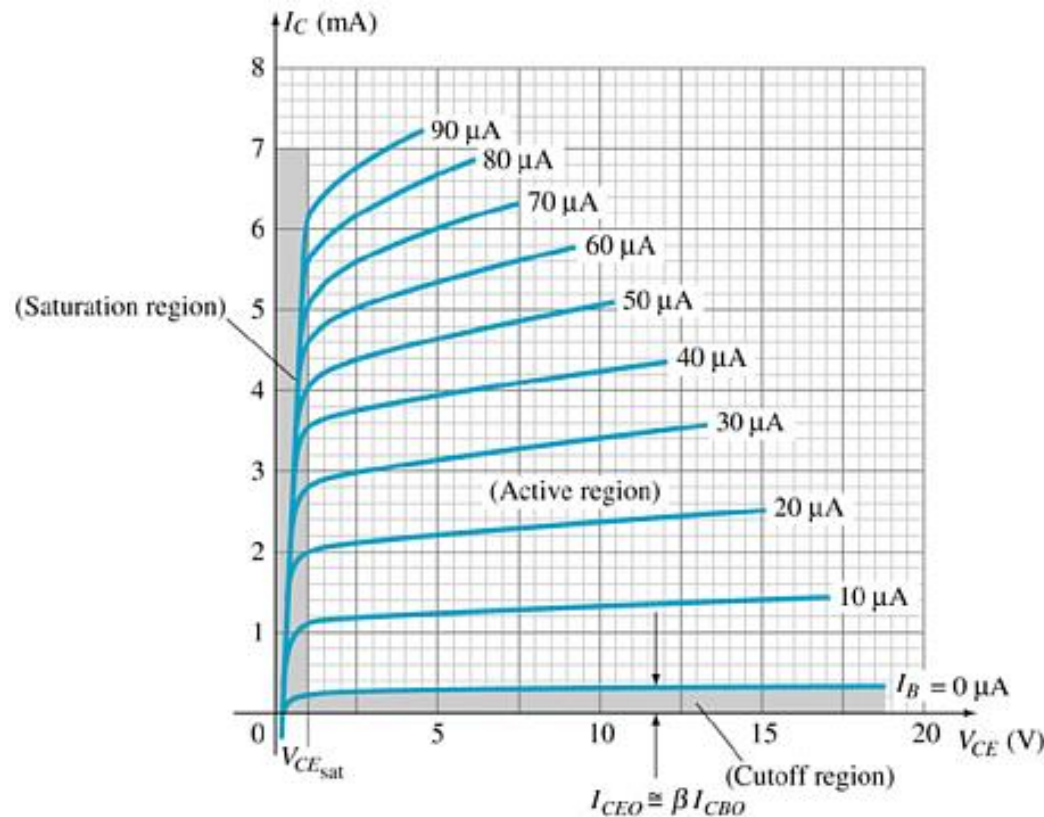
# Common-Collector Configuration

- The characteristics are similar to those of the common-emitter configuration, except the vertical axis is  $I_E$ .


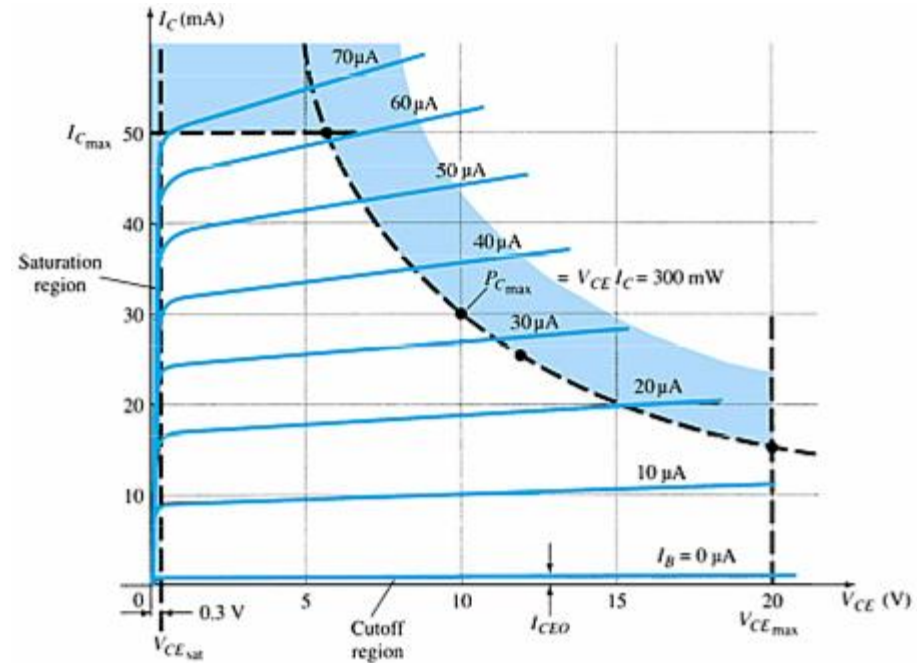
# Limits Of Operations

- ❑  $V_{CE}$  is at maximum and  $I_C$  is at minimum ( $I_{Cmax} = I_{CEO}$ ) in the cutoff region.
- ❑  $I_C$  is at maximum and  $V_{CE}$  is at minimum ( $V_{CEmax} = V_{CEsat} = V_{CEO}$ ) in the saturation region.
- ❑ The transistor operates in the active region between saturation and cutoff.



## Power Dissipation

Common-base:

$$P_{C \max} = V_{CB} I_C$$

Common-emitter:

$$P_{C \max} = V_{CE} I_C$$

Common-collector:

$$P_{C \max} = V_{CE} I_E$$




# Transistor Specification Sheet

## MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	$V_{CE0}$	30	Vdc
Collector-Base Voltage	$V_{CB0}$	40	Vdc
Emitter-Base Voltage	$V_{EB0}$	5.0	Vdc
Collector Current – Continuous	$I_C$	200	mA dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	$T_J, T_{stg}$	-55 to +150	°C

## THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C/W

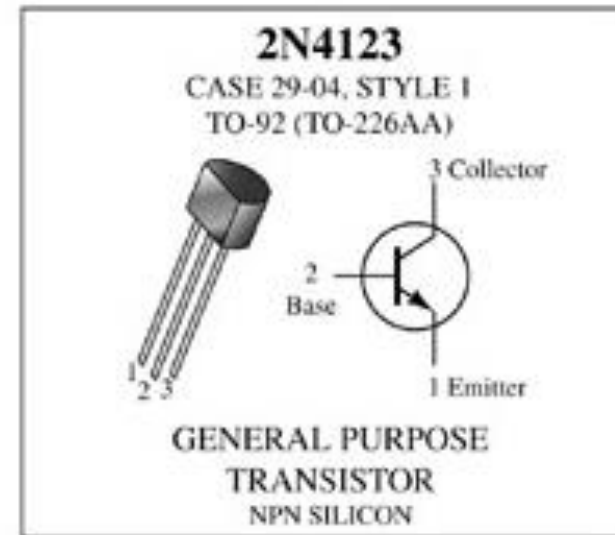



# Transistor Specification Sheet

## ELECTRICAL CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
<b>OFF CHARACTERISTICS</b>				
Collector-Emitter Breakdown Voltage (1) ( $I_C = 1.0\text{ mAdc}$ , $I_E = 0$ )	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ( $I_C = 10\text{ }\mu\text{Adc}$ , $I_E = 0$ )	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ( $I_E = 10\text{ }\mu\text{Adc}$ , $I_C = 0$ )	$V_{(BR)EBO}$	5.0	–	Vdc
Collector Cutoff Current ( $V_{CE} = 20\text{ Vdc}$ , $I_E = 0$ )	$I_{CBO}$	–	50	nAdc
Emitter Cutoff Current ( $V_{BE} = 3.0\text{ Vdc}$ , $I_C = 0$ )	$I_{EBO}$	–	50	nAdc
<b>ON CHARACTERISTICS</b>				
DC Current Gain(1) ( $I_C = 2.0\text{ mAdc}$ , $V_{CE} = 1.0\text{ Vdc}$ ) ( $I_C = 50\text{ mAdc}$ , $V_{CE} = 1.0\text{ Vdc}$ )	$h_{FE}$	50 25	150 –	–
Collector-Emitter Saturation Voltage(1) ( $I_C = 50\text{ mAdc}$ , $I_B = 5.0\text{ mAdc}$ )	$V_{CE(sat)}$	–	0.3	Vdc
Base-Emitter Saturation Voltage(1) ( $I_C = 50\text{ mAdc}$ , $I_B = 5.0\text{ mAdc}$ )	$V_{BE(sat)}$	–	0.95	Vdc
<b>SMALL-SIGNAL CHARACTERISTICS</b>				
Current-Gain – Bandwidth Product ( $I_C = 10\text{ mAdc}$ , $V_{CE} = 20\text{ Vdc}$ , $f = 100\text{ MHz}$ )	$f_T$	250		MHz
Output Capacitance ( $V_{CE} = 5.0\text{ Vdc}$ , $I_E = 0$ , $f = 100\text{ MHz}$ )	$C_{obo}$	–	4.0	pF
Input Capacitance ( $V_{BE} = 0.5\text{ Vdc}$ , $I_C = 0$ , $f = 100\text{ kHz}$ )	$C_{ibo}$	–	8.0	pF
Collector-Base Capacitance ( $I_E = 0$ , $V_{CB} = 5.0\text{ V}$ , $f = 100\text{ kHz}$ )	$C_{ob}$	–	4.0	pF
Small-Signal Current Gain ( $I_C = 2.0\text{ mAdc}$ , $V_{CE} = 10\text{ Vdc}$ , $f = 1.0\text{ kHz}$ )	$h_{fe}$	50	200	–
Current Gain – High Frequency ( $I_C = 10\text{ mAdc}$ , $V_{CE} = 20\text{ Vdc}$ , $f = 100\text{ MHz}$ ) ( $I_C = 2.0\text{ mAdc}$ , $V_{CE} = 10\text{ V}$ , $f = 1.0\text{ kHz}$ )	$h_{fe}$	2.5 50	– 200	–
Noise Figure ( $I_C = 100\text{ }\mu\text{Adc}$ , $V_{CE} = 5.0\text{ Vdc}$ , $R_S = 1.0\text{ k ohm}$ , $f = 1.0\text{ kHz}$ )	NF	–	6.0	dB

(1) Pulse Test: Pulse Width = 300  $\mu\text{s}$ . Duty Cycle = 2.0%



# Transistor Specification Sheet

