

BCN1043

COMPUTER ARCHITECTURE & ORGANIZATION

By
Dr. Mritha Ramalingam

Faculty of Computer Systems & Software Engineering
mritha@ump.edu.my

<http://ocw.ump.edu.my/>



CAO – Chapter 3 – P2. Mritha Ramalingam

AUTHORS

- **Dr. Mohd Nizam Mohmad Kahar** (mnizam@ump.edu.my)
- **Jamaludin Sallim** (jamal@ump.edu.my)
- **Dr. Syafiq Fauzi Kamarulzaman** (syafiq29@ump.edu.my)
- **Dr. Mritha Ramalingam** (mritha@ump.edu.my)

Faculty of Computer Systems & Software Engineering

BCN1043

COMPUTER ARCHITECTURE & ORGANIZATION



Chapter 3 continues...



SIMPLIFICATION


Simplification of Boolean function

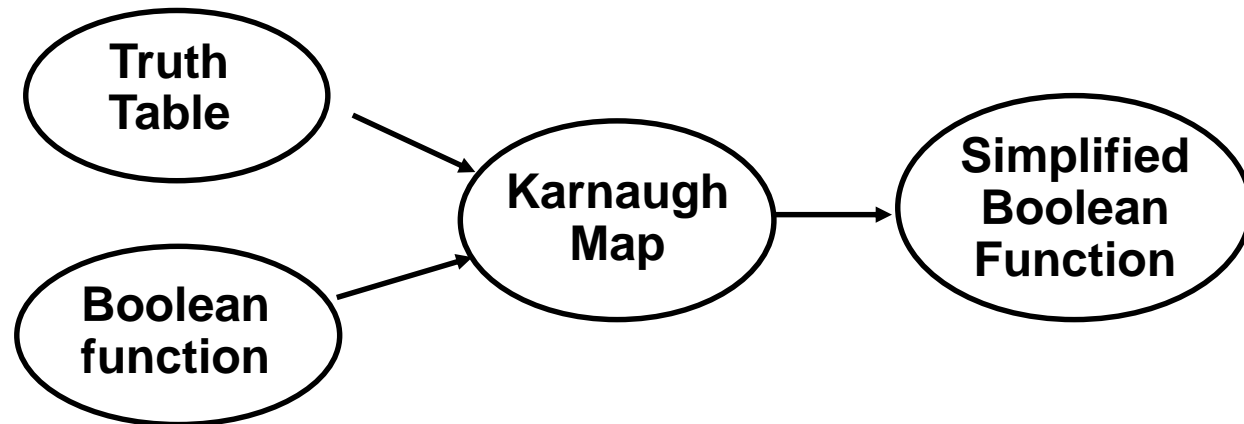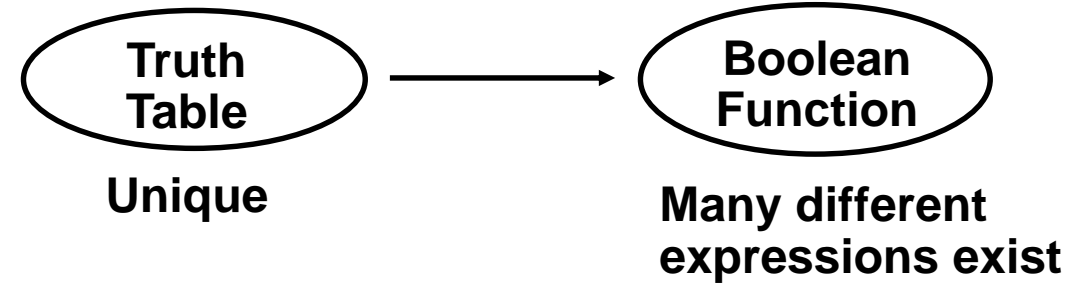- Reducing to lesser number of Boolean literals
- for least cost implementation
- Karnaugh Map (K-map) is a tabular method to reduce Boolean expressions.





SIMPLIFICATION: KARNAUGH MAP

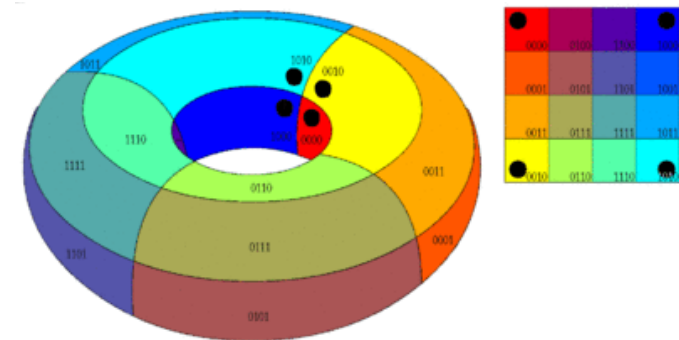

K-map Terminology

- K-map is a tabular method derived from output values of Boolean function.
- *minterm* is a product term with all possible combinations of input variables
- E.g
- minterms of an expression with inputs x and y :

$\bar{x}\bar{y}$, $\bar{x}y$, $x\bar{y}$, and xy


Minterm	X	Y
$\bar{x}\bar{y}$	0	0
$\bar{x}y$	0	1
$x\bar{y}$	1	0
xy	1	1

- Minterms with three inputs

Minterm	X	Y	Z
$\bar{X}\bar{Y}\bar{Z}$	0	0	0
$\bar{X}\bar{Y}Z$	0	0	1
$\bar{X}Y\bar{Z}$	0	1	0
$\bar{X}YZ$	0	1	1
$X\bar{Y}\bar{Z}$	1	0	0
$X\bar{Y}Z$	1	0	1
$XY\bar{Z}$	1	1	0
XYZ	1	1	1

K-map

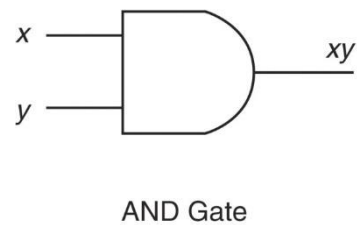- K-map is referred as a cell for each minterm.
- truth table and k-map of function $F(x,y) = xy$ is shown below



$F(X, Y) = XY$


X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1



	Y	0	1
X			
0		0	0
1		0	1

K-map

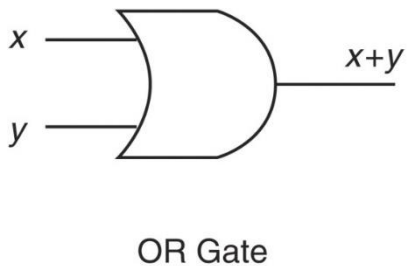- E.g.2, $F(x,y) = x + y$
- Similar to **OR** gate



$F(X, Y) = X + Y$		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1



X \ Y	0	1
0	0	1
1	1	1



X \ Y	0	1
0	0	1
1	1	1

$$F(x, y) = x + y = \bar{x}y + x\bar{y} + xy$$

$$F(x,y) = x + y$$

Kmap Simplification for Two Variables

rules for simplification :

- Group can contain only 1s; no 0s.
- Groups can occur only at right angles; no diagonal groups.
- In a group, number of 1s must be a power of 2
- Groups need to be as large as possible.
- Groups can overlap and wrap around the sides of the Kmap.

3-variable K-map Simplification

X \ YZ	00	01	11	10
0	$\bar{X}\bar{Y}\bar{Z}$	$\bar{X}\bar{Y}Z$	$\bar{X}YZ$	$\bar{X}Y\bar{Z}$
1	$X\bar{Y}\bar{Z}$	$X\bar{Y}Z$	XYZ	$XY\bar{Z}$

3-variable K-map Simplification

- E.g:

$$F(X, Y, Z) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

What could be the largest group of 1s?

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	1	0

3-variable K-map Simplification

- Simplified Boolean function, $F(x) = z$.

$$F(x, y) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$$

X \ YZ	00	01	11	10
0	0	1	1	0
1	0	1	1	0

3-variable K-map Simplification

- E.g:

$$F(X, Y, Z) = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z}$$

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

3-variable K-map Simplification

- E.g of side wrapping groups.

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

The K-map shows two groups of 1s: a green group of four 1s in the top row (YZ=00, 01, 11, 10) and a pink group of two 1s in the first and last columns (YZ=00 and 10) across both rows (X=0 and 1). The pink group illustrates side wrapping.

3-variable K-map Simplification

- Simplified function is: $F(X, Y, Z) = \bar{X} + \bar{Z}$

X \ YZ	00	01	11	10
0	1	1	1	1
1	1	0	0	1

4-variable K-map Simplification

- With four variables, k-map can use 16 minterms

		YZ			
		00	01	11	10
WX	00	$\bar{W}\bar{X}\bar{Y}\bar{Z}$	$\bar{W}\bar{X}\bar{Y}Z$	$\bar{W}\bar{X}YZ$	$\bar{W}\bar{X}Y\bar{Z}$
	01	$\bar{W}X\bar{Y}\bar{Z}$	$\bar{W}X\bar{Y}Z$	$\bar{W}XYZ$	$\bar{W}XY\bar{Z}$
	11	$WX\bar{Y}\bar{Z}$	$WX\bar{Y}Z$	$WXYZ$	$WXY\bar{Z}$
	10	$W\bar{X}\bar{Y}\bar{Z}$	$W\bar{X}\bar{Y}Z$	$W\bar{X}YZ$	$W\bar{X}Y\bar{Z}$

4-variable K-map Simplification

$$F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}Y\bar{Z} \\ + \bar{W}XY\bar{Z} + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}\bar{Y}Z + W\bar{X}Y\bar{Z} + WXY\bar{Z}$$

WX \ YZ	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

4-variable K-map Simplification

- three groups
- So we will have three terms in simplified function:

$$F(W, X, Y, Z) = \bar{W}\bar{Y} + \bar{X}\bar{Z} + \bar{W}YZ$$

WX \ YZ	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

4-variable K-map Simplification

- E.g of group formation

WX \ YZ	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

Groupings in the K-map:

- A vertical group of four 1s in the 00 column (WX 00, 01, 11, 10) is circled in green.
- A vertical group of three 1s in the 11 column (WX 00, 01, 11) is circled in blue.
- A horizontal group of two 1s in the 01 row (WX 00, 01) is circled in pink.
- A horizontal group of two 1s in the 10 row (WX 01, 10) is circled in pink.

WX \ YZ	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

Groupings in the K-map:

- A vertical group of four 1s in the 00 column (WX 00, 01, 11, 10) is circled in blue.
- A vertical group of two 1s in the 11 column (WX 00, 01) is circled in green.
- A horizontal group of two 1s in the 01 row (WX 01, 10) is circled in pink.

Don't Care Conditions

- a circuit is designed in such a way that any particular input sets will never happen- *don't care* condition.
- Used while grouping for simplification

Don't Care Conditions

- Denoted by X or “d” in the K-map cell

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

- E.g:

$$F(W, X, Y, Z) = \bar{W}\bar{Y} + YZ$$

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

- E.g:

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

- truth table of: $F(W, X, Y, Z) = \bar{W}\bar{Y} + YZ$

differs from the truth table of: $F(W, X, Y, Z) = \bar{W}Z + YZ$

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Will continue...



