

BEE2143 – Signals & Networks

Chapter 9 – Filters

Raja M. Taufika R. Ismail

Universiti Malaysia Pahang

October 5, 2017



Introduction

Types of filters

Decibel scale

The cutoff frequency

Frequency response: Bode plot


Reference

Introduction


- ▶ A filter is a circuit that is designed to pass signals with desired frequency and reject others.
- ▶ Passive filters: consists only passive elements (R , L and C)
- ▶ Active filters: consists of active elements (transistors, op-amps, etc.)

Types of filters

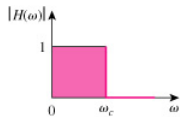
1. Lowpass filter: passes LF and rejects HF
2. Highpass filter: passes HF and rejects LF
3. Bandpass filter: passes frequencies within a frequency band and blocks frequencies outside the band
4. Bandstop filter: passes frequencies outside a frequency band and blocks frequencies within the band




(a)

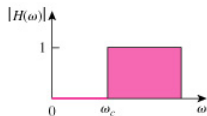


(b)

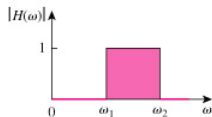

(c)

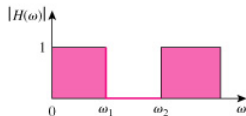(d)
5

Typical lowpass filter

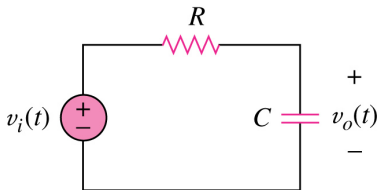

The transfer function is

$$\mathbf{H}(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$

or

$$\mathbf{H}(\omega) = \frac{1}{1 + j\omega RC}$$


Typical lowpass filter (cont.)

The magnitude of $\mathbf{H}(\omega)$ is


$$H(\omega) = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

The value of $H(\omega)$ at zero and large frequencies are respectively
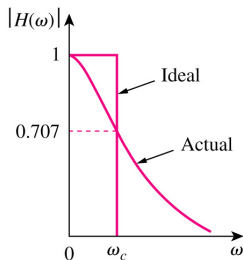
$$H(0) = 1 \quad \text{and} \quad H(\infty) = 0$$



Typical highpass filter

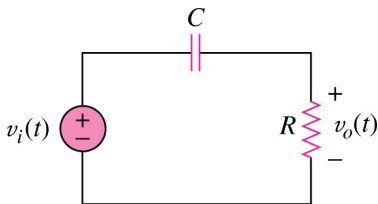

The transfer function is

$$\mathbf{H}(s) = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC}$$

or

$$\mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$


Typical highpass filter (cont.)

The magnitude of $\mathbf{H}(\omega)$ is


$$H(\omega) = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

The value of $H(\omega)$ at zero and large frequencies are respectively
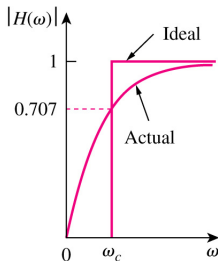
$$H(0) = 0 \quad \text{and} \quad H(\infty) = 1$$



Typical bandpass filter

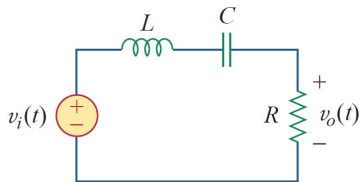

The transfer function is

$$\mathbf{H}(s) = \frac{R}{R + sL + \frac{1}{sC}}$$

or

$$\mathbf{H}(\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$


Typical bandpass filter (cont.)

The magnitude of $\mathbf{H}(\omega)$ is


$$H(\omega) = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

The value of $H(\omega)$ at zero and large frequencies are respectively
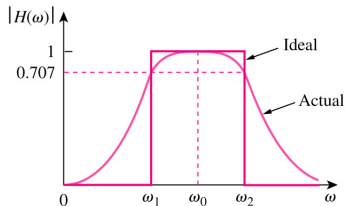
$$H(0) = 0 \quad \text{and} \quad H(\infty) = 0$$



Typical bandstop filter

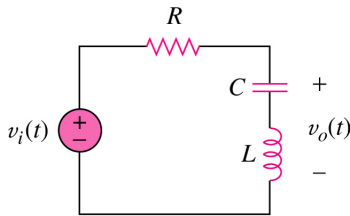

The transfer function is

$$\mathbf{H}(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}}$$

or

$$\mathbf{H}(\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\left(\omega L - \frac{1}{\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$


Typical bandstop filter (cont.)

The magnitude of $\mathbf{H}(\omega)$ is

$$H(\omega) = \frac{\left| \omega L - \frac{1}{\omega C} \right|}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$

The value of $H(\omega)$ at zero and large frequencies are respectively
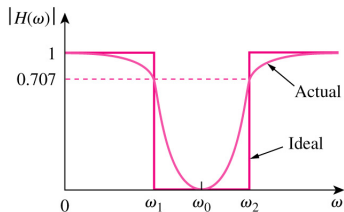
$$H(0) = 1 \quad \text{and} \quad H(\infty) = 1$$



Decibel scale

- ▶ Power gain is defined as

$$\text{Gain} = \frac{P_2}{P_1} = \frac{V_2^2}{V_1^2} = \left(\frac{V_2}{V_1}\right)^2 = H^2$$

- ▶ In bels,

$$\begin{aligned}\text{Gain} &= \log \frac{P_2}{P_1} \text{ bel} \\ &= 10 \log \frac{P_2}{P_1} \text{ decibel (dB)}\end{aligned}$$

- ▶ Substituting $P_1 = V_1^2$ and $P_2 = V_2^2$ in the last equation gives

$$\begin{aligned}\text{Gain} &= 10 \log \left(\frac{V_2}{V_1} \right)^2 \text{ dB} \\ &= 20 \log \frac{V_2}{V_1} \text{ dB} \\ &= 20 \log H \text{ dB}\end{aligned}$$

The cutoff frequency

- ▶ The cutoff frequency (also known as the half power frequency) is the frequency which the power gain is half of the maximum gain
- ▶ The cutoff frequency occurs when

$$\text{Gain} = \frac{\text{Gain}_{\max}}{2}$$

$$H^2 = \frac{H_{\max}^2}{2}$$


$$H = \frac{H_{\max}}{\sqrt{2}}$$

- ▶ Or in dB, the cutoff frequency occurs when

$$\begin{aligned}20 \log H &= 20 \log \left(\frac{H_{\max}}{\sqrt{2}} \right) \\ &= 20 \log H_{\max} - 20 \log \sqrt{2} \\ H_{\text{dB}} &\approx H_{\max(\text{dB})} - 3 \text{ dB}\end{aligned}$$

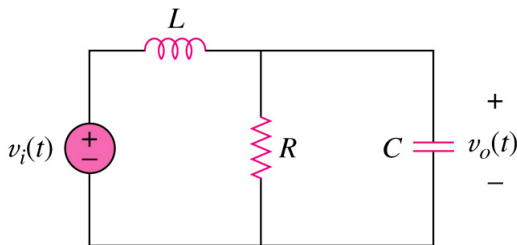Example 14.10, pg. 640 (Alexander & Sadiku, 2009)


Determine what type of filter is shown in Fig. 14.39. Calculate the corner or cutoff frequency. Take $R = 2 \text{ k}\Omega$, $L = 2 \text{ H}$ and $C = 2 \text{ }\mu\text{F}$.




Answer: Lowpass filter, $\omega_c = 742 \text{ rad/s}$.

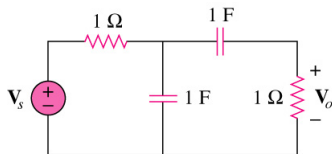Problem 14.57, pg. 669 (Alexander & Sadiku, 2009)

Determine the center frequency and bandwidth of the bandpass filters in Fig. 14.88.



(a)

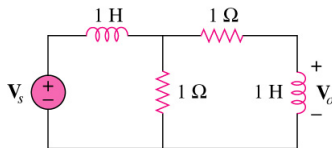

(b)

Answer: 1 rad/s, 3 rad/s

Frequency response: Bode plot

- ▶ A transfer function can be expressed as the combination of factors such that

$$\mathbf{H}(s) = \frac{As(s + z_1)(s + z_2) \dots (s^2 + 2\zeta_1\omega_k s + \omega_k^2) \dots}{(s + p_1)(s + p_2) \dots (s^2 + 2\zeta_2\omega_n s + \omega_n^2) \dots}$$

$$\mathbf{H}(\omega) = \frac{Aj\omega(j\omega + z_1)(j\omega + z_2) \dots ((j\omega)^2 + j2\zeta_1\omega_k\omega + \omega_k^2) \dots}{(j\omega + p_1)(j\omega + p_2) \dots ((j\omega)^2 + j2\zeta_2\omega_n\omega + \omega_n^2) \dots}$$

- ▶ The magnitude of $\mathbf{H}(\omega)$ is

$$H(\omega) = \frac{A|\omega||j\omega + z_1||j\omega + z_2| \dots |(j\omega)^2 + j2\zeta_1\omega_k\omega + \omega_k^2| \dots}{|j\omega + p_1||j\omega + p_2| \dots |(j\omega)^2 + j2\zeta_2\omega_n\omega + \omega_n^2| \dots}$$

► or




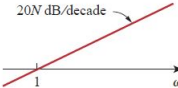





$$H(\omega) = \frac{K|\omega| \left| 1 + \frac{j\omega}{z_1} \right| \left| 1 + \frac{j\omega}{z_2} \right| \dots \left| 1 + \frac{j2\zeta_1\omega}{\omega_k} + \left(\frac{j\omega}{\omega_k} \right)^2 \right| \dots}{\left| 1 + \frac{j\omega}{p_1} \right| \left| 1 + \frac{j\omega}{p_2} \right| \dots \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right| \dots}$$


► or in dB

$$\begin{aligned} H_{\text{dB}}(\omega) &= 20 \log K + 20 \log |\omega| + 20 \log \left| 1 + \frac{j\omega}{z_1} \right| + \dots \\ &+ 20 \log \left| 1 + \frac{j2\zeta_1\omega}{\omega_k} + \left(\frac{j\omega}{\omega_k} \right)^2 \right| \dots - 20 \log \left| 1 + \frac{j\omega}{p_1} \right| - \\ &- \dots - 20 \log \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right| \dots \end{aligned}$$

- and the phase of $\mathbf{H}(\omega)$ is
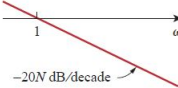
$$\begin{aligned} \angle H(\omega) = & 90^\circ + \tan^{-1} \left(\frac{\omega}{z_1} \right) + \tan^{-1} \left(\frac{2\zeta_1\omega/\omega_k}{1 - (\omega/\omega_k)^2} \right) + \dots \\ & - \tan^{-1} \left(\frac{\omega}{p_1} \right) - \tan^{-1} \left(\frac{2\zeta_2\omega/\omega_n}{1 - (\omega/\omega_n)^2} \right) + \dots \end{aligned}$$

Factor	Magnitude	Phase
K	$20 \log_{10} K$  	0° 
$(j\omega)^N$	$20N \text{ dB/decade}$  	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$  	$-90N^\circ$ 


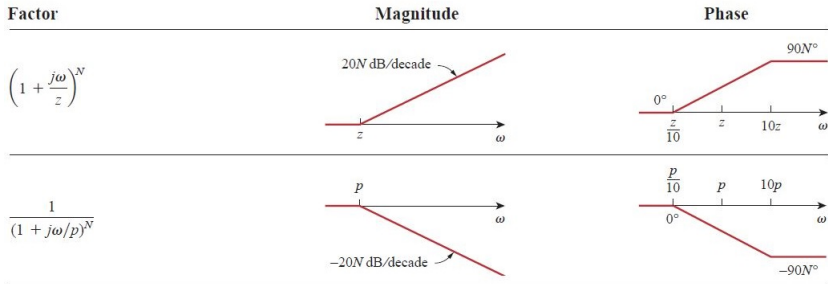


Factor



Magnitude

Phase
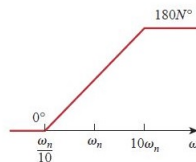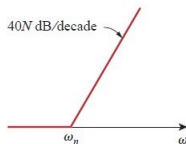
$$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2 \right]^N$$



$$\frac{1}{\left[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2 \right]^N}$$

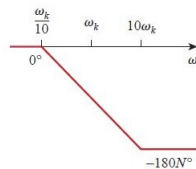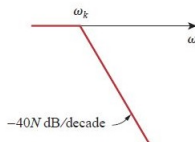



Example 14.3, pg. 624 (Alexander & Sadiku, 2009)

Construct the Bode plots for the transfer function

$$\mathbf{H}(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$

Example 14.3, pg. 624 (cont.)

Answer:

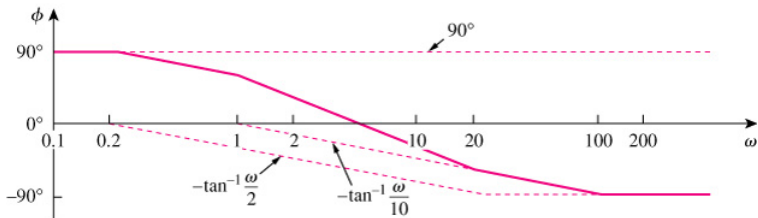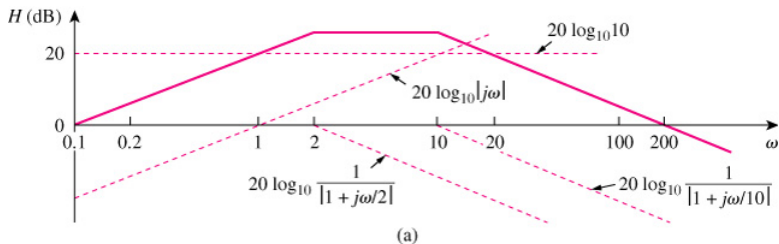

List of References

1. C.K. Alexander and M.N.O. Sadiku (2009), Fundamentals of Electric Circuits 4th ed., New York: McGraw-Hill.