

BEE1133 Circuit Analysis

Chapter 1A Basic Concept

by

Nor Rul Hasma Abdullah
Faculty of Electrical & Electronics Engineering
hasma@ump.edu.my



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Chapter Description

Aims

This chapter is aimed to:

1. Introduce the basic component related to electric circuit analysis
2. Introduce the SI unit to the students
3. Explain the circuit elements in electric circuit

Expected Outcomes

Student should be able to

1. Recognize the electric circuit component
2. Use the SI unit correctly
3. Explain and recognize the basic circuit element in electric circuit



References

1. C. Alexander and M. Sadiku, "Fundamentals of Electric Circuits", 4th ed., McGraw-Hill, 2008.
2. J. Nilsson and S. Riedel, "Electric Circuits", 8th ed., Prentice Hall, 2008.



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>


BASIC CONCEPT

- 1.1 Introduction of circuit analysis
- 1.2 Electrical quantities: Systems of units, charge, current, voltage, power and energy
- 1.3 Circuit elements: Passive and active elements, independent and dependent sources




1.1 Introduction of circuit analysis

DC characteristics

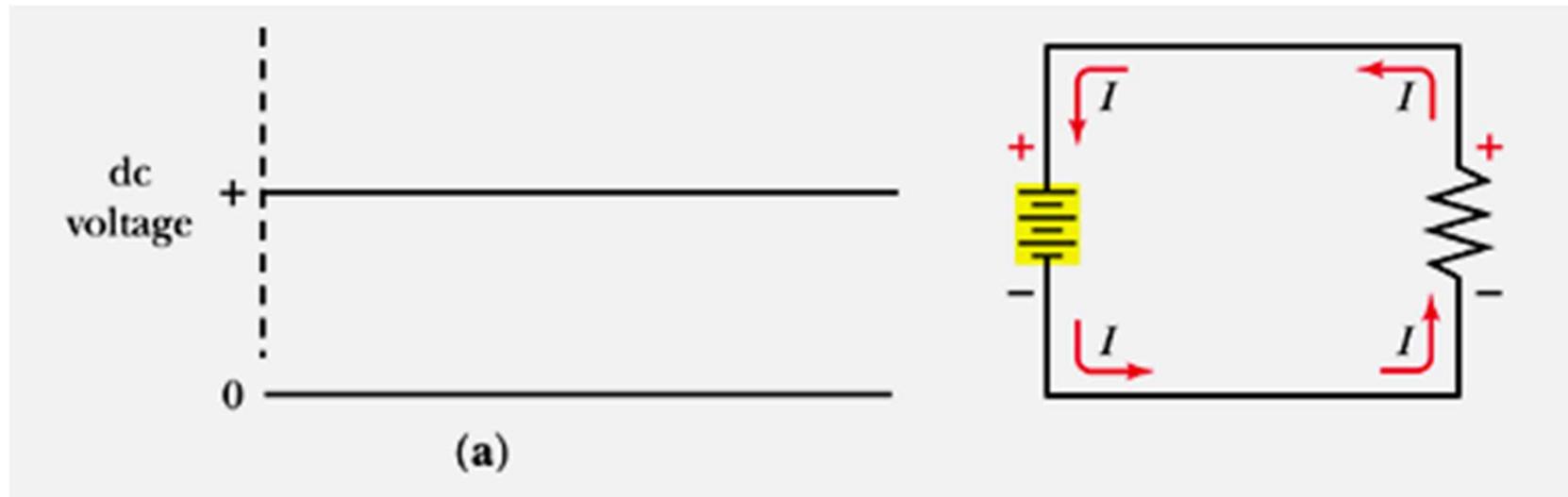


Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

AC characteristics

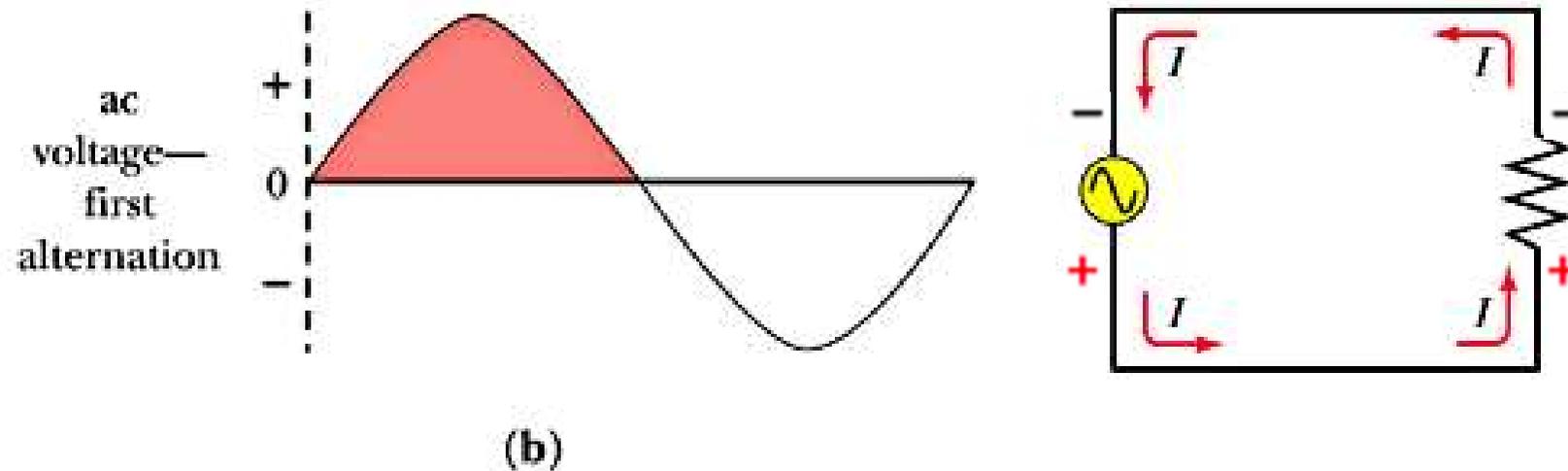

SIMPLE ELECTRIC CIRCUIT

Should consist of

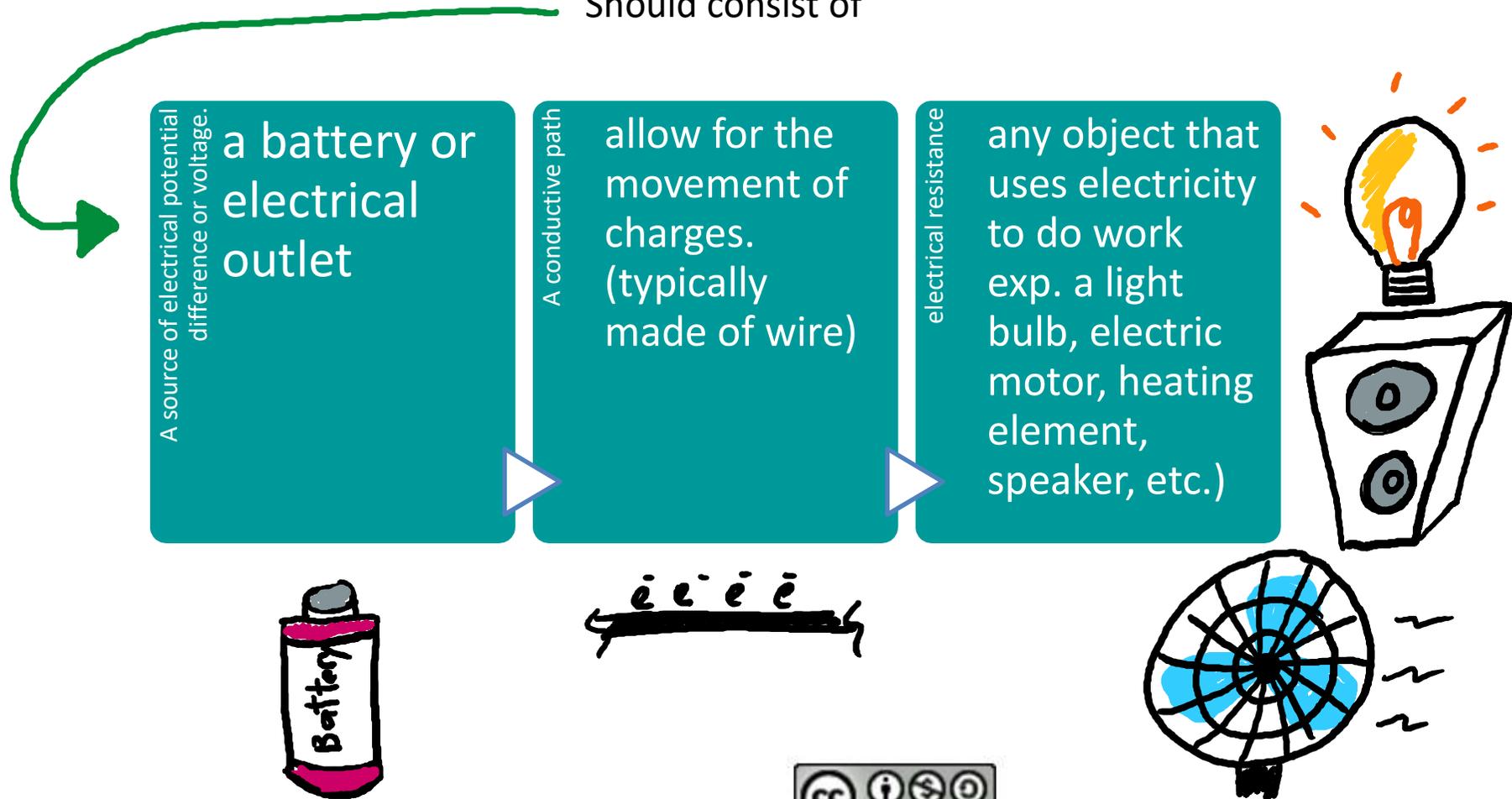

Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>


ELECTRICAL QUANTITIES: SYSTEMS OF UNITS

International System of Units(SI):
International measurement language which enables engineers to communicate their results.


Multiplier	Prefiz	Symbol	Quantity	Basic Units	Symbol
10^{18}	exa	E	Length	meter	m
10^{15}	peta	P	Mass	kilogram	kg
10^{12}	tera	T	Time	Second	S
10^9	giga	G	Electric current	Ampere	A
10^6	mega	M	Thermodynamic temperature	Kelvin	K
10^3	kilo	k	Luminous intensity	Candela	cd
10^2	hecto	h			
10^1	deka	da			
10^0	deci	d			
10^{-1}	centi	c			
10^{-2}	milli	m			
10^{-3}	micro	μ			
10^{-6}	nano	n			
10^{-12}	pico	p			
10^{-15}	femto	f			
10^{-18}	atto	a			



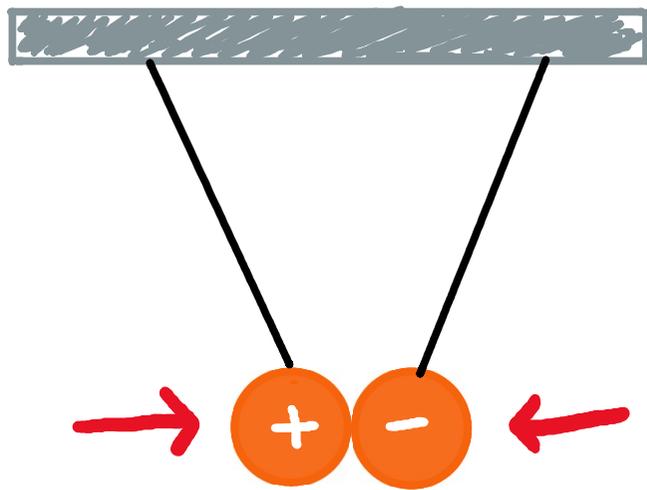Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>



Opposite charge attract

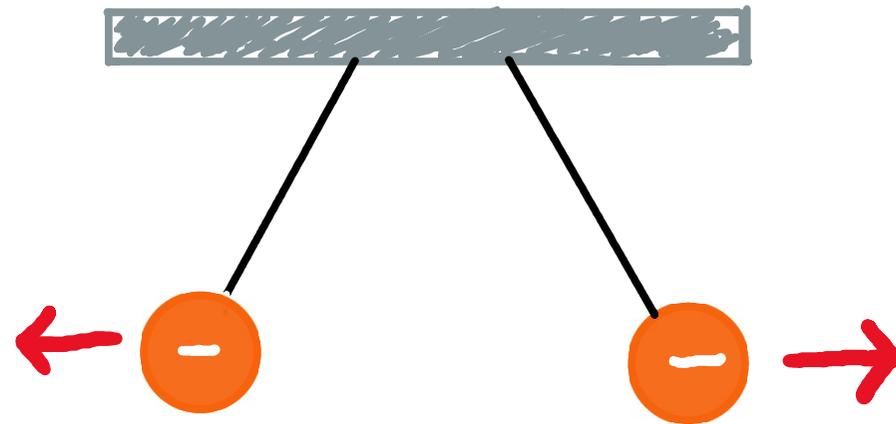


Like charge repel





Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

FORCE FIELDS ASSOCIATED WITH CHARGED PARTICLES

- Lines of force between charges

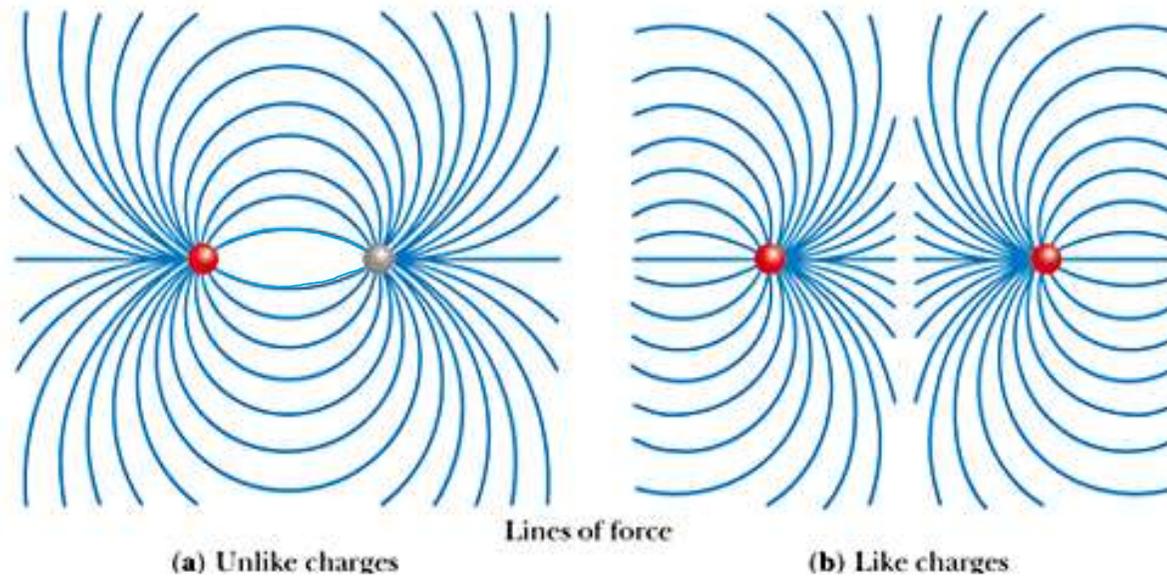



THE UNIT OF CHARGE

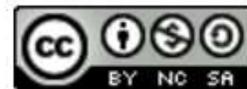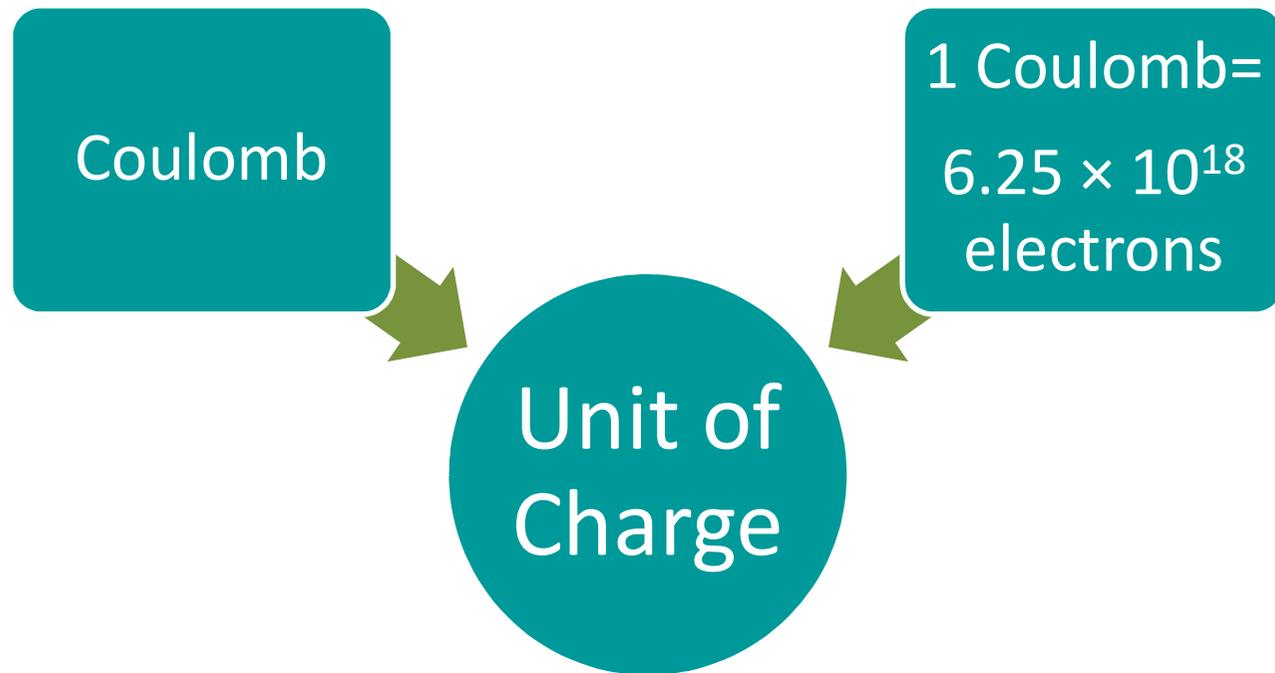

CURRENT FLOW

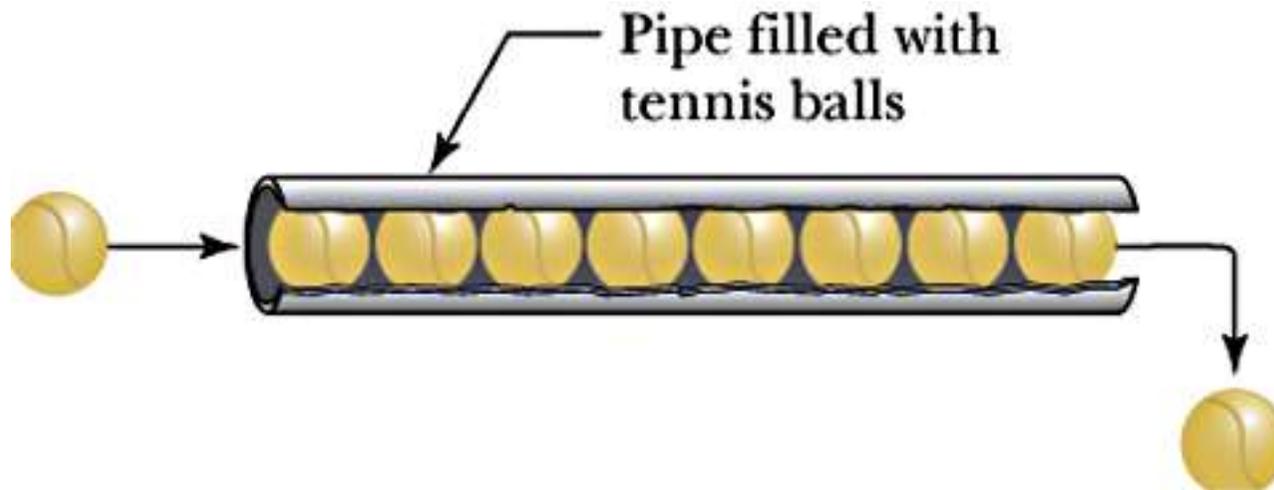- Analogy for the concept of current flow



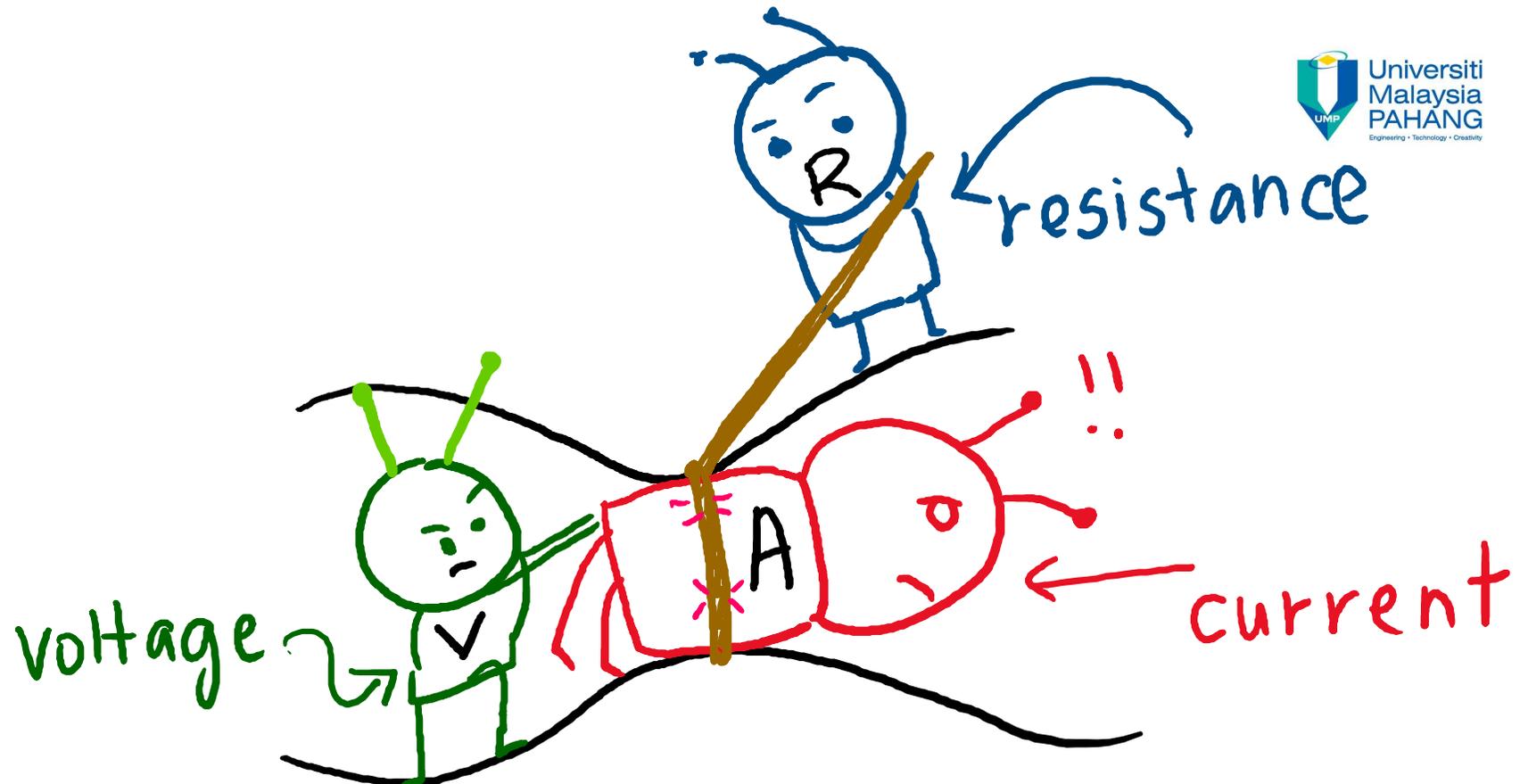

Can you explain ?



CURRENT DEFINITION




$$i = \frac{dq}{dt}$$


i = current flow (amperes)

q = charge (coulombs)

t = time (seconds)

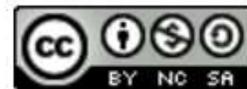



CURRENT FLOW

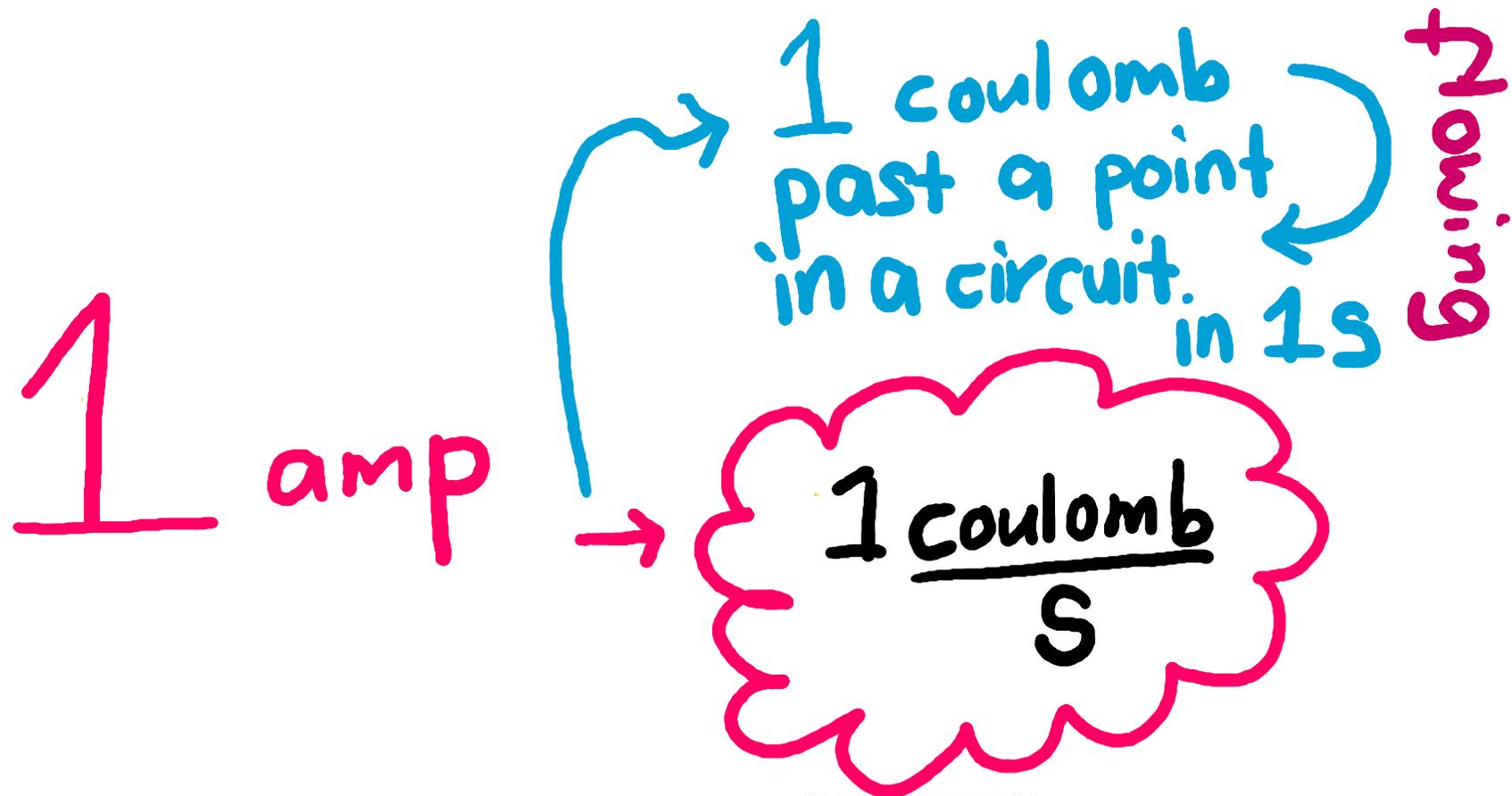



CURRENT

2 Informations

Unit : Ampere

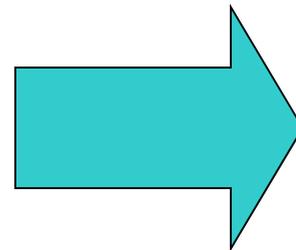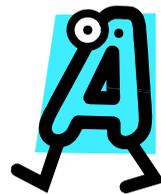

Arrow
Direction of
current flow

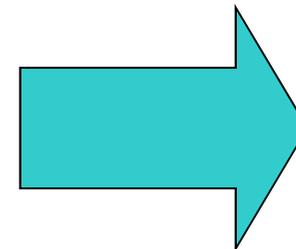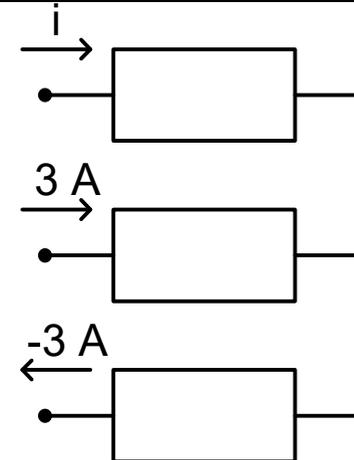

Value
Variable or
a known value


$I \times$
 $20A$



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>


ACTIVE ELEMENT: CURRENT SOURCE

Independent

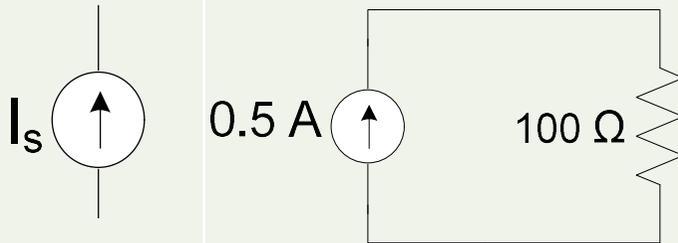

The I_s through the source is completely independent of the voltage across the source

Dependent

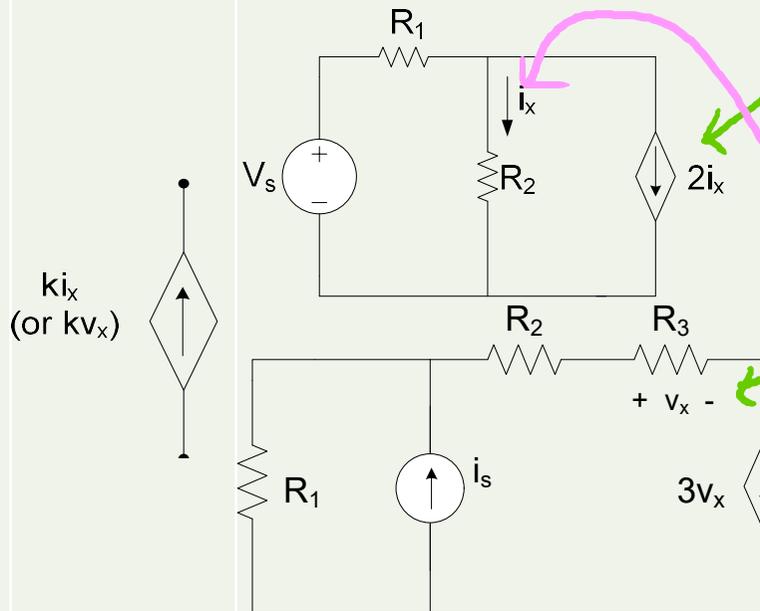

DCS " $2i_x$ " depends on the current " i_x " which is at another location in the circuit.

The value of the current " $3v_x$ " depends on the value of the voltage " v_x "

VOLTAGE

When a current flows through a circuit element, it develops a voltage drop across the terminals of that element.



The voltage across an element is the work (energy W) required to move a unit positive charge from the $-ve$ terminal to the $+ve$ terminal.

$$v = \frac{dw}{dq}$$

When work is linear in the formula reduces to: \rightarrow (here, Q is total charge and W is total work).


$$v = \frac{W}{Q}$$

$$\text{volt} = \text{joule/coulomb or } V = J/C$$

.bdullah


<http://ocw.ump.edu.my/course/view.php?id=251>

VOLTAGE

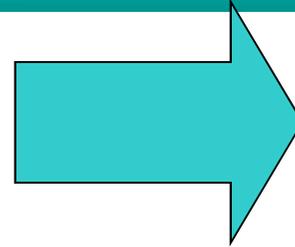


+ / - sign
Voltage
reference direction

2 Informations

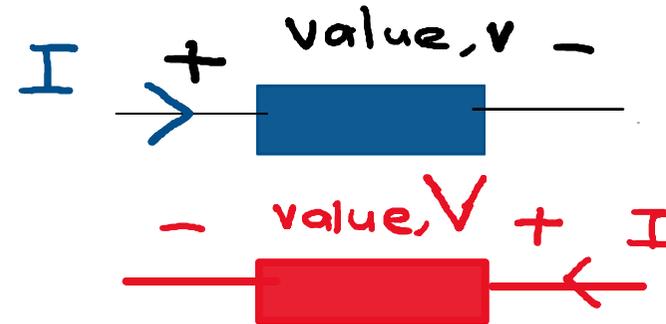

Unit : Volts

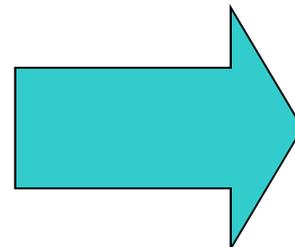



Value
variable or
a known value

V_x
 $I V$




Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

How to identify the voltage value?

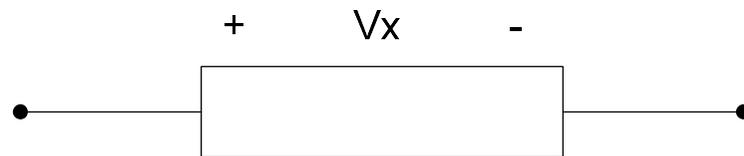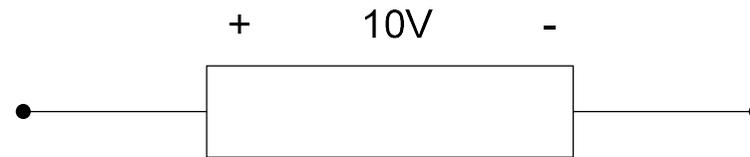


$$V_x = 10 \text{ V}$$

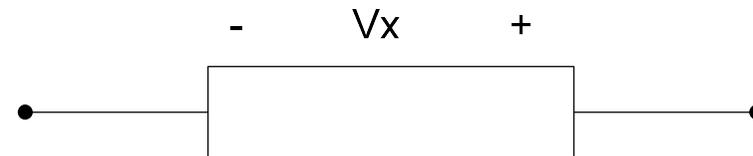


$$V_x = -10 \text{ V}$$



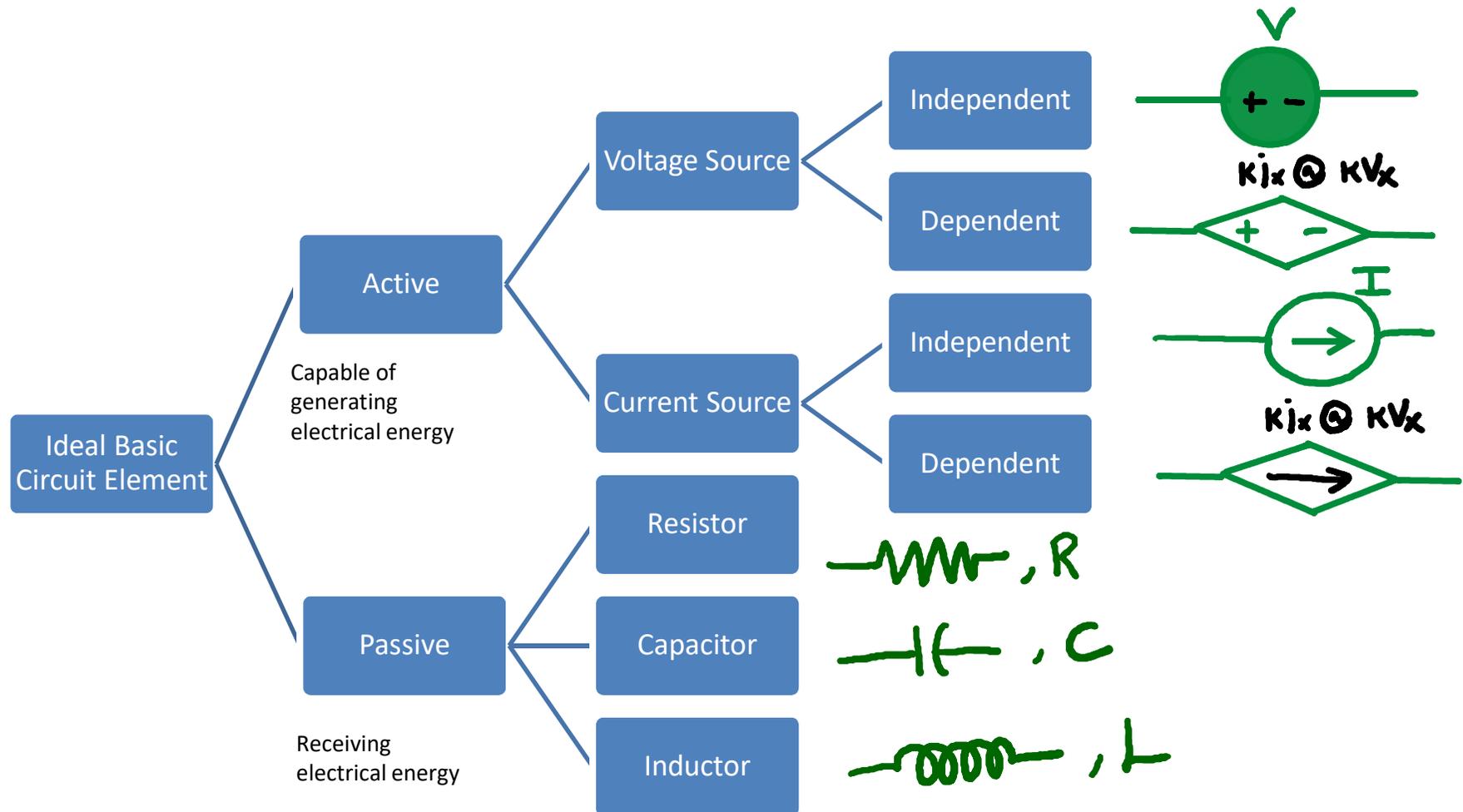

ACTIVE ELEMENT: VOLTAGE SOURCE

Independent

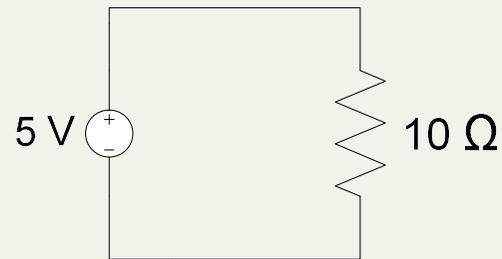


The 5V across the source is completely independent of the current through the source.

Dependent




KV_y
 KI_y

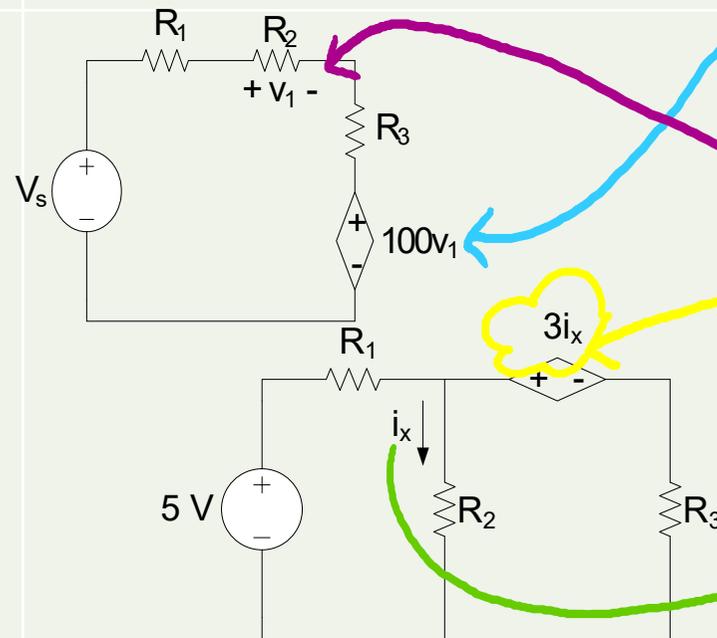

DVS " $100V_1$ " depends on the voltage " V_1 " which is at another location in the circuit.

The value of the voltage " $3i_x$ " depends on the value of the current " i_x ".

Resistors

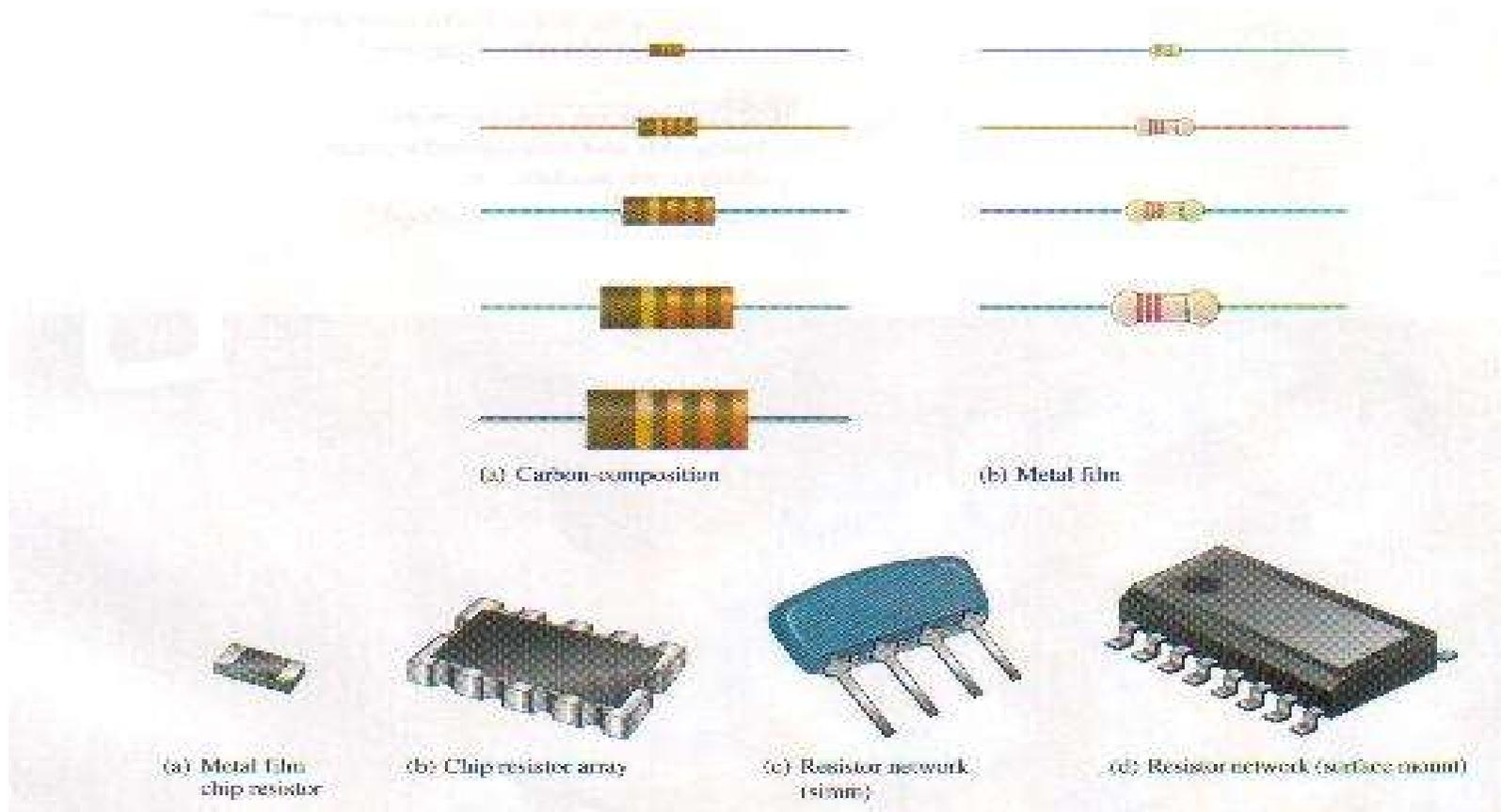


Source
<http://slideplayer.com>



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Capacitors

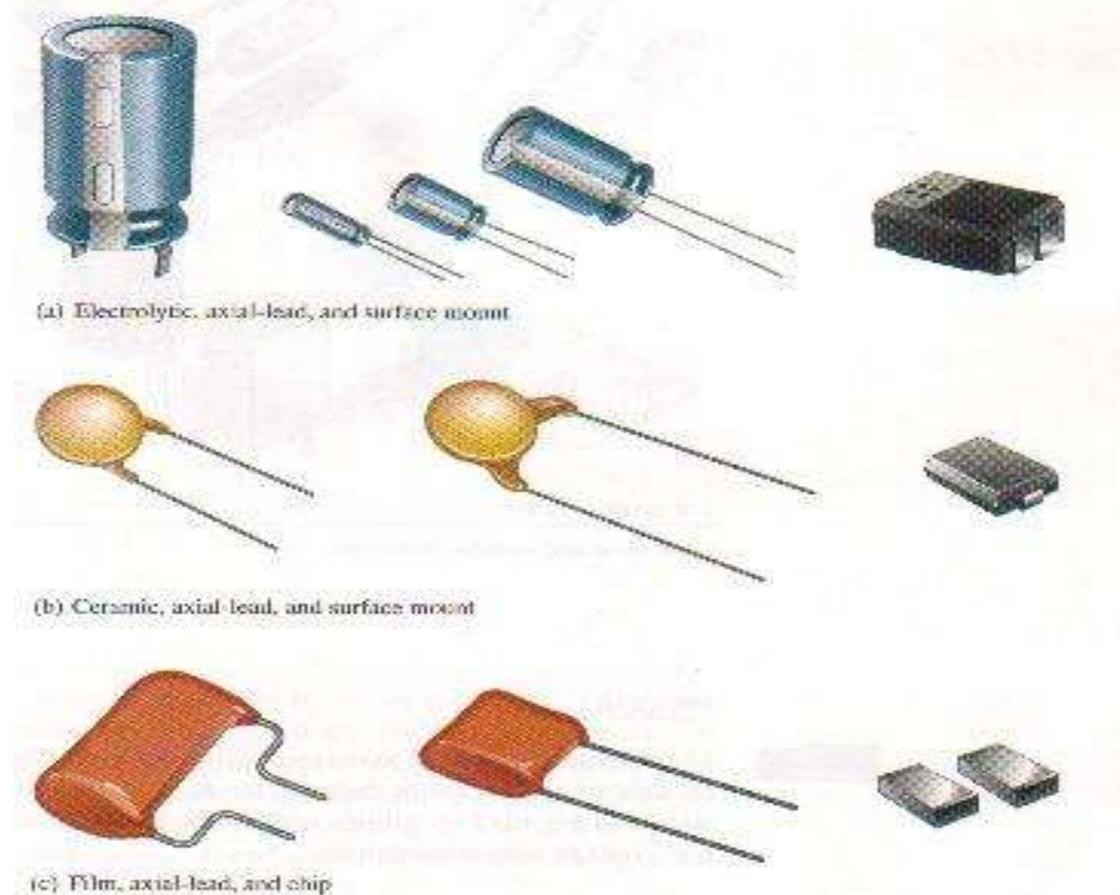

Source
<http://slideplayer.com>



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Inductors



Source
<http://slideplayer.com>



Basic Concept by N.R.H. Abdullah
<http://ocw.ump.edu.my/course/view.php?id=251>

Author Information

Nor Rul Hasma Abdullah (Ph. D)
Senior Lecturer

Email:

hasma@ump.edu.my

Google Scholar:

[Nor Rul Hasma](#)

Scopus ID :

35791718100



Basic Concept by N.R.H. Abdullah

<http://ocw.ump.edu.my/course/view.php?id=251>

Communitising Technology