



**FACULTY OF ELECTRICAL & ELECTRONICS ENGINEERING
FINAL EXAMINATION**

COURSE	:	CIRCUIT ANALYSIS I
COURSE CODE	:	BEE1133
LECTURER	:	NOR RUL HASMA BINTI ABDULLAH MAHFUZAH BINTI MUSTAFA MARLINA BINTI YAKNO NORMANIHA BINTI ABD GHANI
DATE	:	
DURATION	:	3 HOURS
SESSION/SEMESTER	:	SESSION 2015/2016 SEMESTER I
PROGRAM	:	BEE/BEC/BEP

INSTRUCTIONS TO CANDIDATES

1. This question paper consists of **FIVE (5)** questions. Answer **ALL** the questions.
2. All answers to a new question should start on new page.
3. All the calculations and assumptions must be clearly stated.
4. Candidates are not allowed to bring any material other than those allowed by the invigilator into the examination room.

EXAMINATION REQUIREMENTS

1. **Appendix 1** : Table of Formulas

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO

This examination paper consists of **EIGHT (8)** printed pages including front page

QUESTION 1

- a) Discuss a basic concept of Kirchhoff Current Law (KCL) and Kirchhoff Voltage Law (KVL).

[4 Marks]
[CO1, PO1, C2]

- b) For the circuit in Figure 1, use the simplification techniques to determine:
- Current, I
 - Voltage, V
 - Power delivered by the 72 V source

[16 Marks]
[CO1, PO1, C3]

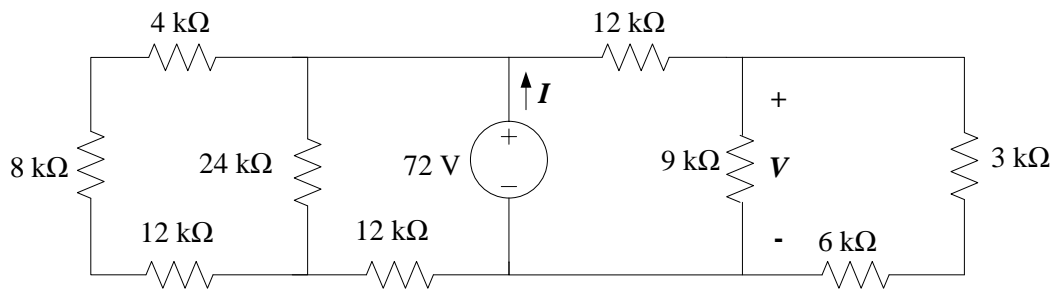


Figure 1

QUESTION 2

For the circuit in Figure 2, use mesh analysis to determine:

- (a) Current, I_1 to I_4 .
- (b) Voltage at point b

[20 Marks]
[CO2, PO1, C3]

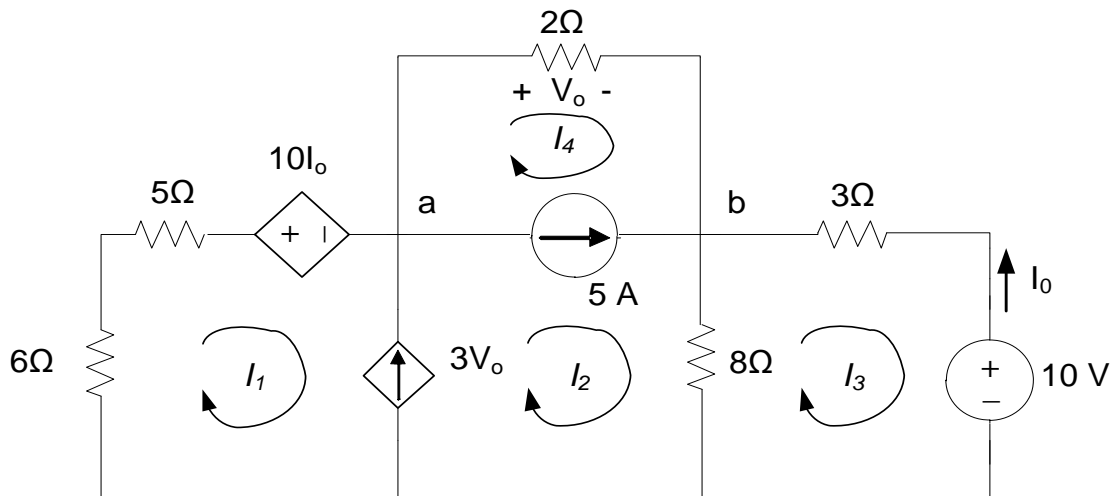


Figure 2

QUESTION 3

- a) For the circuit shown in Figure 3, determine the current, i by using superposition theorem.

[10 Marks]
[CO2, PO1, C3]

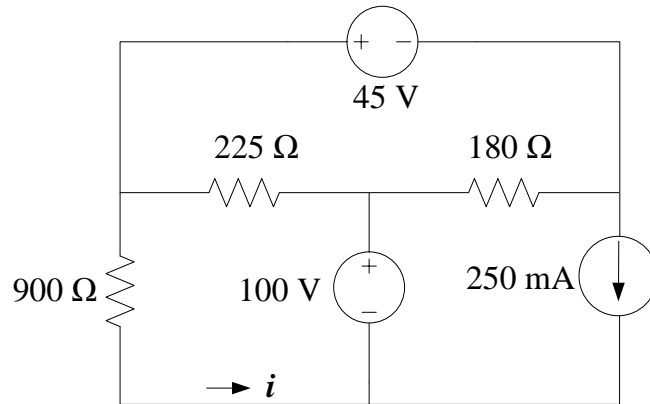


Figure 3

- b) Use a sequence of source transformation to find i as shown in Figure 4.

[5 Marks]
[CO2, PO1, C3]

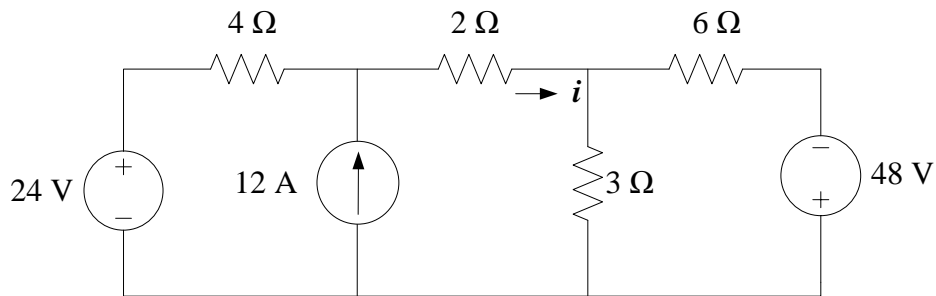


Figure 4

QUESTION 4

By using Norton theorem for the circuit shown in Figure 5:

- (a) Find the Norton equivalent resistance, R_N at terminal a-b.
- (b) Find the Norton current, I_N flow through terminal a-b.
- (c) Draw the Norton equivalent circuit.
- (d) From 4(c), draw the Thevenin equivalent circuit and find the voltage across $R_L=2 \Omega$.
- (e) Calculate the maximum power, P_{max} transferred to the load.

[20 Marks]
[CO2, PO1, C3]

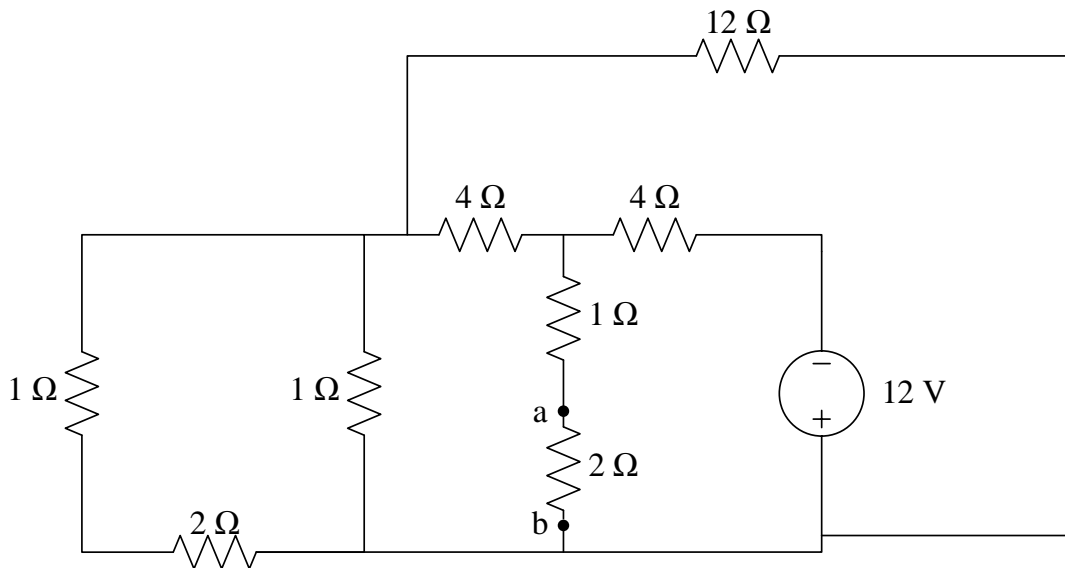


Figure 5

QUESTION 5

- a) The switch **1** in Figure 6 has been in position **a** for a long time. At $t = 0$, the switch moves instantaneously to position **b**. At the instant the switch makes contact with terminal **b**, switch **2** opens. Determine:
- (i) The capacitor voltage $V_0(t)$ for $t > 0$
 - (ii) The capacitor voltage at $t = 5$ ms and $t = 10$ ms.

[16 Marks]
[CO3, PO1, C3]

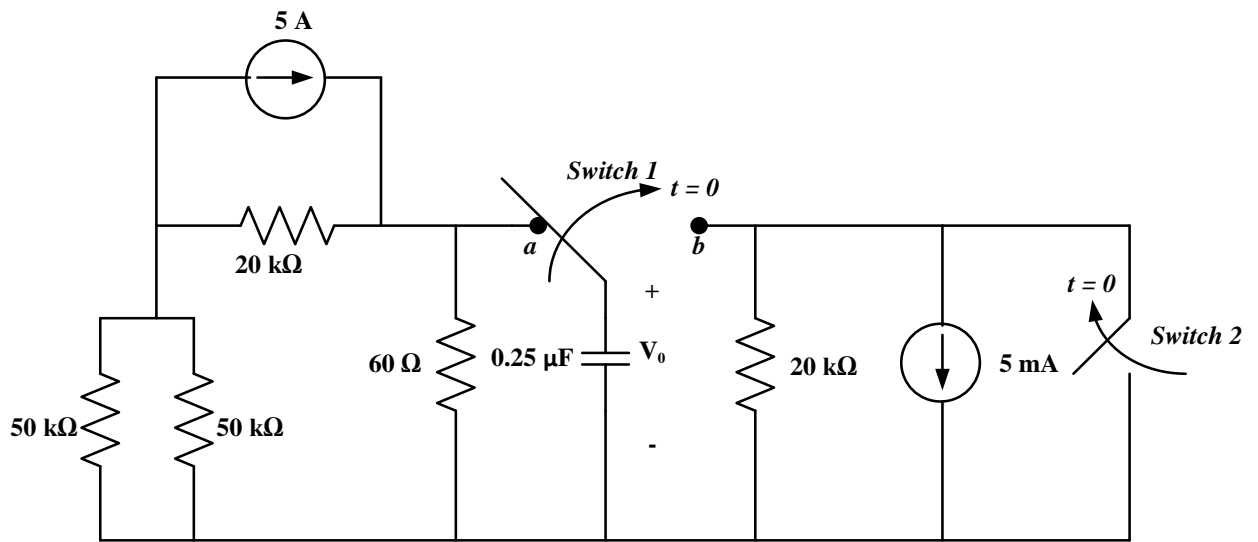


Figure 6

- b) The switch in Figure 7 has been open for long time before closing at $t = 0$. Find the inductor voltage $V_o(t)$ for $t > 0$.

[14 Marks]
[CO3, PO1, C3]

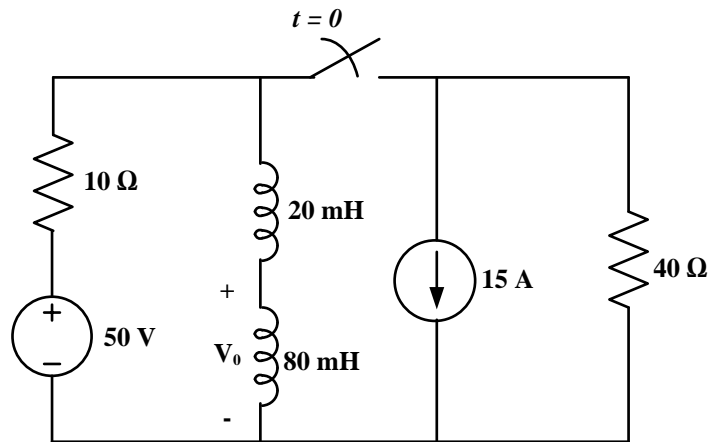


Figure 7

END OF QUESTION PAPER

APPENDIX - Table of Formulas

$$1. P_{\max} = \frac{V_{th}^2}{4R_{th}}$$

2. The unit step function

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

$$3. V_C = \frac{1}{C} \int_{t_0}^t i dt + v(t_0);$$

$$i_L = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

$$4. i_C = C \frac{dv}{dt};$$

$$V_L = L \frac{di}{dt}$$

$$5. \tau = RC;$$

$$\tau = L/R$$

$$6. v(t) = V_0 e^{-t/\tau};$$

$$i(t) = I_0 e^{-t/\tau}$$

$$7. v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$8. i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$9. R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, R_2 = \frac{R_a R_c}{R_a + R_b + R_c}, R_3 = \frac{R_b R_a}{R_a + R_b + R_c}$$

$$10. R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}, R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$