

Chapter 12

Parallel Interfacing

Expected Outcomes

- Identify the internal registers of MC6821
- Design the hardware interface for various I/O devices using MC6821
- Develop and write codes using MC6821

Parallel Interface/Timer

- I/O interface using a simple I/O device such as latch or buffer has its drawbacks
- One of them is the circuit design must be reconstructed if a user decide to change its I/O devices
- A dedicated peripheral such as the 68230 (PI/T - Parallel Interface/Timer)
 - Its primary function is to provide parallel interface
 - Its secondary function is a programmable timer
- It provides 4 modes of operation with various handshaking and buffering capabilities
 - Unidirectional 8-bits
 - Unidirectional 16-bits
 - Bidirectional 8-bits
 - Bidirectional 16-bits

Parallel Interface/Timer


- The programmable timer provides a variety of services
 - Periodic interrupt generation
 - Square wave generator
 - Interrupt after time-out
 - Elapse time measurement
 - System watchdog
- Since, it is part of 68xxx family, the PI/T is expensive due to its capability to provide wider functions
- A simple 8-bit family can be used in certain cases to provide parallel I/O interface
- PIA 6821 peripheral interface adapter is introduced to give flexibility in I/O system

PIA 6821

- PIA was initially designed for use in 6800-based system
- However, it is widely used in 68000-based system due its flexibility and cost
- Since it is part of 6800 family, additional pin connections are needed to operate in asynchronous mode
 - The port A and B may be programmed individually to be an input or an output – allowing the software to adjust to a new system requirement
 - Additional signal lines may be programmed to allow interrupts and strobe signals for each port
 - Internal register to allow storage of data temporary thus allowing to interface with a slower devices such as printer

PIA 6821

- PIA has two port with each port may drive two TTL loads
- Each individual signal line (PA0 through PA7 and PB0 through PB7) can be programmed as an input or an output

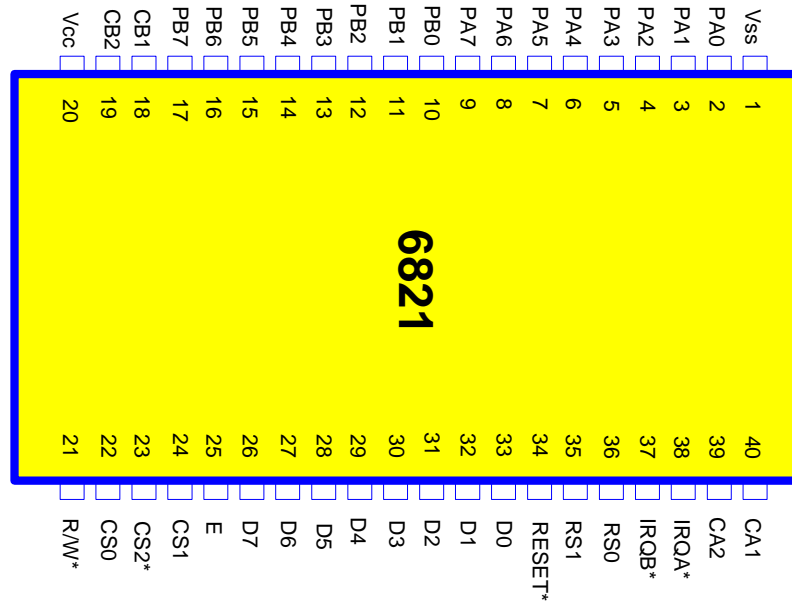


PIA 6821

- PIA has 6 internal registers that can be programmed to its need
 - Each port has three registers
-
- **For Port A**
 - **Data Register A (DRA)**
To transfer data in or out
 - **Data Direction Register A (DDRA)**
Determine direction of each line
 - **Control Register A (CRA)**
Control the operation of port A
 - **For Port B**
 - **Data Register B (DRB)**
To transfer data in or out
 - **Data Direction Register B (DDRB)**
Determine direction of each line
 - **Control Register B (CRB)**
Control the operation of port B


PIA 6821

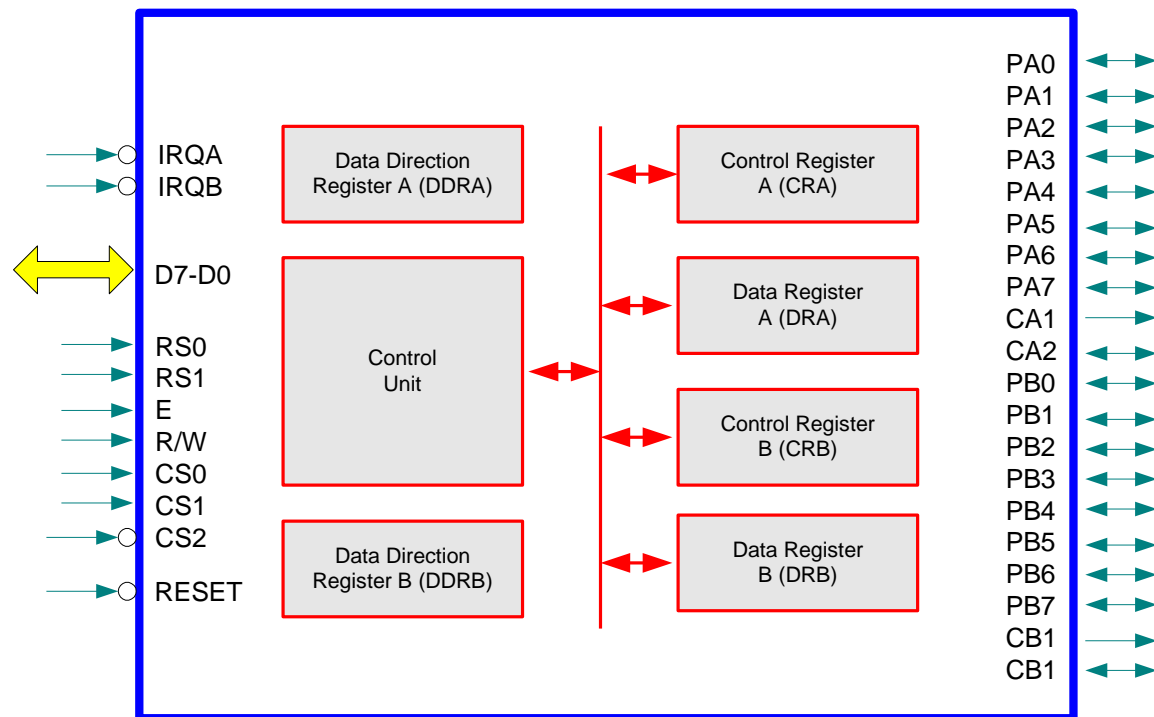- Internal structure of PIA consist of six registers and control unit







Interface With 68000

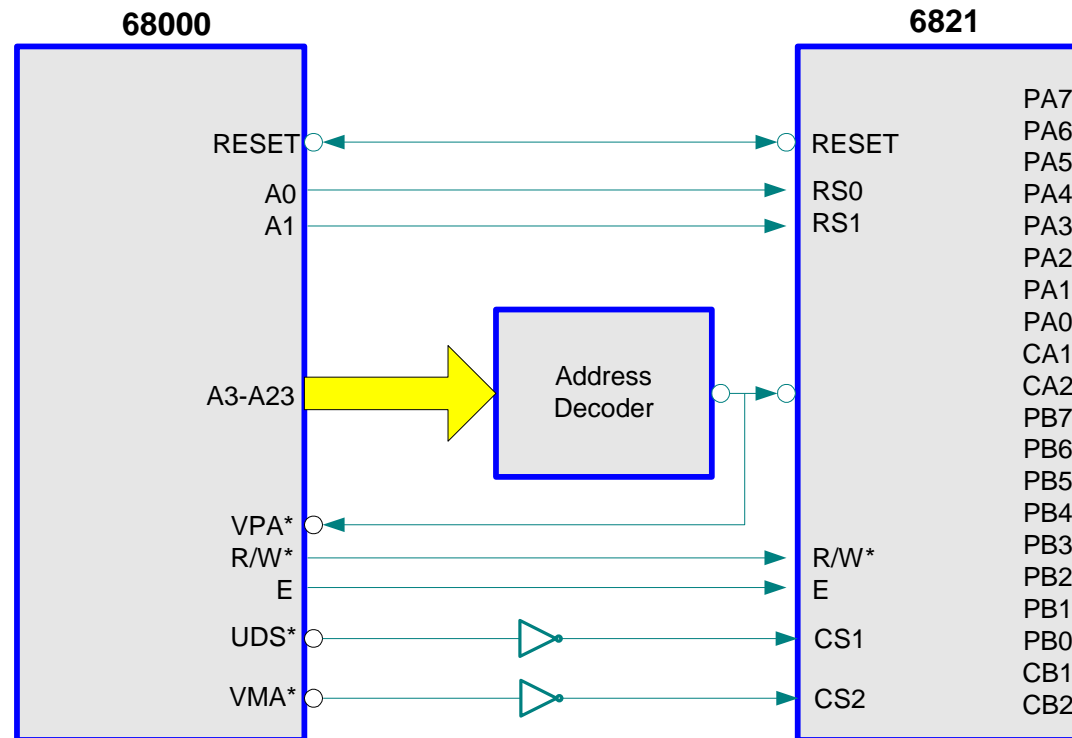- Since 6821 is operating in synchronous mode, additional pin connections are required



PIA Registers

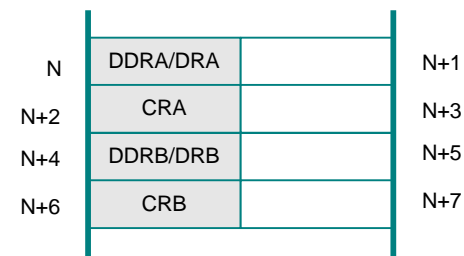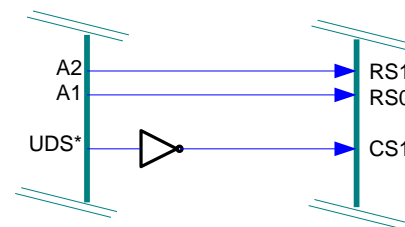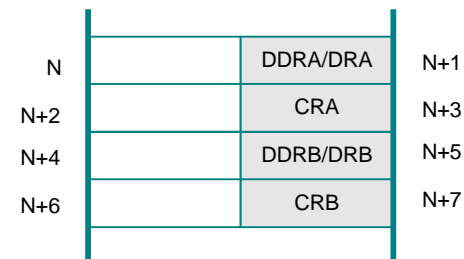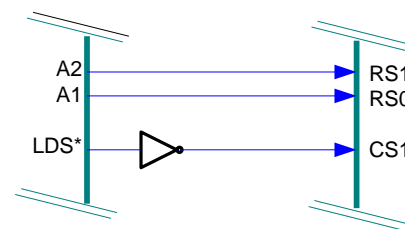- The address of 6 internal registers of PIA depends on
 - Address decoder
 - Data Strobe connection (UDS or LDS)



PIA Registers

- Since there is 6 registers and only four locations, two registers are located in the same address
- To distinguish these registers, bit2 of control register is used

RS1	RS1	Register
0	0	Data Register A/Data Direction Reg. A
0	1	Control Register A
1	0	Data Register B/Data Direction Reg. B
1	1	Control Register B

RS1	RS0	CRA2	CRB2	Register
0	0	0	X	Data Direction Reg. A (DDRA)
0	0	1	X	Data Register A (DRA)
0	1	X	X	Control Register A (CRA)
1	0	X	0	Data Direction Reg. B (DDRB)
1	0	X	1	Data Register B (DRB)
1	1	X	X	Control Register B (CRB)

PIA Registers

■ Data Register A (DRA)

bit7	bit6	bit5	bit4	bit3	bit2	bit1	bit0
DRA7	DRA6	DRA5	DRA4	DRA3	DRA2	DRA1	DDRA0

■ Data Direction Register A (DDRA)

bit7	bit6	bit5	bit4	bit3	bit2	bit1	bit0
DDRA7	DDRA6	DDRA5	DDRA4	DDRA3	DDRA2	DDRA1	DDRA0

Logic 1 in each DDRA_i causes the signal line PA_i to become **output line**

Logic 0 in each DDRA_i causes the signal line PA_i to become **input line**

For example:

If DDRA = \$4C, PA₆, PA₃ and PA₂ are output and others are input

Control Register

CRA7	CRA6	CRA5	CRA4	CRA3	CRA2	CRA1	CRA0
IRQA	IRQB	CA2	CA2	CA2	DDRA/ DRA	CA1	CA1

Set if transition in CA1

Set if transition in CA2

0: CA2 is input
1: CA2 is output

If CRA5=0, CRA3 & CRA4
follow

←→
Refer to data sheet
for complete
information

0: IRQA disabled
1: IRQA is activated


0: CA1 is recognized on
positive -to negative
transition

1: CA1 is recognized on
positive -to negative
transition

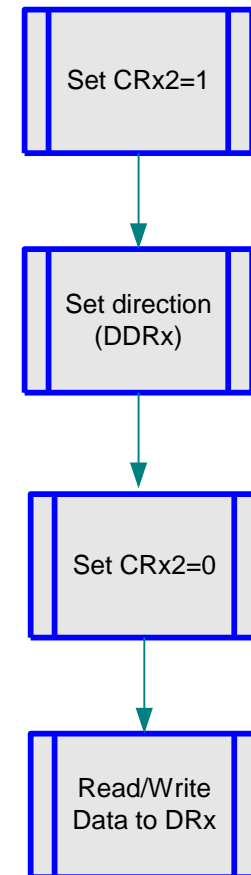0: DDRA is chosen
1: DRA is chosen

Initialize PIA

- Initializing PIA is the most crucial steps in programming a system using this I/O device
- Followings are brief procedure to initialize PIA for simple I/O (Assuming port A)
 - Fill bit 2 of `CRA` with 0 to access `DDRA`
 - Fill `DDRA` with proper value to determine the role of each signal line of the port A (1 for output and 0 for input)
 - Fill bit 2 of `CRA` with 1 to access `DRA`
 - Write or read data using `DRA`



Initialize PIA

- **Example** : Initialize PIA assuming port A is an output port and port B is an input port

```
; Initialize Port A
MOVE.B #0,CRA
MOVE.B #$FF,DDRA
MOVE.B #4,CRA


; Initialize Port B
MOVE.B #0,CRB
MOVE.B #0,DDRB
MOVE.B #4,CRB
```

More Examples..

- Write a program to switch on the LED as the respective switch is pressed assuming all ports are initialized

```

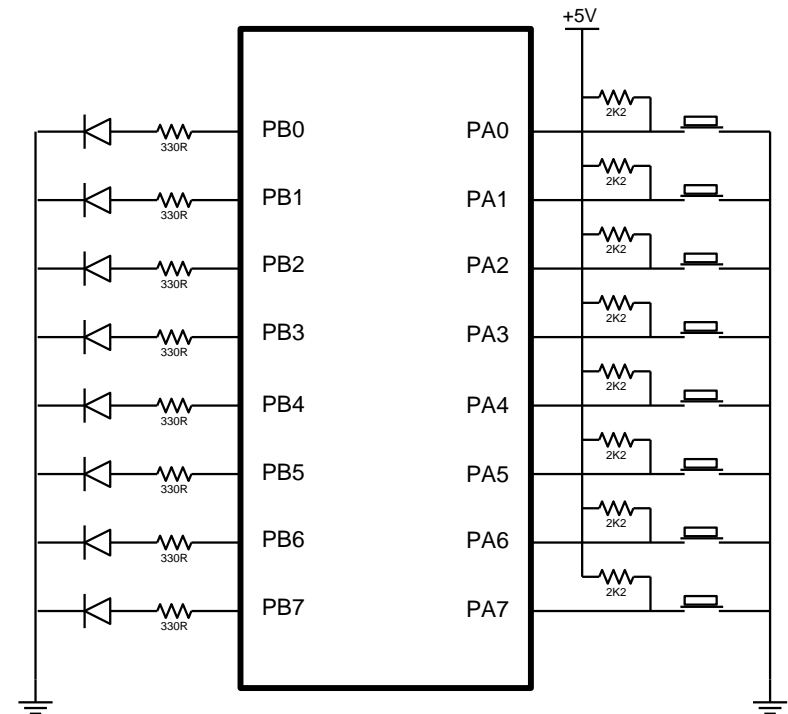START  MOVE .B DRA ,D0
        NOT .B D0
        MOVE .B DRB
        BRA  START
    
```




More Examples..

- Write a program to display a pressed number on seven segment display

```

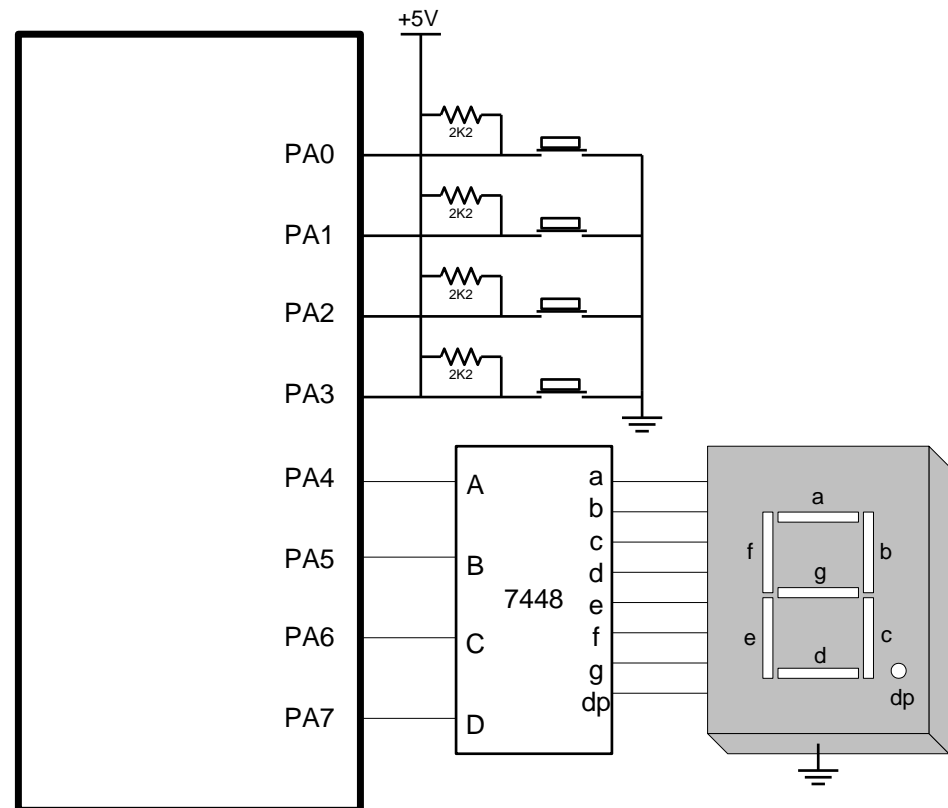CLR .B  CRA
MOVE .B  #$F0 ,DDRA
MOVE .B  #4 ,CRA
LOOP MOVE .B  DRA ,D0
ASL .B  #4 ,D0
MOVE .B  D0 ,DRA
BRA  LOOP
  
```




More Examples..

- Write a program to display an upward counter (0,1,2..8,9,0...) continuously

```

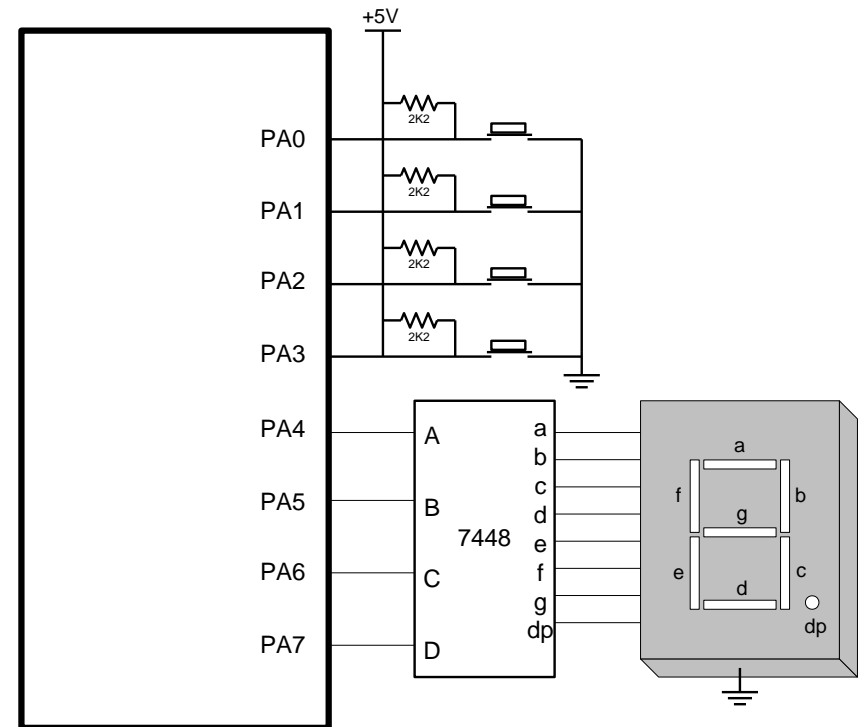MAIN CLR.B D0
LOOP MOVE.B D0,DRA
      BSR DELAY
      ADDQ.B #1,D0
      CMPI.B #10,D0
      BNE LOOP
      BRA MAIN
  
```



Self-Test

■ Exercise

Write as simple program to initialize port A where PA0-PA3 are output and PA4-PA7 are input

■ Exercise

If port B is connected to 7-segment display, write a program to initialize port B. Then, write a program to display downward counter on port B

■ Exercise

If PB0 is connected to a low current speaker, write a program to generate continuous tone with frequency of 1kHz to the speaker

Self-Test

■ Exercise

Write a program to meet following requirements,

- If switch 1 is pressed, the segment will display upward counter
- If switch 2 is pressed, the segment will display downward counter
- If switch 3 is pressed, the segment will display random value continuously
- If switch 4 is pressed, the program is terminated

