

# Electricity, Magnetism & Optics

## Direct Current Circuit

by

Muhammad Hafiz bin Mazwir  
Faculty of Industrial Sciences & Technology  
muhammadhafiz@ump.edu.my



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# Chapter Description

- Aims

Students will understand how to calculate the effective resistance in a circuit, and describe the rules of current flow in direct current circuits.

- Expected Outcomes

- Able to analyse electrical circuits with multiple resistors connected in parallel or in series
- Able to describe the rules for circuits with more than one loop
- Able to use ammeters and voltmeters correctly



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# Content

- 6.1 Resistance in Series and Parallel
- 6.2 Kirchhoff's Rules
- 6.3 Electrical Measuring Equipment



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# 6.1 Resistance in Series and Parallel

- Just like capacitors, resistors in come in specific resistance ratings such as  $100\ \Omega$ ,  $330\ \Omega$  and  $1\ \text{k}\Omega$
- In order to use a specific resistance value in an electrical circuit, several resistors can be connected either in series or in parallel to achieve resistance value that may not be available in a single resistor




*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# Resistor in Series

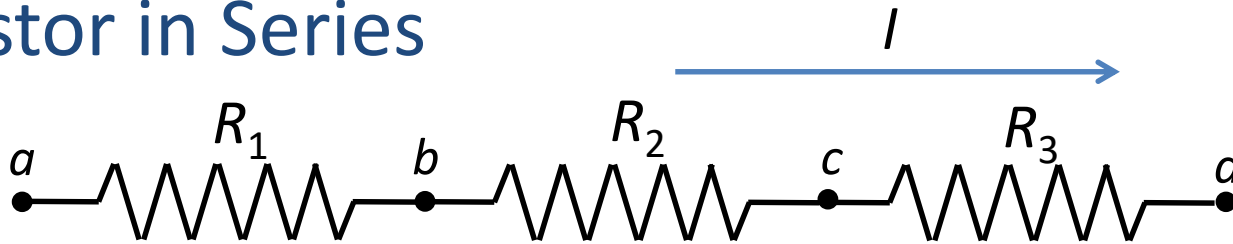

- In a series, the current is the same in all resistors. From Ohm's law,  $V_{ab} = IR_1$        $V_{bc} = IR_2$        $V_{cd} = IR_3$
- The potential difference across the entire combination is the sum of the individual potential differences,

$$V_{ab} = V_{ax} + V_{xy} + V_{yb} = I(R_1 + R_2 + R_3)$$

$$\therefore R_{\text{eq}} = R_1 + R_2 + R_3$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots \quad (\text{resistors in series})$$



Direct Current Circuit


by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>
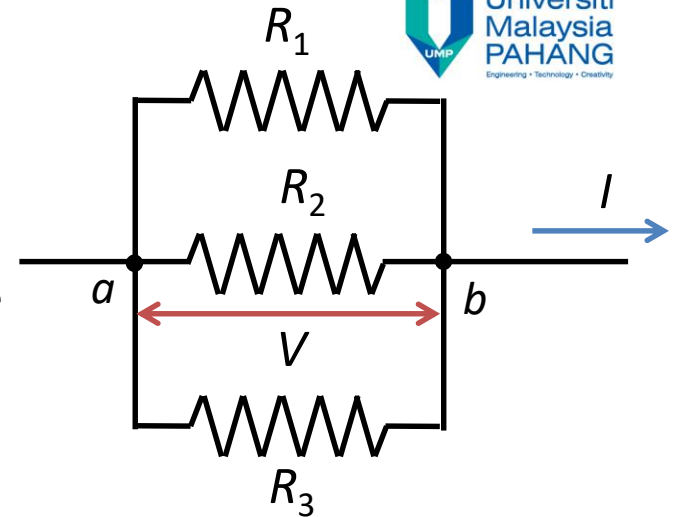
# Resistor in Parallel

- If the resistors are in parallel, current through each resistor is different.
- However, the potential difference between the terminals must be the same and equal to  $V_{ab}$

$$I_1 = \frac{V_{ab}}{R_1} \quad I_2 = \frac{V_{ab}}{R_2} \quad I_3 = \frac{V_{ab}}{R_3}$$



- Total current must equal the sum of all three currents in the resistors

$$I = I_1 + I_2 + I_3 = V_{ab} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \quad (\text{resistors in parallel})$$

Circuit

Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

## 6.2 Kirchhoff's Rules

- Many practical resistor networks cannot be reduced to simple series-parallel combinations. And current calculation is complex for circuits with more than one power source.
- A technique developed by German physicist, Gustav Kirchhoff can be employed in cases like these.
- Two important terms:
  - 1. Junction:** A point in the circuit where three or more conductors meet
  - 2. Loop:** Any closed conducting path.



Direct Current Circuit  
by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

# Kirchhoff's Junction Rule


- The sum of the currents into any junction is zero. That is

$$\sum I = 0 \quad (\text{junction rule, valid at any junction})$$

- For example, in the complex junction shown to the right, all the current going into the junction  $I_1$  and  $I_3$  flows out as current  $I_2$ ,  $I_4$  and  $I_5$
- If the current going into the junction is taken as positive, the junction rule can be written as

$$\sum I = I_1 - I_2 + I_3 - I_4 - I_5 = 0$$

$$I_1 + I_3 = I_2 + I_4 + I_5$$

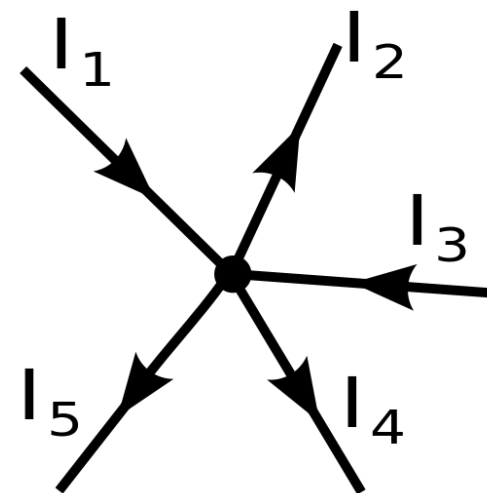

Source: Philnate,  
Wikimedia Commons



Direct Current Circuit

by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>




# Kirchhoff's Loop Rule

The sum of the potential differences in any closed loop, including those associated with emfs and those of resistive element, must equal zero.

$$\sum V = 0 \quad (\text{loop rule, valid at any closed loop})$$

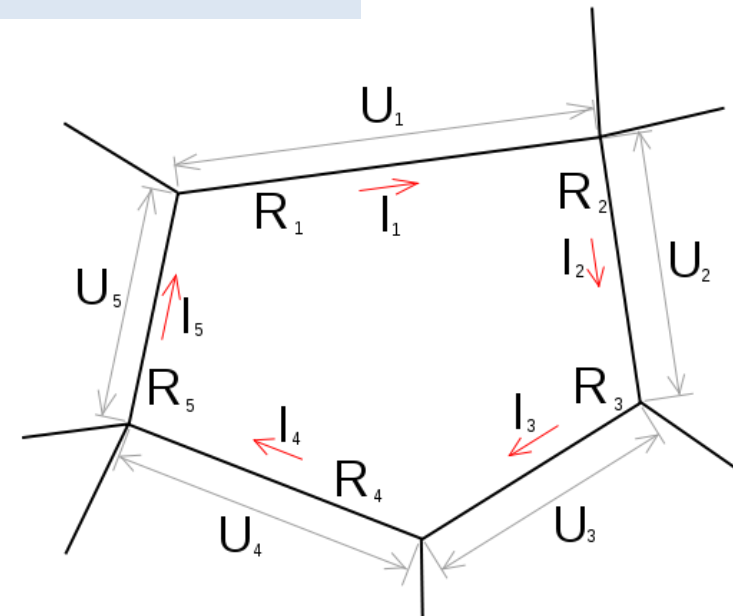- For sources of emfs, the voltage is positive when going from – to +
- While for resistors etc, the voltage is negative when going from – to +



Source: Pajs, Wikimedia Commons



Direct Current Circuit

by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

## 6.2 Electrical Measuring Instruments

- Potential difference, current and resistance in a circuit can be measured using a *d'Arsonvale galvanometer*
- A coil of wire is placed in a magnetic field of a permanent magnet. When there is current in the coil, the magnetic field exerts a torque on the coil. As the coil turns, the spring exerts a restoring torque to push it back to zero.
- The maximum deflection, typically  $90^\circ$ , is called *full-scale deflection*. The current at this deflection is called full-scale current,  $I_{fs}$
- The difference between the method of measuring the three parameters has something to do with the meter's internal connections



Direct Current Circuit

by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

# Ammeters

- A meter to measure current passing through it.
- An ideal ammeter would have zero resistance
- Real ammeters always have some finite resistance, denoted  $R_C$ , which is the resistance of the coil.
- The ammeter can be adapted to measure current larger than its full-scale reading by connecting a resistor in parallel to the coil, so that some of the current bypasses the meter coil.
- The parallel resistor is called a **shunt resistor**, denoted as  $R_{sh}$
- For example, suppose we want to make a meter with full-scale current  $I_{fs}$  into an ammeter with full scale reading  $I_a$ . To determine the shunt resistor needed, note that at full-scale deflection, the total current through the parallel combination is  $I_a$ , the current through the coil of the meter is  $I_{fs}$ , and the current through the shunt resistor is  $I_a - I_{fs}$ . Since  $V$  is the same for both  $R$ ,

$$I_{fs} R_C = (I_a - I_{fs}) R_{sh}$$



Direct Current Circuit

by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

# Voltmeters

- The same basic meter used as ammeters can also be used to measure voltage.
- An ideal voltmeter would have infinite resistance
- Real voltmeters should always have some large enough resistance, so connecting it between two points in a circuit does not change the current in the circuit
- Like the ammeter, full scale reading in voltmeters can be changed by connecting a shunt resistor,  $R_S$  in series with the coil.
- Then only a fraction of the total potential difference appears across the coil itself, and the remainder appears across  $R_S$ . For a voltmeter with full scale reading  $V_a$ , we need series resistor so that

$$V_a = I_{fs} (R_C + R_S)$$



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# Conclusion

- Resistance calculation
  - Resistors are typically connected in series and parallel to achieve desired resistance value
  - The calculation for resistors in series and parallel are different
- Kirchhoff's Rules
  - Kirchhoff's rules are useful to analyse the current flowing in a circuit with more than one loop
- Ammeters and Voltmeters
  - Ammeters and voltmeters are similar to each other except for the way the shunt resistor is connected inside them



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# References

- **University Physics 14<sup>th</sup> Edition**, Hugh D. Young, Roger A. Freedman, IOP Publishing Ltd, 2015
- **Physics for Scientists & Engineers 4th Edition**, Douglas C. Giancoli, Pearson, 2008
- **Physics for Scientists & Engineers 9<sup>th</sup> Edition**, Raymond A. Serway & John W. Jewett, Cengage Learning, 2014



*Direct Current Circuit*  
by Muhammad Hafiz bin Mazwir

<http://ocw.ump.edu.my/course/view.php?id=32>

# Thank you!

## Next chapter: Magnetic Forces and Fields



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>

# Authors Information

Muhammad Hafiz bin Mazwir  
Siti Aisah binti Harun

Material Technology Programme,  
Faculty of Industrial Sciences & Technology  
Universiti Malaysia Pahang



*Direct Current Circuit*

*by Muhammad Hafiz bin Mazwir*

<http://ocw.ump.edu.my/course/view.php?id=32>