

Faculty of Electrical & Electronics Engineering
Low Voltage Electrical Installation

Name: _____

ID No. : _____

Section: _____

Date: ____/____/2017

(Failed to complete all the particulars above will be penalized 2 marks)

QUIZ 3

Question 1: What is the name of this accessory? And, what it is used for?

[2 marks]



Fig. 2

Name:

Function:

Question 2: Mahdi wants to construct a simple wiring layout in his small workshop based on below picture. He needs several things to be prepared before he starts his project. Help him by listing up **only EIGHT** equipment or tools that he may use even he needs more than that.

[8 marks]

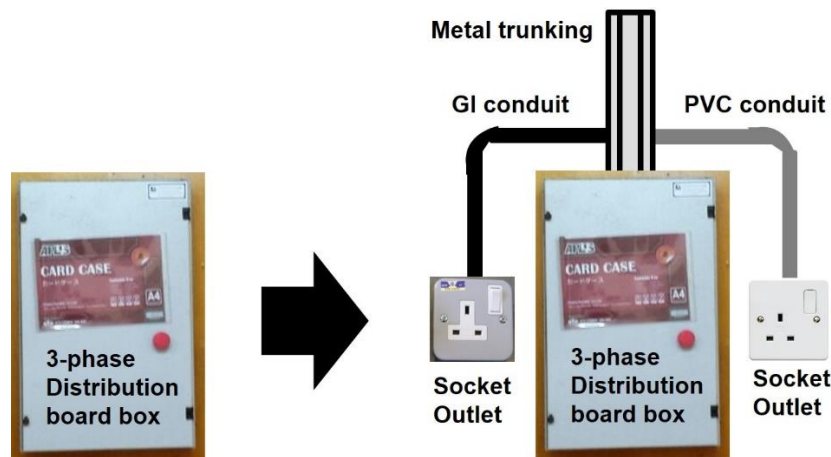


Fig. 3

- a. _____
- b. _____
- c. _____
- d. _____

- e. _____
- f. _____
- g. _____
- h. _____

